


Design of Driver for a Digital Hearing Aid

Amrith Sukumaran,
Electrical Dept, IIT-M
Advisor: Dr.Y.Shanthi Pavan

Outline

- Introduction to digital hearing aids
- Digital portion
- Analog portion
- Performance summary

Digital hearing aid

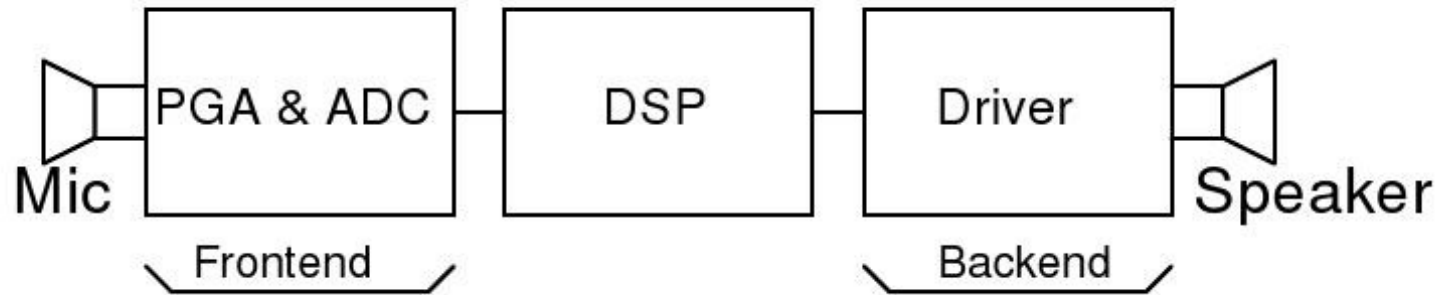


- Frontend converts analog input to digital for further processing
- DSP processes the digital signal
- Backend drives the speaker using DSP's output

Target Specifications


- SNR > 95 dB
- THD > -70 dB
- O/p Thermal noise < 12 micro V rms
- Minimal power consumption

Backend driver

 


- DSP outputs a 16-bit signal
- Speaker requires analog signal as input

Digital DAC

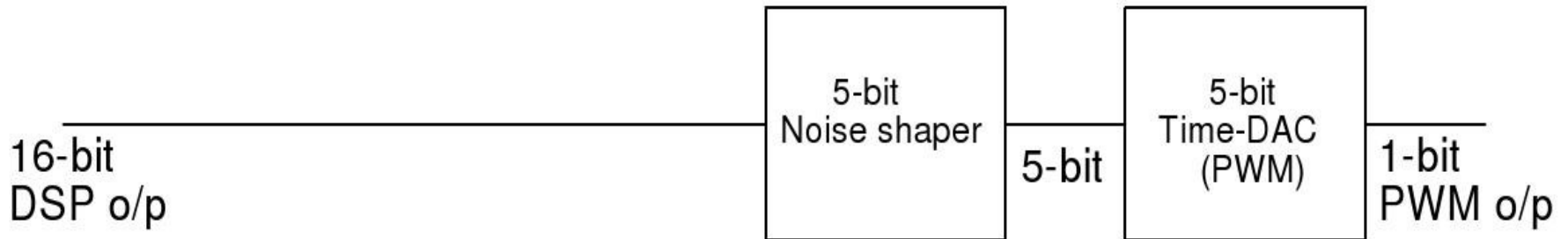


- 16-bit to 1-bit conversion in 2 steps
- Digital Delta Sigma(DDS) used for noise shaper
- 5-bit DDS o/p mapped into pulse widths

Digital Noise Shaper (DDS)

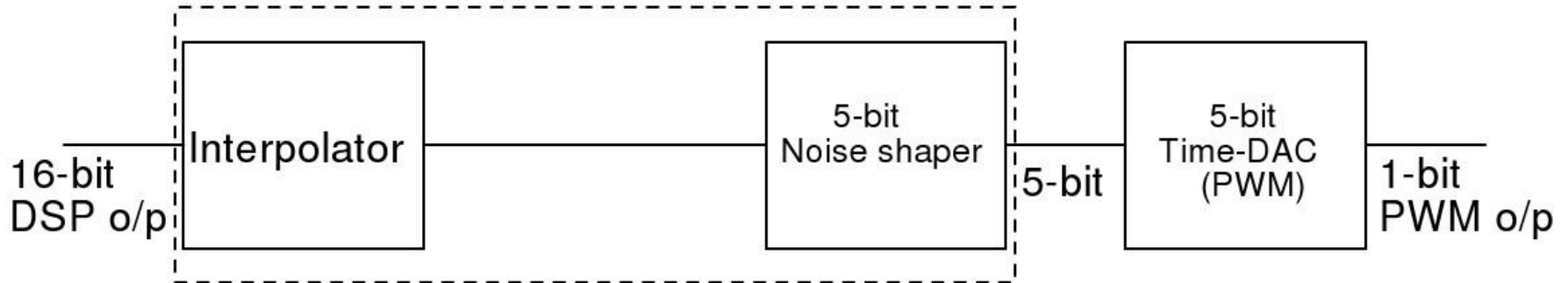


- From MATLAB simulations, an OSR of 32 and a 5-bit internal quantizer was chosen
- DSP o/p is a 40 kHz PCM signal
- Hence a 16x interpolator is used

DDS-Architecture

 


- An error feedback architecture is adopted
- $Y(z) = X(z) + [1+(z^{-1})L(z)]E(z)$
- The coefficient of $E(z)$ is NTF(z)
- $L(z) = z[NTF(z)-1]$. If NTF is FIR, so is L .

DDS-Loop filter

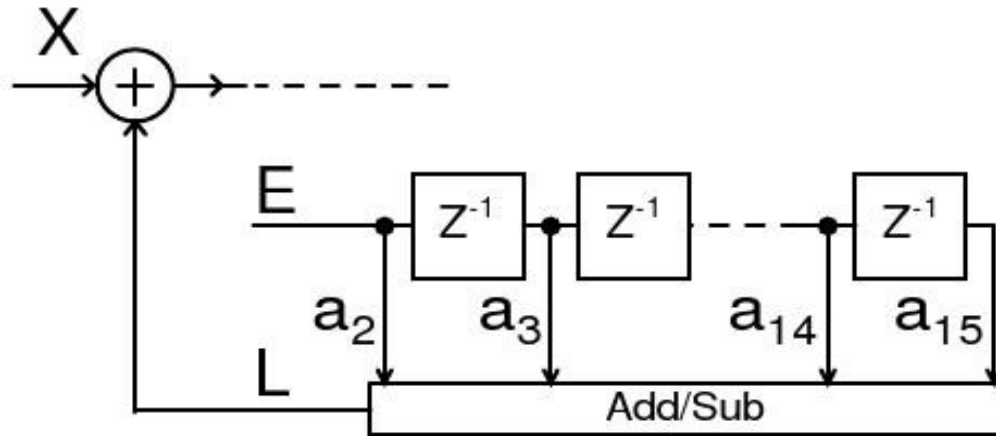


- A 15th order FIR-NTF is used
- Hence a 14-tap loop filter

DDS-NTF Frequency response

 


Interpolator

 

- Repeating the same value 4 times is cosine filtering
- In addition to above inherent filtering an explicit filter H is used


Interpolator – Filter (H)

 


$$H_1(z) = 1 + 2Z^{-1} + 2Z^{-2} + 2Z^{-3} + Z^{-4}$$

- A simple low-pass FIR filter is used
- Has notch at $0.5f_s$ (80 kHz) and $0.25f_s$ (40 kHz)

Interpolator-Spectrum

 


Predistortion – Time DAC

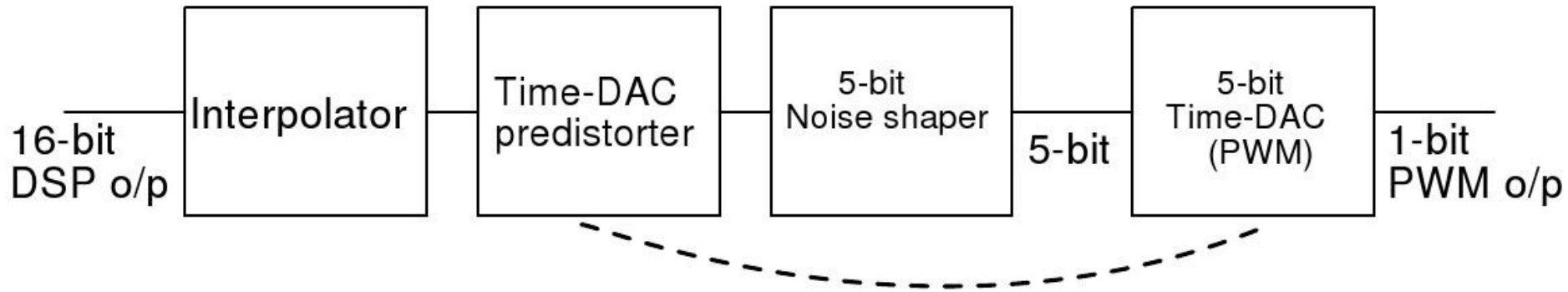

- To accurately represent a sine wave (or any signal) in PWM format, there are only 2 ways; comparing it with a triangle or a sawtooth
- Blind mapping of amplitude to time leads to signal distortion
- A predistorter emulates the comparison process

Predistorter- Algorithm

 


$$y_0 = \frac{k(s_1 + s_2)}{2k + s_1 - s_2}$$
$$\approx \frac{1}{4k} (s_1 + s_2)(2k - s_1 + s_2)$$

s_1, s_2 are sampled message amplitudes

- All the calculations gets implemented digitally
- Sawtooth carrier is used for both simplicity and to prevent foldback


Digital DAC – output spectrum

 

Digital DAC – Performance summary


- Area: 250 μm x 250 μm
- Power
 - Interpolator - 17 %
 - Algorithm - 7 %
 - Noise shaper- 32 %
 - Time-DAC - 38 %
- SNDR = 95.662 dB
- THD = -102.225 dB

Analog driver amplifier

 

- Class D principle- good efficiency
- V_p, V_m are PWM input signals (digital DAC o/p)

H-Bridge driver

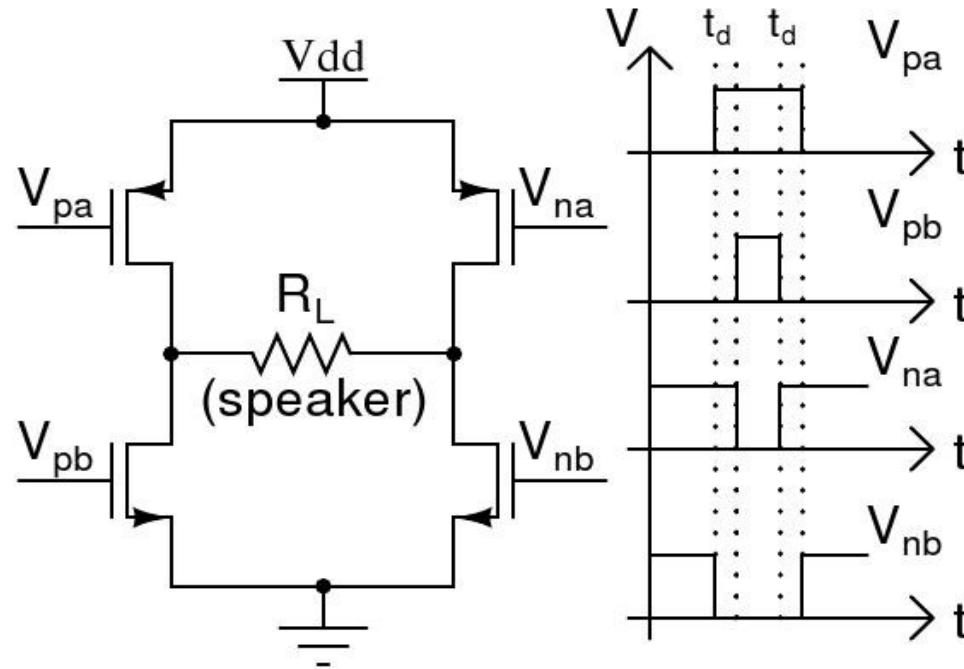


- I/p PWM signal must be non-overlapping to prevent supply shoot-through
- The actual speaker acts as a low-pass filter

Known problems with open loop


- Power supply noise modulates directly with the input signal
- Non-overlap-time non-linearities
- Finite rise and fall times of H-bridge
- Nonlinear triangular carrier generation
- Comparator offsets
- Load dependence

Forming a closed loop driver

 


- Single ended version illustrated for compactness
- V_{in} is digital DAC's PWM o/p
- $L(s)$ needs to be a low-pass filter

Closed loop – Loop filter

 


- $L(s)$ is 2nd order integrator loop filter
- Coefficients chosen to give sufficient loop gain in signal band
- Triangular carrier chosen to be 640 kHz
- Loop's u_{gf} fixed at 170 kHz


Loop- Compensation

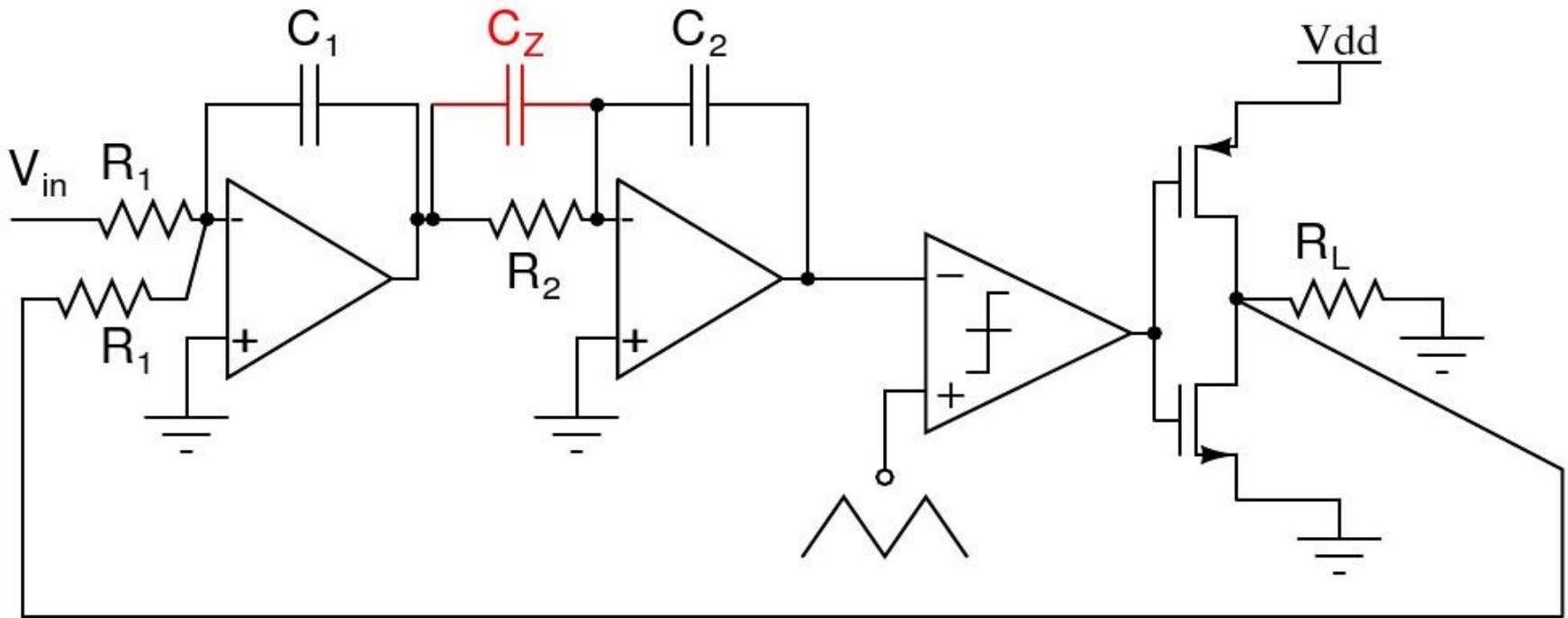

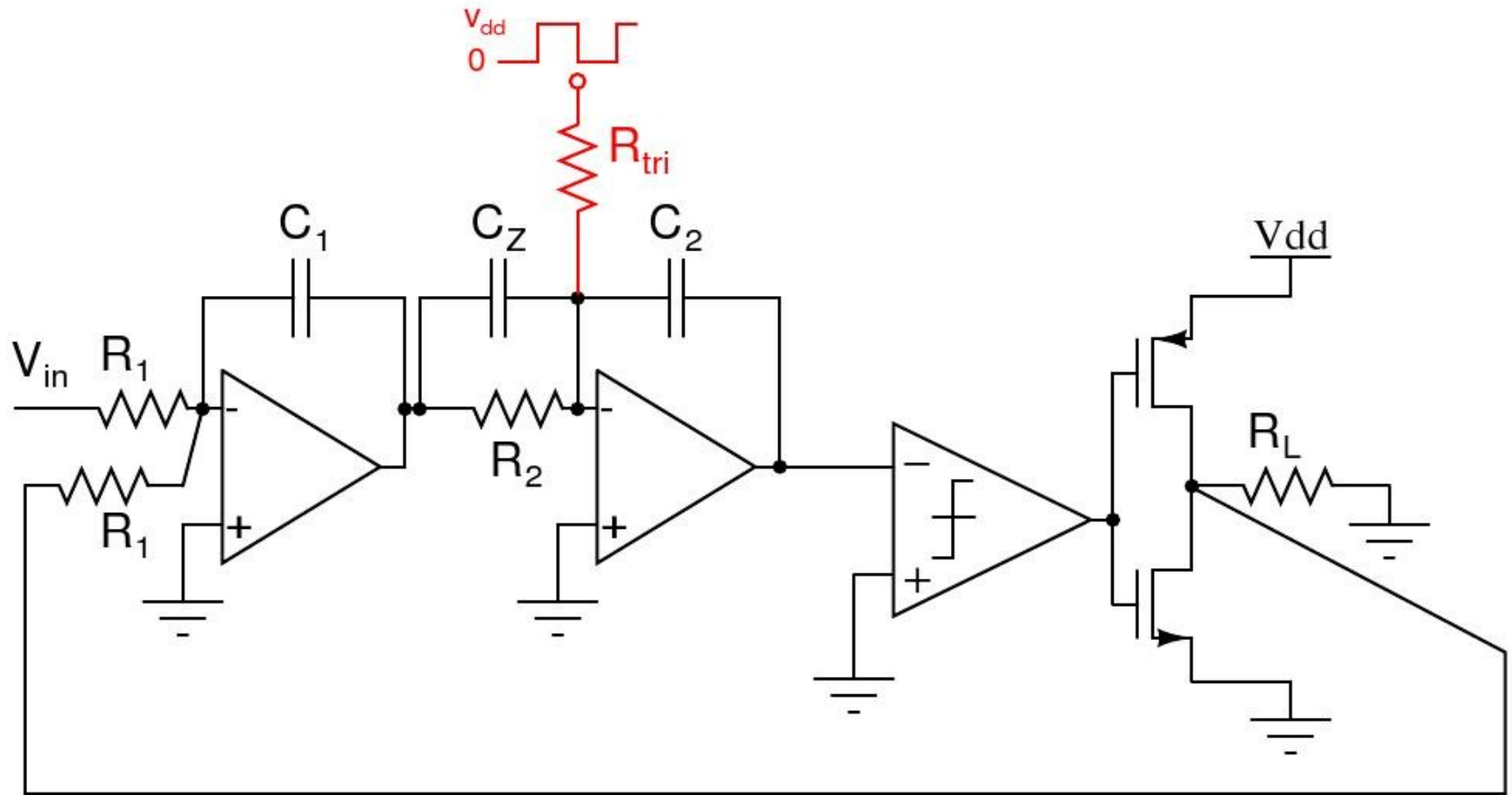- The loop cuts the ugf at -40 dB per decade
- Compensation achieved through C_z and C_2
- C_z & C_2 provides a path to bypass 2nd integrator above the $C_z \cdot R_2$ pole frequency




 - Triangular carrier generation is done by integrating a square-wave voltage
- R_{tri} and C_2 together decide triangle amplitude




- Digital dac's o/p has large high frequency power
- Input resistor converted to an LPF
- Input resistor splitted into FIR structure
- Reduces high frequency jitter from digital clocks


FIR-DAC Architecture

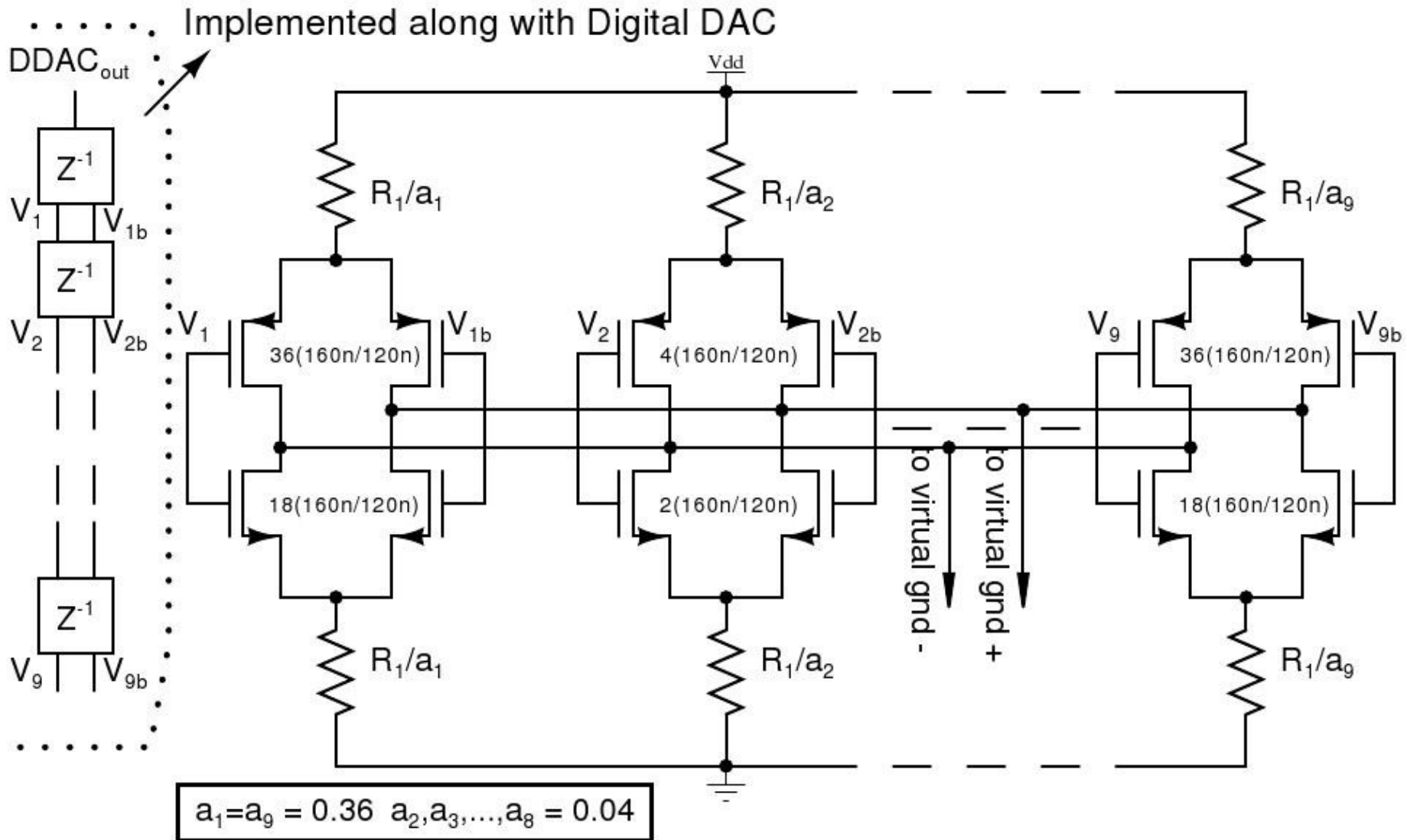

FIR-DAC frequency response

 


Linearizing the loop

 


- The comparator with H-Bridge is linearized as V_{DD}/V_{tri}
- This linear model is valid at frequencies much lower than triangle frequency

Loop – frequency response

mag * phase...

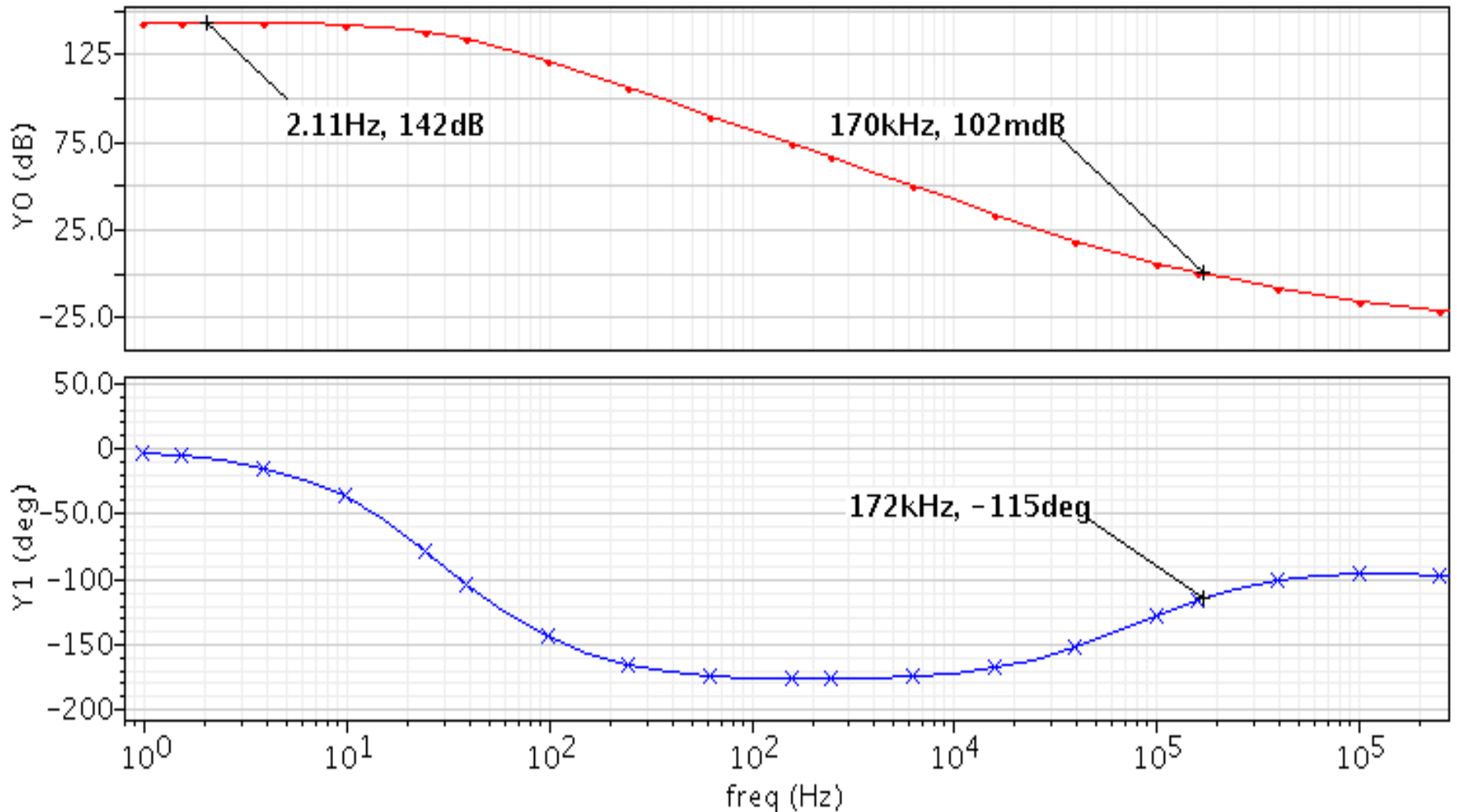


Integrator 1 - Amplifier

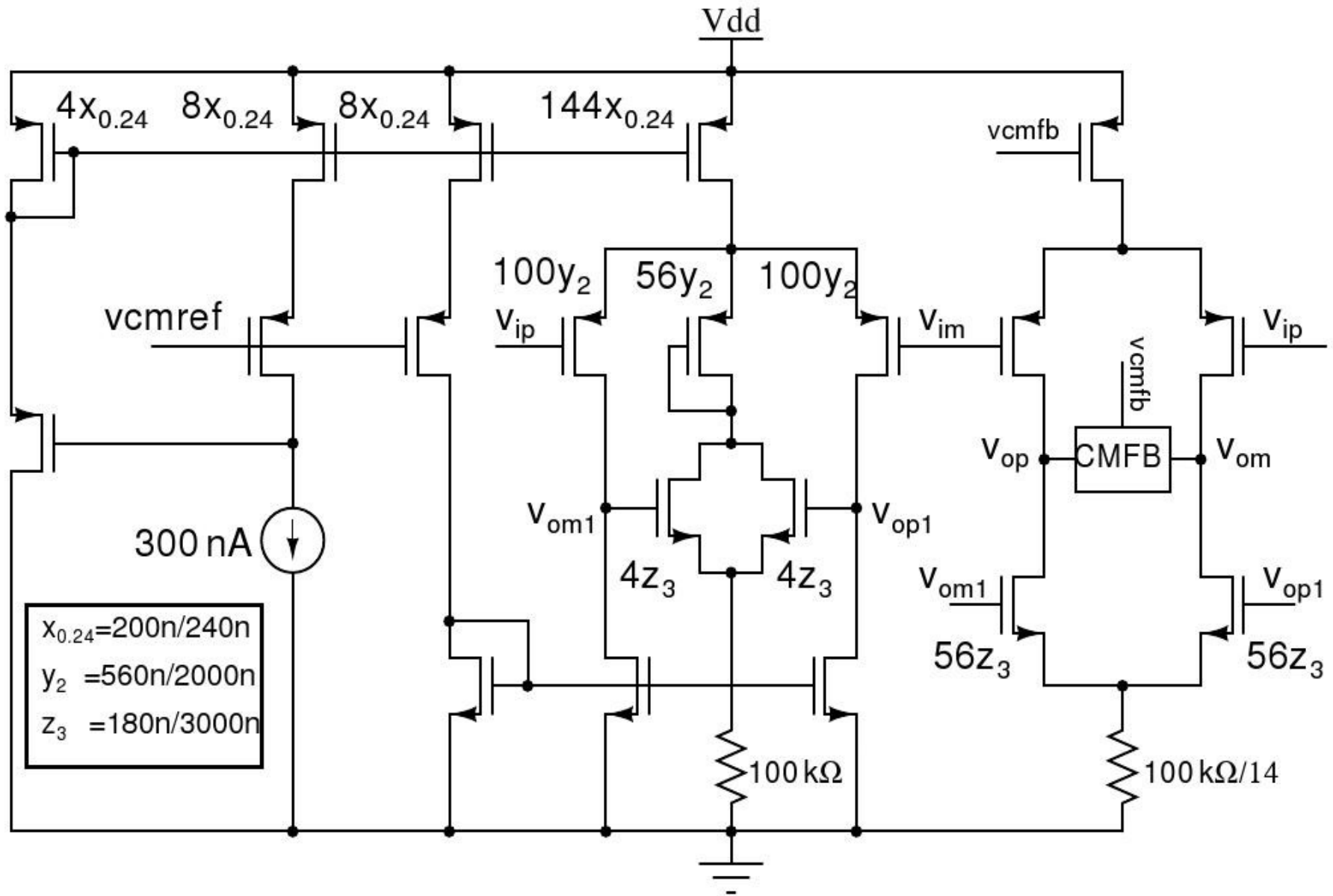


Improving linearity

- The output signal current to input signal voltage is nonlinear for a differential amplifier
- By making the output signal current 0, the input signal becomes 0 by virtue of negative feedback and hence implies no nonlinearity
- First amplifier needs to accept both feedback DAC signal and input FIR-DAC signal currents
- An alternate source is provided to accept these currents


Assistant- Architecture

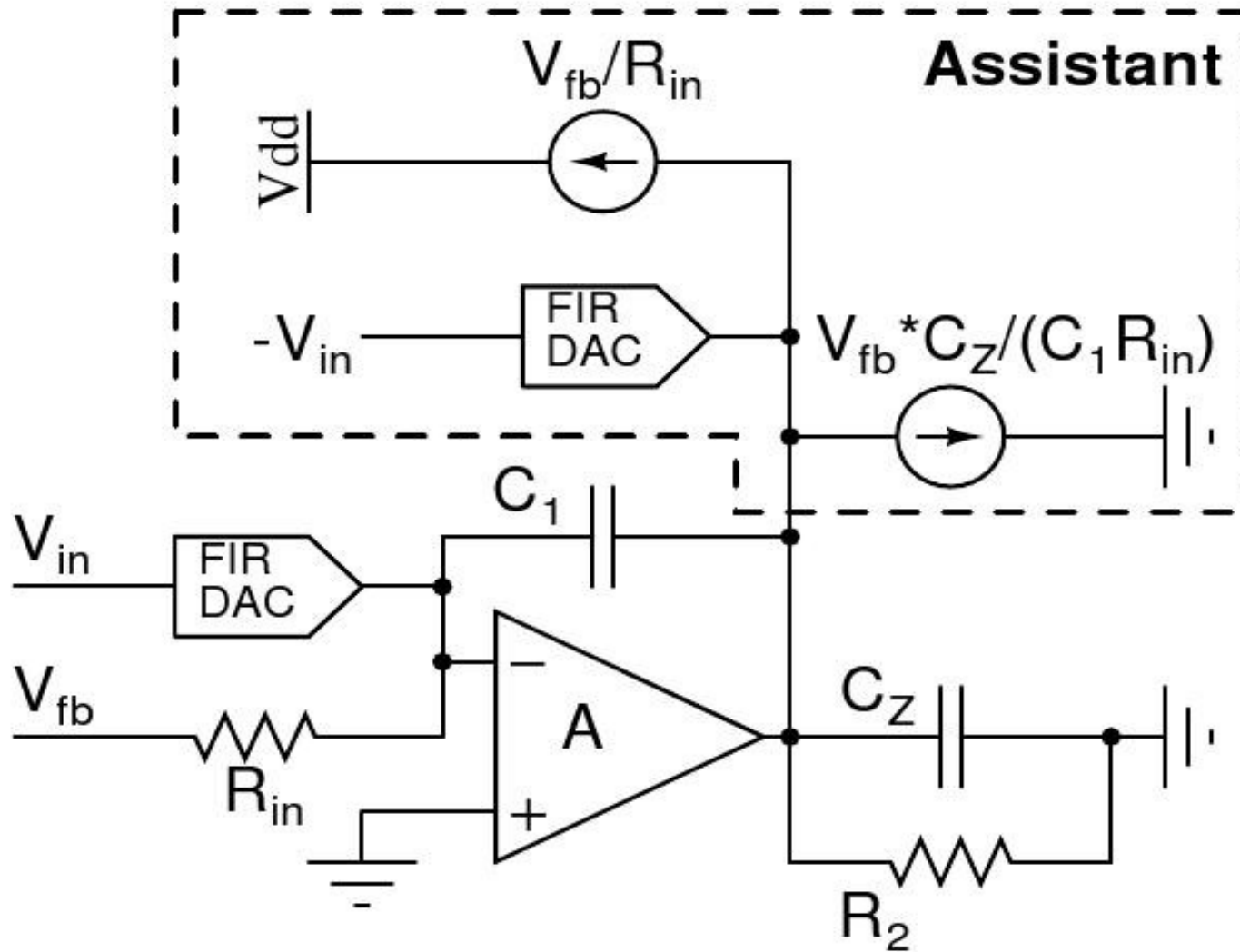


Assistant to feedback DAC

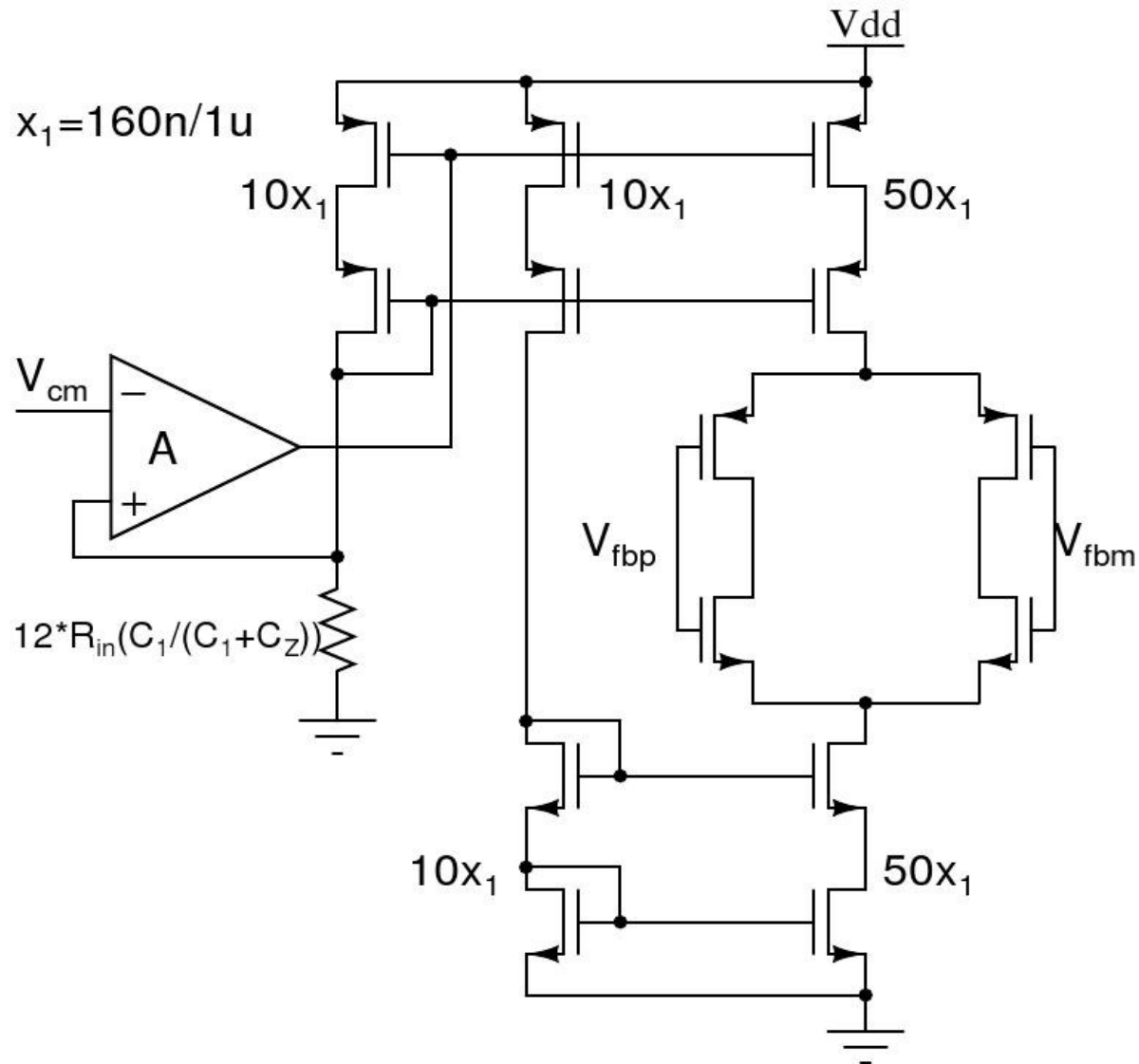


Assistant to input FIR-DAC

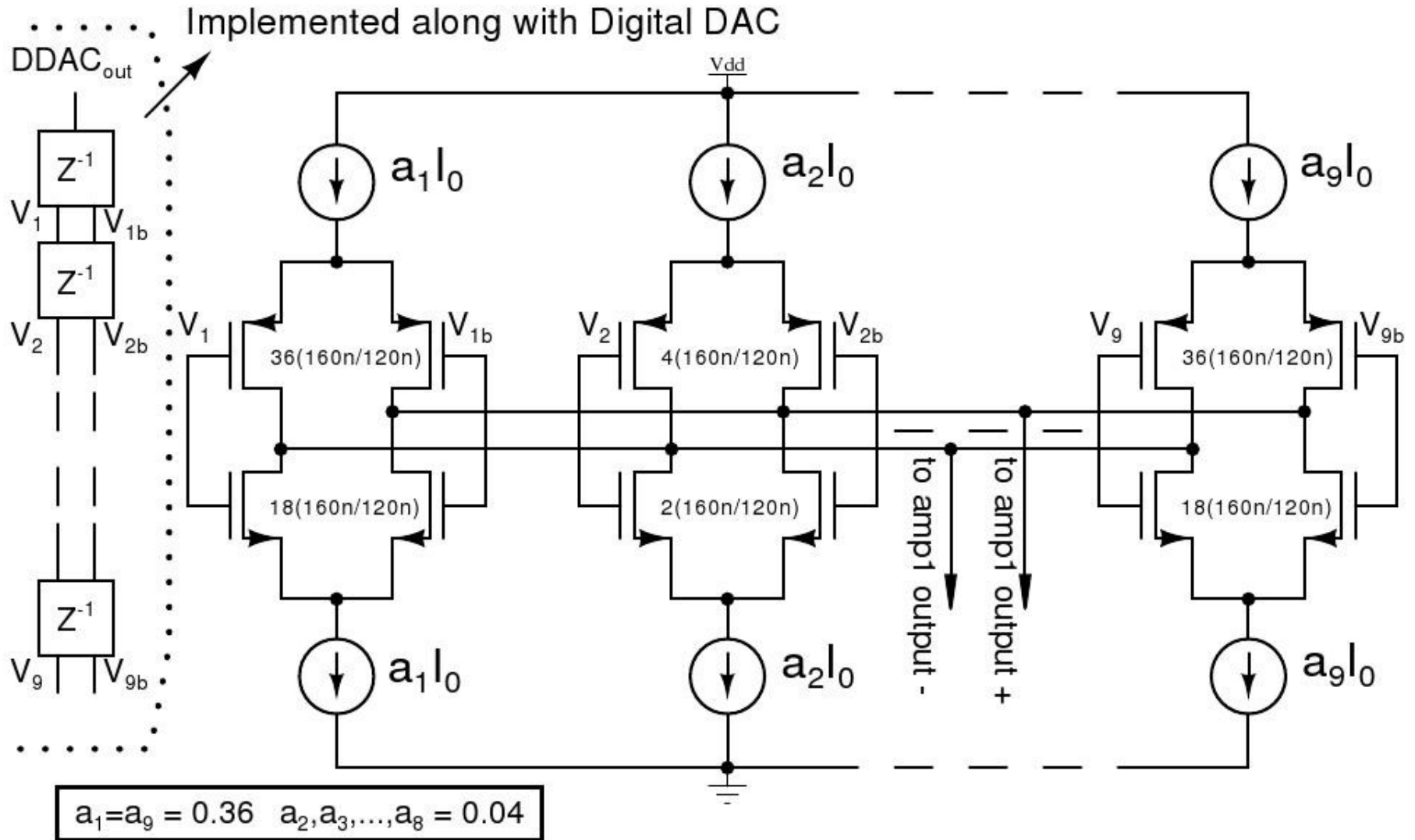

Integrator 2 - Amplifier

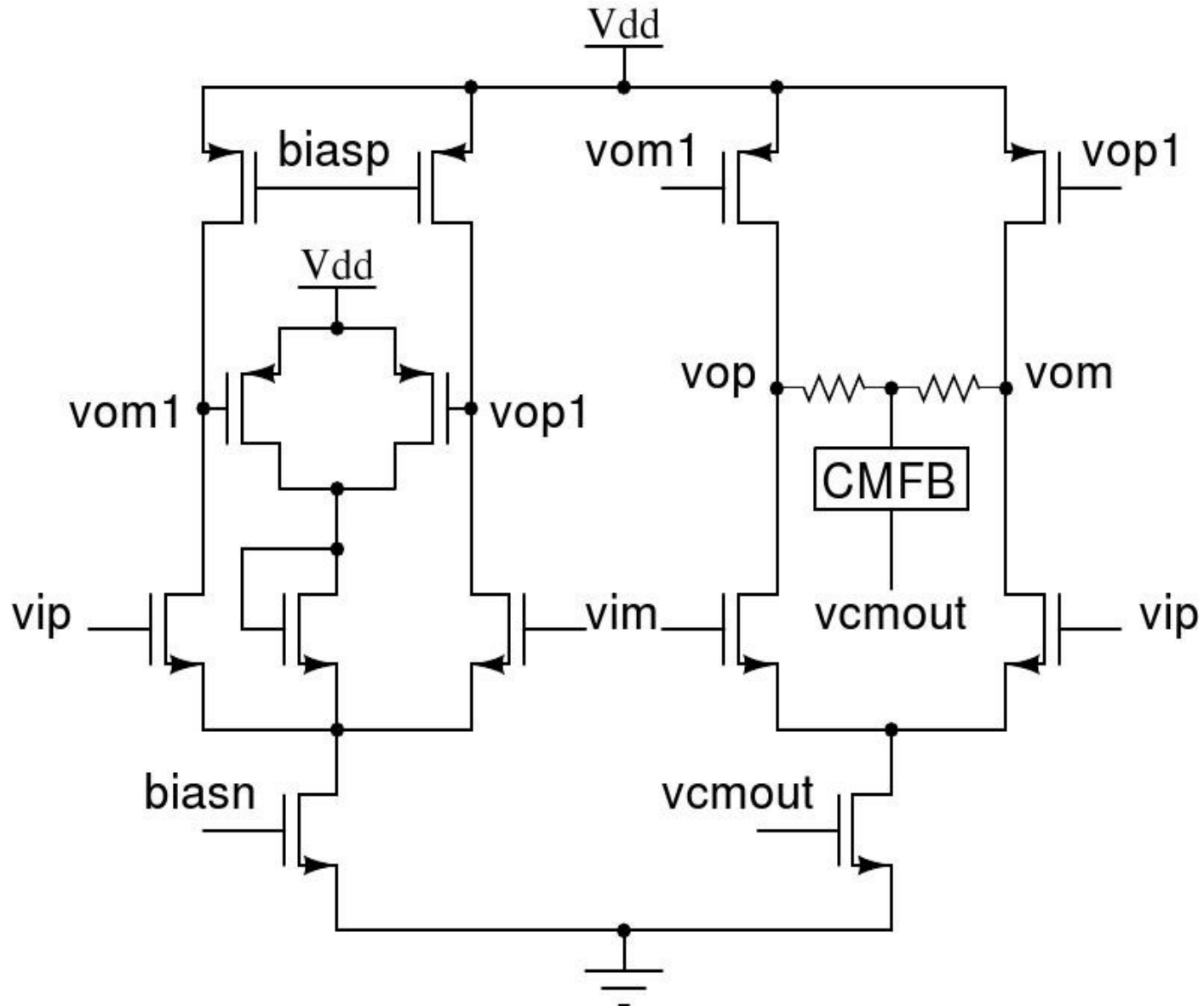


Comparator

 

*Without compensation


- Amplifier Schematic same as that of amp 2
- Buffer is just 2 inverters

Nonoverlap pulse generation

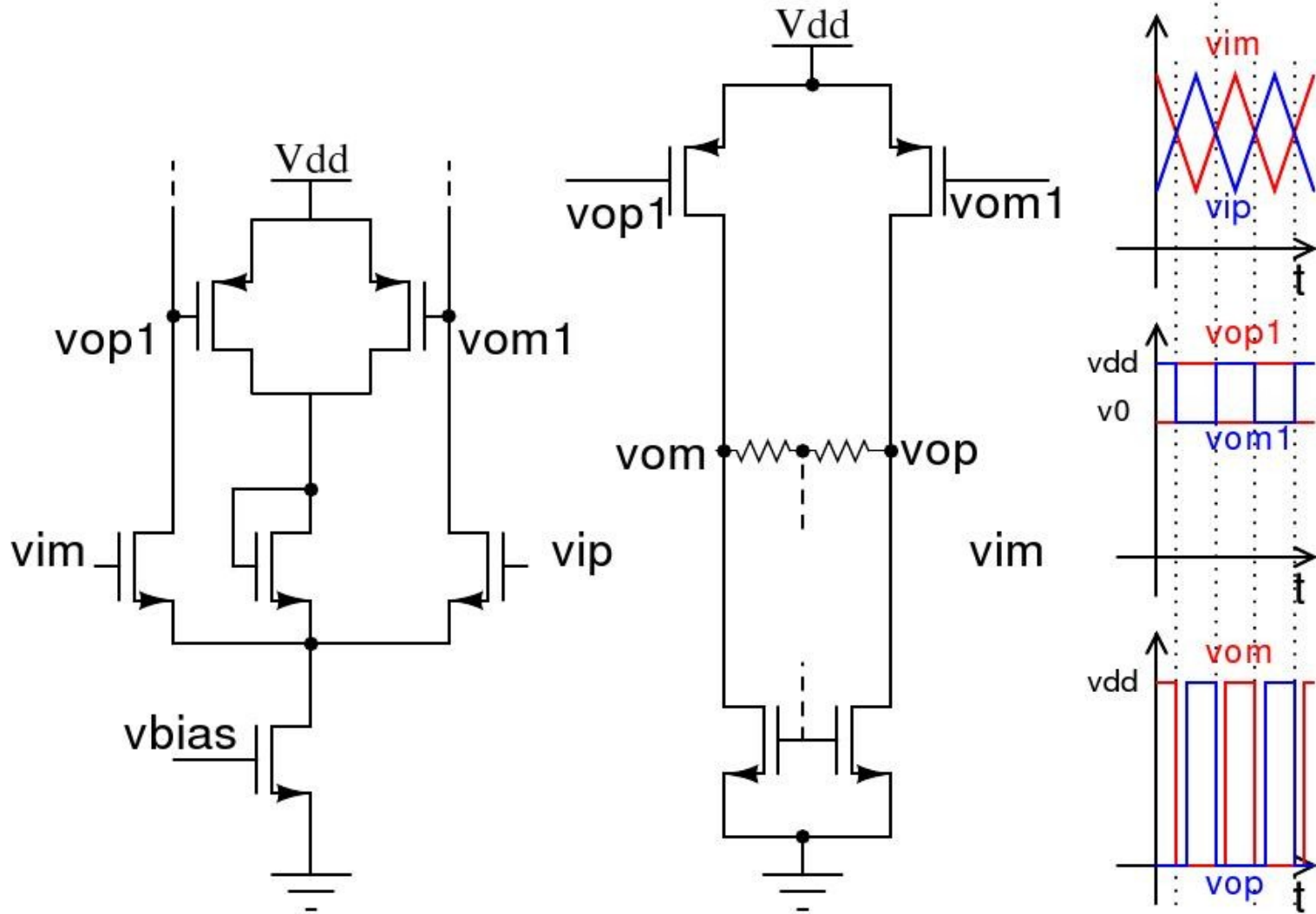

- 2-stage architecture adopted for comparator inherently makes its output non-overlapping
- Individual outputs of 1st stage swing only between v_{dd} and $v_{dd} - 2 \cdot (v_{dd} - v_{cm1})$
- This causes unequal drive strengths for the 2nd stage input transistors
- The above causes non-overlapping outputs

Simulation results

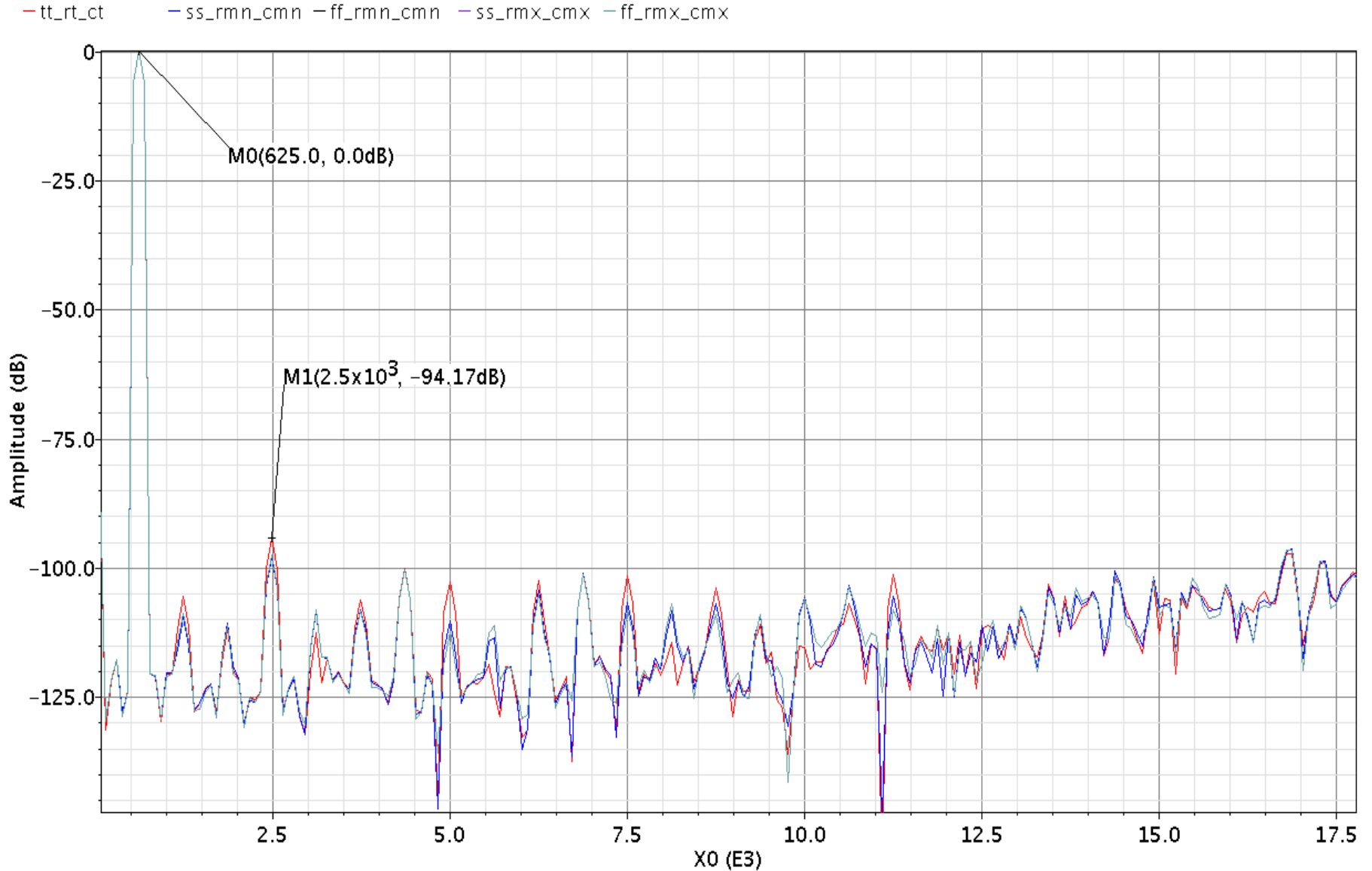

Performance summary

Power	Digital	33 μ W
	Analog(Q)	84 μ W
Area	Digital	250 μ m \times 250 μ m
	Analog	600 μ m \times 700 μ m
SNDR		90.37dB
THD		-92.68 dB
Output thermal noise		12 μ Vrms

References

- [1] Berkhout, M., "An integrated 200-W class-D audio amplifier," *IEEE Journal of Solid-State Circuits* volume 38, number 7, pages 1198 - 1206, 2003
- [2] Chang, J.S. and Bah Hwee Gwee and Yong Seng Lon and Meng Tong Tan, "A novel low-power low-voltage Class D amplifier with feedback for improving THD, power efficiency and gain linearity," in *IEEE International Symposium on Circuits and Systems, ISCAS 2001*, pp. 635 -638
- [3] El-Hamamsy, S.-A, "Design of high-efficiency RF Class-D power amplifier," in *IEEE Transactions on Power Electronics* 1994
- [4] Goldberg, J.M. and Sandler, M.B, "New high accuracy pulse width modulation based digital-to-analogue convertor/power amplifier," in *IEE Proceedings- Circuits, Devices and Systems*, 1994, pp. 315 -324.
- [5] Bah-Hwee Gwee and Chang, J.S. and Adrian, V, "A micropower low-distortion digital class-D amplifier based on an algorithmic pulsewidth modulator," in *Circuits and Systems I: Regular Papers, IEEE Transactions on*, 2005, pp. 2007-2022
- [6] Adrian, V. and Bah-Hwee Gwee and Chang, J.S, "A Review of Design Methods for Digital Modulators," in *Integrated Circuits, 2007. ISIC '07. International Symposium on*, 2007, pp. 85-88