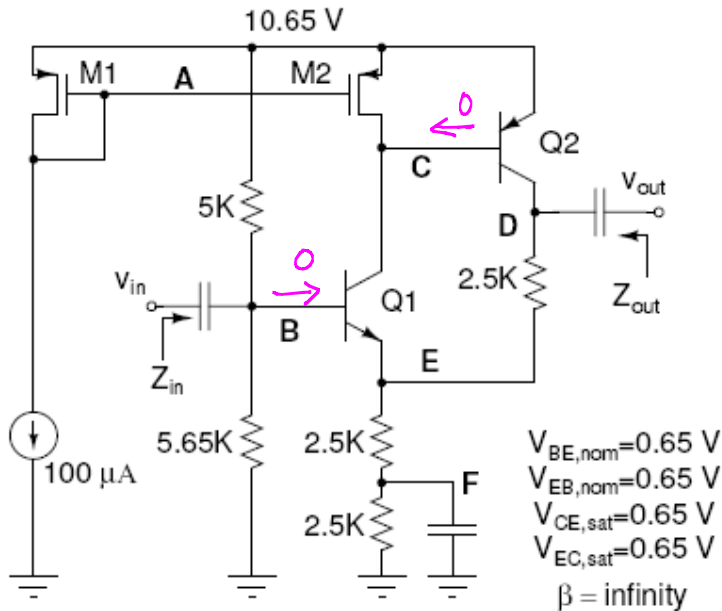


QUIZ 2 : Solutions

Note Title

10/21/2007



$$V_{TP} = 0.45 \text{ V}$$

$$(1/2)\mu C_{ox}(W/L) = 2.5 \text{ mA/V}^2$$

Figure 1: Circuit diagram for Problem 1.

$$(a) \quad V_B = \frac{5.65K}{5.65K + 5K} \cdot 10.65$$

$$= 5.65 \text{ V}$$

$$V_E = V_B - 0.65 \text{ V}$$

$$= 5 \text{ V}$$

$$V_F = \frac{V_E \cdot 2.5K}{2.5K + 2.5K}$$

$$= 2.5 \text{ V}$$

$$V_C = 10.65 - 0.65 \text{ V}$$

$$= 10 \text{ V}$$


$$\text{For } M1, \quad 100 \mu\text{A} = \frac{2500 \mu\text{A}}{\text{V}^2} (V_{SG} - 0.45)^2$$

$$\Rightarrow V_{SG} - 0.45 = 0.2 \text{ V}$$

$$\Rightarrow V_{SG} = 0.65 \text{ V}$$

$$V_A = 10.65 - V_{SG}$$

$$= 10 \text{ V}$$

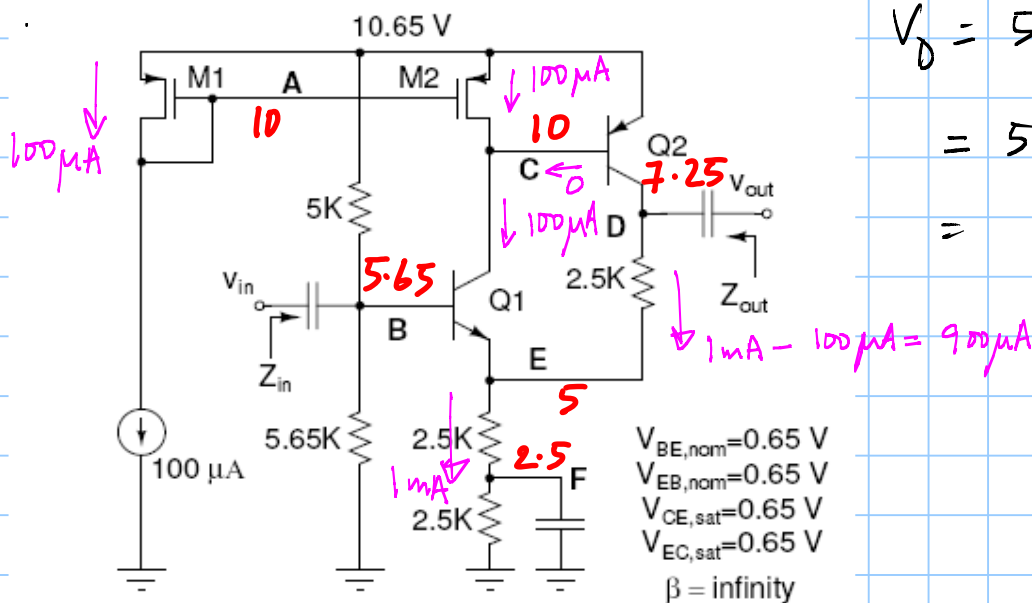

$$\begin{aligned}
 V_D &= 5 + 0.9 \text{ mA} \cdot 2.5 \text{ K} \\
 &= 5 + 2.25 \\
 &= 7.25 \text{ V}
 \end{aligned}$$

$$V_{TP} = 0.45 \text{ V} \quad (1/2)\mu C_{ox}(W/L) = 2.5 \text{ mA/V}^2$$


Figure 1: Circuit diagram for Problem 1.

(b) Quiescent currents:

$$I_{M1} = 100 \mu\text{A} \quad I_{M2} = 100 \mu\text{A}$$

$$I_{Q1} = 100 \mu\text{A} \quad I_{Q2} = 900 \mu\text{A}$$

(c) Now replace all devices by their small signal equivalent circuits.

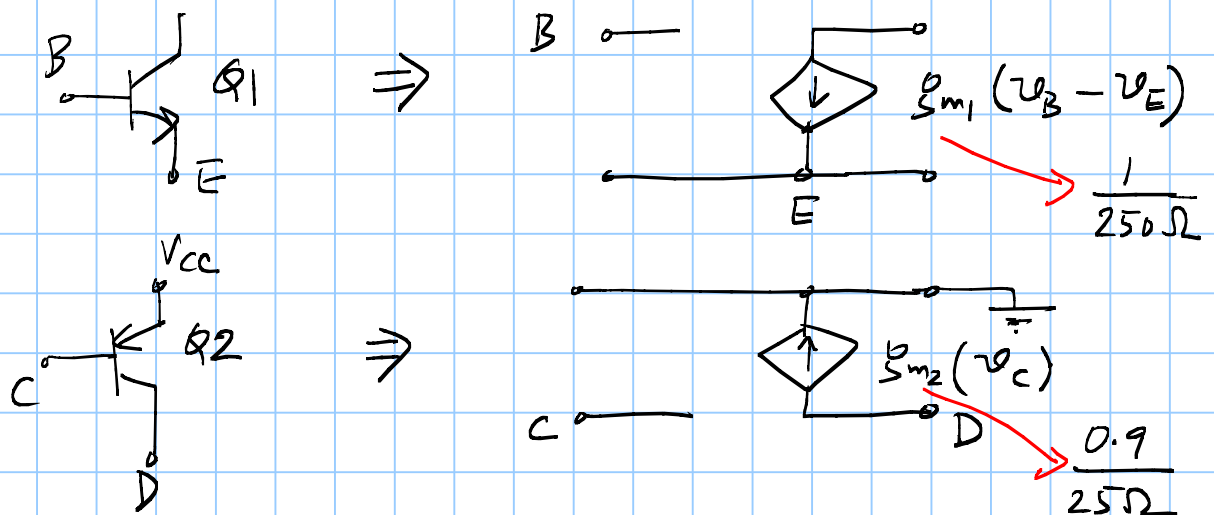


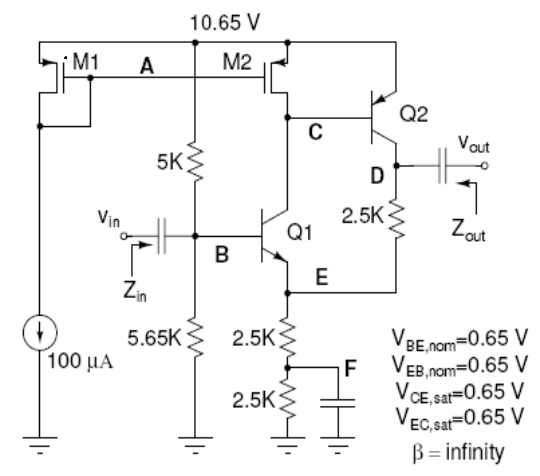


Figure 1: Circuit diagram for Problem 1.

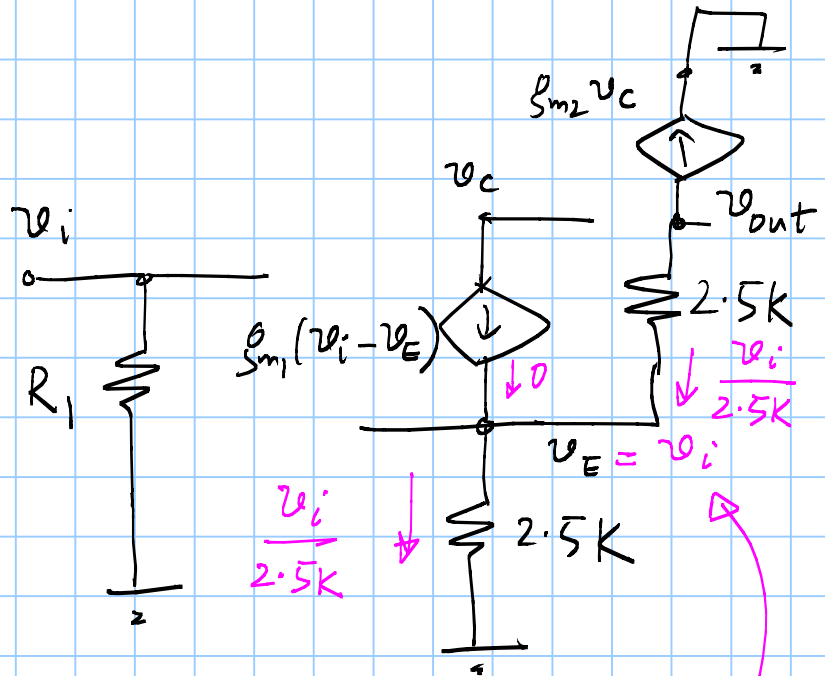

$$R_1 = 5.65k \parallel 5k$$

KCL at v_c

$$g_{m1}(v_i - v_E) = 0$$

$$\Rightarrow v_E = v_i$$


$$v_{out} = v_E + \frac{v_E \cdot 2.5K}{2.5K}$$

$$= v_i + v_i = 2v_i$$

$$\Rightarrow \text{Incremental Gain} = 2$$

(d)

Z_{in}

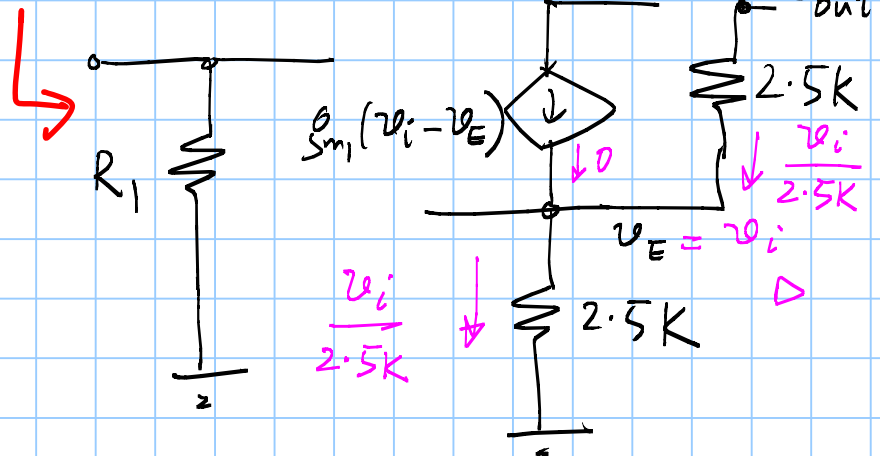

$$R_1 = 5.65k \parallel 5k$$


$$Z_{in} = R_1$$

$$= 5.65k \parallel 5k$$

$$= \frac{5.65 \times 5}{10.65}$$

$$= 2.653 \text{ k}\Omega$$

Finding Z_{out}

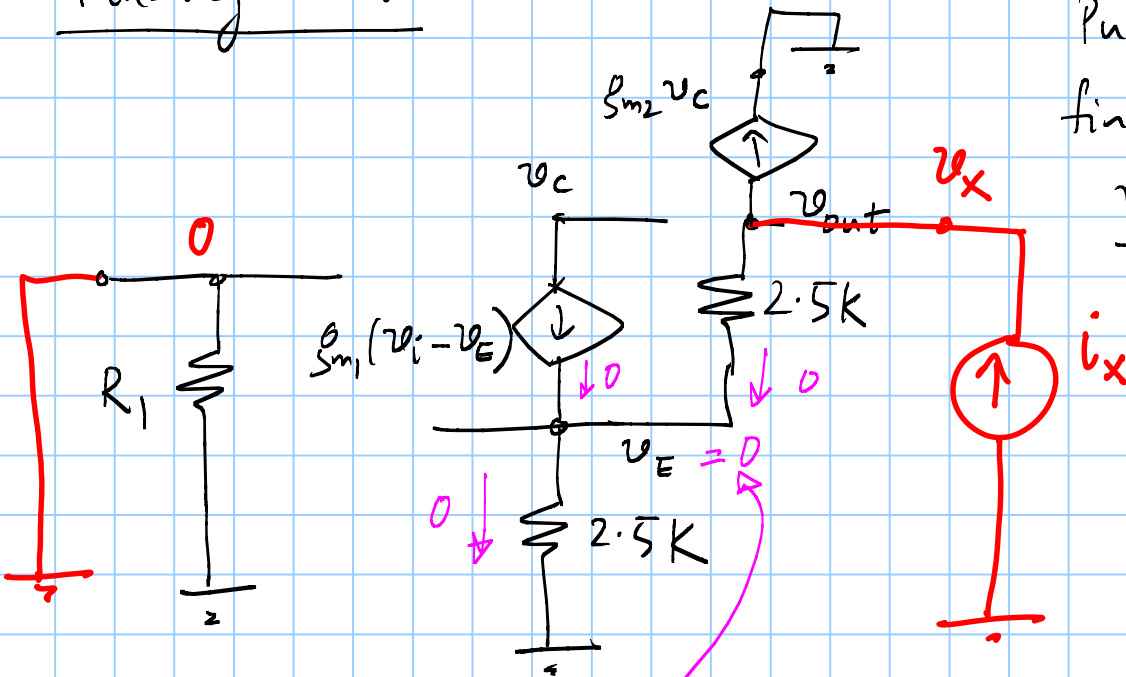


Push i_x ,
find v_x .

$$\frac{v_x}{i_x} = Z_{out}$$

Remember, $v_E = v_i = 0 \Rightarrow v_x = 0 \Rightarrow Z_{out} = 0$
 (What happens to i_x ?)

(e). Swing Limits

First, find all small signal quantities

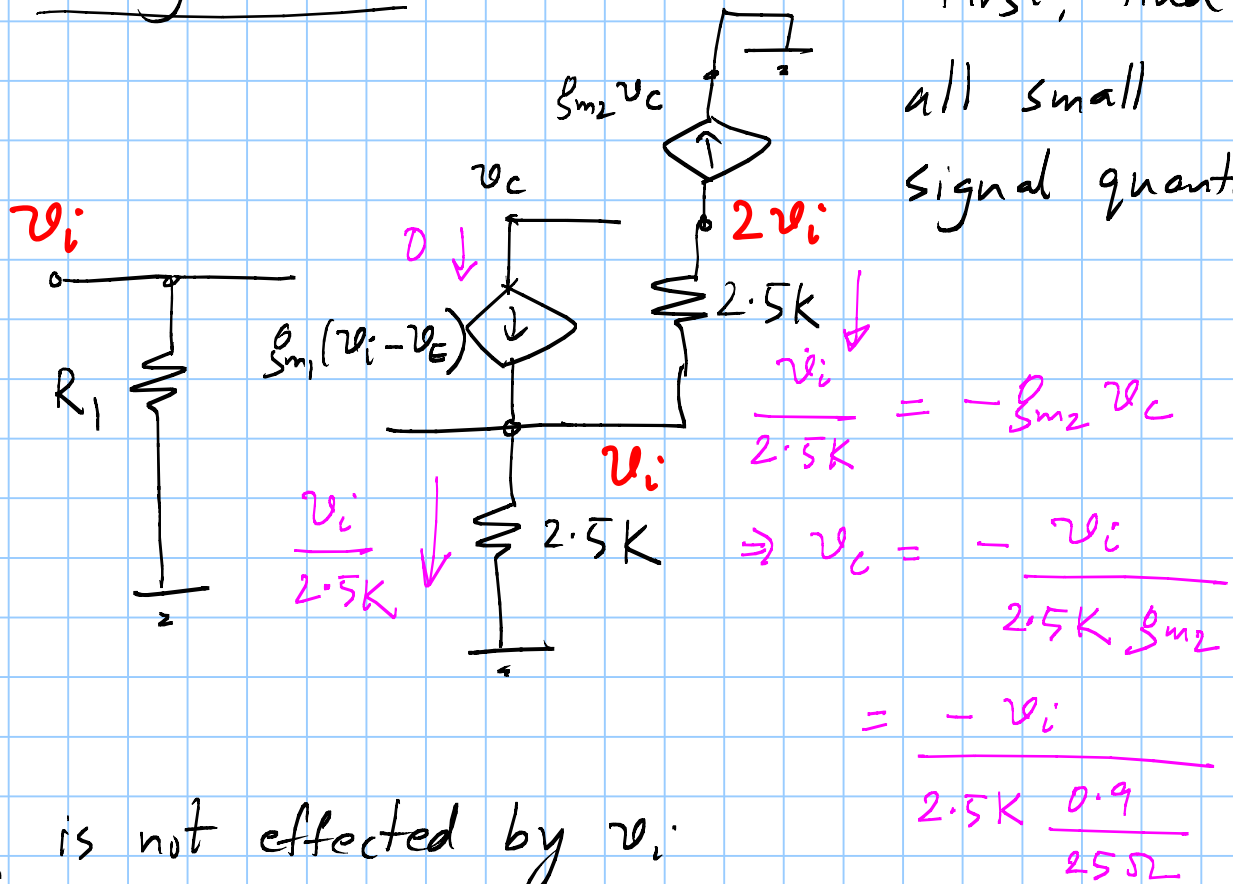

M1 is not effected by v_i :

\Rightarrow It cannot influence swings

M2 : Total drain current = Quiescent $\left. \vphantom{\begin{matrix} \text{Total} \\ \text{drain} \\ \text{current} \end{matrix}} \right\} 100\mu$
+ Incremental $\left. \vphantom{\begin{matrix} \text{Total} \\ \text{drain} \\ \text{current} \end{matrix}} \right\} 0$

$\Rightarrow I_{M2} = \text{constant}$

$$V_{SD, M2} = 10.65 - \left[\begin{array}{l} \text{Quiescent drain voltage} \\ + \text{Incremental drain voltage} \end{array} \right]$$
$$= 10.65 - \left[\begin{array}{l} 10 \\ + v_c \end{array} \right] = 0.65 - v_c$$
$$= 0.65 + v_i / 90$$

For M2 to get into triode,

$$v_i = 90 \times 0.65 \approx 58.5V !$$

Q1:

$$I_c = \left. \begin{array}{l} 100 \mu A \\ + \text{increment} \end{array} \right\} = 100 \mu A$$

Q1 does not go into cutoff.

$$\begin{aligned} V_{CE} &= V_C - V_E \\ &= 10 + \frac{v_i}{90} - [5 + v_i] \\ &= 5 - \frac{89}{90} v_i \end{aligned}$$

\Rightarrow Q1 gets saturated when $V_{CE} = 0.65$

$$5 - \frac{89}{90} v_i = 0.65$$

$$\Rightarrow v_i \approx 4.35 \text{ V}$$

Q2:

$$I_c = \underbrace{900 \mu A}_{\text{Quiescent}} + \underbrace{\frac{v_i}{2.5K}}_{\text{Increment}}$$

For cutoff, $v_i = 2.5K \cdot 0.9 \text{ mA}$

$$\Rightarrow v_i = 2.25 \text{ V}$$

Base potential of Q2 = $10 + \frac{v_i}{90}$

Collector potential = $7.25 + 2v_i$

\Rightarrow Q2 is saturated when $7.25 + 2v_i = 10 + \frac{v_i}{90}$

$$\Rightarrow v_i = 2.75 / (2 + 1/90)$$

$$\Rightarrow v_i = 1.37 \text{ V}$$

The largest amplitude of the Sinewave that results in distortion free operation is $\min \{58.5, 4.35, 2.25, 1.37\}$

Largest permissible amplitude is 1.37 V

I-

Problem 1

Answers

(a)	A	10 V	B	5.65 V	1
	C	10 V	D	7.25 V	1
	E	5 V	F	2.5 V	1
(b)	M1	$100\text{ }\mu\text{A}$	M2	$100\text{ }\mu\text{A}$	1
	Q1	$100\text{ }\mu\text{A}$	Q2	$900\text{ }\mu\text{A}$	1
(c)	v_{out}/v_{in}		2		5
(d)	Z_{in}	$= 2.653\text{ K}$	Z_{out}	$= 0$	4
(e)	Max. amplitude		1.37 V		6