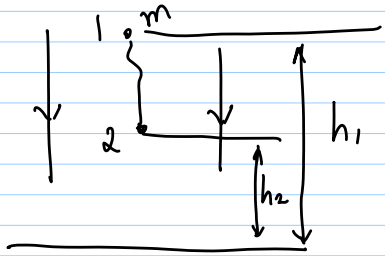



13/1/15

Lec 1

13-01-2015



$$\Delta E = mg(h_1 - h_2)$$

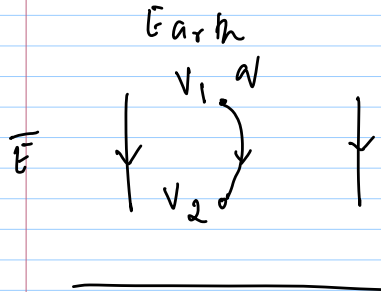

$\Delta E \Rightarrow$ potential difference
 \Rightarrow voltage
 $\Delta E = q(V_1 - V_2)$

Physics

EE


q & \bar{E}

I & V



$I =$ rate of flow of charge
 $= \frac{dq}{dt}$

* Electromagnetic Fields
 * Solid State Devices

Electrical elements

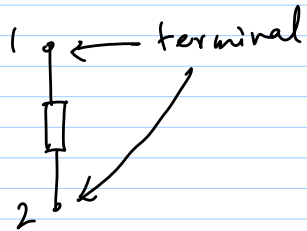


2-T element

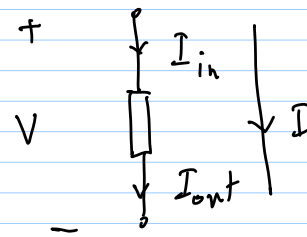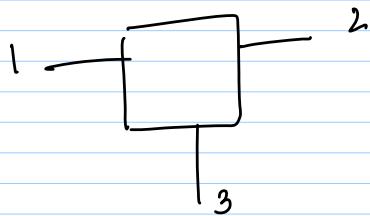

+ no accumulation of charge
 $I_{in} = I_{out}$


$$I = f(V)$$

$$V = g(I)$$

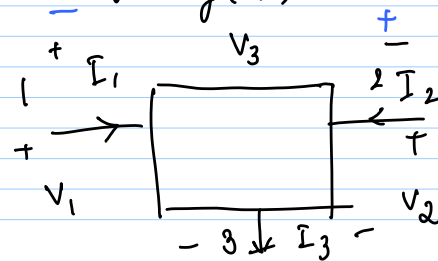


$$I_3 = I_1 + I_2$$

$$V_3 = V_1 - V_2$$

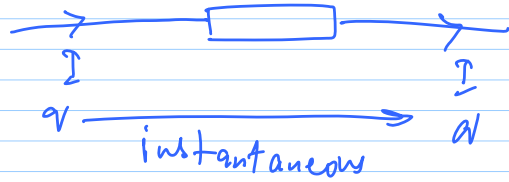

Kirchhoff's Laws

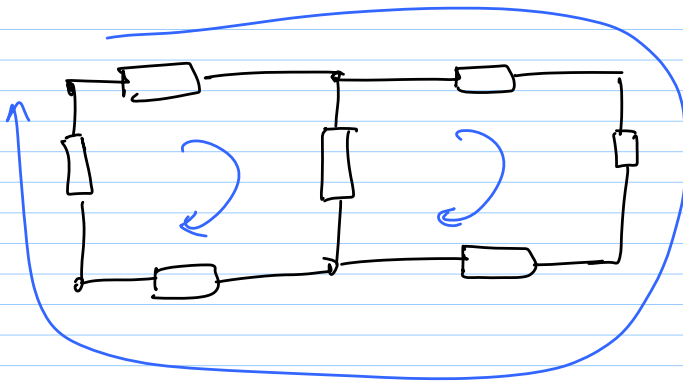- 1) Kirchhoff's Voltage Law (KVL)
- 2) Kirchhoff's Current Law (KCL)




KVL

$$\sum V_{\text{around a loop}} = 0$$


Electrical Circuit

Interconnection of 2 or more elements

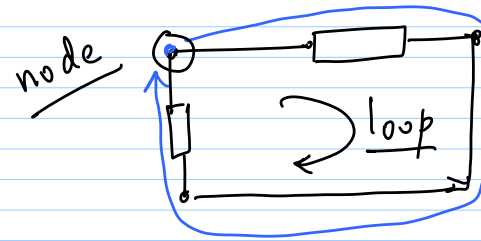

node - point of connection between 2 terminals of diff. elements

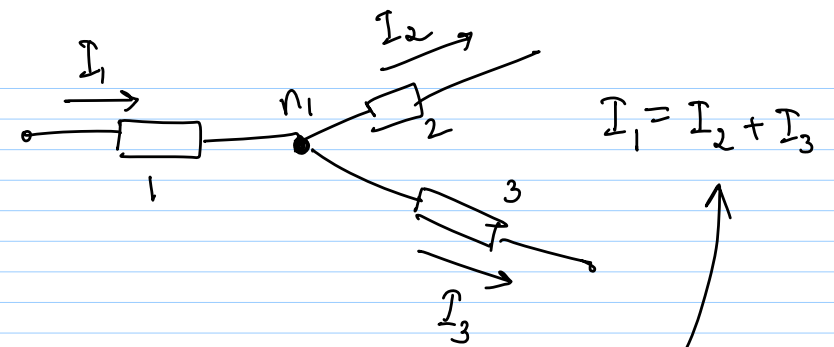
loop - start from a node
traverse through elements
arrive back @ same node



KCL


$$\sum I_{\text{entering a node}} = 0$$

@ n_1 $I_1 + (-I_2) + (-I_3) = 0$

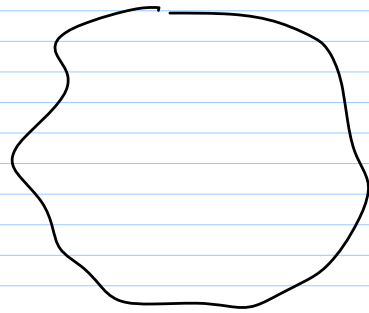

N nodes


M loops

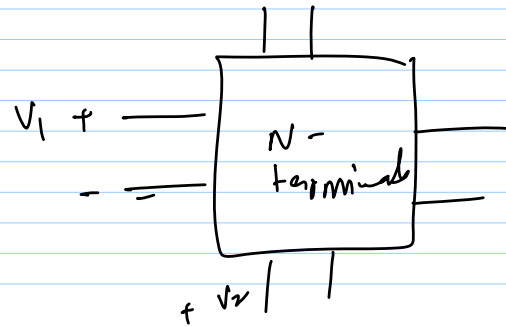

N terminals

2-T elements


1) Resistor

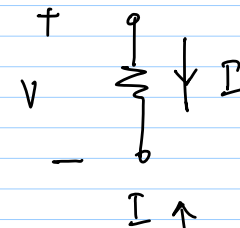


$V = IR$ ← resistance (Ω)

$I = G \cdot V$; $G = 1/R$

↑ conductance (S)

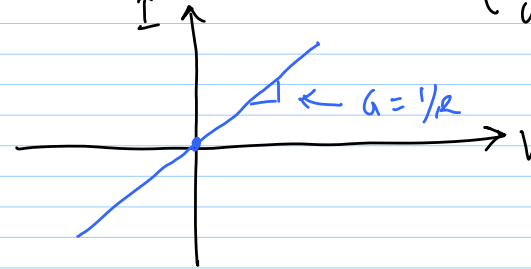


2) Capacitor

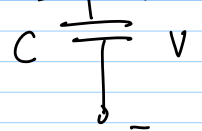


$I = C \frac{dV}{dt}$


3) Inductor

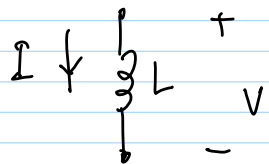


$V = L \frac{dI}{dt}$

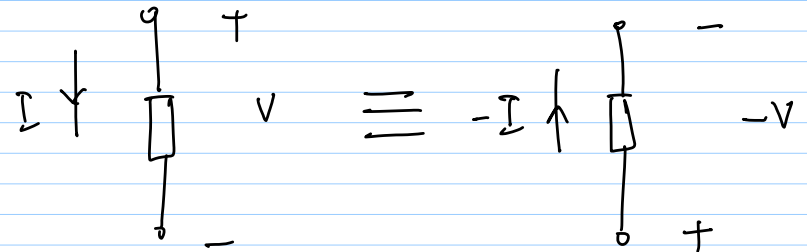


4) Voltage Source

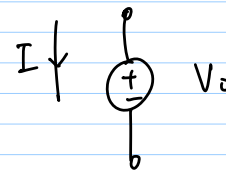

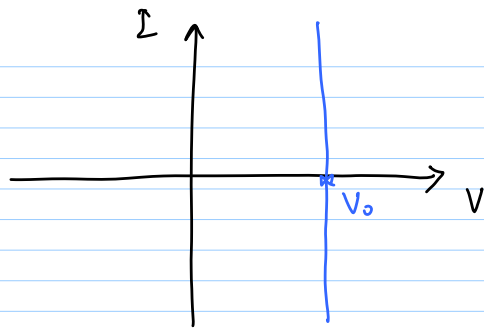pot. diff. across terminals is V_0 regardless of I



5) Current Source

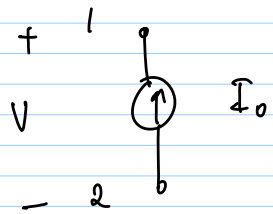

Current through element
independent of V

