

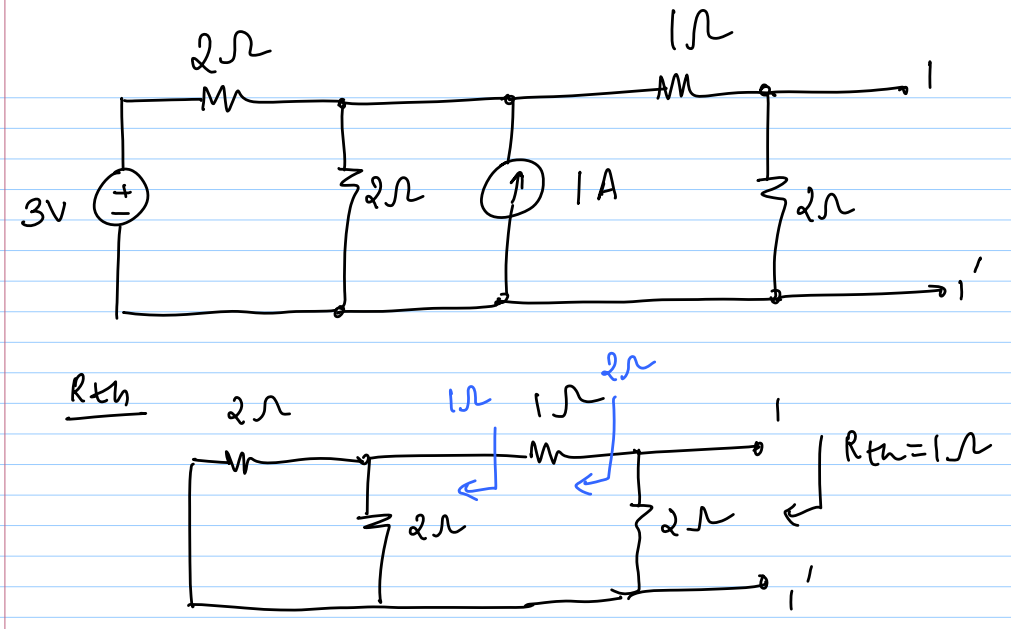
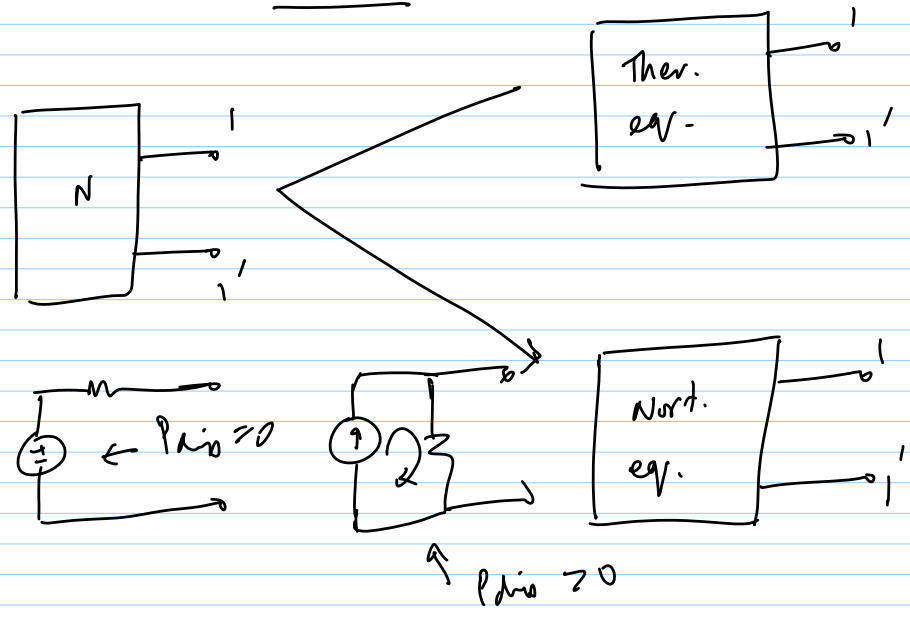
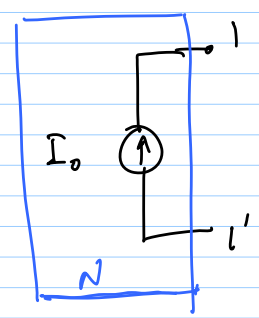


5-2-15

Lec 12

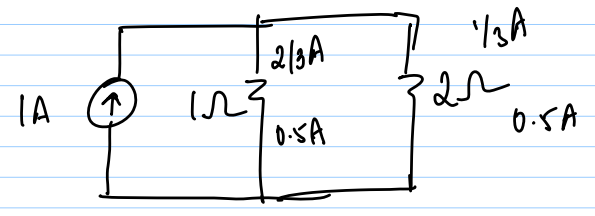


$V_{th} : V_{o.c.} = 5/4V$

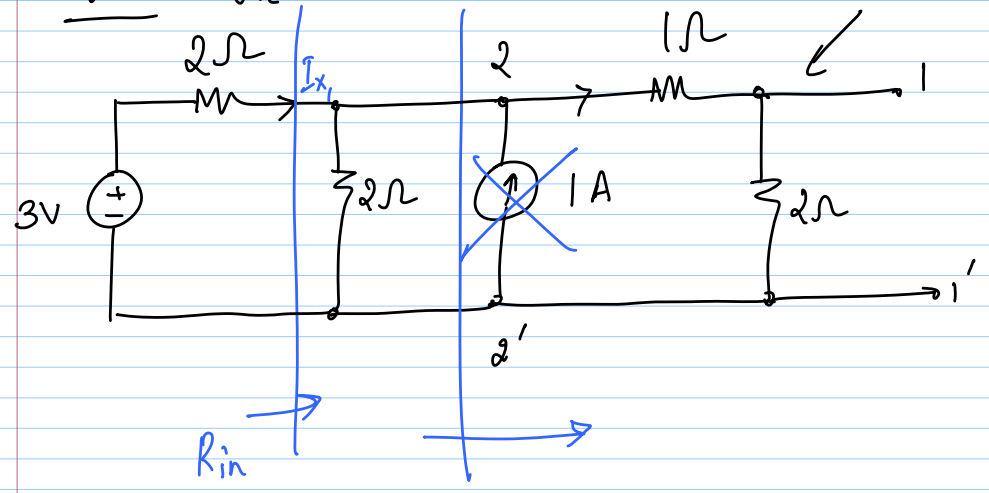

$R_{th} = \infty$


$V_{th} = \infty$

$I_0 = \frac{V_m}{R_m}$

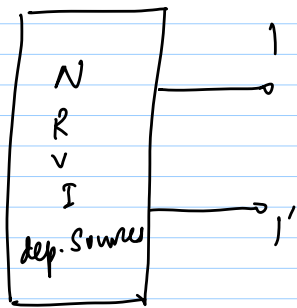



$$V_{th} : V_{o.c.}$$

$$R_{th} :$$

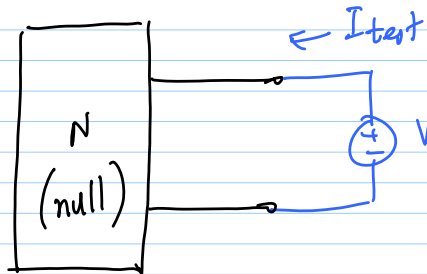


$$R_{th} = \frac{V_{test}}{I_{test}}$$

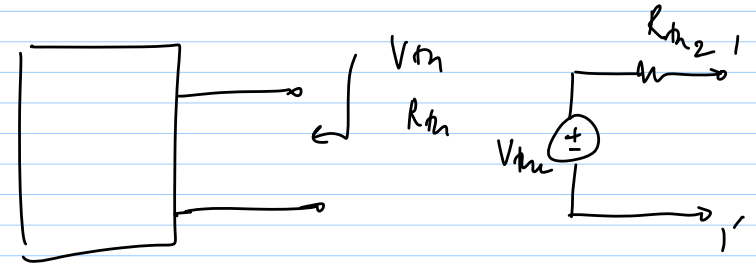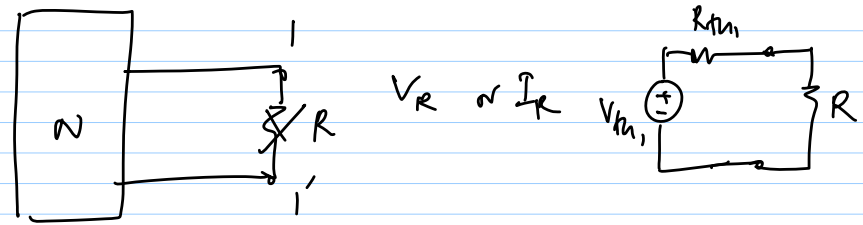alternatively apply I_{test} & measure V_{test}



Maximum power transfer theorem

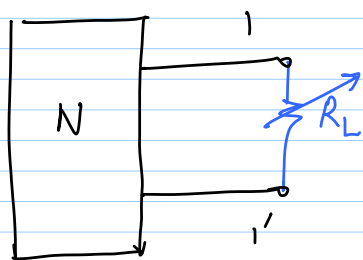


Objective: Maximise power delivered to R_L

$$P_L = V_L I_L$$

$$P_L = \frac{R_L V_{th}}{R_L + R_{th}} \cdot \frac{V_{th}}{R_L + R_{th}}$$
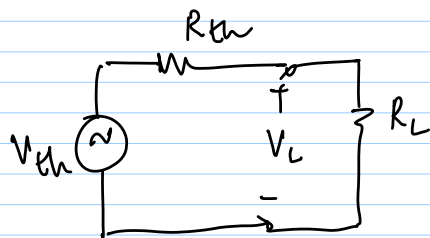
$$= V_{th}^2 \cdot \frac{R_L}{(R_L + R_{th})^2}$$



$R_L = R_{th}$ gives maximum P_L

$$P_L = V_{th}^2 \cdot \frac{R_L}{(R_L + R_{th})^2}$$

$$= \frac{V_{th}^2}{R_{th}} \cdot \frac{R_L}{\left(\frac{R_L}{\sqrt{R_{th}}} + \sqrt{R_{th}}\right)^2}$$

$$= \frac{V_{th}^2}{R_{th}} \cdot \frac{1}{\left(\sqrt{\frac{R_L}{R_{th}}} + \sqrt{\frac{R_{th}}{R_L}}\right)^2} \quad \swarrow R_L = R_{th}$$