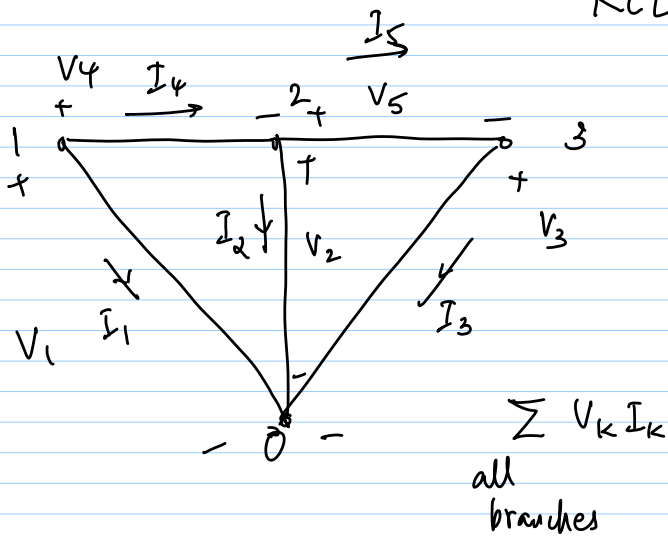



7/2/15

Lec 13

KCL: $\sum_n I_{\text{leaving}} = 0$
node



name nodes 1, 2, 3 ... N

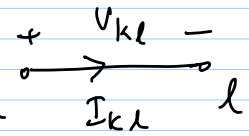

current leaving k, entering l

$\sum_{\text{all branches}} V_{kl} \cdot I_{kl} = \sum (V_k - V_l) I_{kl}$


$$= \sum_m \left\{ V_m \sum_k I_{mk} \right\} - \left\{ V_m \sum_k I_{km} \right\}$$

all nodes $m=1 \dots N$ currents leaving m (under the first sum), currents entering m (under the second sum)

Tellegen's theorem


1) $\sum_k V_k I_k = 0$

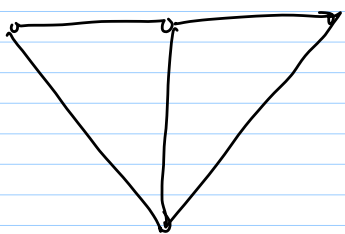2) N, \hat{N} : 2 networks that have same graph



$\sum V_k \hat{I}_k$

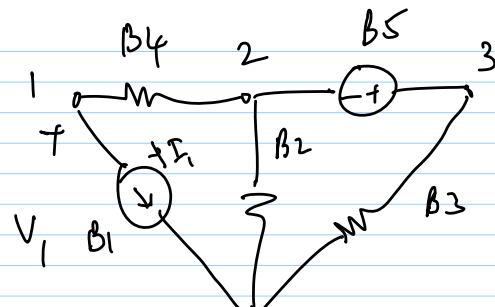
N : V_k, I_k
 \hat{N} : \hat{V}_k, \hat{I}_k



I_1, I_2, \dots, I_5


N

$\sum V_k \hat{I}_k$

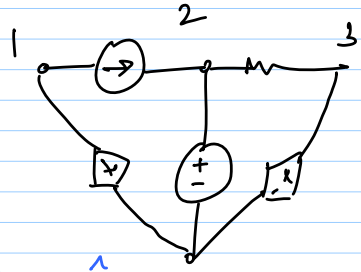

$\hat{I}_1, \hat{I}_2, \dots, \hat{I}_5$


\hat{N}

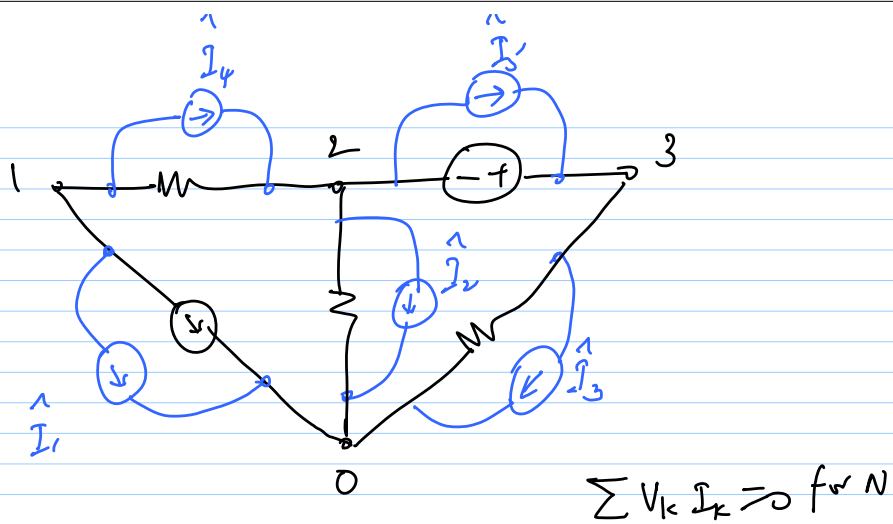

$$\sum V_k I_k = 0 \text{ for } N$$

$$\sum_B V_k [I_k + \hat{I}_k] = 0 \Rightarrow \boxed{\sum_B V_k \hat{I}_k = 0}$$
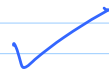
$$\boxed{\begin{aligned} \sum V_k \hat{I}_k &= 0 \\ \sum \hat{V}_k I_k &= 0 \end{aligned}}$$



$$\begin{matrix} N & & N \\ \downarrow & & \downarrow \\ V_k, I_k & & \hat{V}_k, \hat{I}_k \end{matrix}$$

$$\boxed{\sum_B V_k(t_1) \cdot \hat{I}_k(t_2) = 0}$$

