

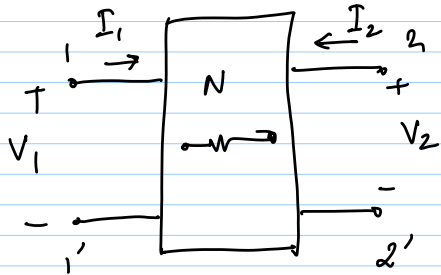


10-2-15


Lec 14

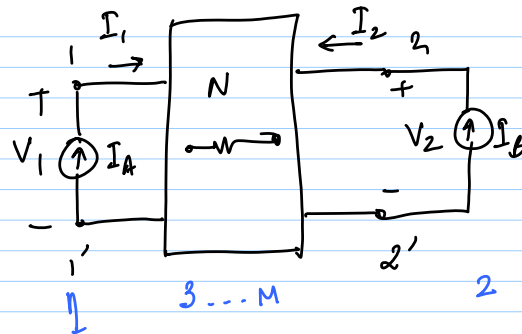


2-port network

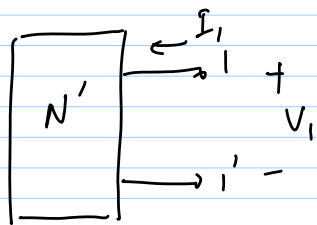

Case 1 $I_B = 0$

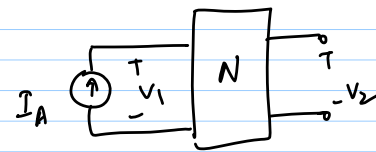

Case 2 $I_A = 0$

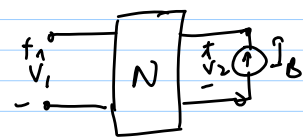

① $\sum V_k \hat{I}_k = 0$

$V_1(0) + V_2(-I_B) + \sum_3^M V_k \hat{I}_k = 0$

② $\sum \hat{V}_k I_k = 0$

$\hat{V}_1(-I_A) + \hat{V}_2(0) + \sum_3^M \hat{V}_k I_k = 0$

① $\sum V_k \hat{I}_k = 0$

$V_1 \cdot (0) + V_2 \cdot (-I_B) + \sum_3^M V_k \hat{I}_k = 0$

② $\sum \hat{V}_k I_k = 0$

$\hat{V}_1 \cdot (-I_A) + \hat{V}_2(0) + \sum_3^M \hat{V}_k I_k = 0$

③ N is resistive

$$\left. \begin{aligned} V_k &= R_k I_k \\ \hat{V}_k &= R_k \hat{I}_k \end{aligned} \right\}$$

Ⓐ : $\sum_3^M V_k \hat{I}_k = \sum_3^M R_k I_k \hat{I}_k$

Ⓑ : $\sum_3^M \hat{V}_k I_k = \sum_3^M R_k \hat{I}_k I_k$

$\therefore V_2 \cdot I_B = \hat{V}_1 \cdot I_A$

$$\boxed{\frac{V_2}{I_A} = \frac{\hat{V}_1}{I_B}}$$

Reciprocity
Theorem

"Reciprocal networks"

