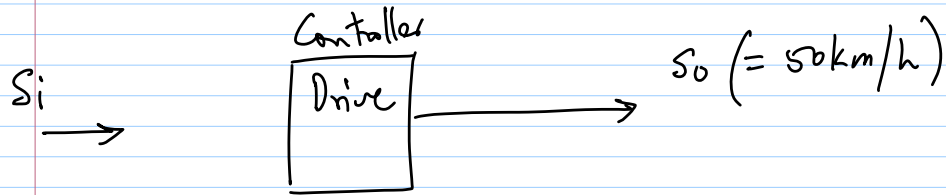






2/3/15

Lec 20


Negative Feedback



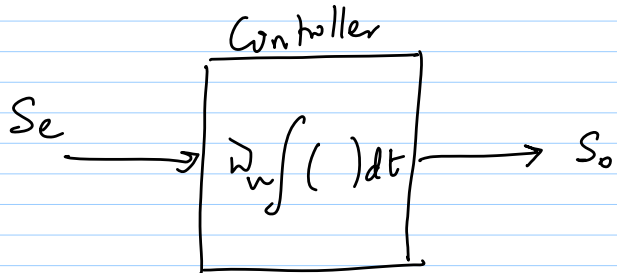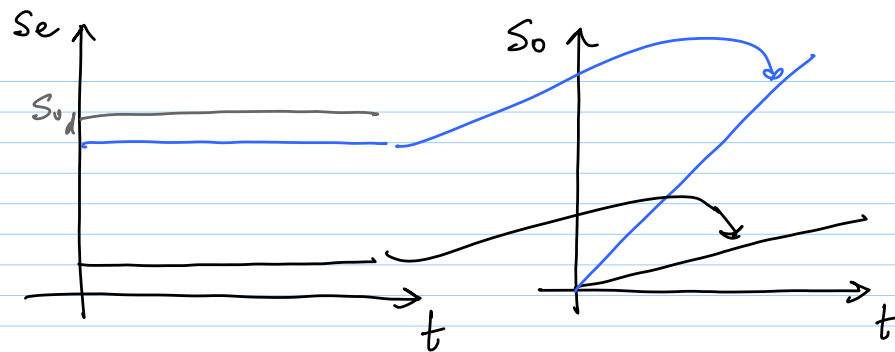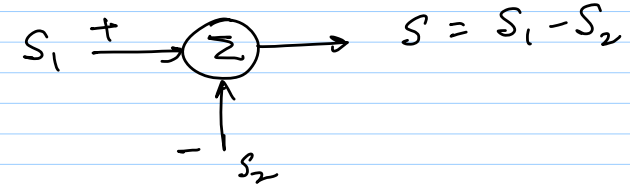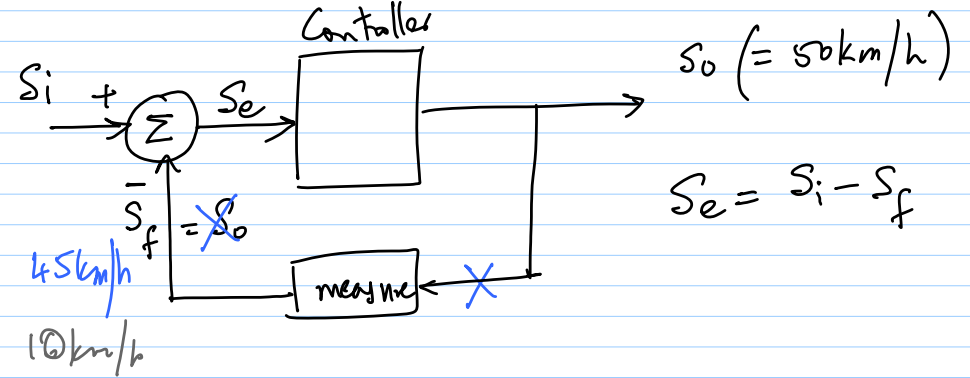- \* Measurement of o/p qty
- \* Compare actual value with desired value
- \* Drive actual value towards desired value



Amplifier of gain 'k' ;  $V_o = kV_i$

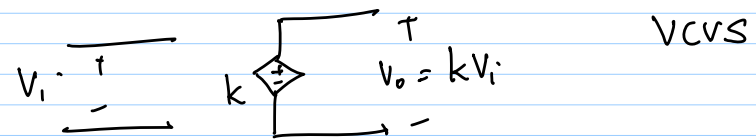

$[Y] = \begin{bmatrix} \text{small} & \text{small} \\ \text{large} & \text{small} \end{bmatrix} = \text{VCCS}$

