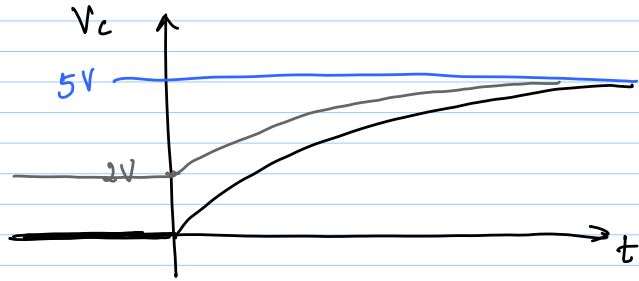


12-3-15


Lec 24



$V_c(0) = 0$
 $\text{slope}(t=0) = \frac{5}{RC}$

$V_c(0) = 2V$
 $\text{slope}(t=0) = \frac{3}{RC}$

$V_c(0^+) = V_c(0^-)$

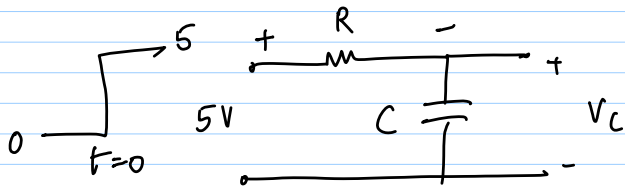


$V_R(0^+) = 3V$




$I_R(0^+) = \frac{3}{R}$

$\frac{dV_c}{dt}(0^+) = \frac{3}{RC}$

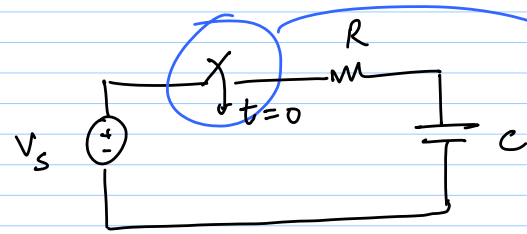$V_c(t) = V_s + (V_c(0) - V_s) \exp\left(-\frac{t}{RC}\right)$









ideal switch 'S'
 S off O.C
 S on S.C

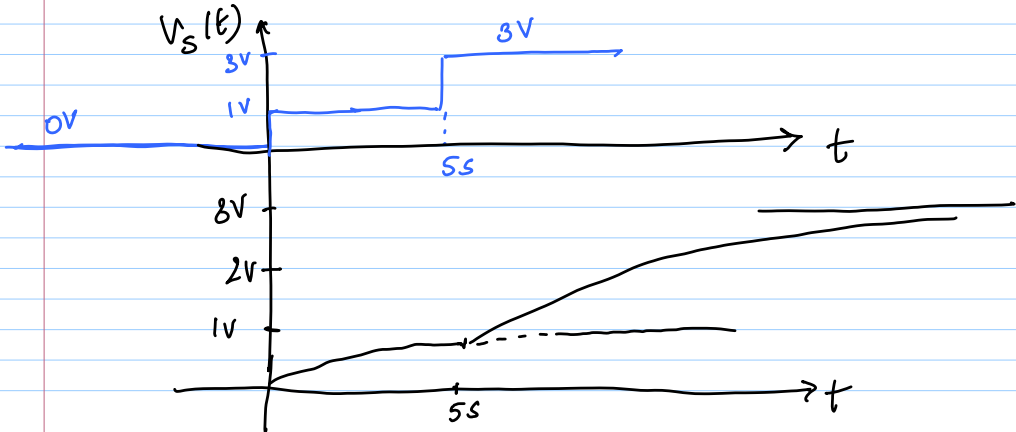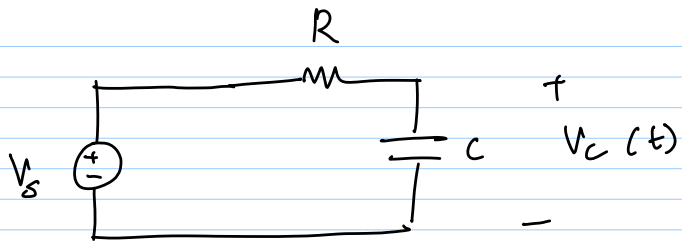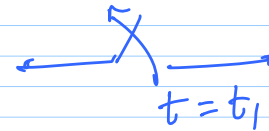

$V_c(t) = 0, t < 0$

$V_c(t) = 1V (1 - \exp(-t/RC)) ; 0 < t < 5s$

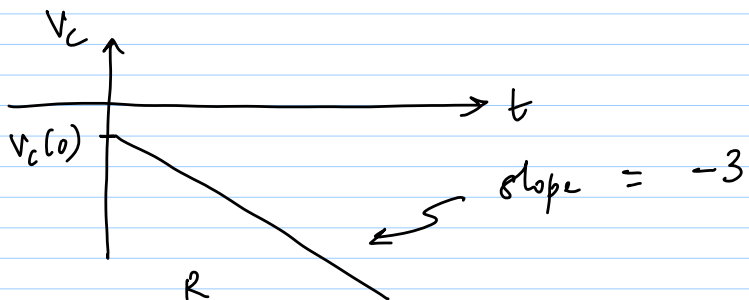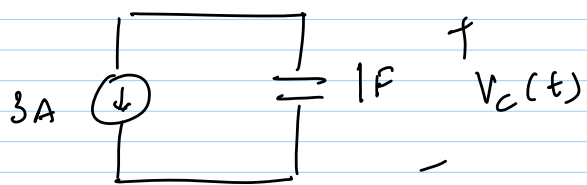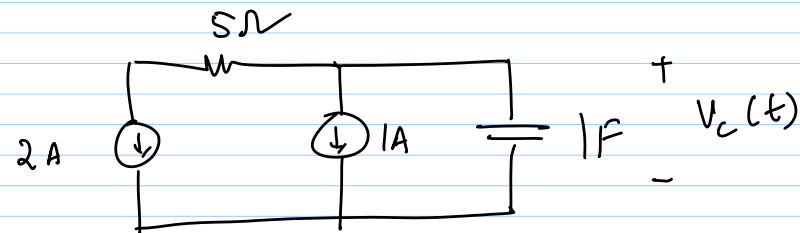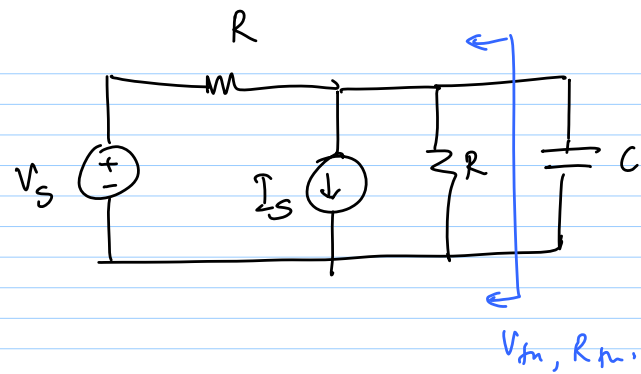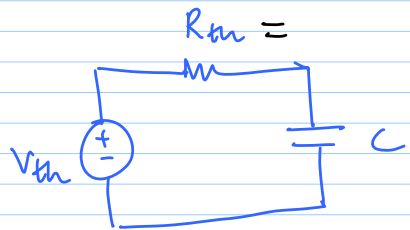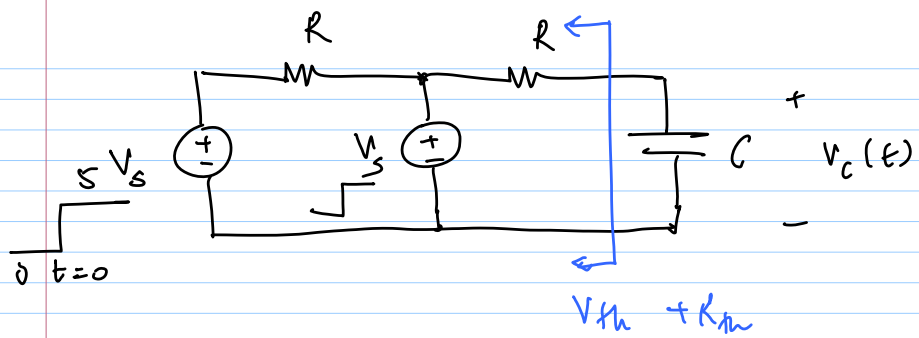$V_c(t) = 3 + (V_c(5) - 3V) \exp(-\frac{t-5s}{RC}) ; t > 5s$



I_R, V_A, I_C
 same time const. RC
 same homogy. eq.

