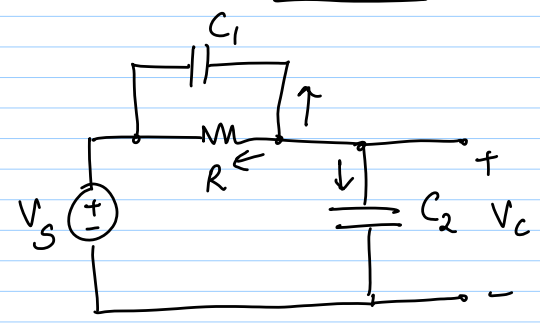


13/3/15

Lec 25



$$C_2 \frac{dV_c}{dt} + \frac{V_c - V_s}{R} + C_1 \frac{d}{dt}(V_c - V_s) = 0$$



$$(C_1 + C_2) \frac{dV_c}{dt} + \frac{V_c}{R} = \frac{V_s}{R} + C_1 \frac{dV_s}{dt}$$

$$R(C_1 + C_2) \frac{dV_c}{dt} + V_c = V_s + RC_1 \frac{dV_s}{dt}$$



→ 1st order system

→ $R(C_1 + C_2)$ is the time constant

If you set $V_s = 0$

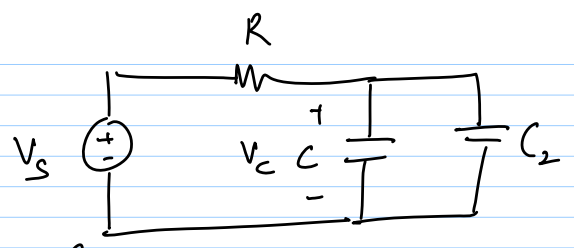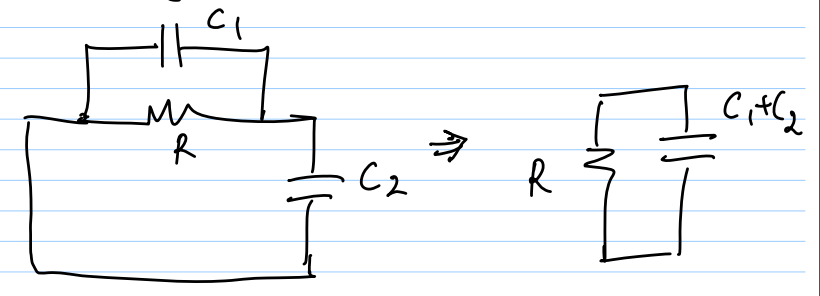


$V_c(0^-) = 0$
 $V_c(0^+) = 0$

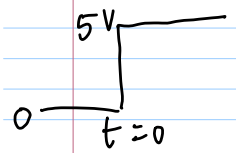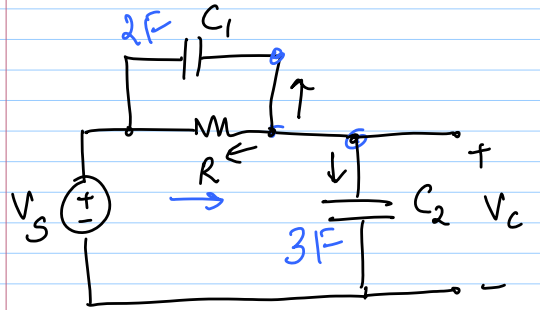


Charge conservation @ $t=0$

$Q(t=0) = 0$

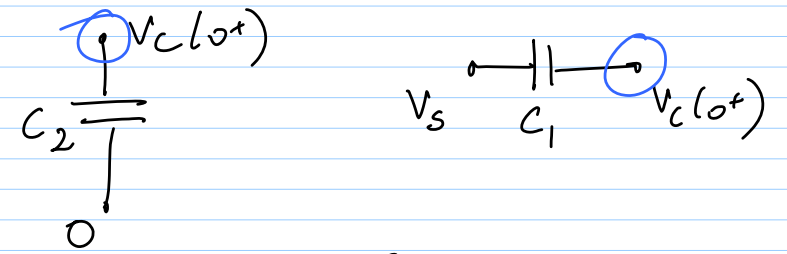$C_2 V_c(0^+) + C_1 (V_c(0^+) - V_s) = 0$



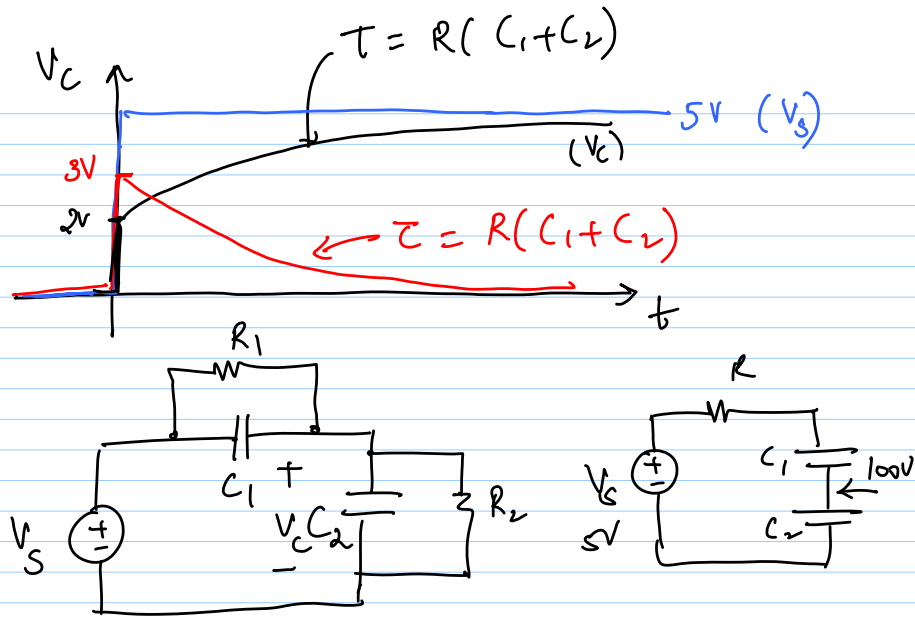$V_c(0^+) = \frac{C_1}{C_1 + C_2} \cdot V_s = 2V$




Step response of a 1st order ckt

- 1) Determine time constant $\tau = R_{in} \cdot C_{eff}$.
 { Set sources to 0 }
- 2) Initial conditions + ckt analysis
 $\Rightarrow V/I @ t=0$
- 3) At $t=0^+$: determine any discontinuities in capacitor voltages @ $t=0$
 - identify voltage source - cap. loops
 - open ckt Resistors & determine cap voltages

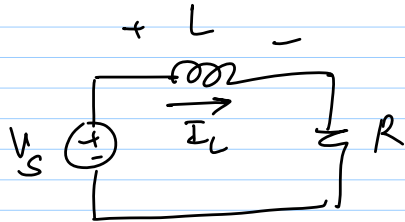- 4) Determine values @ $t=\infty$
 - open ckt all capacitors

$$V_x = V_x(\infty) + [V_x(0^+) - V_x(\infty)] \exp\left(\frac{-t}{\tau}\right)$$



$$V_s - I_L \cdot R = L \frac{dI_L}{dt}$$

$$\frac{L}{R} \frac{dI_L}{dt} + I_L = \frac{V_s}{R}$$

$$\tau = \frac{L}{R}$$

