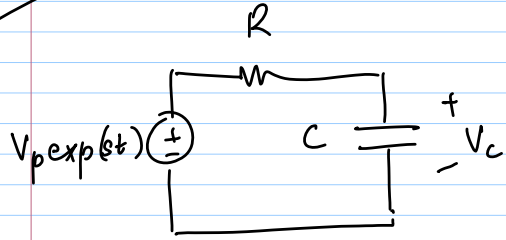


16/3/15

Lec 26



$$RC \frac{dV_c}{dt} + V_c = V_p \exp(st) \quad \text{--- (1)}$$

$$V_{c1} = V_c - V_p \exp(st)$$

$$RC \frac{dV_{c1}}{dt} + V_{c1} = -sCR V_p \exp(st) \quad \text{--- (2)}$$


input $e^{st} \exp(st)$

output (SSR) = scaled version.

Linear system

SSR — obeys superposition

TR — does not

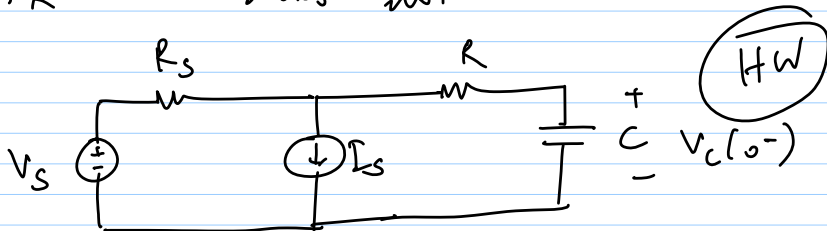

apply superposition.

(1) x SCR + (2) gives:

$$RC \frac{d}{dt} [V_{c1} + sCR V_c] + [V_{c1} + sCR V_c] = 0$$

$$V_{c2} = V_{c1} + sCR V_c$$


$$V_{c2} = V_{c20} \exp(-t/RC)$$

$$= sCR V_c + V_c - V_p \exp(st)$$

$$V_c(t) = \frac{V_p \exp(st)}{1+sCR} + (V_0) \exp(-\frac{t}{RC})$$

forced response

natural response
(initial condition)

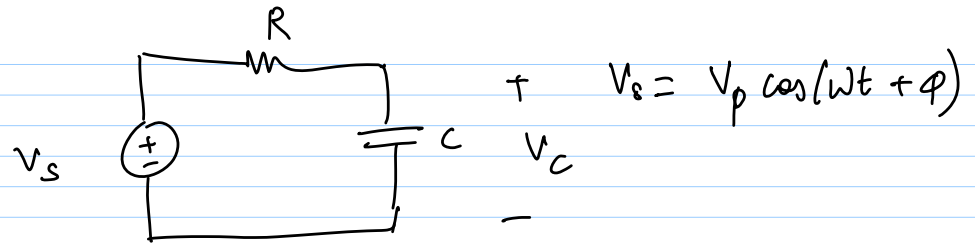

Ⓡ

$$RC \frac{dV_c}{dt} + V_c = V_p \cos(\omega t + \phi)$$

$$V_c = \alpha \cos(\omega t + \phi) + \beta \sin(\omega t + \phi)$$

equate sine & cosine coefficients

II

$$\sqrt{-1} = i \quad X$$

$$\text{in EE} \quad \sqrt{-1} = j$$


$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$V_p \cos(\omega t + \phi) = \frac{V_p}{2} \left[\exp(j(\omega t + \phi)) + \exp(-j(\omega t + \phi)) \right]$$


$$\text{set } s = j\omega$$

$$V_p' = \frac{V_p}{2} \exp(j\phi)$$

III

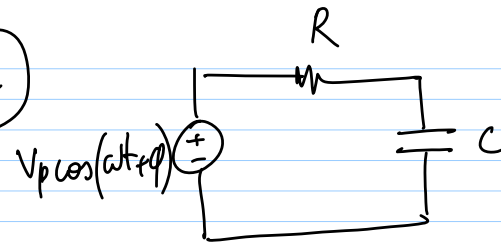
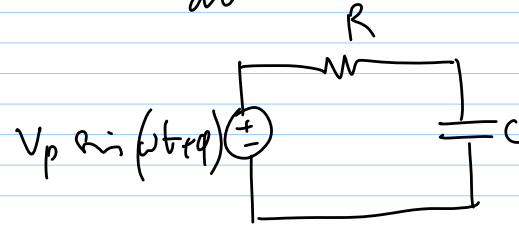
$$RC \frac{dV_c}{dt} + V_c = V_p \cos(\omega t + \phi) \quad \text{--- (3)}$$



$$RC \frac{dV_c}{dt} + V_c = V_p \sin(\omega t + \phi) \quad \text{--- (4)}$$

$$1 \times (3) + j \times (4)$$

$$\text{input} = V_p \exp(j(\omega t + \phi))$$

$$V_p \exp(st) \rightarrow \frac{V_p}{1 + sCR} \cdot \exp(st)$$

$$s = j\omega$$

$$\text{output} = \frac{V_p \exp(j\phi)}{1 + j\omega CR} \exp(j\omega t)$$

$$V_c = \frac{V_p}{1 + j\omega CR} \exp(j(\omega t + \phi))$$

Output when input is $V_p \cos(\omega t + \phi)$:

$$V_{c1} = \text{Re} \{ V_c \} \quad \leftarrow \text{corresponds to cosine input}$$

$$x + jy = A e^{j\theta}$$

$$V_{c1} = \frac{V_p}{\sqrt{1 + (\omega RC)^2}} \cdot \cos \left[\omega t + \phi - \tan^{-1}(\omega RC) \right]$$

"sinusoidal steady state response"