

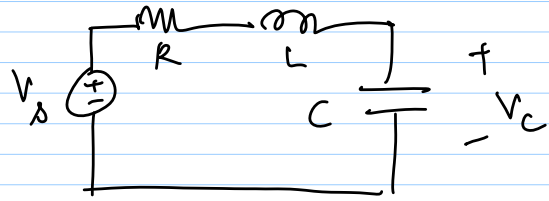


20/3/15

Lec 28

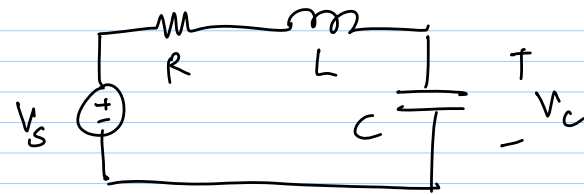



$\zeta < 1$
 $\zeta = 1$
 $\zeta > 1$

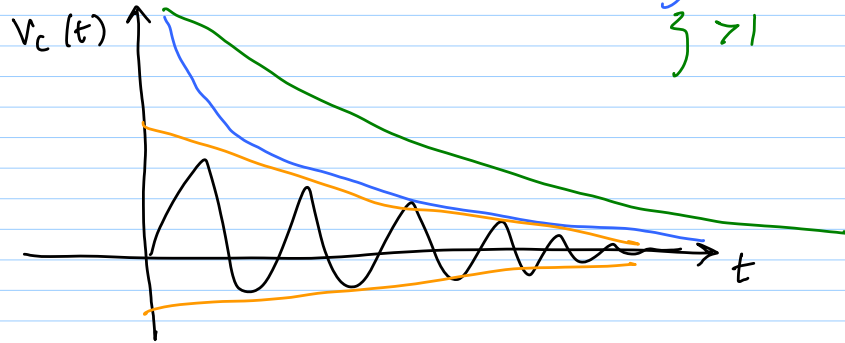

$\omega_n = 1/\sqrt{LC}$ L, C - fixed

$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

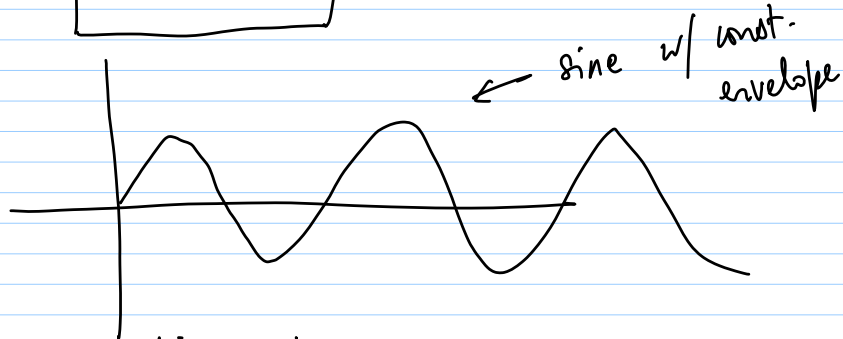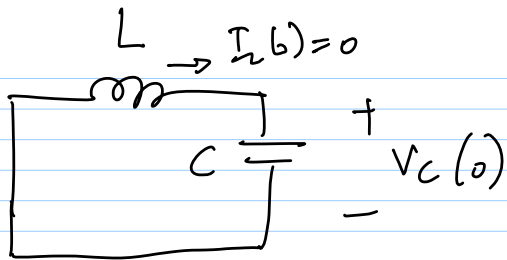- 1) R is very small
 Q - v. large \rightarrow complex conjugate roots
 \rightarrow sinusoidal solution




No dissipation of energy $\Rightarrow Q = \infty$

2) $Q = 1/2$

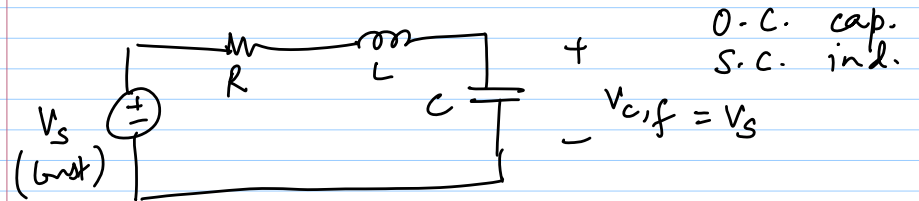3) $Q < 1/2$ $\{ R \uparrow \}$

----- X ----- X -----
 Forced response w/ constant V_s



$$LC \frac{d^2 V_{c,f}}{dt^2} + RC \frac{dV_{c,f}}{dt} + V_{c,f} = V_s$$

$$LC \frac{d^2 V_{c,n}}{dt^2} + RC \frac{dV_{c,n}}{dt} + V_{c,n} = 0$$

$$V_c(t) = V_{c,f}(t) + k V_{c,n}(t)$$

$$V_c(t) = V_s + (N.R.)$$

Forced response w/ $V_p \exp(st)$

① $V_s = V_p \exp(st) ;$

$V_c(t) = V_{c0} \exp(st) \rightarrow$ plug into
diff. eq.

$$(LC \cdot s^2 + RC \cdot s + 1) \cdot V_{c0} \exp(st) = V_p \exp(st)$$