
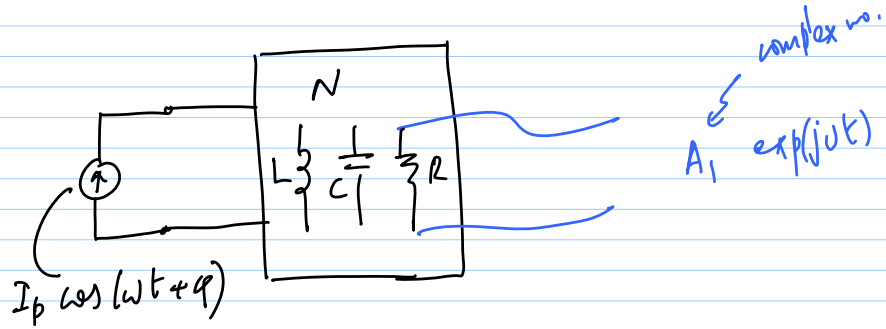


24/3/15

Lec 29

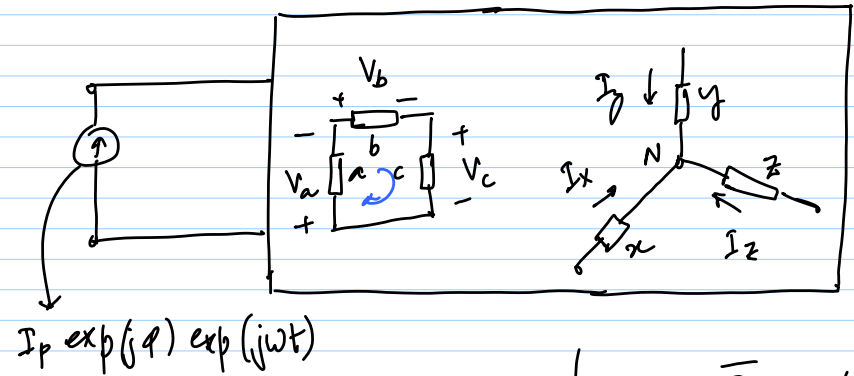

$I_p \cos(\omega t + \phi)$
 $I_p \exp(j(\omega t + \phi))$
 $I_p \exp(j\phi) \exp(j\omega t)$



phasors

$V_a = \bar{V}_a \exp(j\omega t)$	$I_x = \bar{I}_x \exp(j\omega t)$
$V_b = \bar{V}_b \exp(j\omega t)$	$I_y = \bar{I}_y \exp(j\omega t)$
$V_c = \bar{V}_c \exp(j\omega t)$	$I_z = \bar{I}_z \exp(j\omega t)$

KVL around loop:

$V_a + V_b + V_c = 0$

$(\bar{V}_a + \bar{V}_b + \bar{V}_c) \exp(j\omega t) = 0$

$\bar{V}_a + \bar{V}_b + \bar{V}_c = 0$

phasors KCL @ N

$I_x + I_y + I_z = 0$

$(\bar{I}_x + \bar{I}_y + \bar{I}_z) \exp(j\omega t) = 0$


$\bar{I}_x + \bar{I}_y + \bar{I}_z = 0$

$\bar{V}_a = V_{ar} + j V_{ai}$
 $= \hat{V}_a \exp(j\theta)$
 $= \hat{V}_a \angle \theta$

magnitude not complex.

$10 \angle 20^\circ \exp(j\omega t)$

All v's & i's \rightarrow same ω

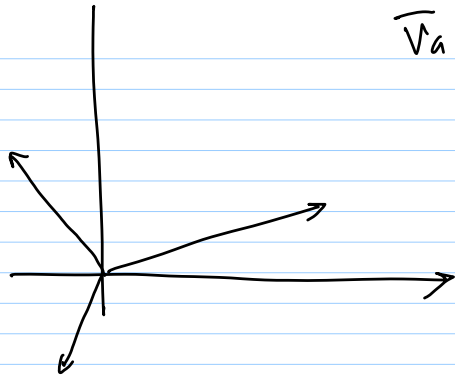

$$\bar{V}_a = \hat{V}_a \exp(j\theta)$$

$$\text{Node 1: } \bar{I}_a + \bar{I}_b + \dots = 0$$

$$\text{Node k: } \bar{I}_x + \bar{I}_y + \dots = \bar{I}_p$$

Elemental relationships

1) R


$$\bar{V}_R = \hat{V}_R \angle \theta$$

$$\bar{I}_R = \hat{I}_R \angle \theta$$

$$\frac{\bar{V}_R}{\bar{I}_R} = R \Rightarrow \hat{V}_R = R \cdot \hat{I}_R$$

$$\theta = \phi$$

2) C :

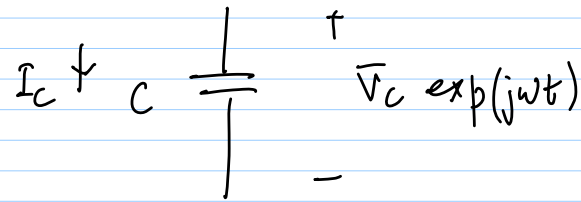


$$I_C = C \frac{dV_C}{dt} = j\omega C \cdot \bar{V}_C \exp(j\omega t)$$

$$\bar{I}_C = j\omega C \bar{V}_C$$

$$\frac{\bar{V}_C}{\bar{I}_C} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

3) L

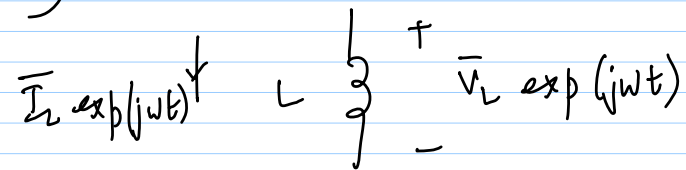

$$V_L = L \frac{dI_L}{dt}$$

$$V_L = j\omega L \bar{I}_L \exp(j\omega t)$$

$$\frac{\bar{V}_L}{\bar{I}_L} = j\omega L$$

* Algebraic eq. instead of differential eq.

* Ratio of V & I is a complex no.

* ratio of V & I can depend on ω

Impedance


$$\bar{Z}_k = \frac{\bar{V}_k}{\bar{I}_k} = R_k + jX_k$$

↓ resistance ↓ reactance


$$R \quad \bar{Z} = R + j0 \rightarrow X=0$$

$$L \quad \bar{Z} = 0 + j\omega L \rightarrow X = \omega L$$
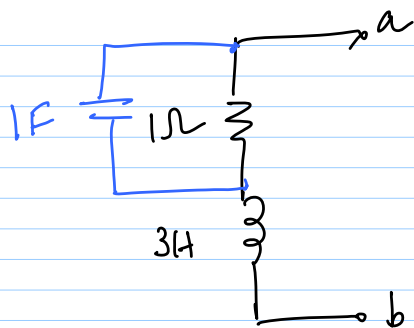
$$C \quad \bar{Z} = 0 - \frac{j}{\omega C} \rightarrow X = \frac{-1}{\omega C}$$




$$\bar{Z}_{ab} = 1 + j\omega \cdot 3$$

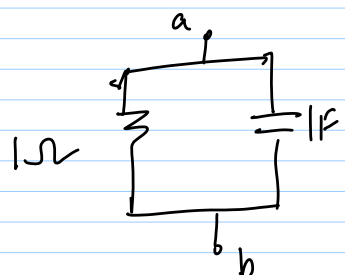

$$Y_{ab} = 1 + j\omega$$

$$\bar{Y} = \frac{\bar{I}_k}{\bar{V}_k} = G + jB$$

↓ Admittance ↓ Susceptance
↓ conductance

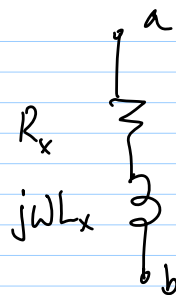

$$\bar{Y}_{ab} = \frac{1}{\bar{Z}_{ab}} = \frac{1}{R_x + j\omega L_x}$$

$$= \frac{R_x}{R_x^2 + (\omega L_x)^2} - \frac{j\omega L_x}{R_x^2 + (\omega L_x)^2}$$

↓ G ↓ jB