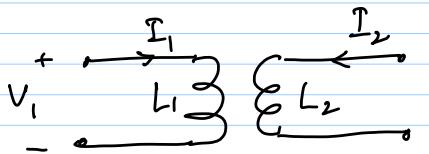


(9/11) 5


Lec 3

Mutual Inductor





$$L = \text{self inductance}$$

$$M = \text{mutual inductance}$$

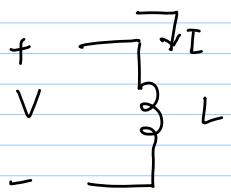

$$V_1 = L_1 \frac{dI_1}{dt} + (M) \frac{dI_2}{dt}$$
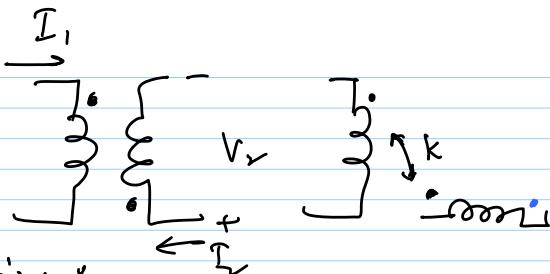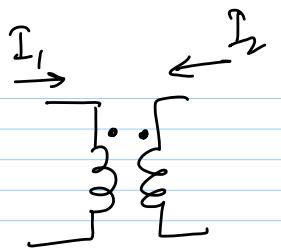
$$V_2 = (M) \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$





Dot point convention:

Currents entering dot points produce additive fluxes i.e. M is positive

$$M = k \sqrt{L_1 L_2} ; k = \text{coupling coefficient}$$


$$|k| \leq 1$$

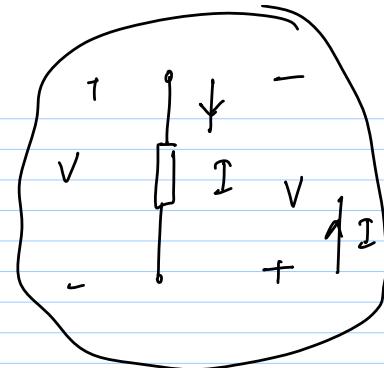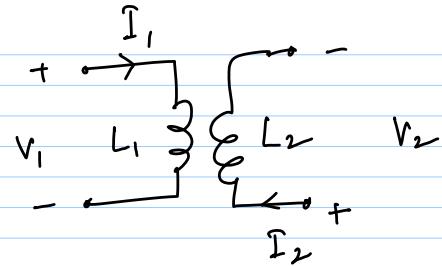

$$V_1 = L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}$$

$$V_2 = -M \frac{dI_1}{dt} + L_2 \frac{dI_2}{dt}$$

Passive sign convention

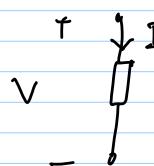

Power $P = V \cdot I$ dissipated
(in Watts)

$$P(t) = V(t) I(t)$$

Passive - power is dissipated

$$V \quad | \quad R \quad I = V/R \quad P = VI = \frac{V^2}{R} \text{ or } I^2 R > 0$$

\Rightarrow power is dissipated

Resistor = passive

$$V - \frac{1}{C} \downarrow I = C \frac{dV}{dt} \Rightarrow \text{Capacitor} = \text{passive}$$



$$P = V \Sigma = CV \frac{dV}{dt}$$

Energy (Joules)

$$E = \int_0^{T_0} P(t) dt = \int_0^{T_0} \left(CV \frac{dV}{dt} \right) dt$$

$$= \frac{1}{2} C \left[V^2(T_0) - V^2(0) \right]$$
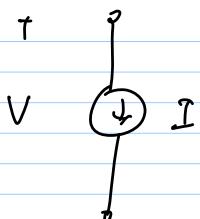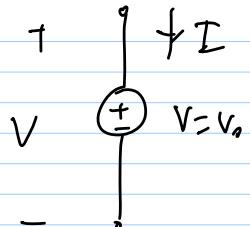
$$\text{If } V(0) = 0 \Rightarrow E > 0$$





$$P = VI$$

$$I$$

$$V = V_0$$

$$P = VI$$

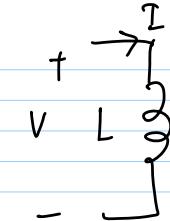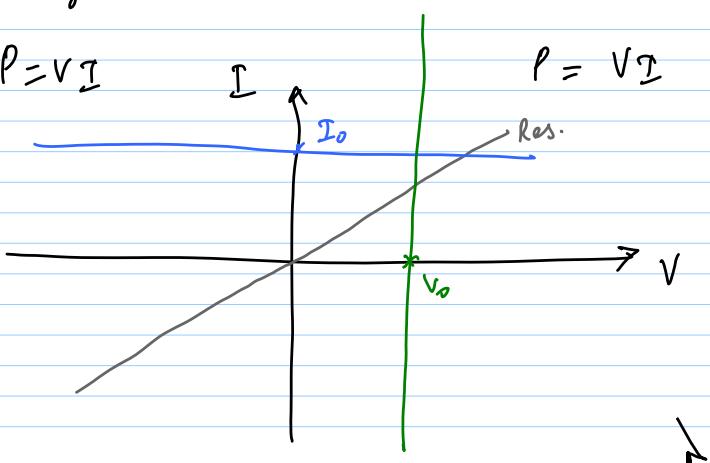


$$E = \frac{1}{2} L \left[I^2(T_0) - I^2(0) \right]$$

Inductor = passive

(or absorbed)

Passive : Electrical energy is dissipated in the element

Active : Electrical energy is generated

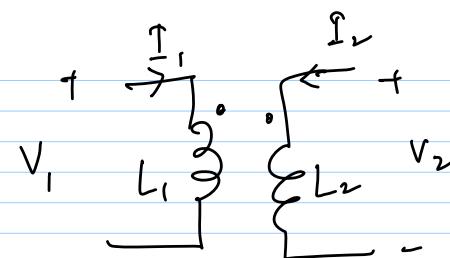

$$P = V_1 I_1 + V_2 I_2$$

$$\left\{ E = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2 > 0 \right.$$

$$M = k \sqrt{L_1 L_2}$$

$$|k| \leq 1$$