

27/3/15


Lec 31

$$\bar{V}_R = \frac{j\omega CR}{1+j\omega CR} \cdot V_p$$

$$\bar{V}_C = \frac{1}{1+j\omega CR} \cdot V_p$$

$$\omega \ll \frac{1}{RC}$$

$$\omega CR \ll 1$$


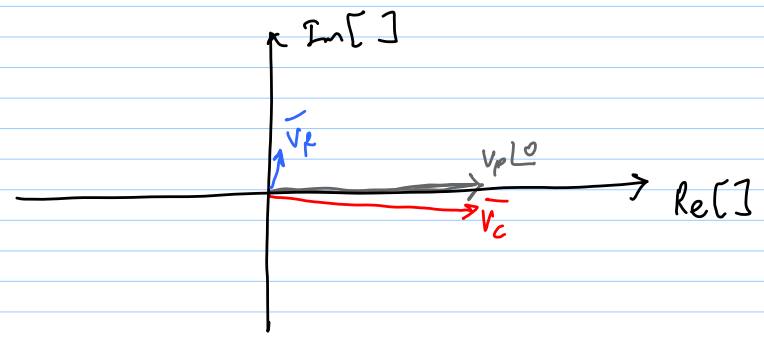


$$\bar{V}_R = \frac{j\omega CR}{1+j\omega CR} \cdot V_p$$




$$\bar{V}_C = \frac{1}{1+j\omega CR} \cdot V_p$$

$$\omega \gg \frac{1}{RC}$$


$$\omega CR \gg 1$$

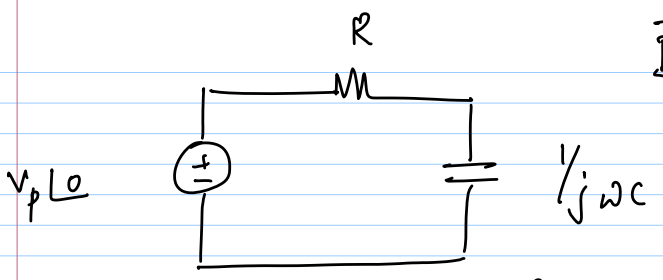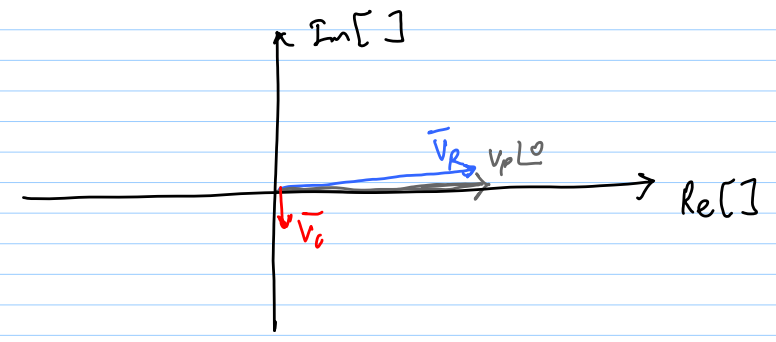
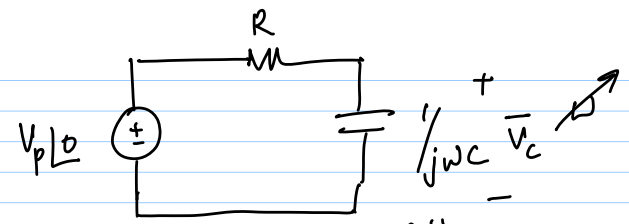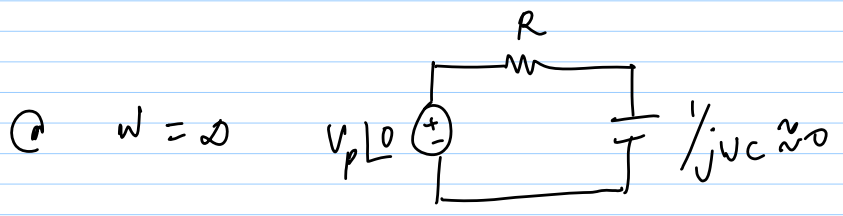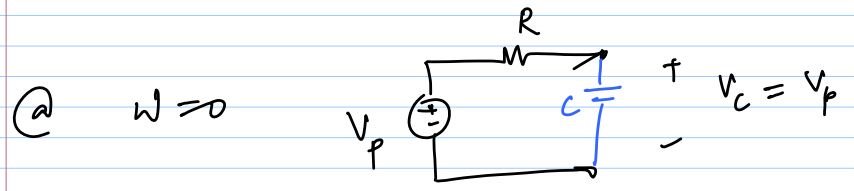
$$\bar{I}_C = j\omega C \cdot \bar{V}_C$$


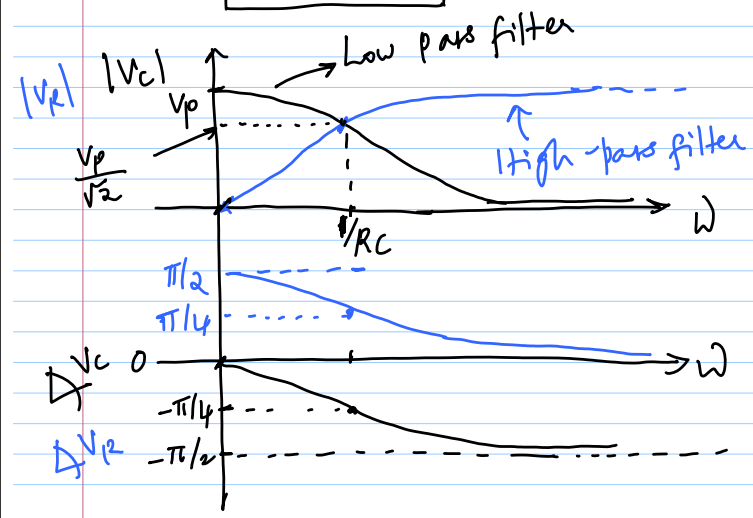
$$\bar{V}_C = \frac{1}{1+j\omega CR} V_p$$




$$|\bar{V}_C| = \frac{1}{\sqrt{1+\omega^2 R^2 C^2}} V_p$$

$$\angle \bar{V}_C = -\tan^{-1}(\omega CR)$$

$$|\bar{V}_R| = \frac{\omega CR}{\sqrt{1+\omega^2 R^2 C^2}} V_p$$

$$\angle \bar{V}_R = \pi/2 - \tan^{-1}(\omega CR)$$

Ideal filter

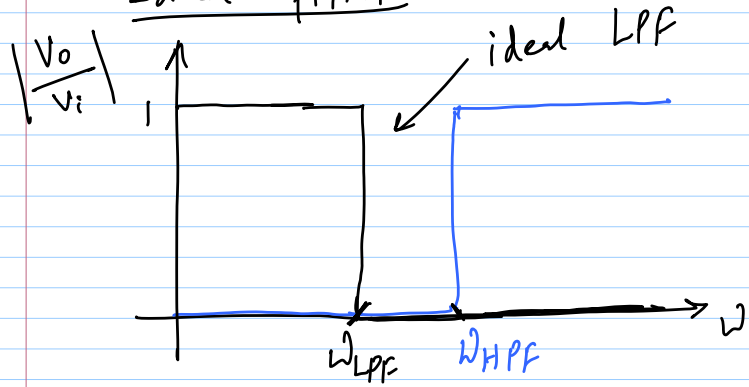

practical filter $BW \equiv$ frequency at which
output goes to $1/\sqrt{2}$ of
max value