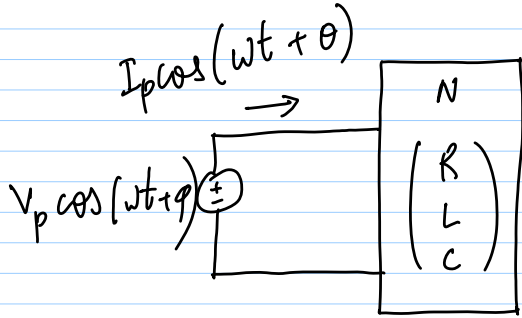


11/15

Lec 34



$\vec{v} = V_p \exp(j\omega t)$
 $\bar{v} = V_p \angle \phi$
 $\vec{i} = I_p \exp(j\omega t + \theta)$
 $\bar{i} = I_p \angle \theta$


$\bar{P} = \bar{v} \bar{i} = V_p I_p \angle \phi + \theta$ X

$\bar{P} = \bar{v} \cdot \bar{i} = V_p I_p \angle \phi - \theta$ X


$\bar{P} = \frac{\bar{v} \cdot \bar{i}^*}{2}$
 $\frac{[V_p I_p / 2] [\cos(\phi - \theta)]}{\text{complex power } + j \sin(\phi - \theta)}$

Average power = $\frac{V_p I_p}{2} \cos(\phi - \theta)$
 = $\text{Re}[\bar{P}]$

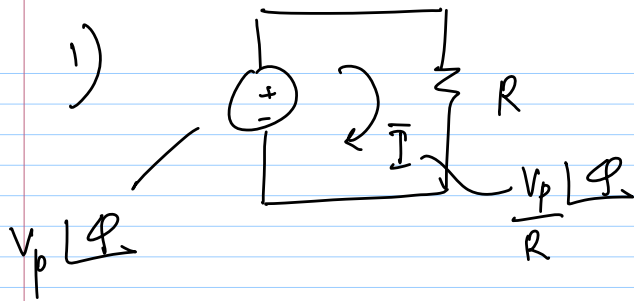
$\bar{P} = P_r + j P_i$
↑
 real or average power




$\bar{P} = \frac{V_p^2}{2R}$

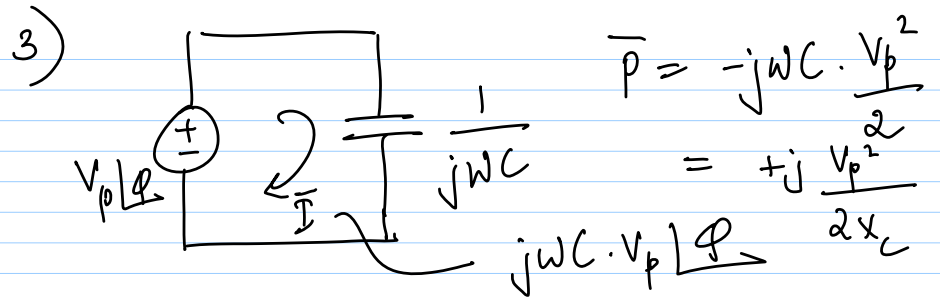

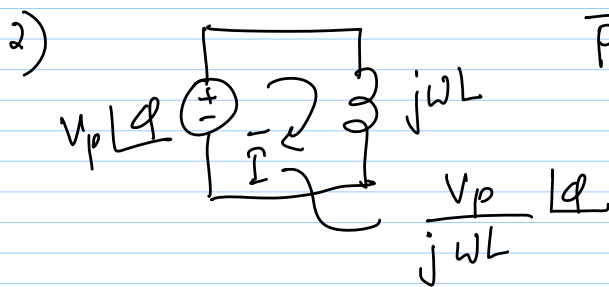$\bar{P} = -jwc \cdot \frac{V_p^2}{2}$
 $= +j \frac{V_p^2}{2X_c}$
 $jwc \cdot V_p \angle \phi$



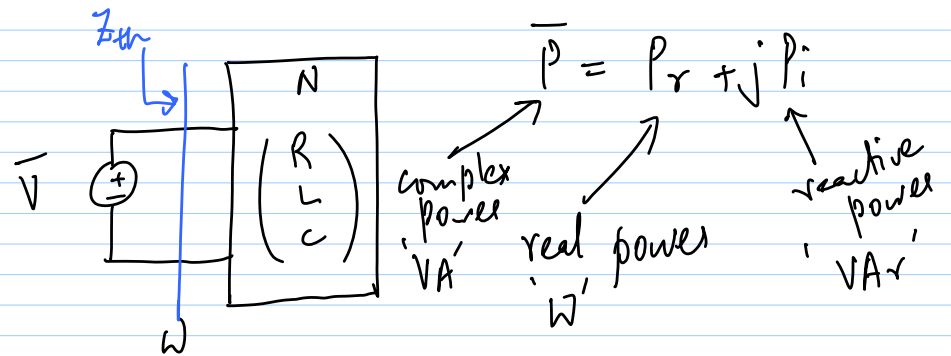$\bar{P} = j \frac{V_p^2}{2wL} = j \cdot \frac{V_p^2}{2X_L}$



$$\bar{V} = V_p \exp(j\varphi) \quad \bar{I} = I_p \exp(j\theta)$$



$$\begin{aligned} \bar{P} &= \frac{V_p I_p}{2} \exp[j(\varphi - \theta)] \\ &= \frac{V_p I_p}{2} \left[\cos(\varphi - \theta) + j \sin(\varphi - \theta) \right] \end{aligned}$$

$$|\bar{P}| = \frac{V_p I_p}{2} \quad \left[\text{VA, apparent power} \right]$$

$$\text{Re}[\bar{P}] = \frac{V_p I_p}{2} \cos(\varphi - \theta) \quad \left[\text{W, real power} \right]$$


$$\text{Im}[\bar{P}] = \frac{V_p I_p}{2} \sin(\varphi - \theta) \quad \left[\text{VAR, reactive power} \right]$$

"power factor" $PF = \frac{\text{Real power}}{\text{Apparent power}} = \frac{\text{Re}[\bar{P}]}{|\bar{P}|}$

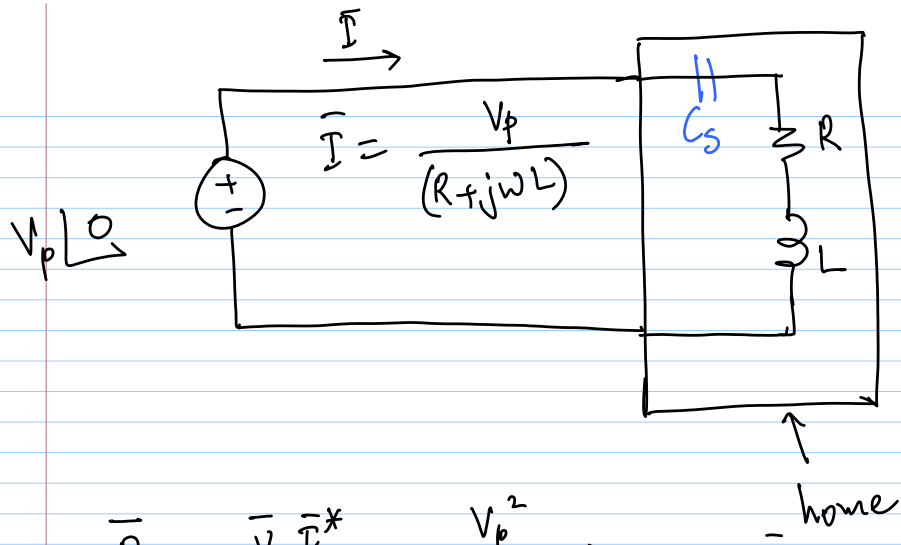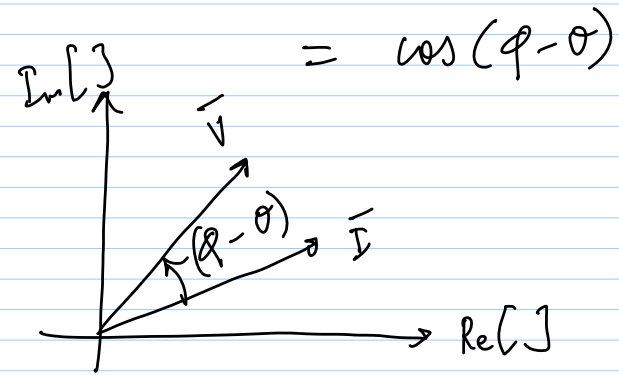

$$\bar{P} = \frac{\bar{V} \cdot \bar{I}^*}{2} = \frac{V_p^2}{2(R - j\omega L)}$$

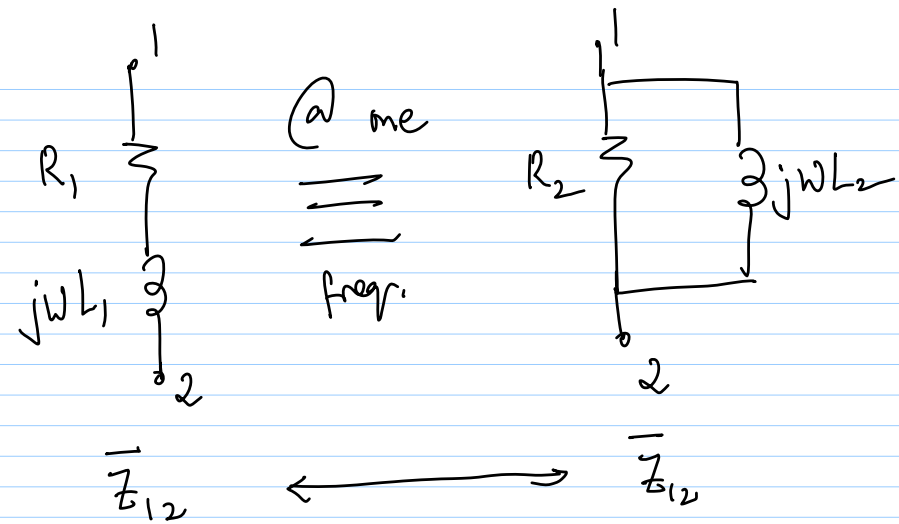
$$= \frac{V_p^2}{2} \left[\frac{R}{R^2 + \omega^2 L^2} + \frac{j\omega L}{R^2 + \omega^2 L^2} \right]$$



$$\begin{aligned} \text{Power delivered to } R &= I_{\text{rms}}^2 \cdot R \\ &= \frac{I_p^2}{2} R \end{aligned}$$

$$\bar{I} = \frac{V_p}{R + j\omega L}$$
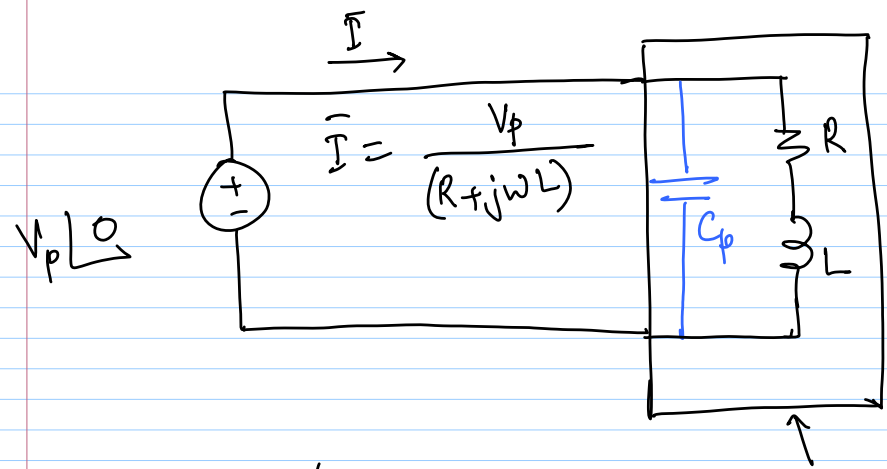
$$\text{PF} = 1 \Rightarrow C_s = \frac{1}{\omega^2 L}$$



$$C_p = \frac{L}{R^2 + \omega^2 L^2}$$