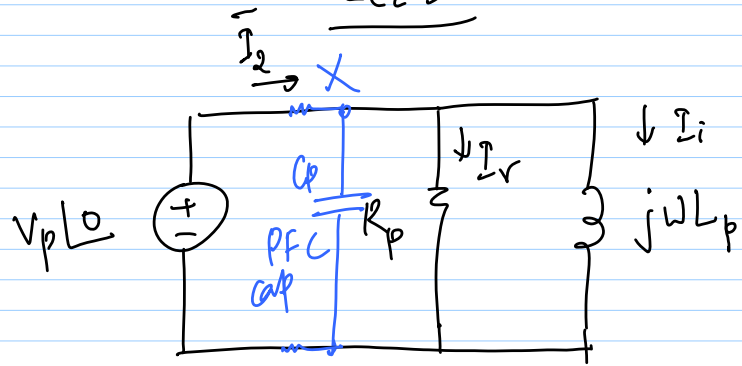


6/4/15

Lec 35



$$\bar{I} = \bar{Y} \cdot V_p L_o$$

$$\bar{Y} = \frac{1}{R_p} - \frac{j}{\omega L_p}$$

Case 1 no L_p (purely resistive) $\bar{V} = V_p L_o$



$$P_r = \frac{V_p^2}{2R_p} \quad ; \quad \bar{I}_1 = \frac{V_p L_o}{R_p} = I_r$$

Case 2 $R_p \parallel L_p$

$$P_r = \frac{V_p^2}{2R_p} \quad \left\{ \begin{array}{l} I_{R_p} = \frac{V_p L_o}{R_p} = I_r \\ I_{L_p} = -\frac{V_p L_o}{\omega L_p} = I_i \end{array} \right.$$


$$\bar{I}_2 = I_r + j I_i$$

Series vs. parallel caps

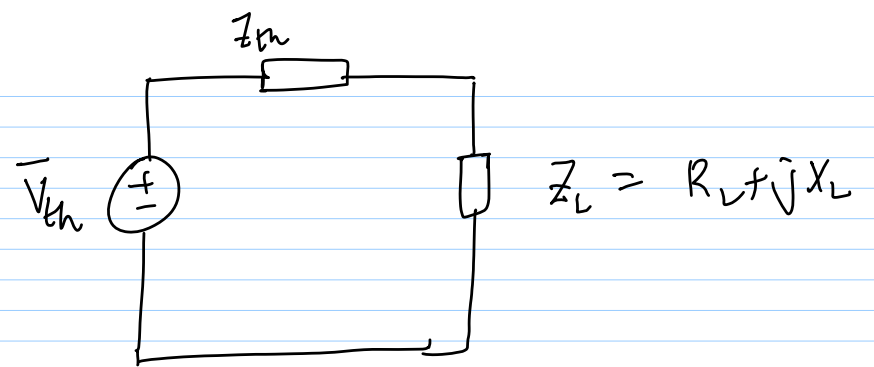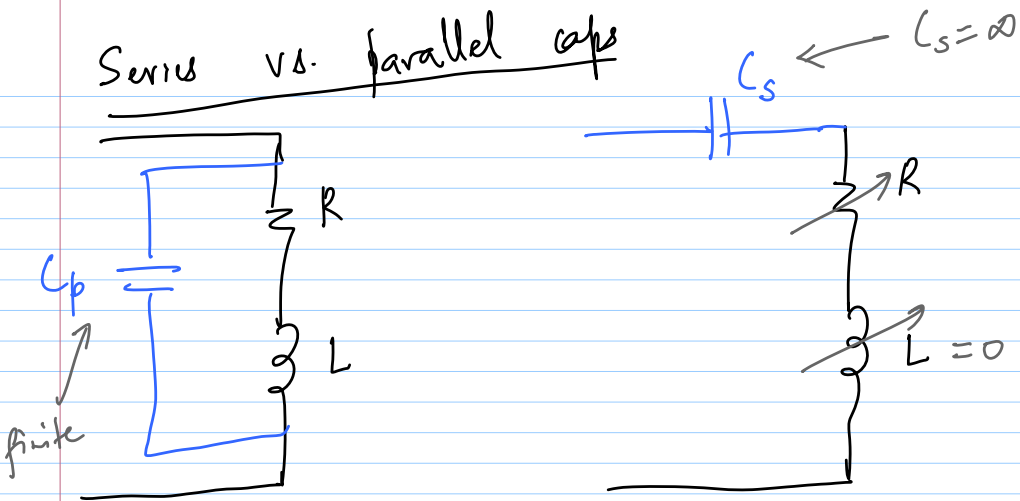

Power delivered to Z_L
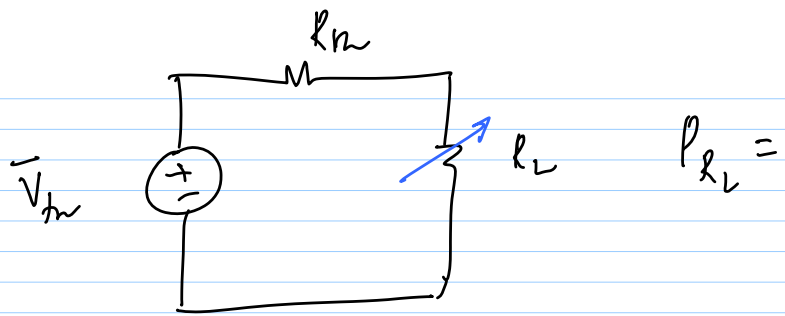
$$P_r = \text{Re} \left[\frac{1}{2} \cdot \frac{\bar{V}_{th} \cdot Z_L}{Z_{th} + Z_L} \cdot \frac{\bar{V}_{th}^*}{Z_{th}^* + Z_L^*} \right]$$



In general $P_r = V_{rms} I_{rms} \cos(\phi)$

$$= \operatorname{Re} \left[\frac{\bar{V}_L \cdot \bar{I}_L^*}{2} \right]$$

$$\bar{V}_L = \frac{R_L}{R_L + R_m} \bar{V}_{th} \quad \bar{I}_L = \frac{\bar{V}_{th}}{R_m + R_L}$$

Power delivered to Z_L

$$P_r = \operatorname{Re} \left[\frac{1}{2} \cdot \frac{\bar{V}_{th} \cdot Z_L}{Z_m + Z_L} \cdot \frac{\bar{V}_{th}^*}{Z_m^* + Z_L^*} \right]$$

$$= \frac{|\bar{V}_{th}|^2}{2 \cdot |Z_m + Z_L|^2} \cdot \operatorname{Re} [Z_L]$$