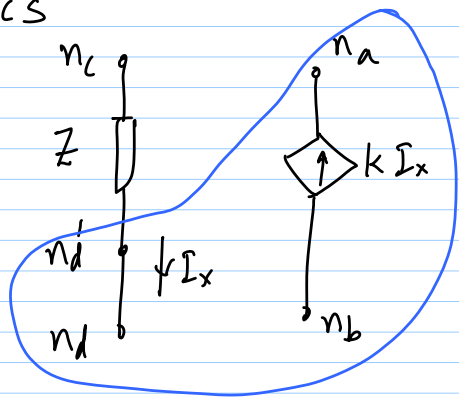


31-1-15


Lec 9

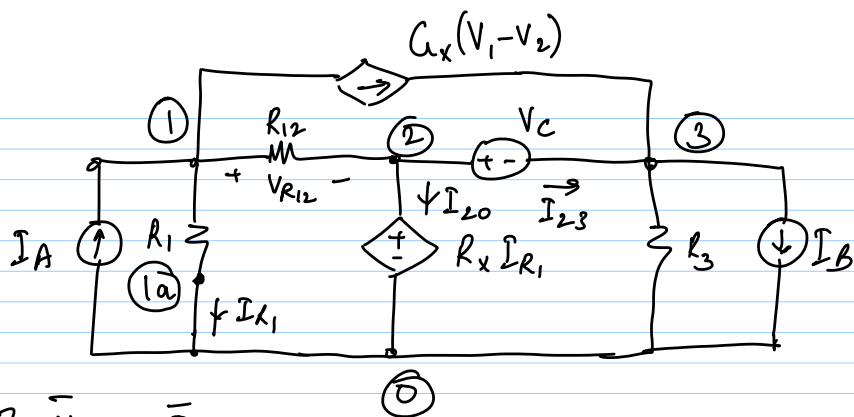7) CCCS

cccs




$$\text{KCL @ } n_a \begin{bmatrix} 0 & 0 & 0 & 0 & -k \\ n_b & 0 & 0 & 0 & +k \\ n_d' & 0 & 0 & 0 & +1 \\ n_d & 0 & 0 & 0 & -1 \\ 0 & 0 & +1 & -1 & 0 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_d' \\ V_d \\ I_x \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix}$$




$$[G] \cdot \bar{V} = \bar{I}$$

$$V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_{1a} \\ I_{23} \\ I_{20} \\ I_{R1} \end{bmatrix}$$
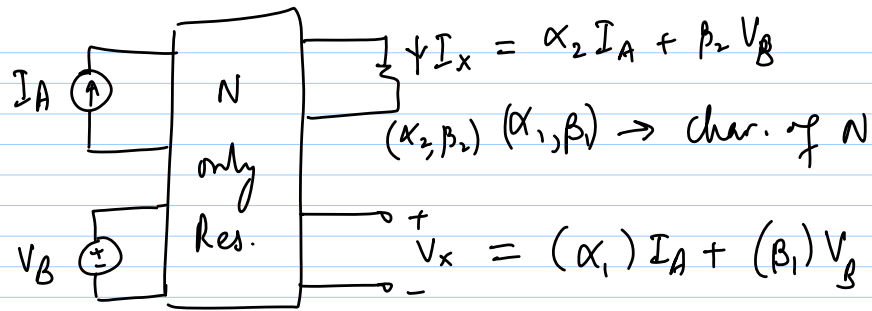
$$\begin{bmatrix} n_1 \\ n_2 \\ n_3 \end{bmatrix} \begin{bmatrix} G_x + G_{12} & -G_x \\ -G_{12} & G_{12} \\ -G_x & G_x \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_{1a} \\ I_{23} \\ I_{20} \\ I_{R1} \end{bmatrix} = \begin{bmatrix} I_A \\ I_B \\ 0 \end{bmatrix}$$



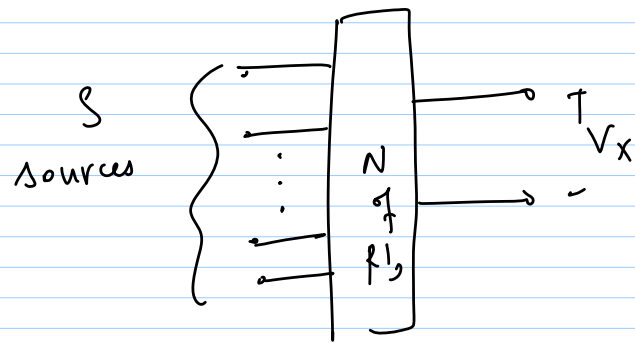$(I_{A1}, V_{B1}) \rightarrow V_{x1}$   
 $(I_{A2}, V_{B2}) \rightarrow V_{x2}$  } given  $\Rightarrow$  find out  $\alpha_1, \beta_1$   
 $(I_{A3}, V_{B3}) \Rightarrow$  Can find out  $V_{x3}$




If  $V_x$  is known for  $S$  unique values of source


For a linear network  $\Rightarrow$  "Superposition" is applicable

### Mesh Loop Analysis


planar graph

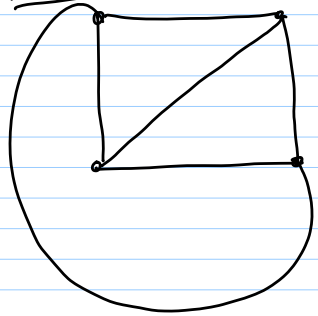

Mesh - planar loop

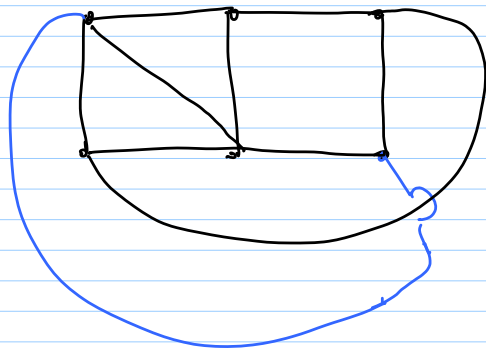

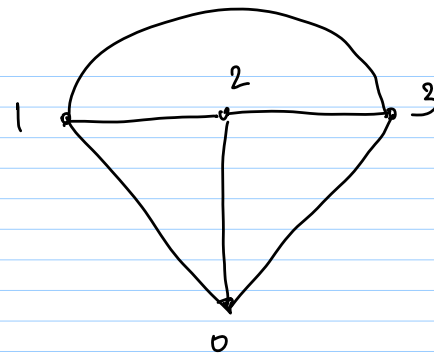$B$  branches }  $B - N + 1$   
 $N$  nodes }



$B - N + 1$  KVL equations

