
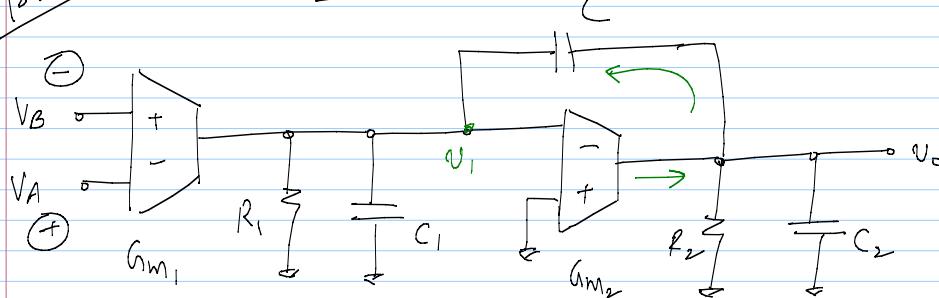


27/8/14

lec 14

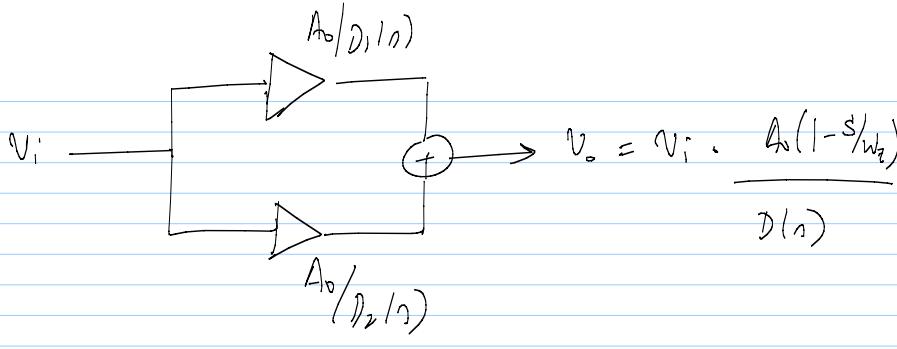

$$\frac{V_o}{V_{i-A}}(s) = -G_{m1} G_{m2} R_1 R_2 \left[\frac{sC}{G_{m2}} - 1 \right] \\ \frac{s^2 [CC_1 + C_1 C_2 + CC_2] R_1 R_2 + s [C \{R_1(1 + G_{m2} R_2) + R_2\} + R_1 C_1 + R_2 C_2]}{+ 1}$$



$$D_1(s) \neq D_2(s)$$

quadratic eqn $an^2 + bn + c = 0$ roots are n_1, n_2

if $n_1 \ll n_2$

$$n_1 \approx -\frac{c}{b}; \quad n_2 \approx -\frac{b}{a}$$

$$DC \text{ gain mag.} = G_{m1} R_1 \cdot G_{m2} R_2 \checkmark$$

$$\text{zero at } Z_1 = +\frac{G_{m2}}{C} (RHP zero) \checkmark$$

$$\frac{A_0 \left(1 - \frac{s}{\omega_2} \right)}{D(s)} = A \left[\frac{1}{D_1(s)} + \frac{1}{D_2(s)} \right]$$

$$D(s) = D_1(s) \cdot D_2(s)$$

$$D_1(s) + D_2(s) = \left(1 - \frac{s}{\omega_2} \right)$$

$$(a) s = \omega_2, \quad \frac{V_o}{V_i}(s) = 0$$

here $p_1 = \text{dominant pole}$

$p_2 = 1^{\text{st ND pole}}$

$$p_1 \approx -\frac{c}{b} = -\frac{G_1 G_2}{[C \{G_{m2} + R_1 + G_2\} + G_1 C_1 + G_2 C_2]} \quad R_1 = \frac{1}{G_1}$$

$$R_2 = \frac{1}{G_2}$$

$$\approx -\frac{G_1 G_2}{G_{m2} C} \approx \frac{-G_1}{\left(\frac{G_{m2}}{G_2}\right) \cdot C}$$

$$G_{m1,2} \gg G_1, G_2$$

$$C \approx C_1 \approx C_2$$

We expected :

$$p_{1_0} \text{ (initial)} = -\frac{1}{R_1 C_1} = -\frac{G_1}{C_1}$$

$$p_{1_{\text{new}}} = -\frac{G_1}{C_1 + (A)C} \approx -\frac{G_1}{\left(\frac{G_{m_2}}{G_2}\right)C}$$

$$A = G_{m_2} R_2 = \frac{G_{m_2}}{G_2}$$

$$(AC) \gg |C_1|$$

$$p_2 = -\frac{b}{a}$$

$$= -\frac{c[G_{m_2} + G_1 + G_2] + C_1 G_1 + C_2 G_2}{C_1 C + C_2 C + C_1 C_2}$$

$$\approx -\frac{c \cdot G_{m_2}}{C_1 C + C_2 C + C_1 C_2} \approx -\frac{G_{m_2}}{C_1 + C_2 + \frac{C_1 C_2}{C}}$$

before adding C_2

$$p_{1_0} = -\frac{G_2}{C_2}$$

