
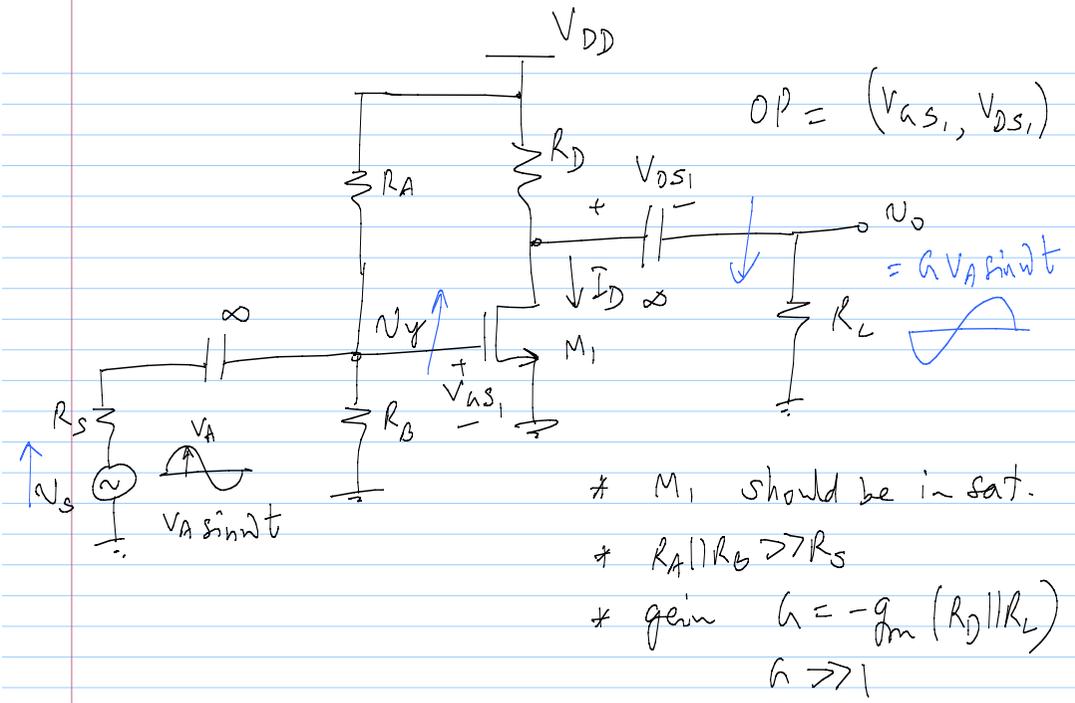


3/9/14

lec 17

Choice of cap:

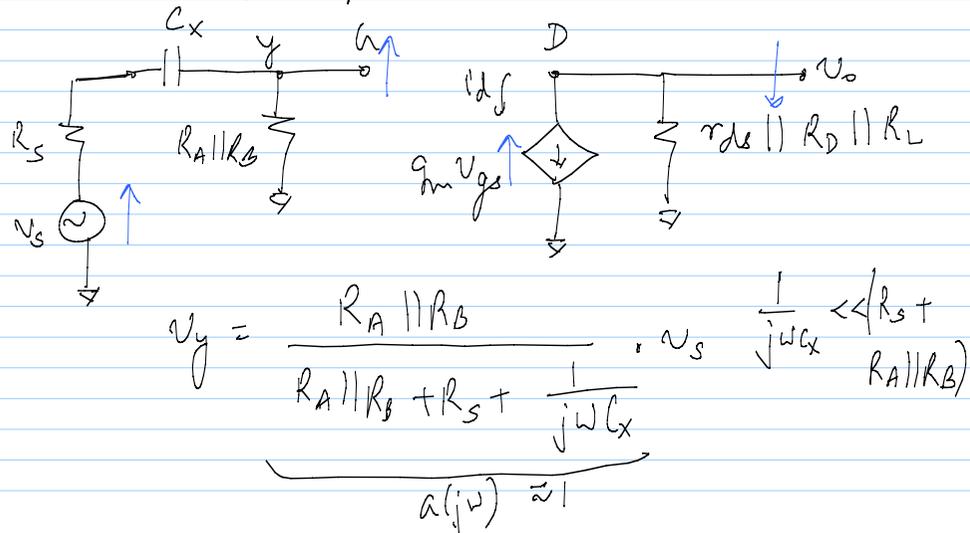

For sat:


$$V_{GS} > V_T$$

$$V_{DS} > V_{GS} - V_T$$

$$V_D - V_S > V_G - V_S - V_T$$

$$V_D > V_G - V_T$$
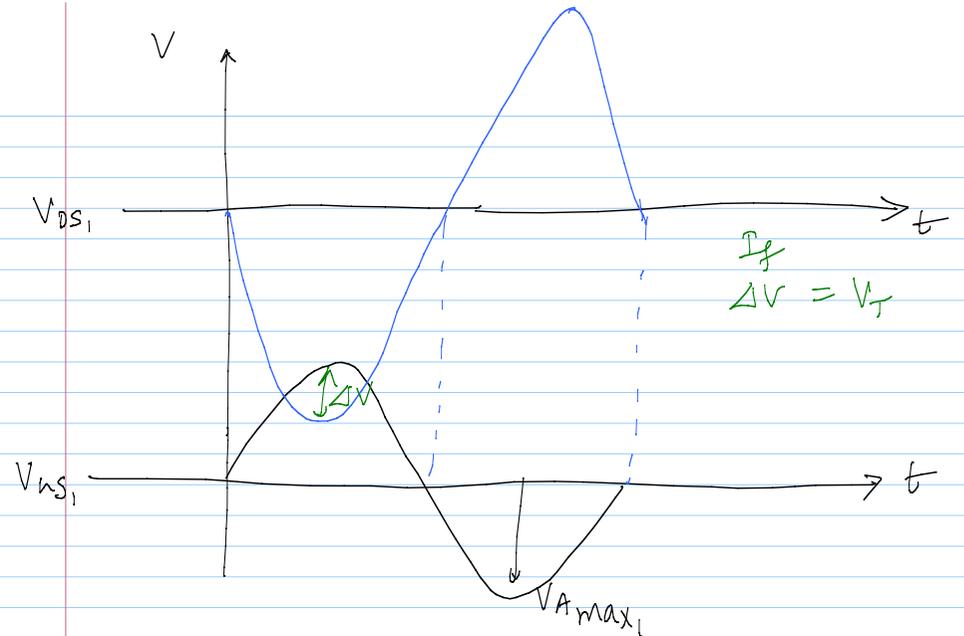
$$V_{D1} > V_{G1} - V_T \quad (\text{DC op})$$



$V_{A_{max,1}} \equiv$ Maximum value of V_A that keeps M_1 from going into triode region at any time (positive half cycle)

$$V_A = V_{GS,1} + V_S$$

$$V_D = V_{DS,1} - g_m(R_D || R_L) \cdot v_s$$

@ $V_{A_{max,1}}$, $V_D = V_A - V_T$

$$\Rightarrow V_{DS,1} - g_m(R_D || R_L) \cdot V_{A_{max,1}} = V_{GS,1} + V_{A_{max,1}} - V_T$$

$$V_{A_{max,1}} = \frac{V_{DS,1} - V_{GS,1} + V_T}{1 + g_m(R_D || R_L)}$$


Negative half cycle

$$I_D = I_{D,1} + g_m v_s$$

DC bias


small-signal current

(in-phase with v_s)

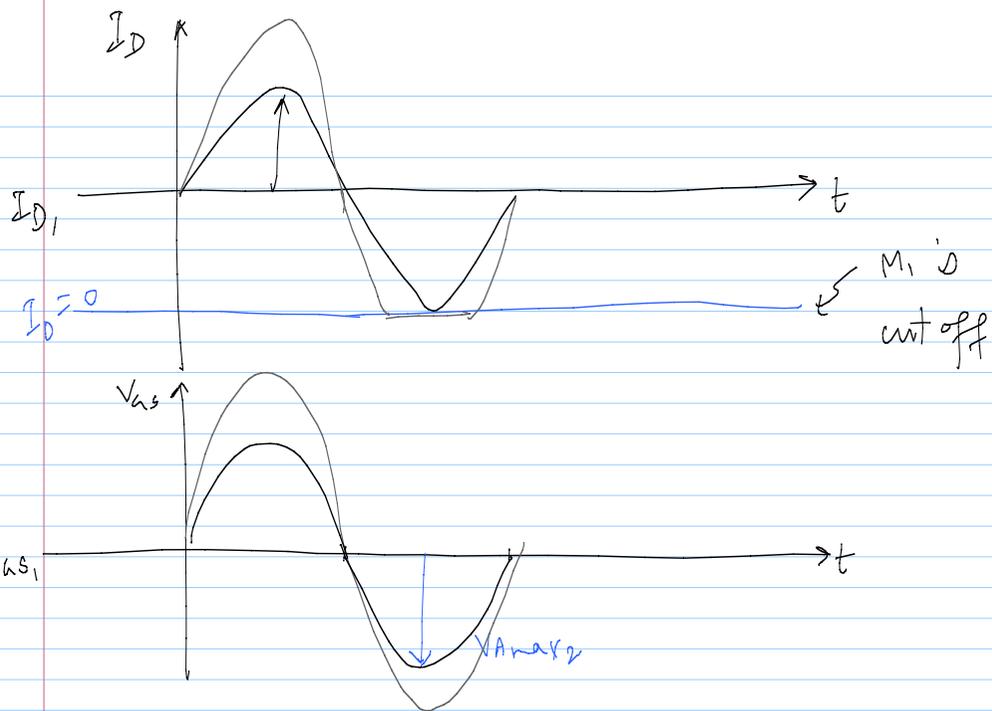

$$I_D = 0 \text{ when } |I_{D,1}| = |g_m V_{A_{max,2}}|$$

$$V_{A_{max,2}} = \frac{I_{D,1}}{g_m}$$

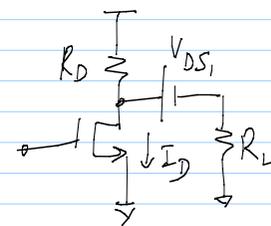

When $I_D = 0$, $V_D = V_{D0}$
 KCL @ Drain: $\frac{V_{DD} - V_{D0}}{R_D} = \frac{V_{D0} - V_{DS,1}}{R_L}$

$$V_{D0} = \frac{R_L V_{DD} + R_D V_{DS,1}}{R_D + R_L}$$