
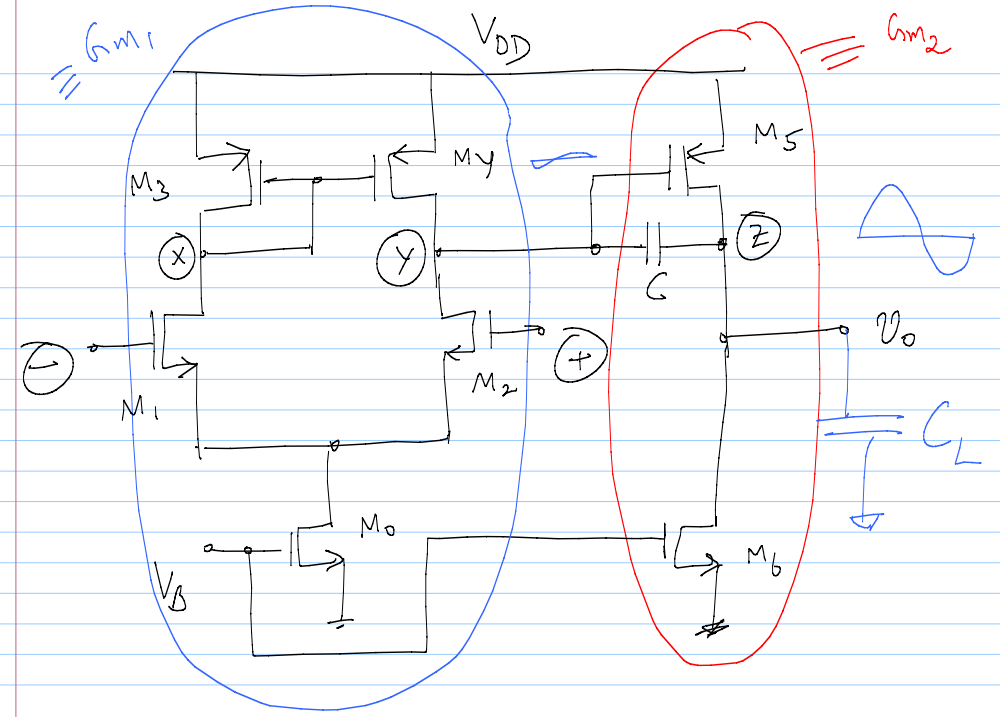


7/11/14


lec 42

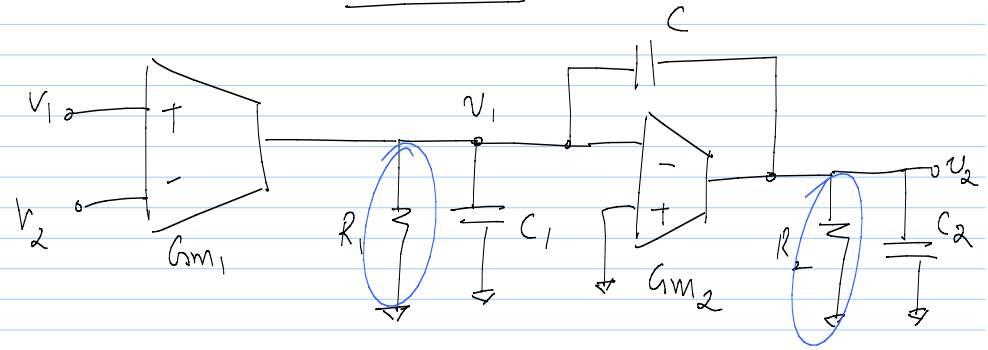

$$R_1 = r_{ds2} \parallel r_{ds4} \quad G_{m1} = g_{m1}$$

$$R_2 = r_{ds5} \parallel r_{ds6} \quad G_{m2} = g_{m5}$$

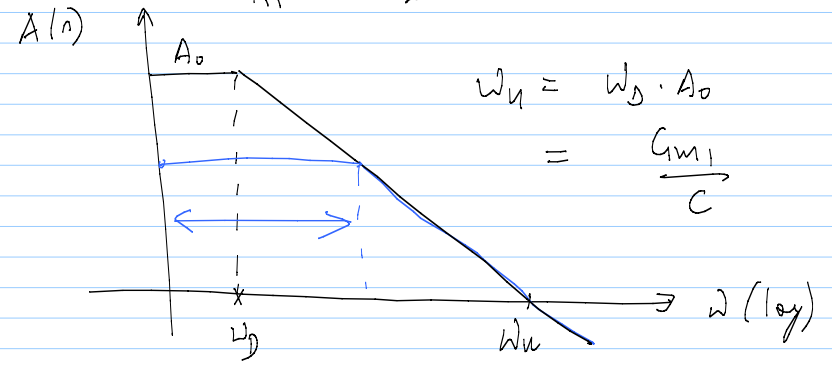
$$\omega_D = \frac{1}{R_1 \cdot G_{m2} R_2 \cdot C} ; A_0 = G_{m1} R_1 \cdot G_{m2} R_2$$








$$\omega_u = \omega_D \cdot A_0 = \frac{G_{m1}}{C}$$

$$V_{out, min} = V_{DSAT6}$$

$$V_{out, max} = V_{DD} - V_{DSAT5}$$

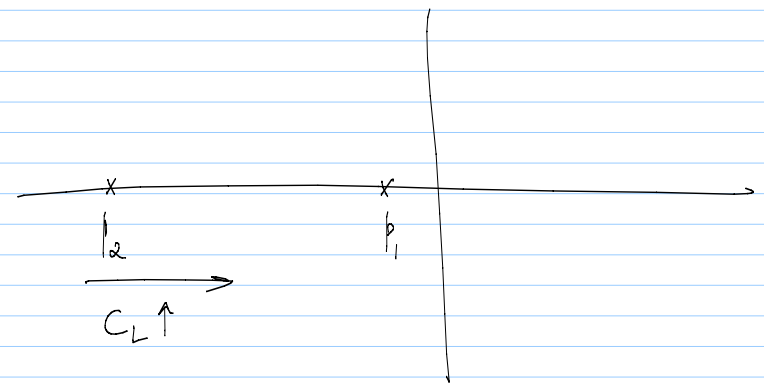

Bipolar Junction Transistors

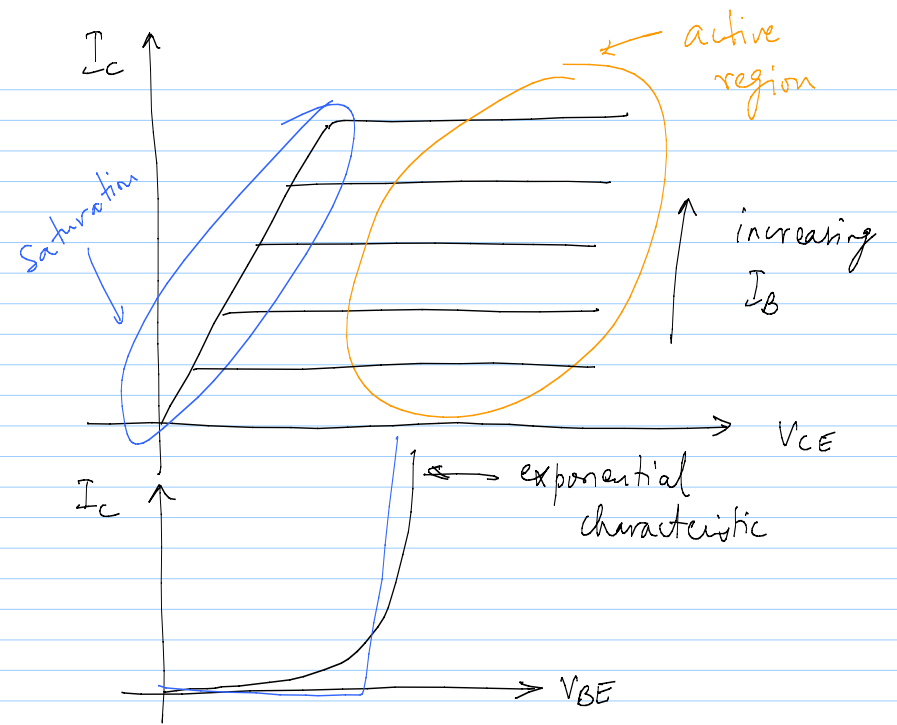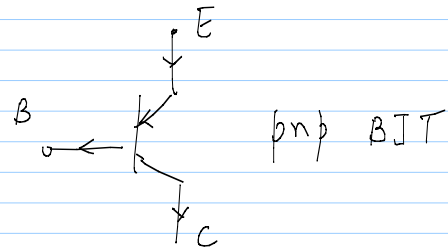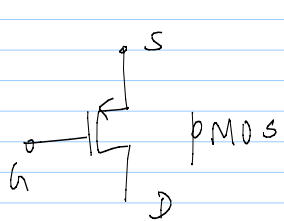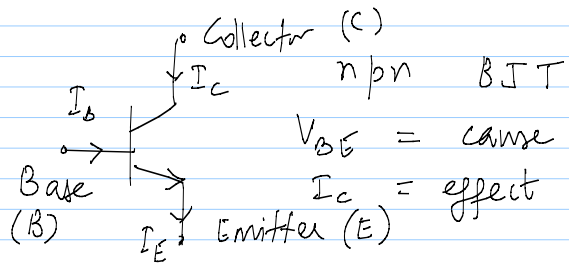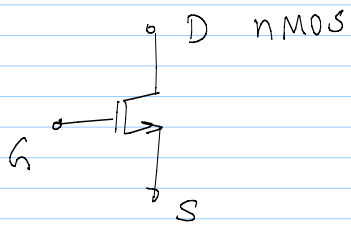

$$I_c = I_s \left[\exp \left\{ \frac{V_{BE}}{V_t} \right\} - 1 \right]$$

$$\approx I_s \exp \left\{ \frac{V_{BE}}{V_t} \right\} \quad \text{if } V_{BE} \gg V_t$$

$$V_t = \frac{kT}{q} \approx 26 \text{ mV @ RT}$$

$$V_{BE} = V_t \ln \left(\frac{I_c}{I_s} \right)$$

$\beta =$ current gain

$\sim 50 - 200$

$$I_B + I_c = I_E ; \quad I_c / I_B = \beta$$