

12/11/14

lec 43

$\frac{I_c}{I_b} = \beta_{dc}$ — DC current gain
 $\beta_{dc} \sim 50 - 200$



$y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$ $I_c = I_s \exp\left(\frac{V_{BE}}{V_t}\right)$
 $I_b = I_c / \beta_{dc}$

$y_{11} = \frac{\partial I_b}{\partial V_{BE}} = \frac{\partial}{\partial V_{BE}} \left[\frac{I_s}{\beta_{dc}} \exp\left(\frac{V_{BE}}{V_t}\right) \right] = \frac{I_c}{\beta_{dc} V_t}$

$y_{12} = \frac{\partial I_b}{\partial V_{CE}} = 0$

$y_{21} = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_c}{V_t} = g_m$

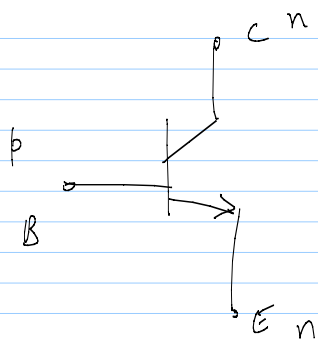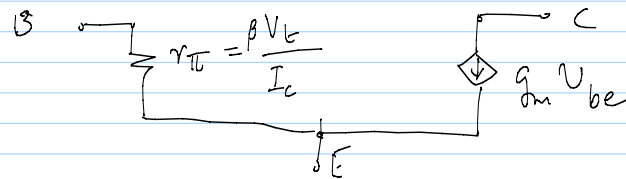$y_{22} = \frac{\partial I_c}{\partial V_{CE}} = 0$




for proper operation
 BE jn. — forward biased

CB jn. — reverse biased

$V_{BE_{on}} = 0.65 V$, CB jn. gets fwd. biased
 when $V_{CE} = V_{CE_{on}}$


$V_{CE_{sat.}} \approx 0.2V$

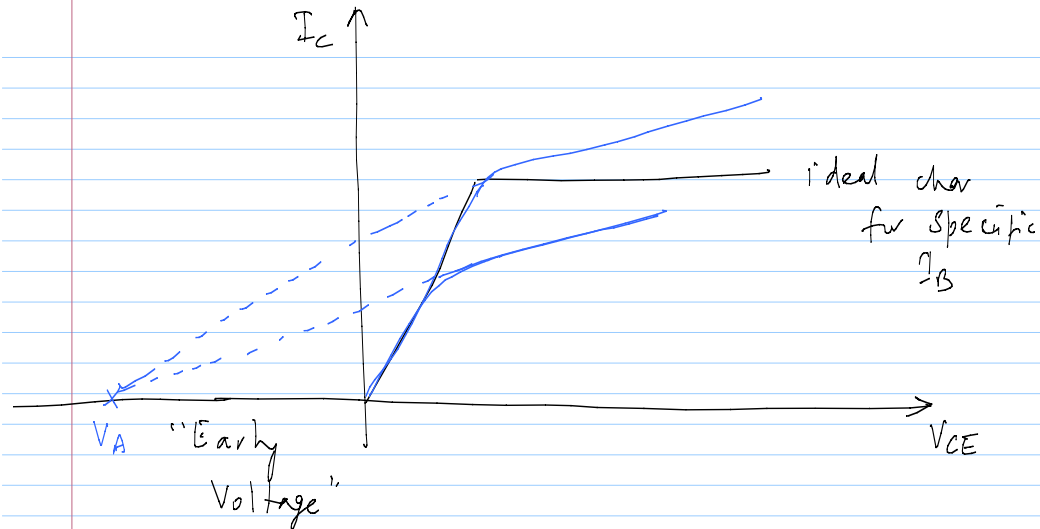




$I_c = I_s \exp\left(\frac{V_{BE}}{V_t}\right) \left\{ 1 + \frac{V_{CE}}{V_A} \right\}$

$$y_{22} = \frac{\partial I_c}{\partial V_{CE}} = \frac{I_c}{V_A}$$


Incremental eq. ckt. of BJT

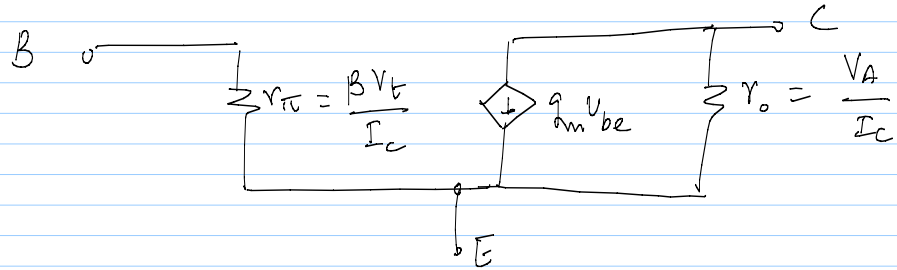

"hybrid- π " model of BJT

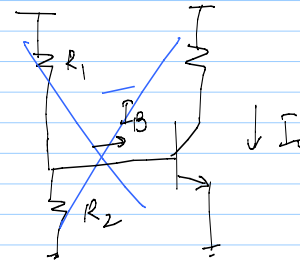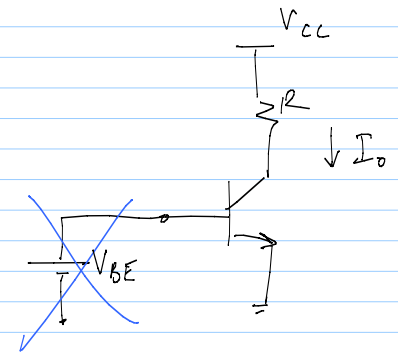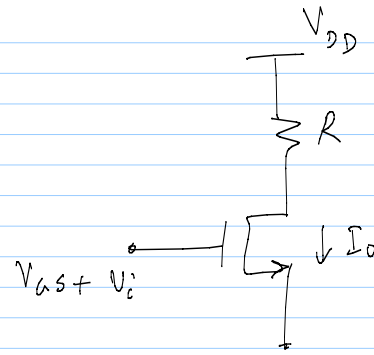

← resistive divider is loaded by I_B

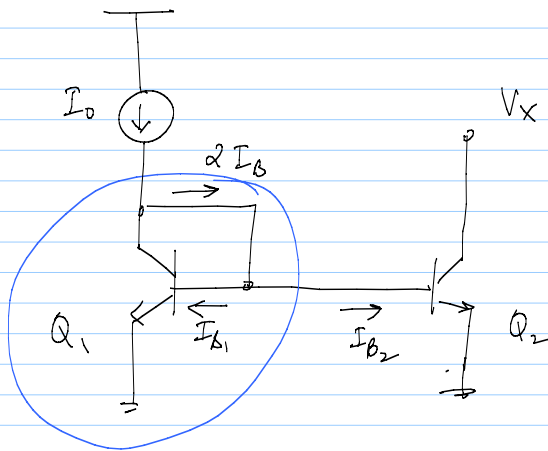

$$V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_S}\right)$$

$$I_{C1} = I_O - 2I_B$$

$$I_{C2} = I_{C1}$$

$$= I_O - 2I_B$$

$$= I_O - 2 \frac{I_{C2}}{\beta}$$

$$I_{C2} = I_O \cdot \frac{\beta}{\beta + 2}$$

Diode