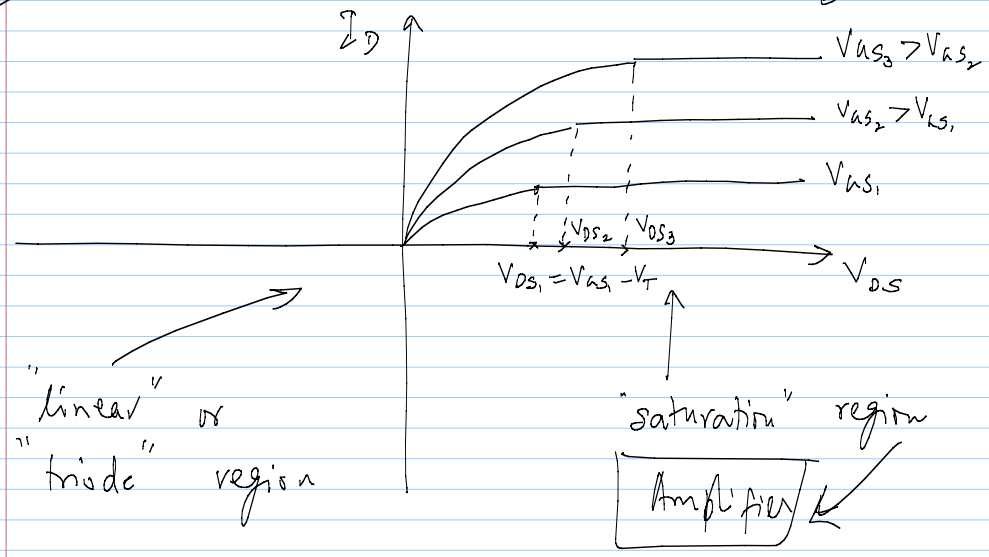


6/8/14

Lec 5

$$V_{DS} > V_{GS} - V_T$$



In linear region:

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$y_{d1} = \frac{\partial f_2}{\partial V_1} = \frac{\partial I_D}{\partial V_{GS}}$$

$$= \mu_n C_{ox} \frac{W}{L} \cdot V_{DS}$$

$$y_{d2} = \frac{\partial f_2}{\partial V_2} = \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_T - V_{DS}]$$

If $V_{DS} \ll (V_{GS} - V_T)$

$$y_{d2} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

⇒ Voltage-controlled resistance

In sat. region:

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [V_{GS} - V_T]^2$$

$$y_{d1} = \frac{\partial f_2}{\partial V_1} = \frac{\partial I_D}{\partial V_{GS}} = g_m \text{ "transconductance"}$$

$$1) g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DSQ}} = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GSQ} - V_T)$$

$$2) g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot \underbrace{\sqrt{\frac{2 I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}}}_{V_{GS} - V_T}$$

$$= \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$





$$3) \quad g_m =$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right) = \frac{2I_D}{(V_{GS} - V_T)^2}$$

$$g_m = \frac{2I_D}{(V_{GS} - V_T)^2} \cdot (V_{GS} - V_T)$$

$$= \frac{2I_D}{(V_{GS} - V_T)}$$

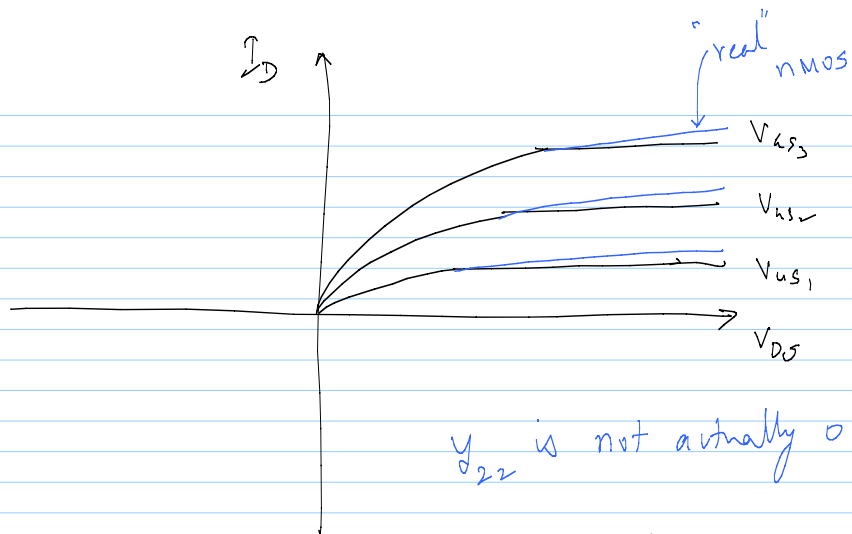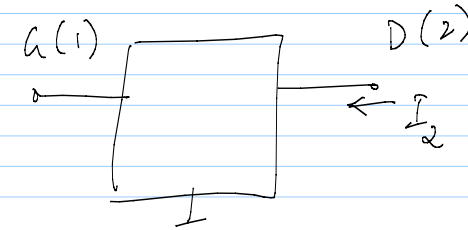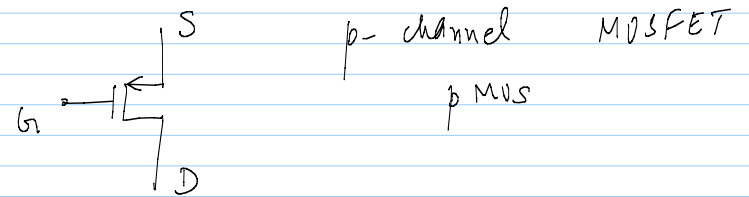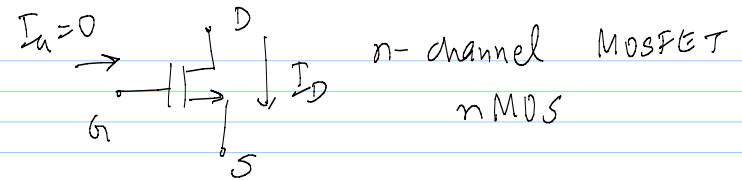

$$\frac{v_L}{v_S} = \frac{-y_{21}}{y_{22} + G_L}$$

as long as $y_{22} \ll G_L$
"good" amplifiers

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

λ is very small