

Tutorial 1: Electric & Magnetic Circuits

Many of these are textbook problems. I have scanned and pasted them here for the benefit of students

13. Employ nodal analysis to obtain a value for v_x as indicated in Fig. 4.43.

Problem 1

By inspection, write the MNA equations.

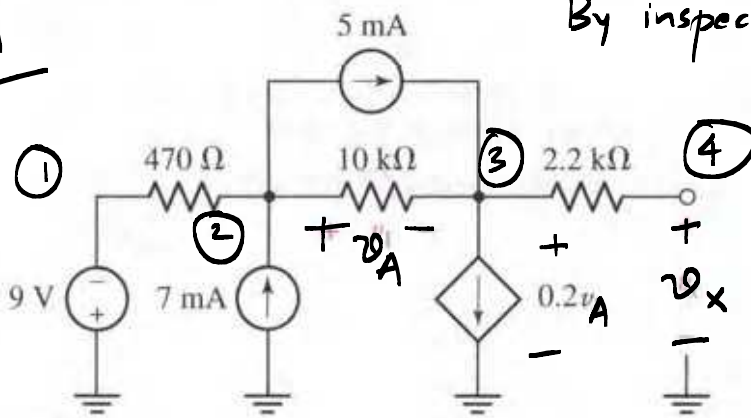


FIGURE 4.43

15. Determine the nodal voltages indicated in the circuit of Fig. 4.45.

Write the MNA equations by inspection.

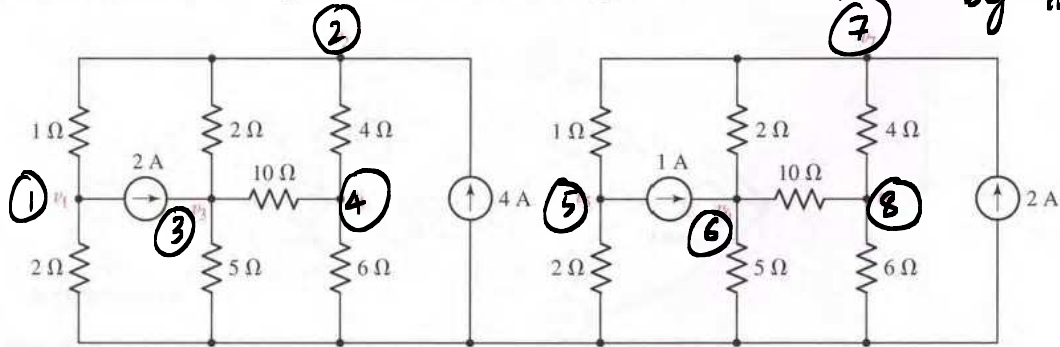


FIGURE 4.45

Modified

17. With the help of nodal analysis on the circuit of Fig. 4.47, find (a) v_A ; (b) the power dissipated in the $2.5\ \Omega$ resistor.

Problem 2

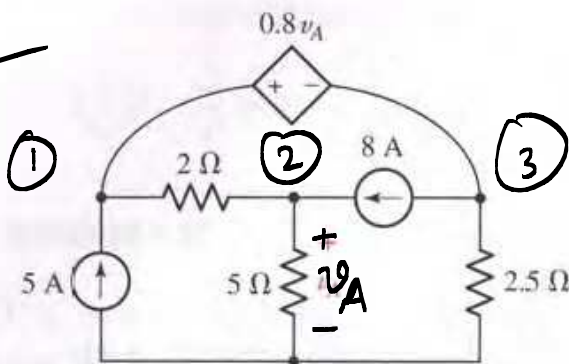


FIGURE 4.47

Problem 3

Modified

19. In Fig. 4.49, use nodal analysis to find the value of k that will cause v_y to be zero.

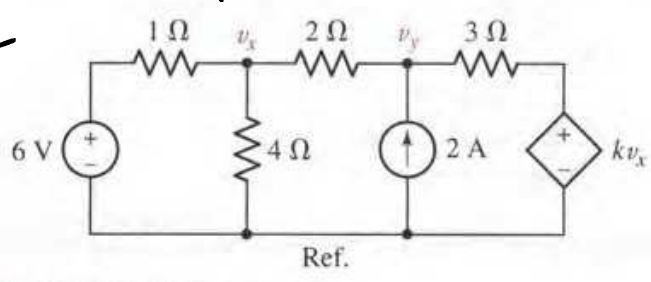


FIGURE 4.49

Problem 4

24. Determine the power supplied by the 2 A source in the circuit of Fig. 4.54.

Use your favorite method of analysis.

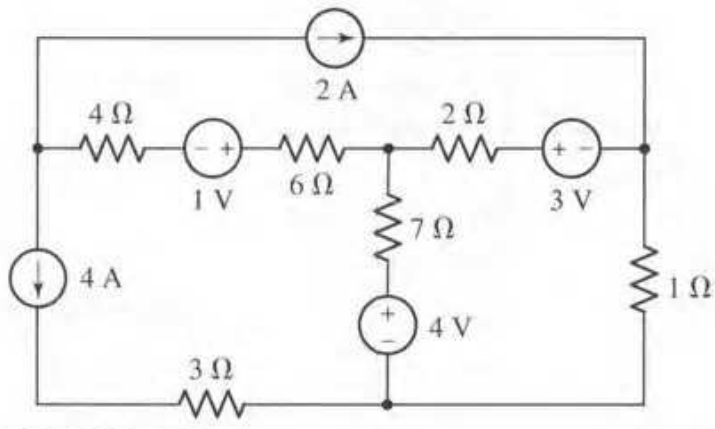


FIGURE 4.54

Problem 5

25. Make use of the supernode concept to assist in the determination of the voltage labeled v_{20} in Fig. 4.51. Crossed wires not marked by a solid dot are not in physical contact.

Write the MNA equations. The nodes are numbered.


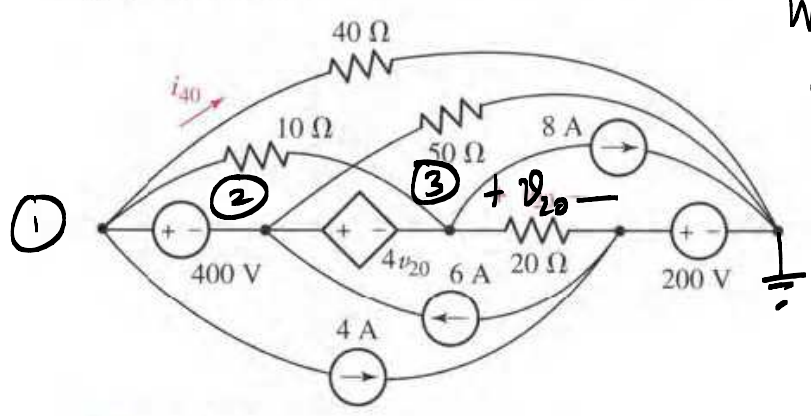



FIGURE 4.51

Problems 6 & 7

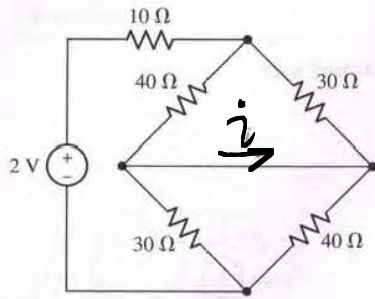

■ FIGURE 4.60

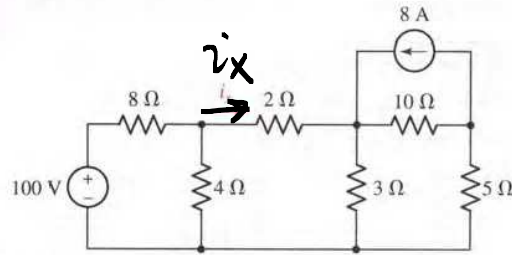
- ✎ Use mesh analysis to determine the current labeled i in the circuit of Fig. 4.60.
- ✎ Use mesh analysis to find i_x in the circuit shown in Fig. 4.61.



■ FIGURE 4.61

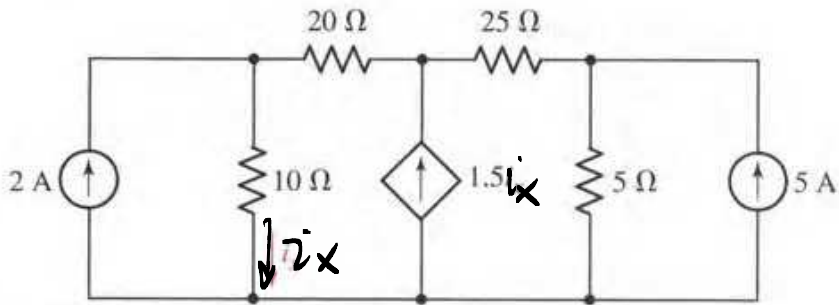
Problem 8

- ✎ Use mesh analysis to find i_x in the circuit shown in Fig. 4.63.




■ FIGURE 4.63

Problem 9 & 10

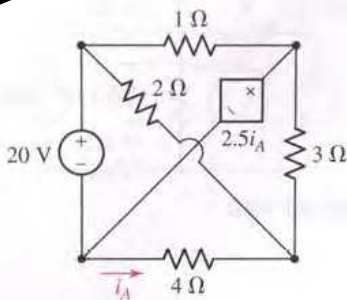

■ FIGURE 4.71

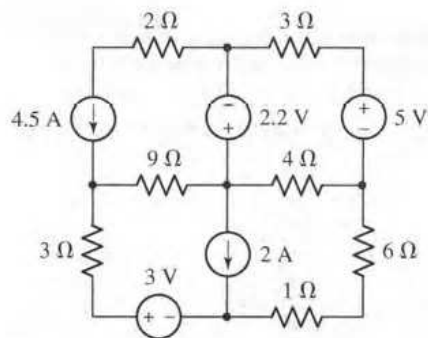
- ✎ Find i_A in the circuit of Fig. 4.71.
- ✎ Use the supermesh concept to determine the power supplied by the 2.2 V source of Fig. 4.72.



■ FIGURE 4.72

Prob. 11


Employ mesh analysis to obtain the voltage across the 2.5Ω resistor of Fig. 4.74.

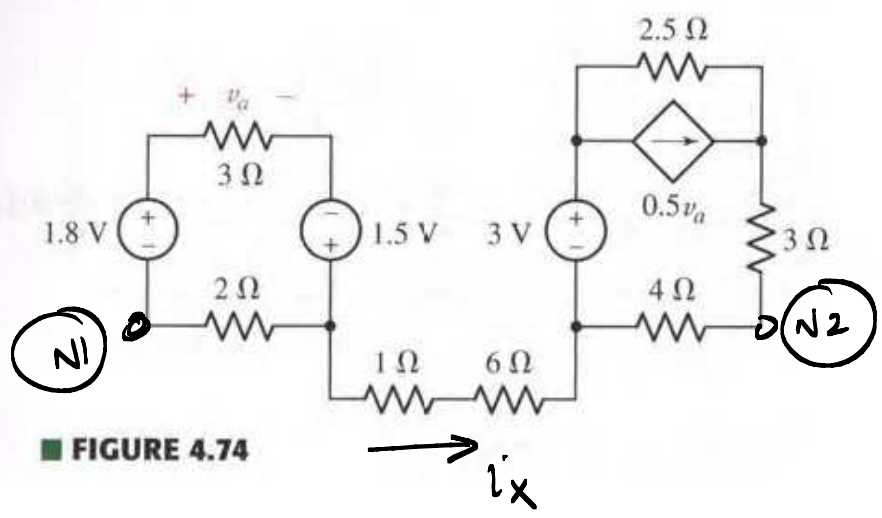

Prob. 12

Determine i_x above if $N1$ & $N2$ are grounded.

Prob. 13

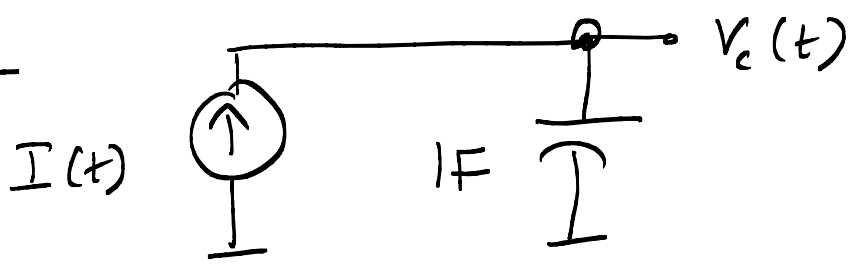


Sketch $V_c(t)$ if $I(t)$ is given by the following.

$$I(t) = 0, \quad t < 0$$
$$= \cos(2\pi t), \quad t \geq 0$$


The capacitor is initially uncharged.

Prob. 14

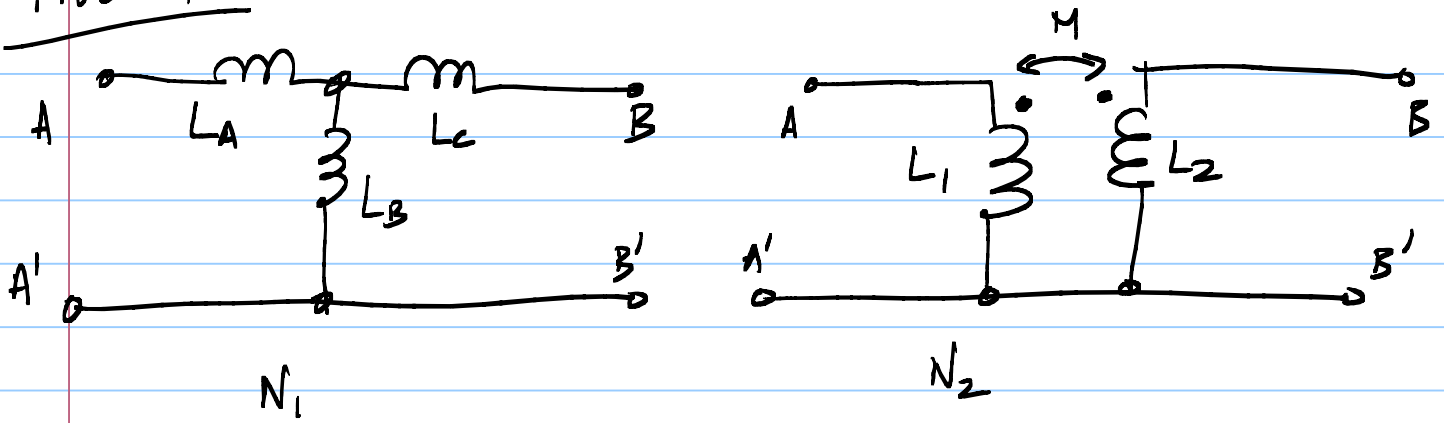


Determine L_A , L_B , L_C if the two networks above are equivalent.

Prob. 15

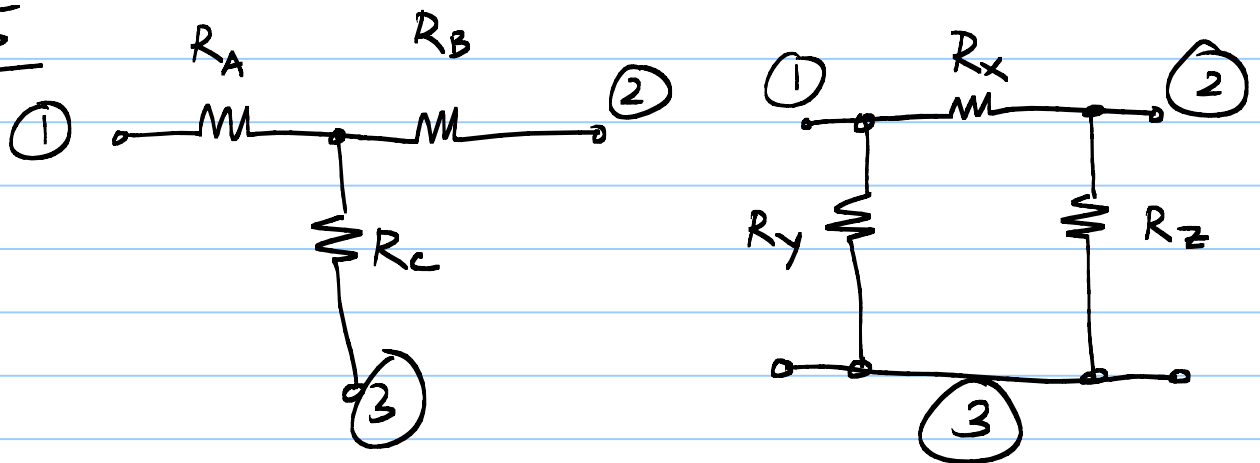


The networks above are equivalent. Determine R_x , R_y & R_z in terms of R_A , R_B , R_C .

Prob. 16

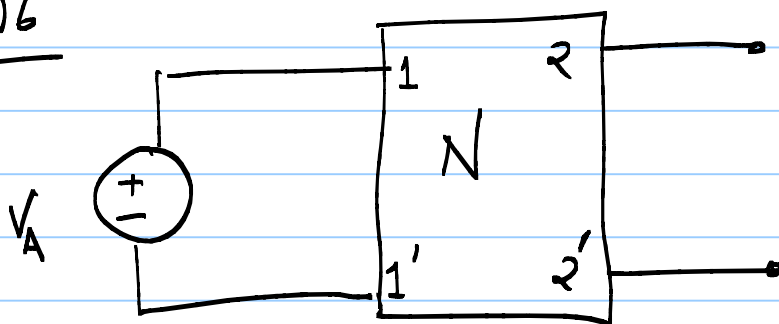


The network N consists of resistors only. Let P_V denote the power dissipated in N

when V_A is present.

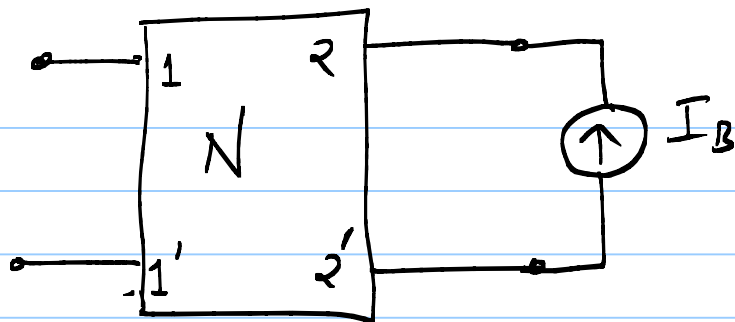

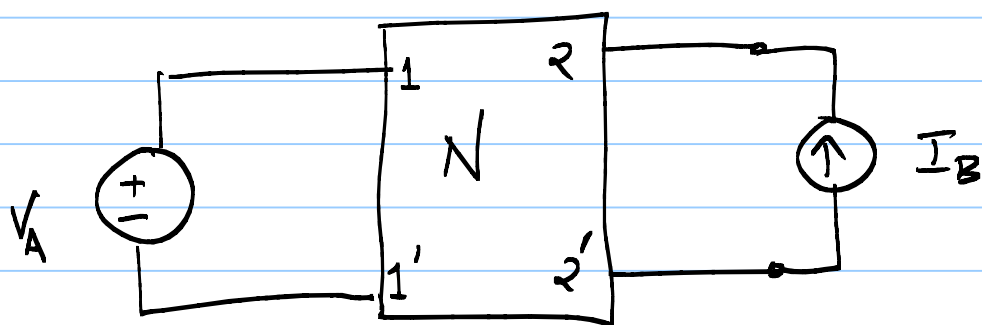Let P_I denote the power dissipation in N when N is excited by I_B .



Determine the power dissipated in N .
 Is this result true for any arbitrary network?