

# Electric & Magnetic Circuits

## Problem Set 2

Note Title

03-02-2012

- 1) Let  $P_{E_1+E_2}$  and  $P_{E_1-E_2}$  be the powers dissipated in a network  $N$  consisting of linear, time-invariant resistances excited by two voltage sources  $E_1$  &  $E_2$  as shown in fig 1(a) & (b) respectively.



Determine

$$(P_{E_1} + P_{E_2})$$

in terms of


$$P_{E_1+E_2} \text{ & } P_{E_1-E_2},$$

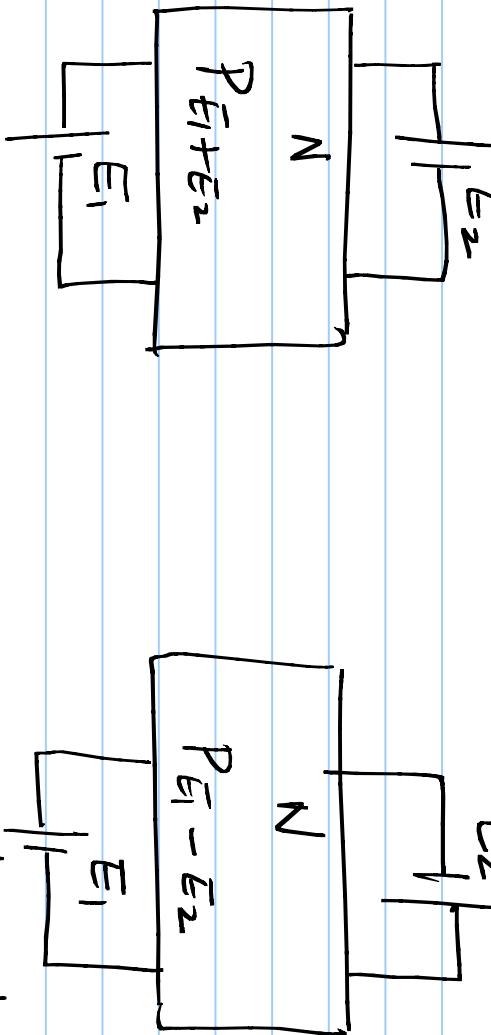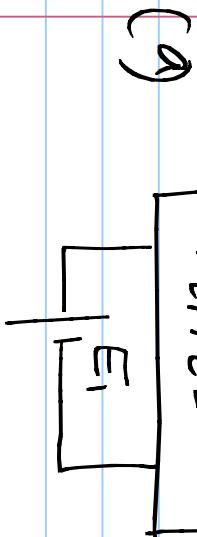where  $P_{E_1}$  &  $P_{E_2}$  are powers dissipated in  $N$  while acting alone.



## Problem 2

All resistors  
are in ohms.

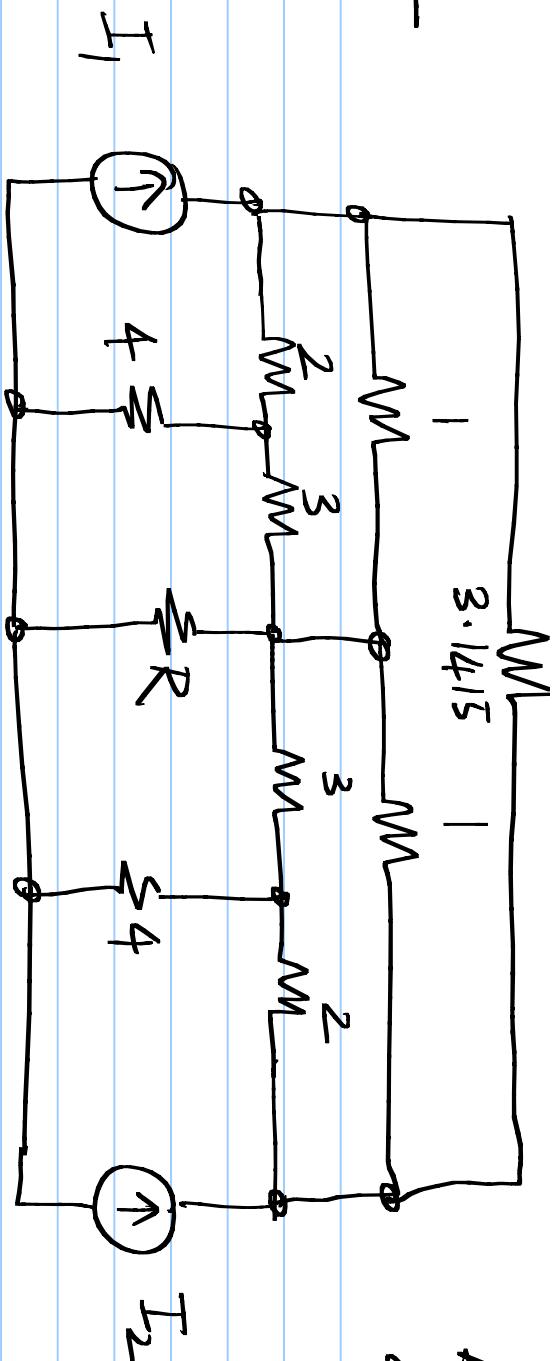

(a) for  $I_1 = I_2 = 1A$ , determine  $R$  so that it dissipates the maximum power. What is the value of the power?

(b) Repeat the above exercise for  $I_1 = -1A$  &  $I_2 = 1A$


(c) Repeat (a) for  $I_1 = 1A$  &  $I_2 = 4A$

Problem 3 :- A network N composed of resistors only has two pairs of terminals brought out. When a voltage source of  $20V$  is connected across the first pair of terminals, resistances of  $2\Omega$  &  $6\Omega$  connected across the other pair of terminals draw  $4A$  &  $2A$  respectively.

- (a) A current source and a variable resistance are now connected in parallel across the second pair of terminals and the resistance is varied till the power consumed by it is maximum, this maximum being  $18W$ . What is the magnitude of current in the current source?

- (b) The voltage source is replaced by an ammeter and a voltage source of  $30V$  is connected at the second pair of terminals. What is the current read by the ammeter?

#### Problem 4

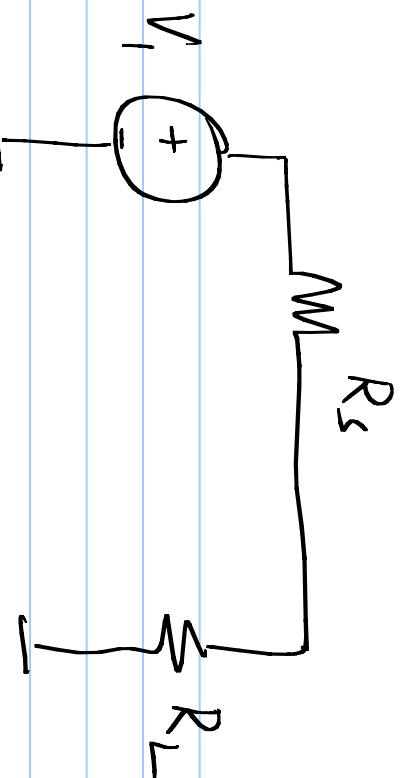

(denoted by  $P_L$ )

Show that the power dissipated in  $R_L$  can be expressed as


$$P_L = P_{\max} \left( 1 - |\Gamma_L|^2 \right)$$

Where  $\Gamma_L = \frac{R_L - R_s}{R_L + R_s}$ , and  $P_{\max}$  is independent of

$$\frac{R_s}{R_L}.$$


Determine  $P_{\max}$ .  $\Gamma_L$  is called the reflection coefficient of the load  $R_L$ . For what  $\Gamma_L$  is maximum power dissipated in  $R_L$ ?

Problem 5:

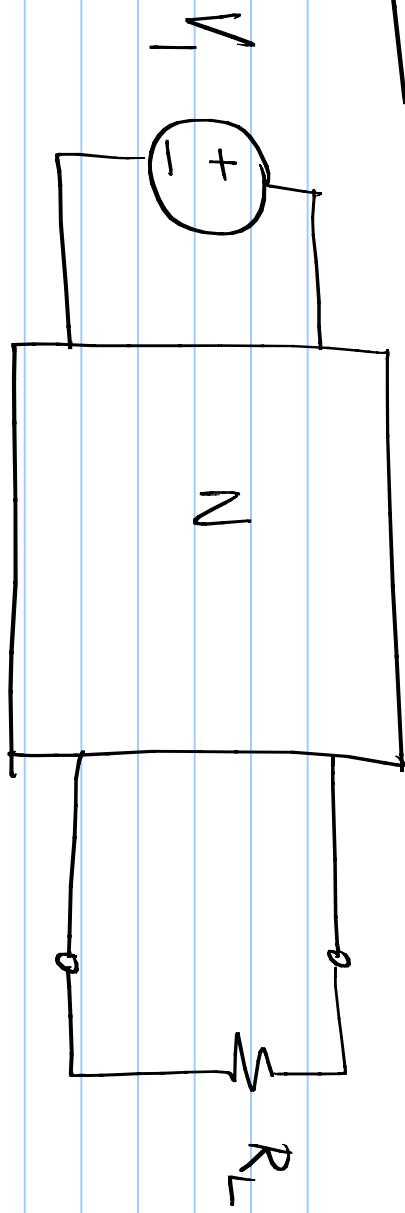

$N$  is a network with resistors only. It is observed that the power dissipated in  $R_L$  is equal to 8W when  $R_L$  is either  $25\Omega$  or  $100\Omega$ . Determine the power dissipated in  $R_L$  when  $R_L = 75\Omega$ .


### Problem b

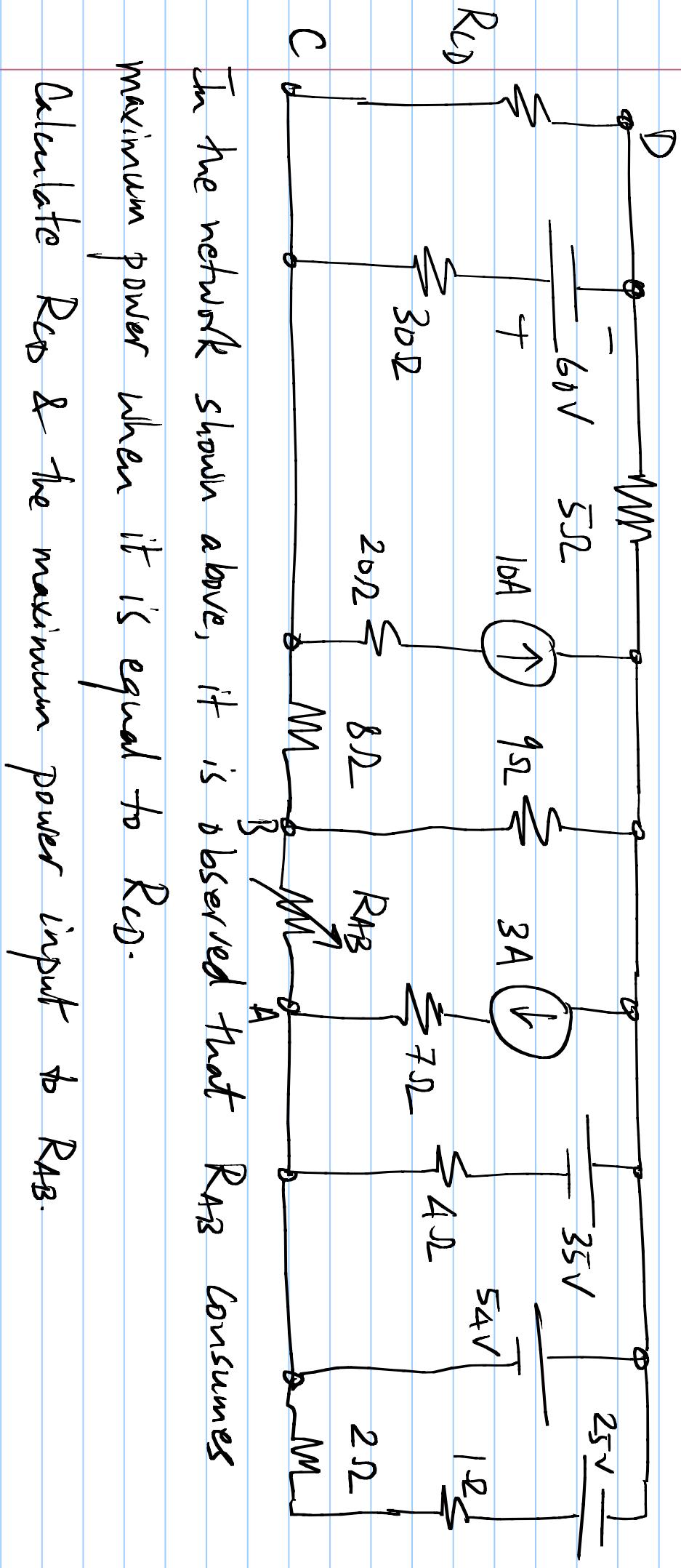

In the network shown above, it is observed that  $R_{AB}$  consumes maximum power when it is equal to  $R_D$ .


Calculate  $R_D$  & the maximum power input to  $R_{AB}$ .

### Problem 7

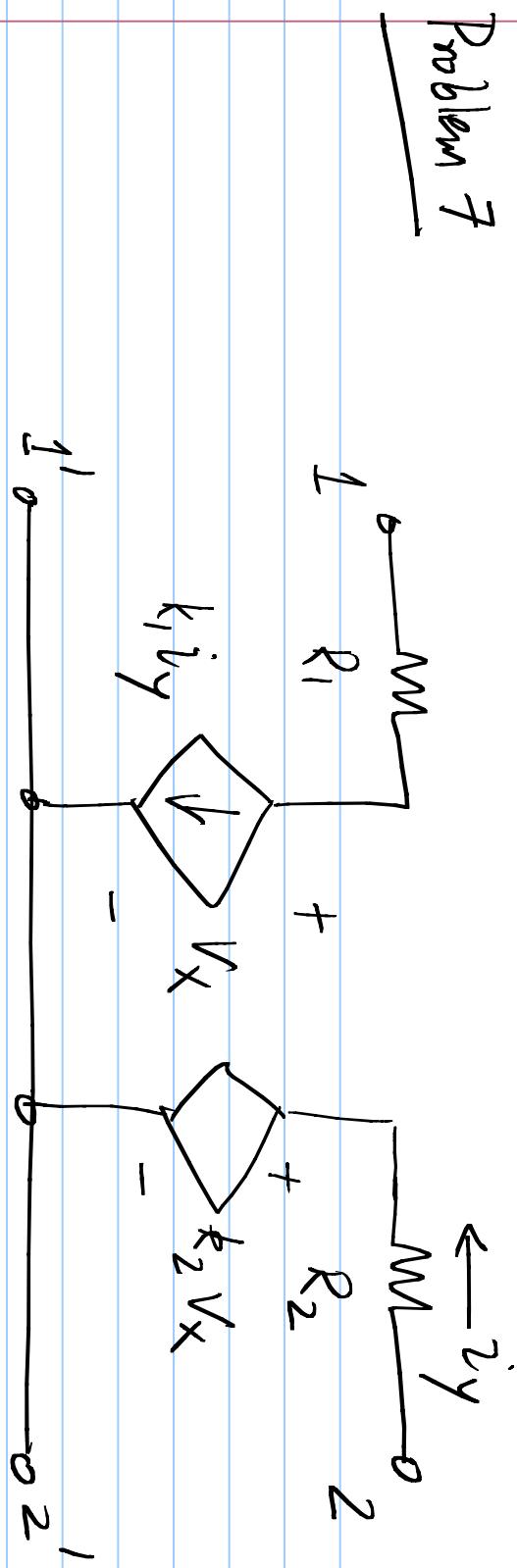

The two port shown above should be reciprocal. Determine the condition that should exist among the constants  $k_1$ ,  $k_2$  and  $R_1$ ,  $R_2$ .

Problem 8

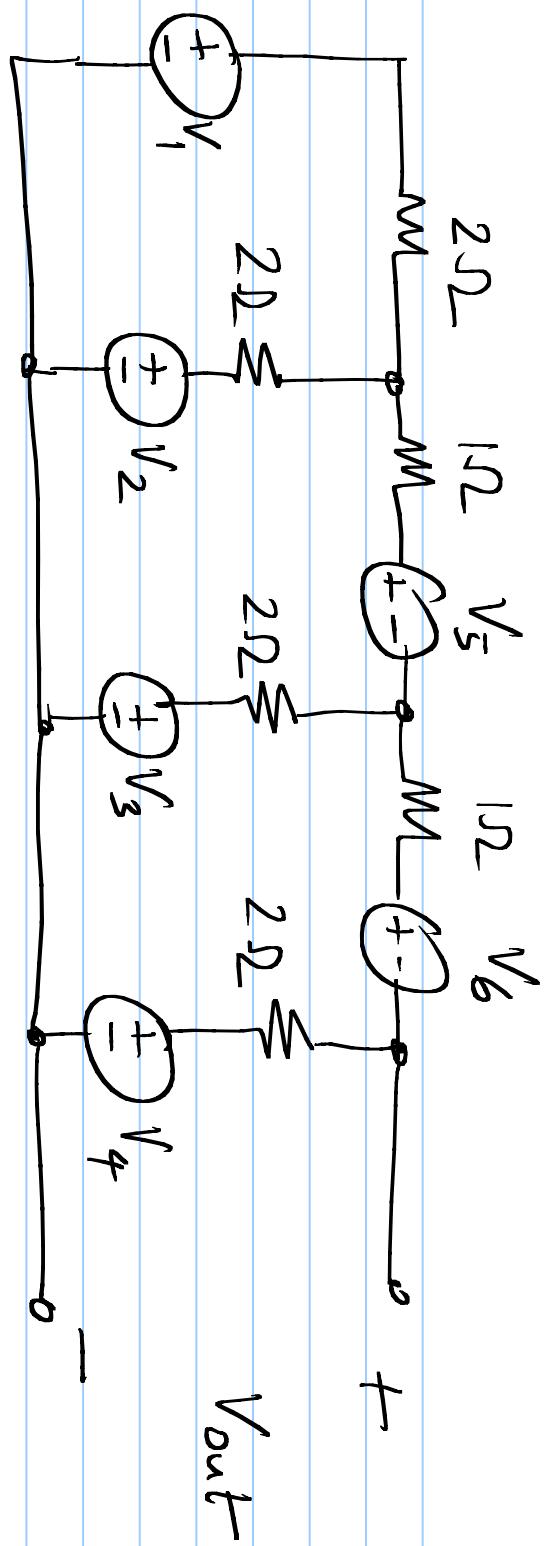


In the circuit above, determine

$$\frac{V_{out}}{V_1}, \frac{V_{out}}{V_2}, \dots, \frac{V_{out}}{V_6}$$

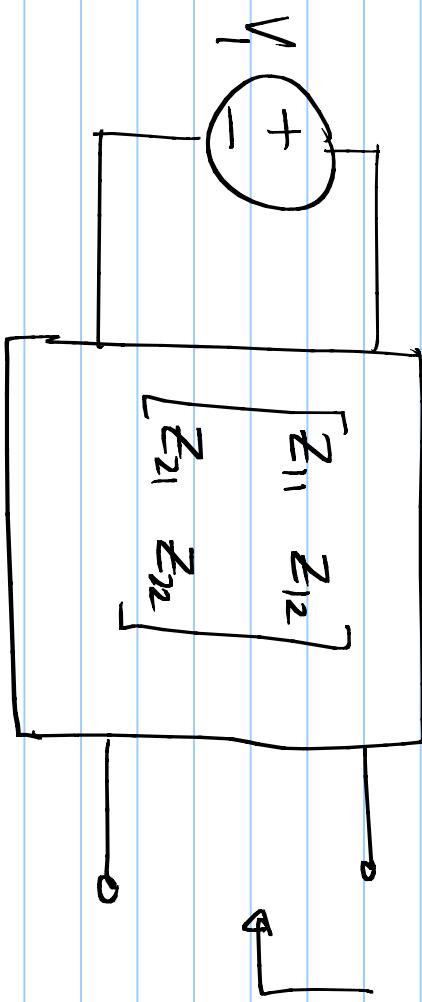Problem 9


Determine the Thevenin equivalent of the following




Thevenin eq.?

Problem 1D

Determine the Norton equivalent of the following

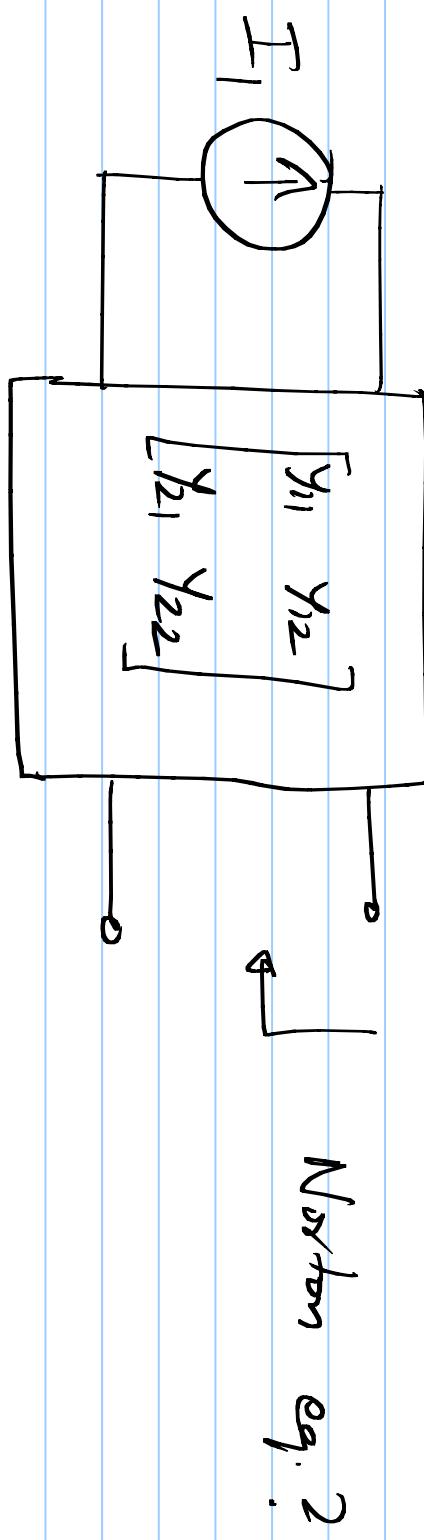

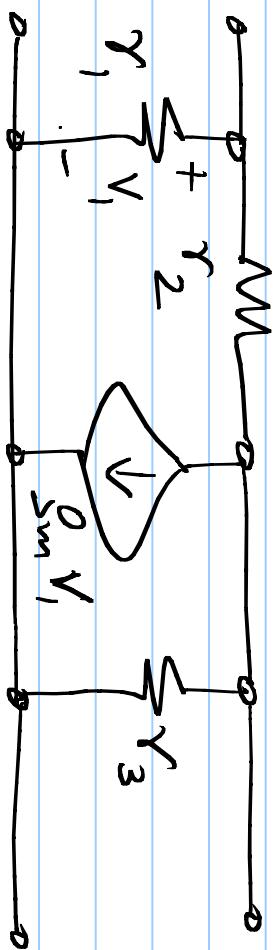
Problem 11: Determine the  $\gamma$ -parameters of



$r_1$ ,  $r_2$  &  $r_3$  are resistors.


Determine  $\mu$  so that

$$\gamma_{12} = 0$$

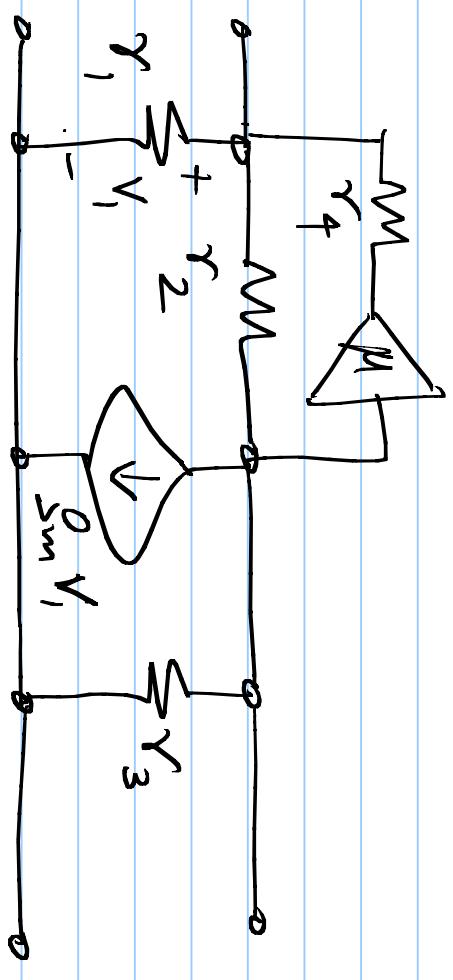


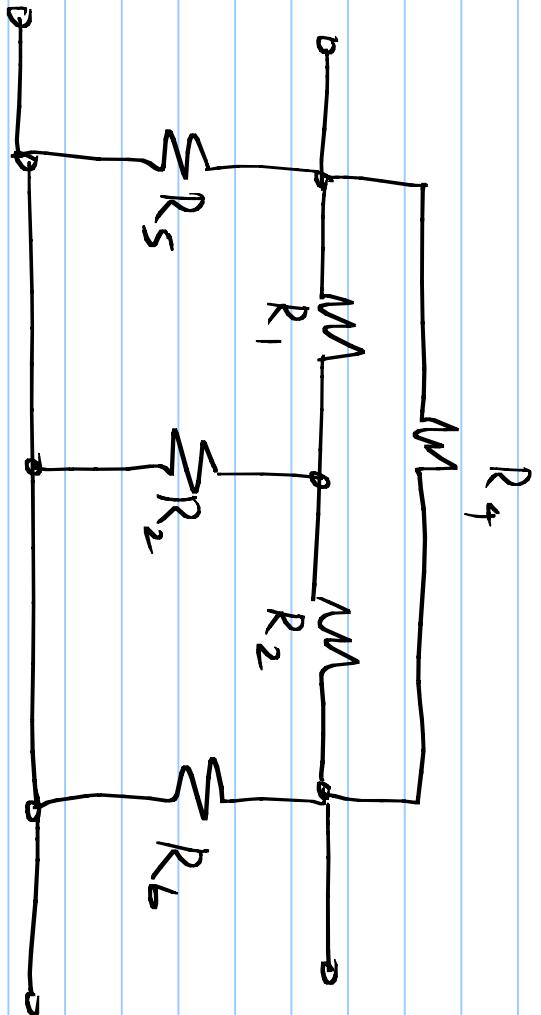
## Problem 12


Determine the  $\gamma$ -parameters of the following



### Problem 13

Determine the signs on the opamps for negative feedback operation. Find  $V_{out}/V_i$ .

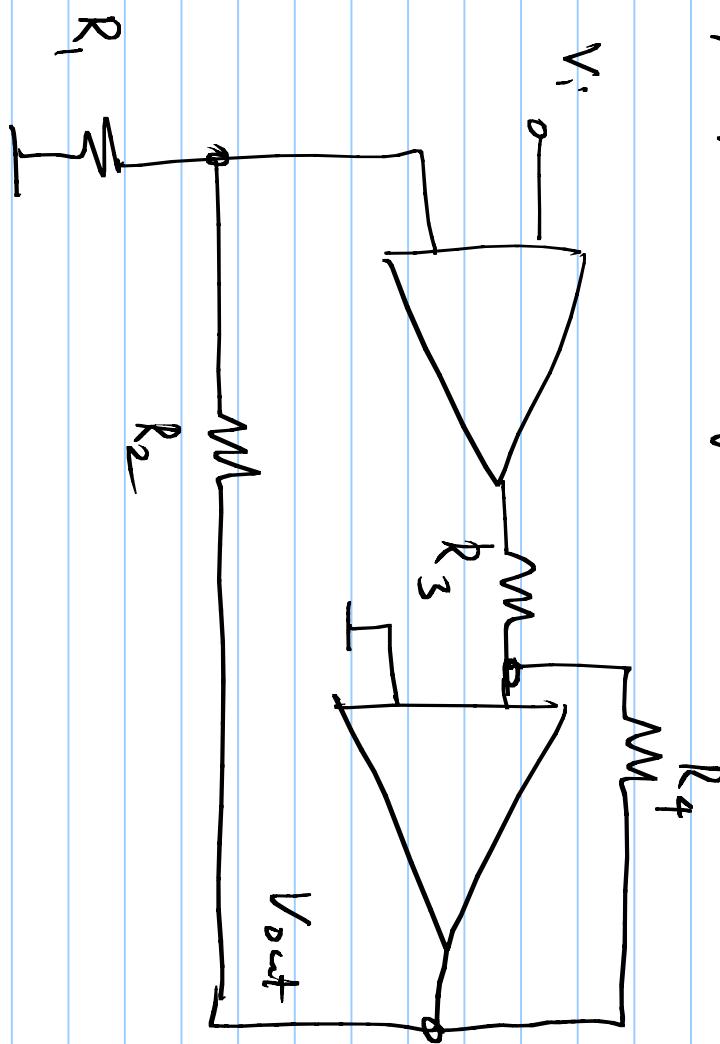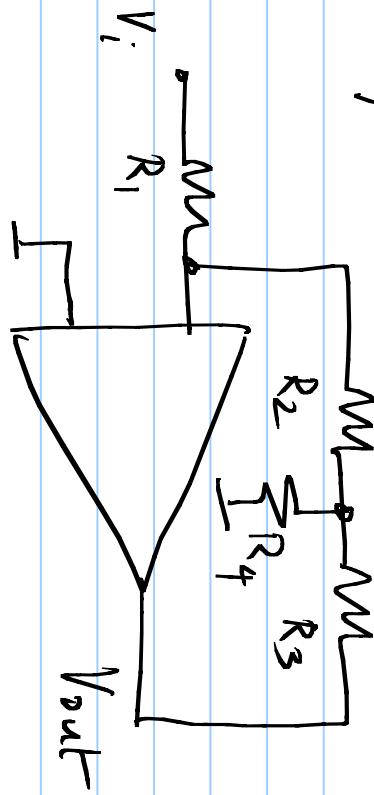

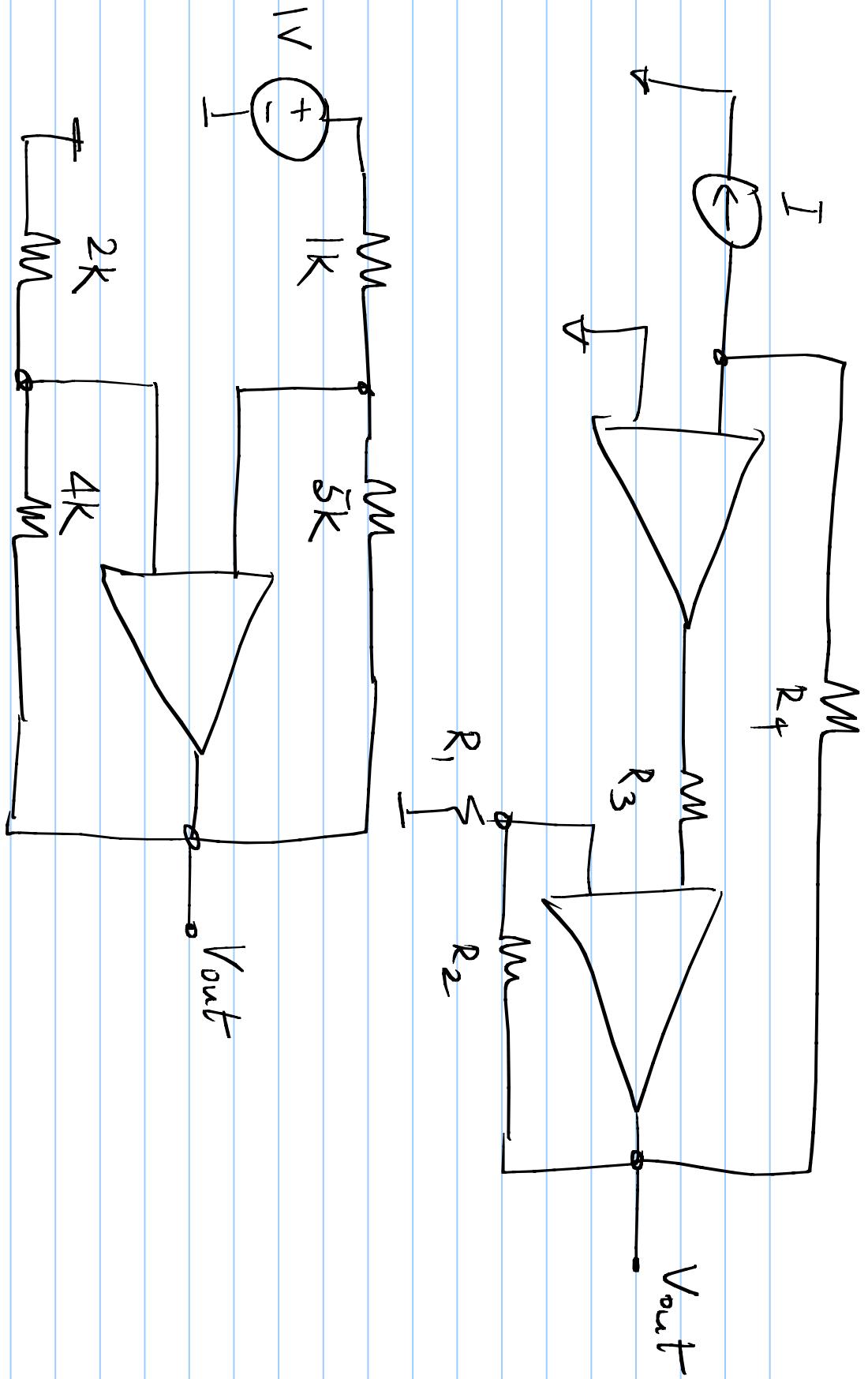

Problem 14

Write the Modified Nodal Analysis (MNA) equations for the following network.

