

# Electric & Magnetic Circuits : Tutorial 4

## Problem 1.

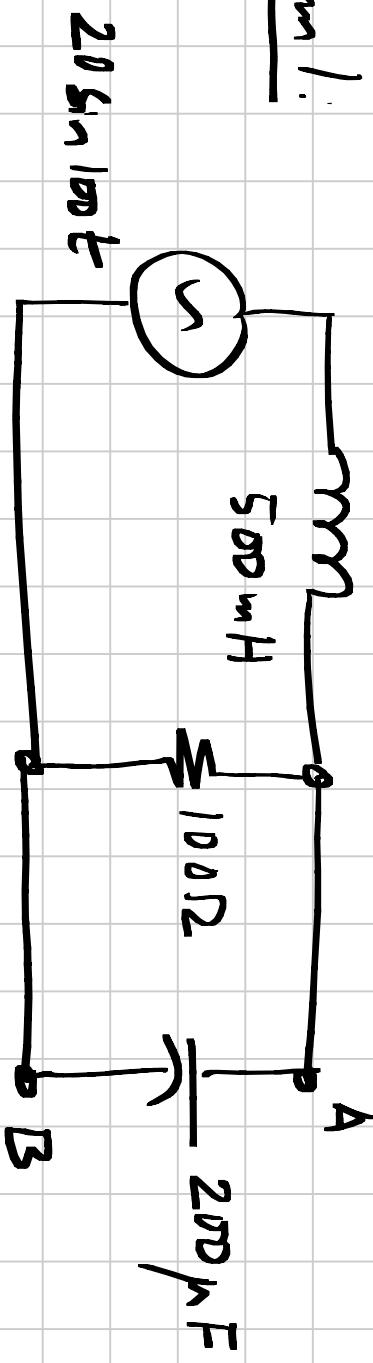


Fig. 1


Determine all branch voltages and currents in steady state, and a phasor diagram representing these voltages and currents.

## Problem 2:




Repeat problem 1 when the current source shown is connected to terminals A & B in Fig. 1.

Problem 3. Determine the  $\gamma$ -parameters of the following network.

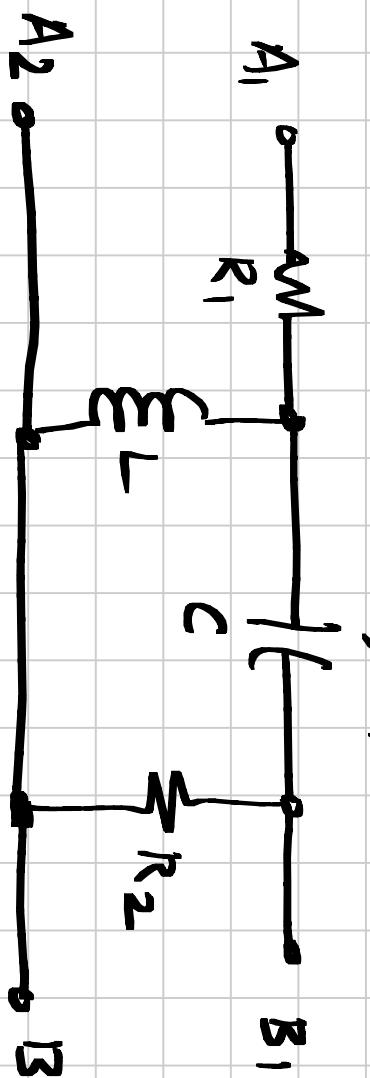

Problem 4.

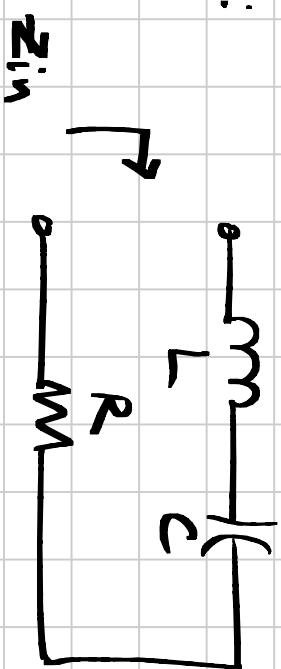

The series RLC network is excited by a voltage at the resonant frequency.

Determine (a) The energy stored in the network at any time.

(b) The energy dissipated in the resistor every cycle


(c) What is the ratio of the two energies above?

Problem 5: Represent the following in phasor notation

(a)  $2 \sin(30t)$  (b)  $2 \sin(30t + 2)$  (c)  $-2 \sin(30t - 5\pi/6)$

(d)  $-2 \cos(-30t + 5\pi/6)$  (e)  $-2 \sin(30t - \frac{5\pi}{2}) + 2 \cos(30t - \frac{5\pi}{2})$

Problem 6:

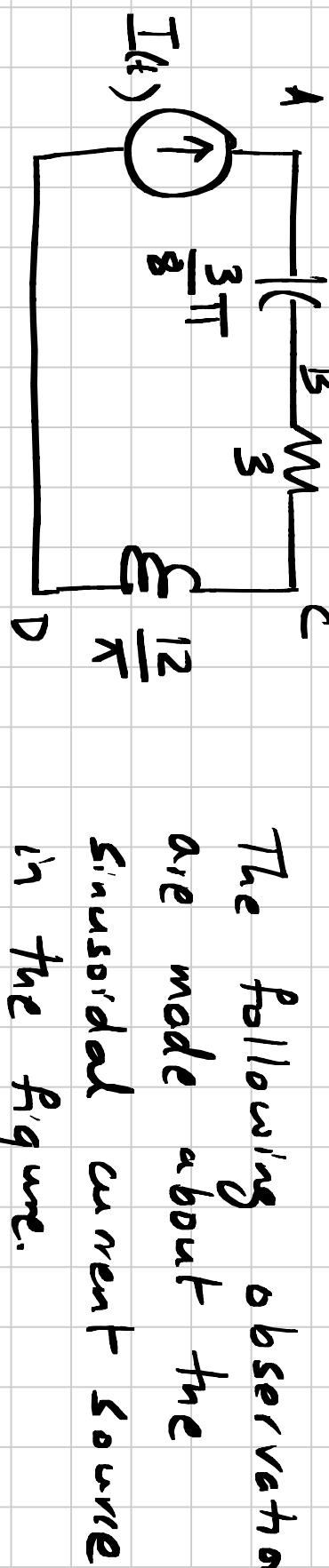

The following observations are made about the sinusoidal current source in the figure.

- (a) At time  $t_1$ ,  $I = 10A$  and  $dI/dt$  is negative.  
(b) At time  $t_1 + 2$ ,  $I = 10A$  and  $dI/dt$  is positive.


(c) In the time interval  $t = t_1$  to  $t = t_1 + 2$ ,  $\mathbb{I}(t)$  has never been more than 10 A.

(d) The energy stored in the inductance has a maximum value of

$$2400 \text{ J} \text{oules}$$

Determine the steady state voltage waveforms across the inductor, resistor and capacitor. What is the energy dissipated in the resistor over one cycle?

Problem 7.

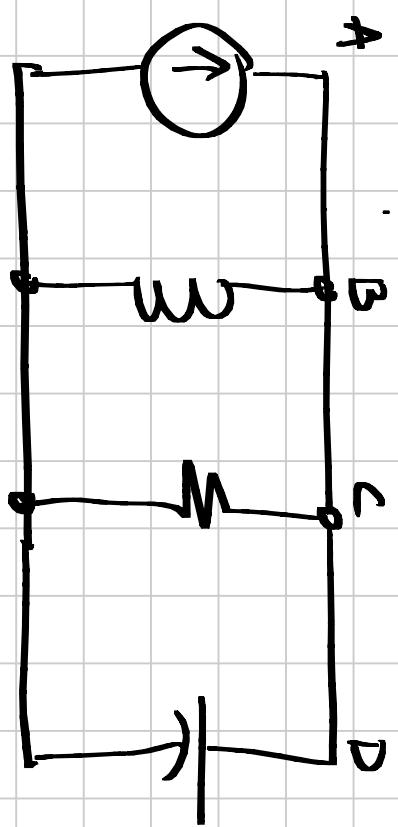

In the network shown in the figure, the currents in the sections AB, BC and CD are

maximum values of 5, 5 and 4 A respectively, and

Determine the values of the impedances of the three branches of the network and the phase angle between  $I_{AB}$  &  $I_{CB}$ .


### Problem 8:

(a) When the element X

across A B is a  $2.5\mu F$

capacitance, the voltage

$$\sqrt{V_{AB}} = E_1, \text{ where } |E_1| = 100V$$

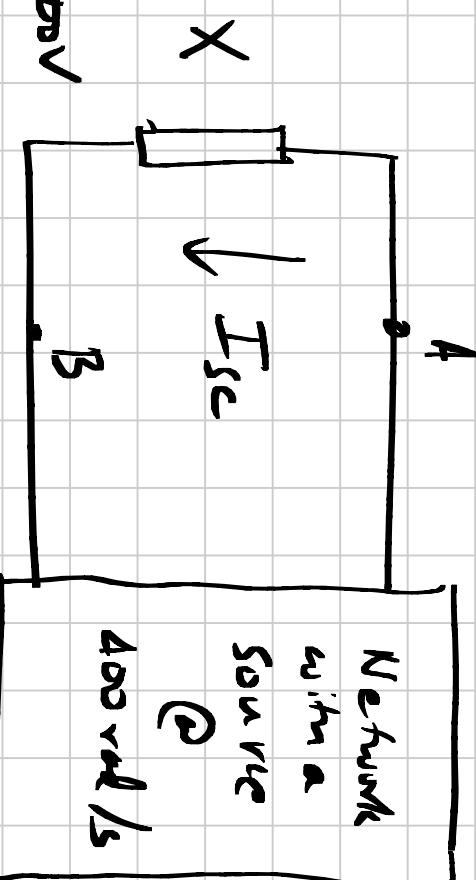


$$400 \text{ ohm/s}$$

(b) When X is a 2 H inductor,  $\sqrt{V_{AB}} = E_2$ , where  $|E_2| = 40V$

$$E_2 \text{ leads } E_1 \text{ by } 90^\circ.$$

(c) Determine  $I_{SC}$ , the short circuit current flowing from A to B if  $x$  is replaced by a short, and its phase angle w.r.t  $E_1$ .

### Problem 7:

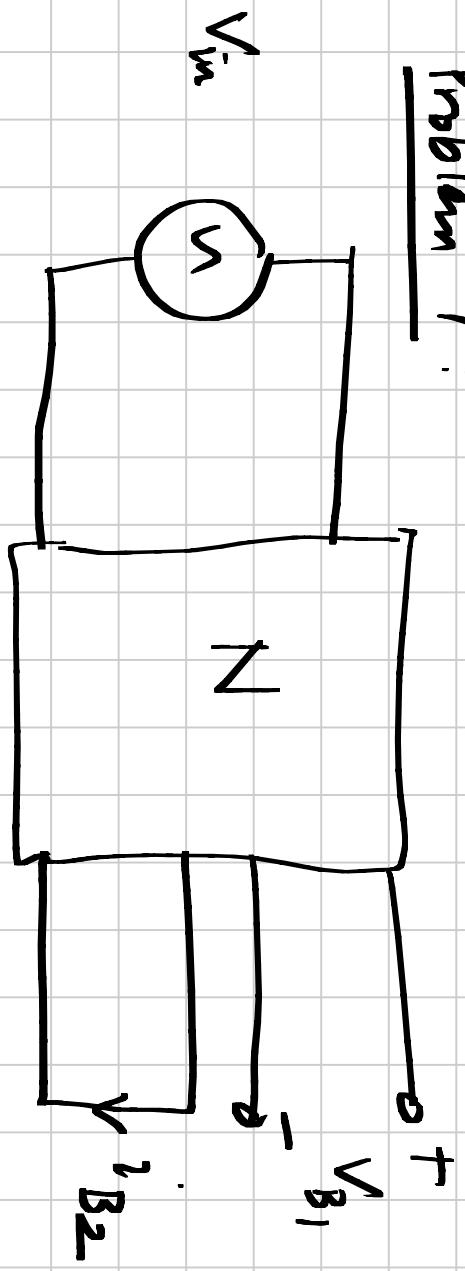

The network N

consists of  $R, L \ \& C$   
and operates in  
steady state at  
freq.  $\omega_1$

A particular branch voltage  $V_B1$  & branch current  $i_B2$   
are denoted in phasor notation by  $\underline{V_A} \ \& \ \underline{I_B}$ .


(a) Now all resistors and inductors in the network are multiplied by

The number  $k$ , while all capacitors are divided by  $k$ . Determine

$V_B$  &  $I_{B2}$ , in phasor notation.


(b) In the original network, all inductors and capacitors are decreased by "k" & input frequency is increased by  $k$ .

Determine  $V_B$  &  $I_{B2}$  now.

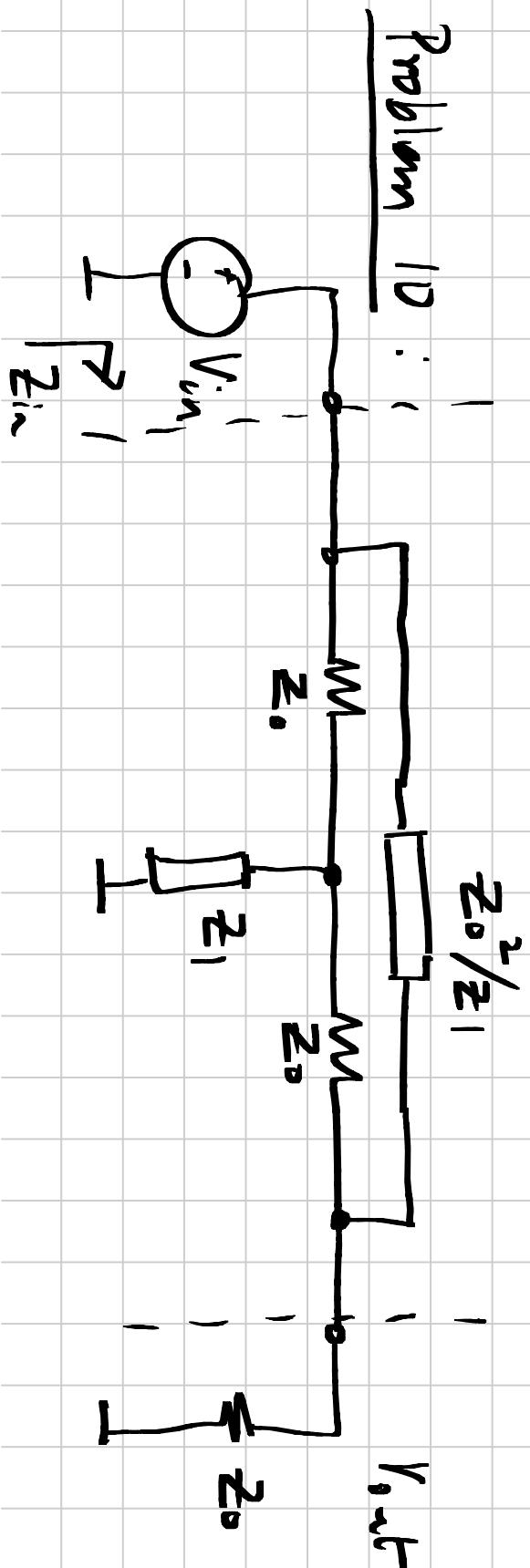


Determine the looking-in impedance  $Z_{in}$  and

$V_{out}/V_{in}$ . Do the same for the network below.

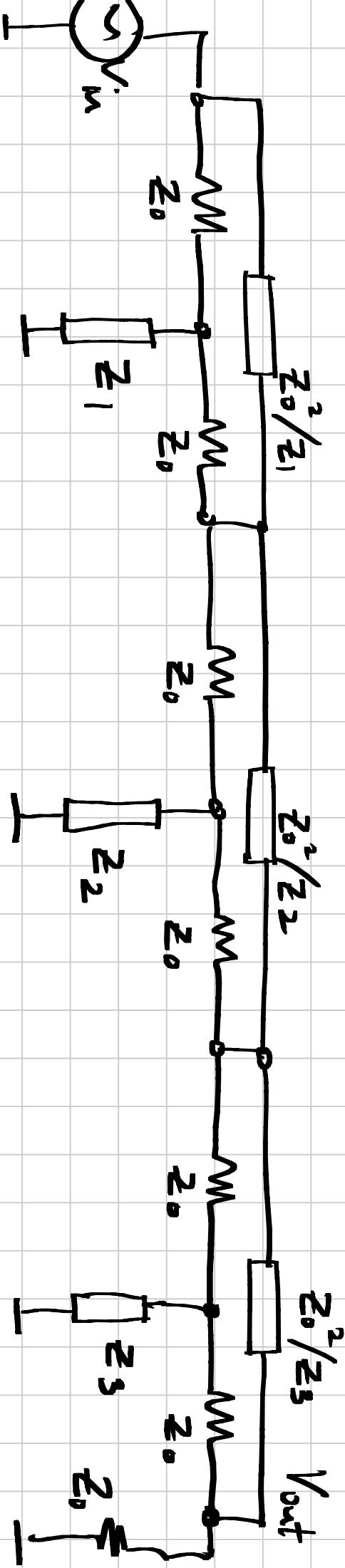


Problem 11:

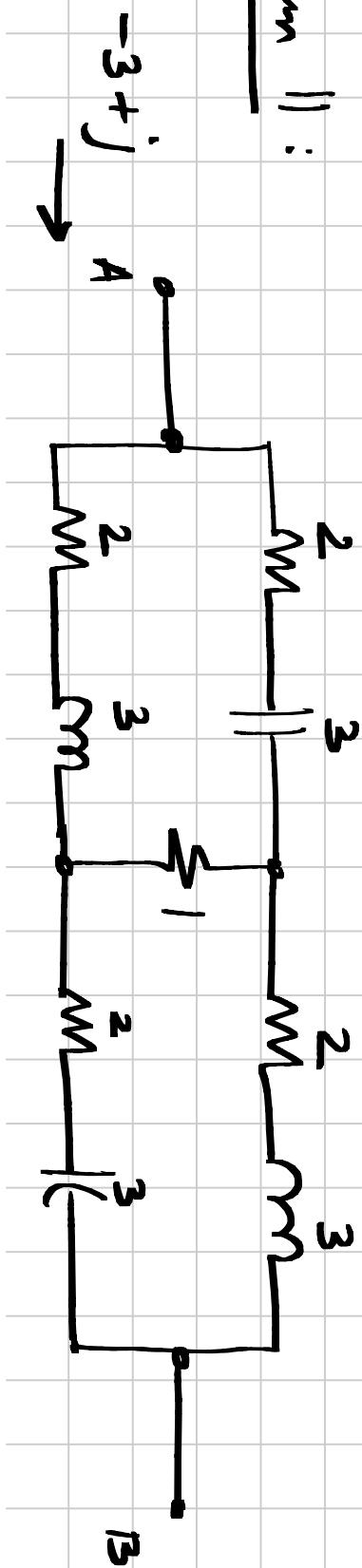

All resistance & reactance values are in ohms.

- A. current  $(-3+j)$  enters the network at A and leaves at B. Determine the current through the  $1\Omega$  resistor.

Problem 12 :

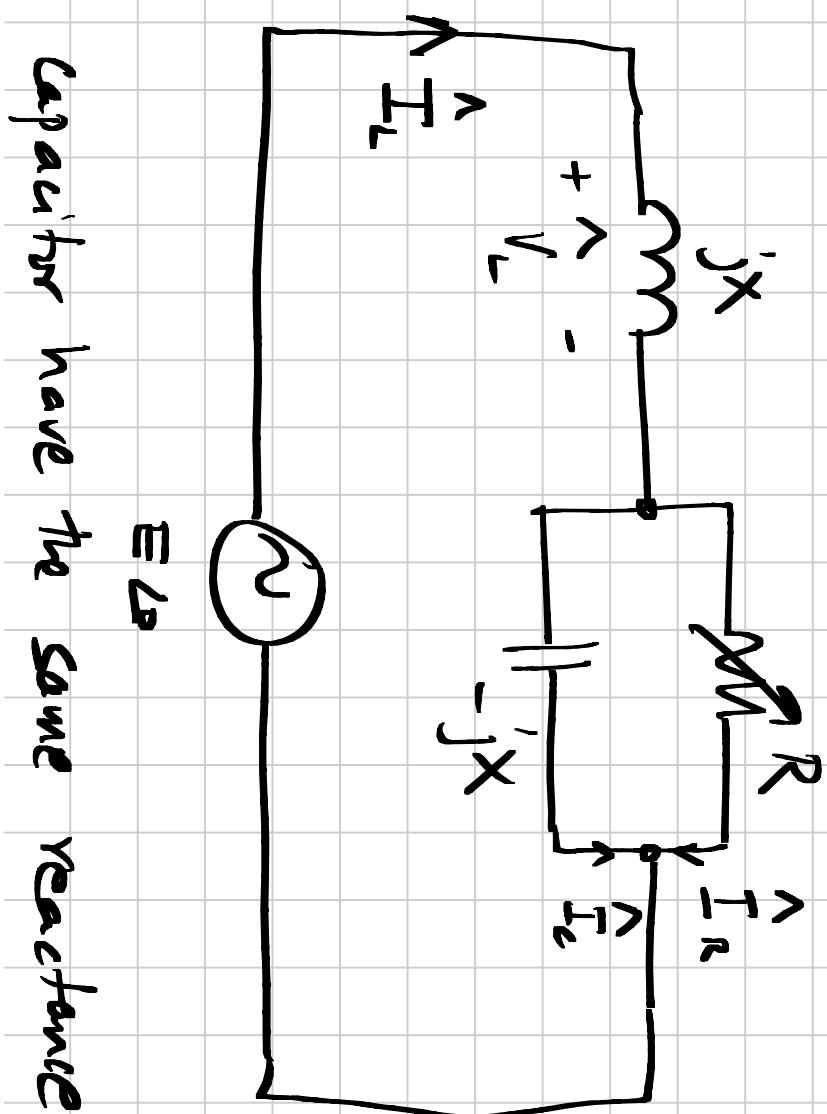

The inductor and capacitor have the same reactance at the

frequency of excitation.


(a) Calculate  $I_R$ , the current through the resistor, in terms of  $E$ ,  $X$  &  $R$ .

(b) Draw a phasor diagram indicating the current through and voltage across  $R$ ,  $L$ ,  $C$  and the source.

(c) Draw the loci of (i)  $V_C$  (ii)  $I_C$  (iii)  $I_L$  and  $V_L$  as  $R$  is varied from 0 to  $\infty$ .

### Problem 13

$$Y(j\omega) \rightarrow$$

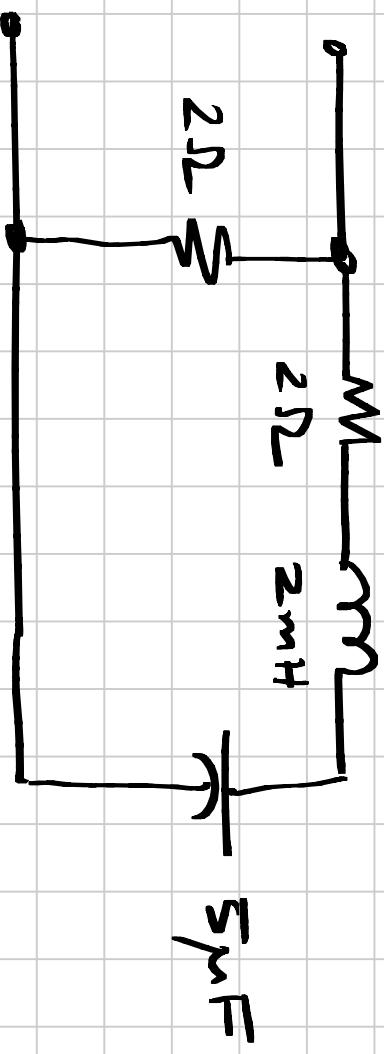


compute  $Y(j\omega)$  and draw its locus as  $\omega$  varies from

$$0 \text{ to } \infty.$$


### Problem 14

$$Y(j\omega) \rightarrow$$

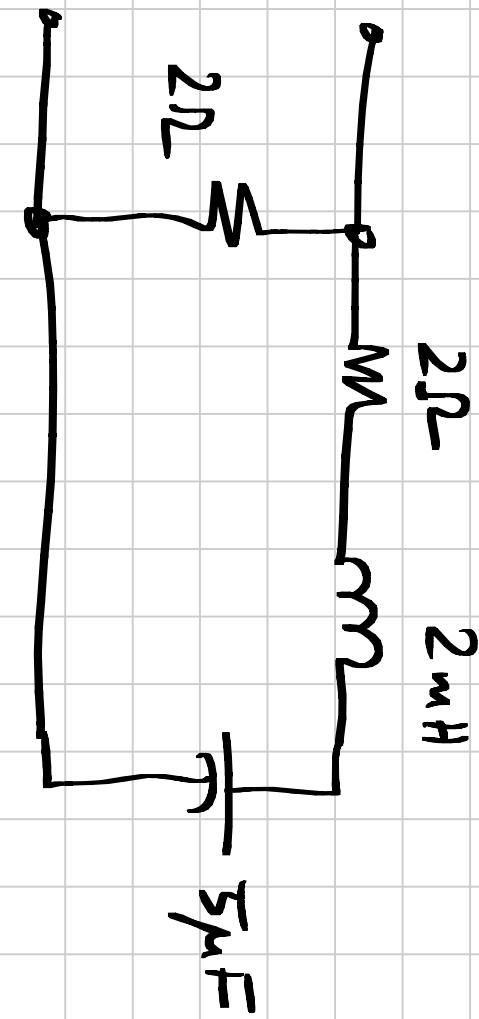


Draw the locus of  $\gamma(j\omega)$  as  $\omega$  varies from 0 to  $\infty$ .

Problem 15

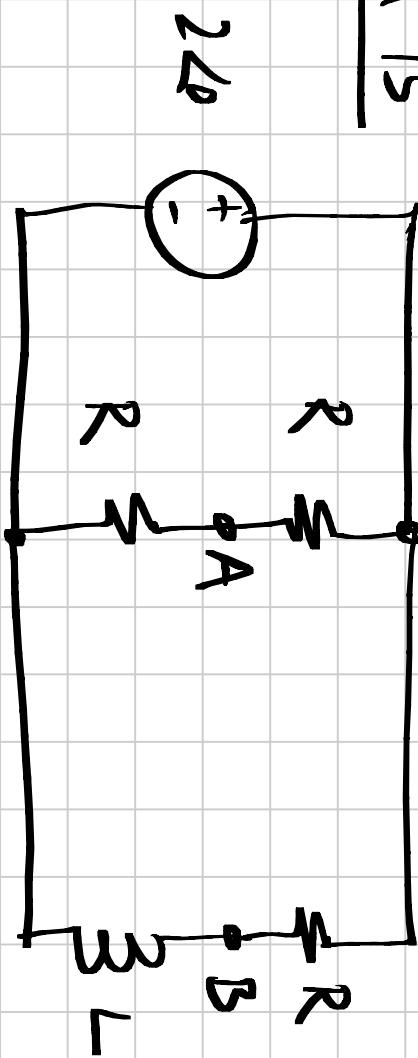


Use a locus diagram to show that the magnitude of  $V_{AB}$  does not change with frequency.

## Problem 16

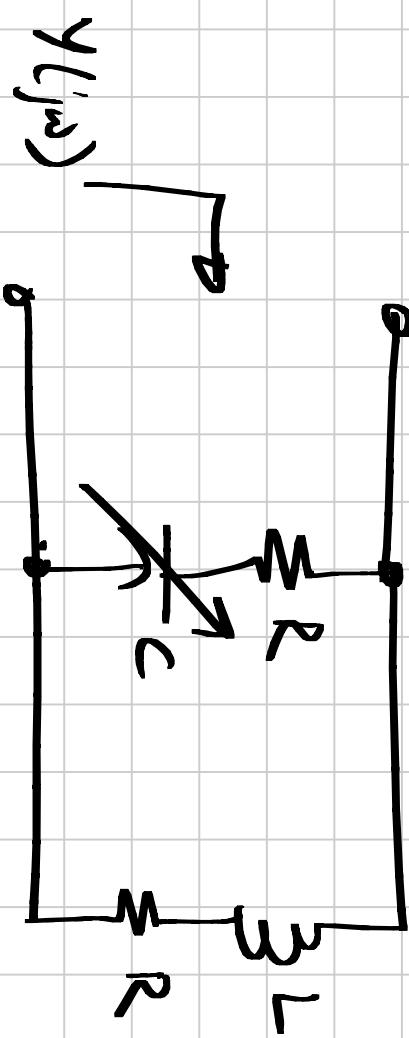

Plot the admittance locus of  $Y$  as  $C$  is varied, for some fixed  $\omega$ .

## Problem 17

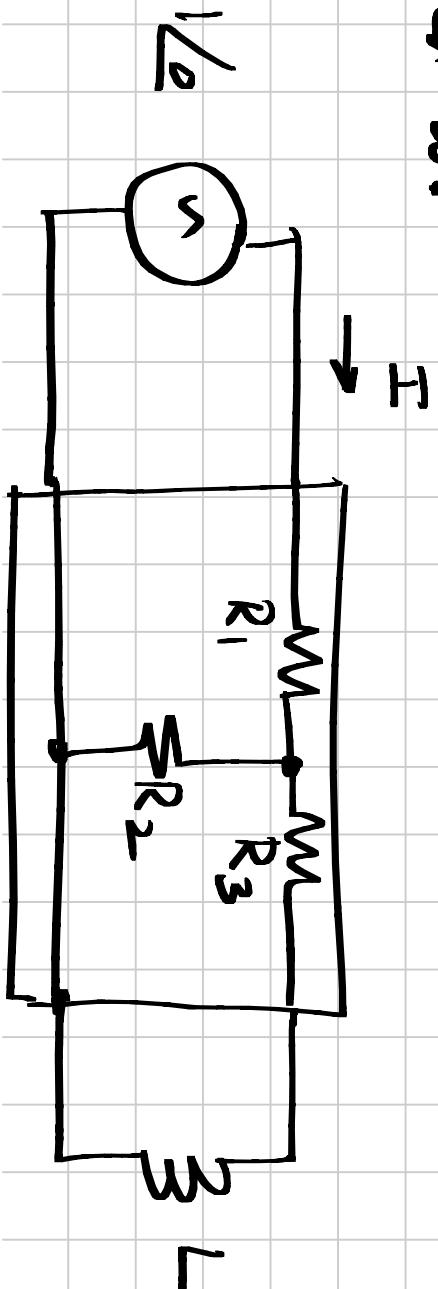

Draw the locus of  $T$  as  $w$  varies from 0 to  $\infty$ .