

EC 1010: Electrical and Magnetic circuits.

Note Title

1/28/2013

Problem set #1 (Due on 2 Feb. 2013)

HKD: Hayt, Kemmerly, and Durbin

Engineering circuit analysis, 7th Edition

Tata McGraw Hill 2010, 2006

Chapter / Problem

① HKD 4.13 (Fig. 4.43)

(label the nodes 1, 2, 3, ... starting from the left)

* Set up the nodal analysis eqn. $[G]V = I$

* Solve for V

* Answer the given question

* Setup the MNA equations

MNA: modified nodal analysis

② HKD 4.16 (Fig. 4.46)

Label the nodes as shown here :)


* Set up the nodal analysis eqn.

$$[G] \underline{V} = \underline{I}$$

* Solve for \underline{V}

* Answer the given question

* Setup the MNA equations

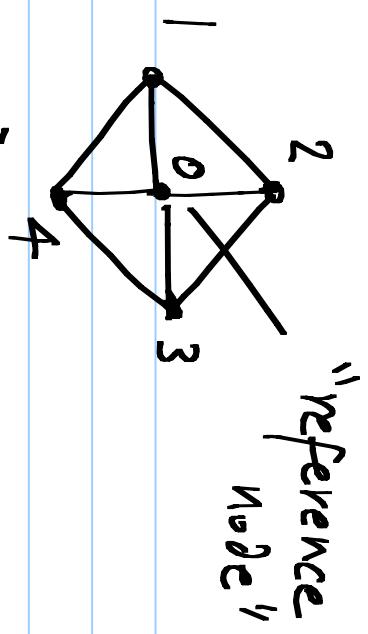

③ HKD 4.17 (Fig. 4.46)


(label the nodes as shown here :)

* Set up the nodal analysis eqn. $[G]V = I$

* Solve for V

* Answer the given question

* Setup the MNA equations

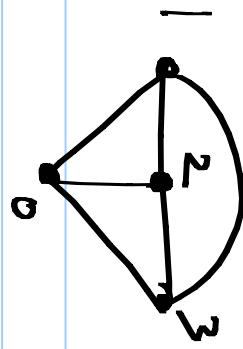

④ HKD 4.19 (Fig. 4.49)


(label the nodes as shown here :)

* Set up the nodal analysis eqn. $[G]V = I$

* Solve for V

* Answer the given question


* Setup the MNA equations

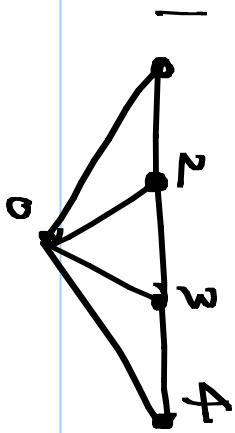

5

$$(a) I(t) = 0 \quad t < 0$$

$$1A \cdot \cos(2\pi t) \quad t \geq 0$$

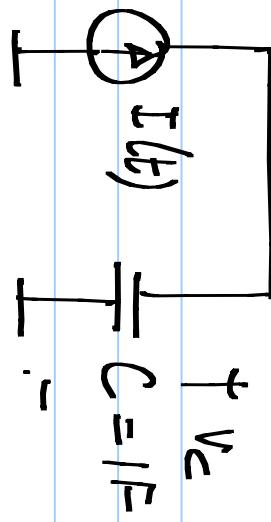

(initially discharged)

$$(b) I(t) = 0 \quad t < 0$$


$$1A \cdot \sin(2\pi t) \quad t \geq 0$$

Determine $V_c(t)$ in the two cases

⑥

The following two networks are equivalent.

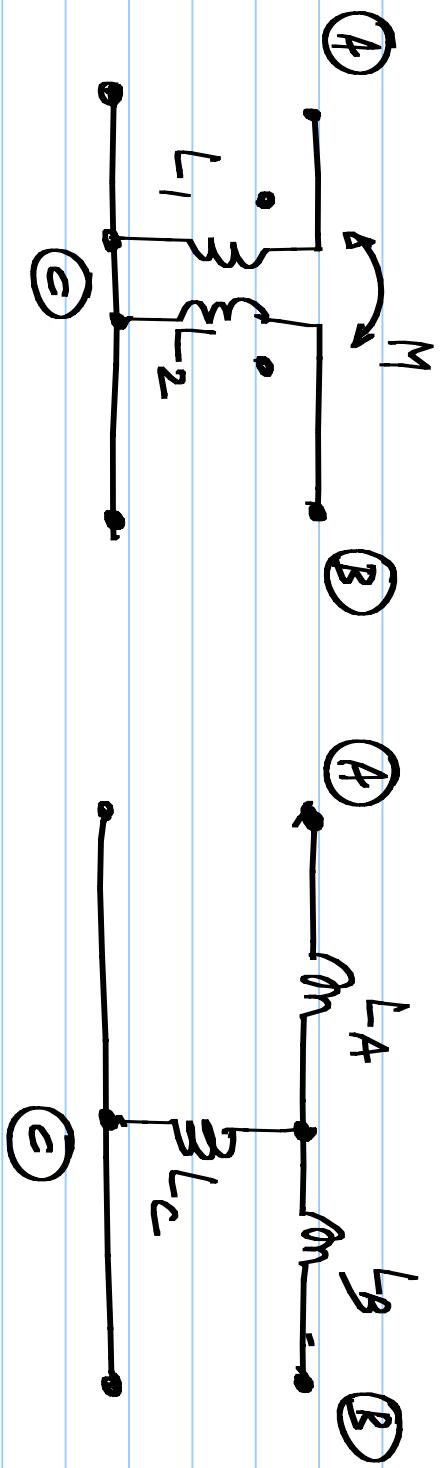Determine L_A , L_B , L_C in terms of L_1 , L_2 , M



(Y)

(a)

V_A

+

1

N

2

1'


N

2'

+

I_B

(b)

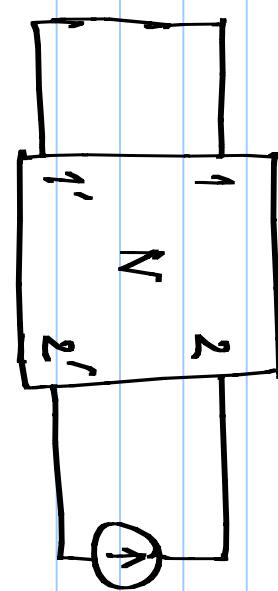


(a)

to that in (b) and

(c).


Is this relationship true
in general?

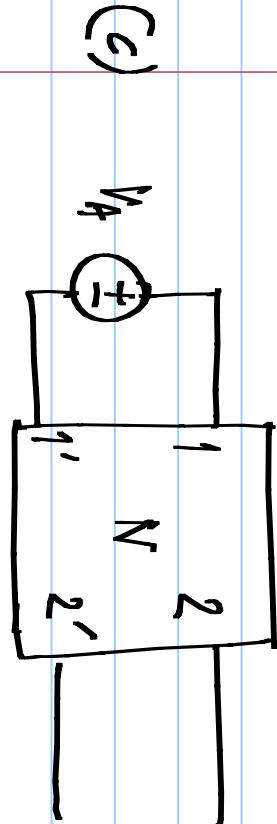

(c)

N consists only of resistors.

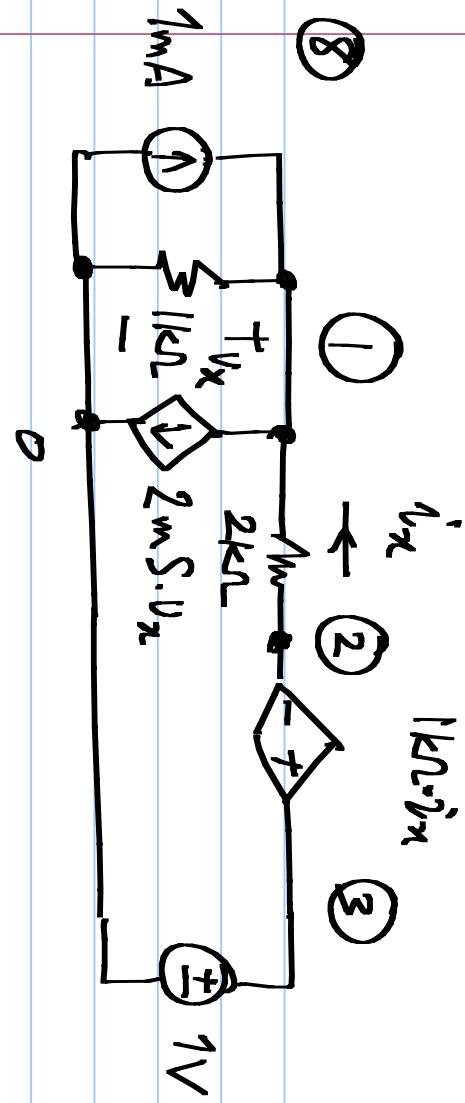Relate the power dissipate
in the network N in



- * Write down the MNA equations
- * Are the 1mA and 1V sources dissipating or generating power? How much?