

EC1010: Electrical and Magnetic circuits.

Note Title

1/28/2013

Problem set #3 (Due on 25th Feb. 2013)

HKD: Hayt, Kemmerly, and Durbin


Engineering circuit analysis, 7th Edition

Tata McGraw Hill 2010, 2006

1. Prove power conservation ($\sum_{\text{branches}} v_k l_k = 0$) for an arbitrary electrical network.


(Hint: Express all branch voltages in terms of node voltages wrt a reference node and group together coefficients of each node voltage)

2.

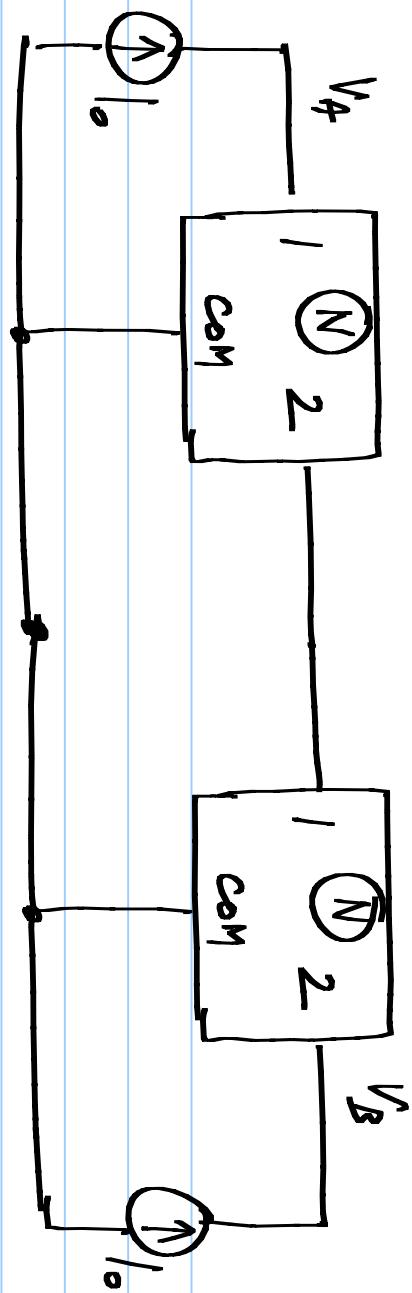

The circuit above is made using two identical resistive current sources I_o . Determine V_A and V_B in terms of I_o and Z parameters of N . (This problem can be solved using brute force, but will be easier if you use reciprocity appropriately).

3.

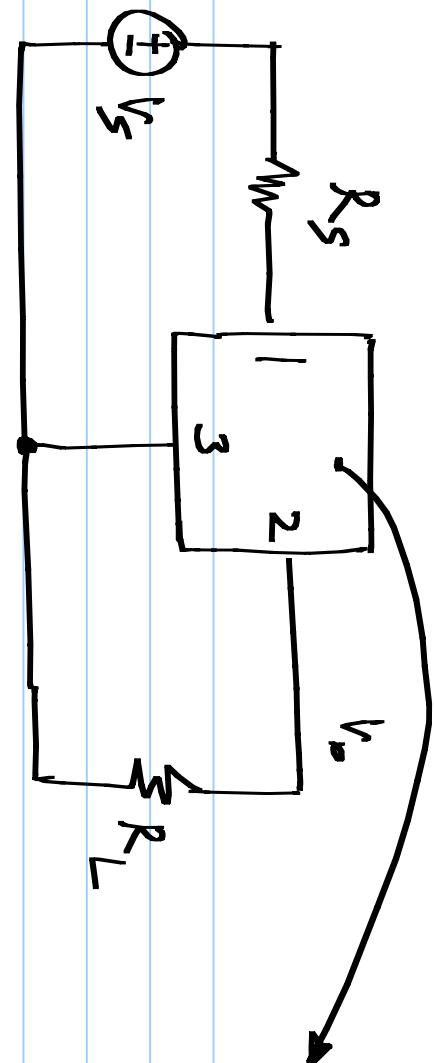


$$\begin{bmatrix} y_{11} & 0 \\ y_{21} & y_{22} \end{bmatrix}$$

Determine V_o/V_s . Assuming all positive y parameters, determine the constraints on them to maximize

$$\left| \frac{V_o}{V_s} \right|$$

4.

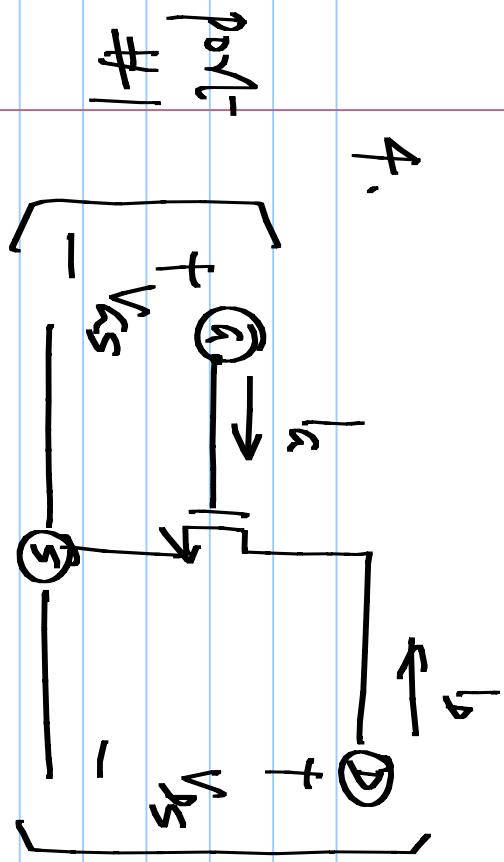

port #2.

An MOS transistor is a
3 terminal two port
relationships between

voltages and currents.

$$I_g = 0, \quad I_D = \frac{\beta}{2} (r_{ds} - V_T)^2 (1 + \gamma V_{tr})$$


β , V_T , and γ are constants.

Determine the incremental y parameters of the
transistor.

5. Evaluate the γ parameters of the previous problem for $\beta = 100mA/V^2$; $V_T = 1V$; $\gamma = 0.01V^{-1}$ at an operating point of $V_{GS} = 3V$, $V_{DS} = 5V$.

If the network in problem 3 has these γ -parameters, determine $\frac{V_0}{V_S}$ for $R_S = R_L = 100k\Omega$.

6.

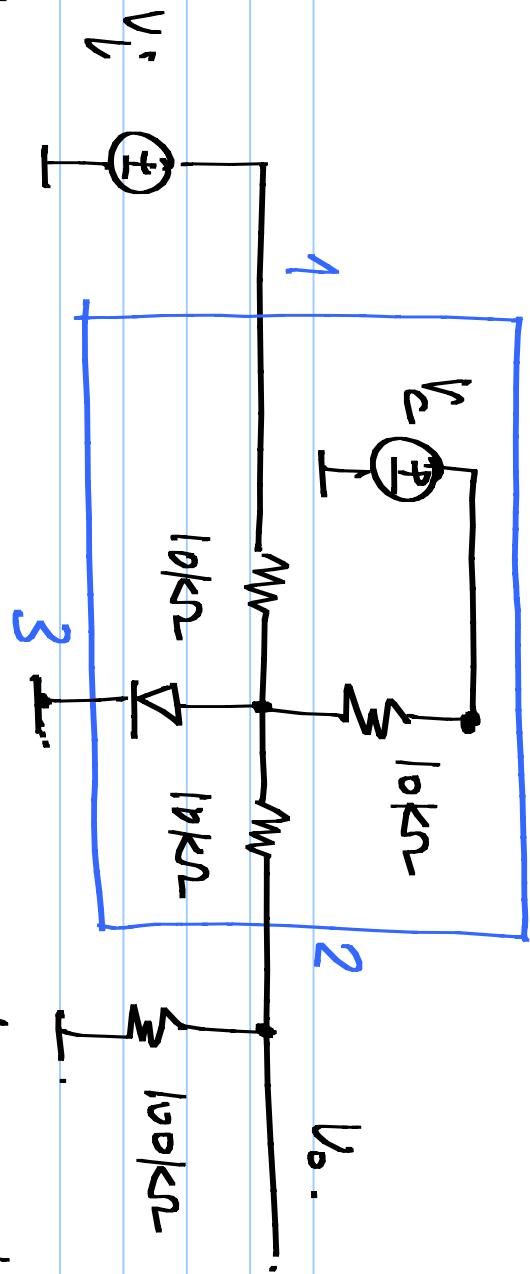

Treat V_i as an incremental input.]

Determine the total output V_o when $V_c = +2.7V$

$$\text{and } V_c = -2.7V$$

7. In the previous problem, determine the small-signal y -parameters of the 3 terminal two port enclosed by the box for $V_c = 2.7V$ and $V'_c = -2.7V$.