

EC 1010: Electrical and Magnetic circuits.

Note Title

1/28/2013


Problem set #4 (Due on 23 Mar. 2013)

HKD: Hayt, Kemmerly, and Durbin


Engineering circuit analysis, 7th Edition

Tata McGraw Hill 2010, 2006

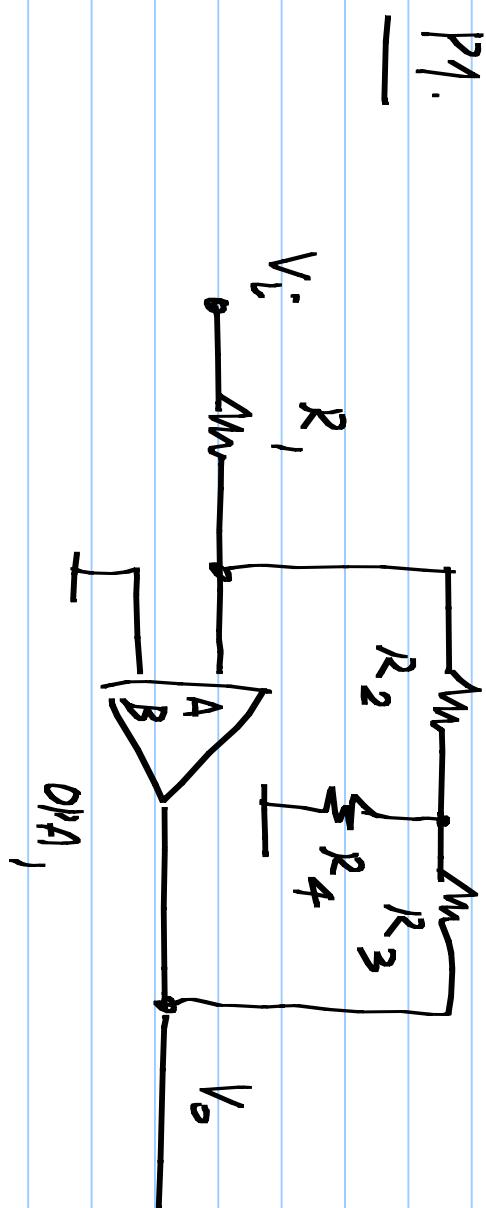
P 1-4 : Determine the opamp signs for negative feedback and calculate V_o/V_i or V_o/I_i




P2.

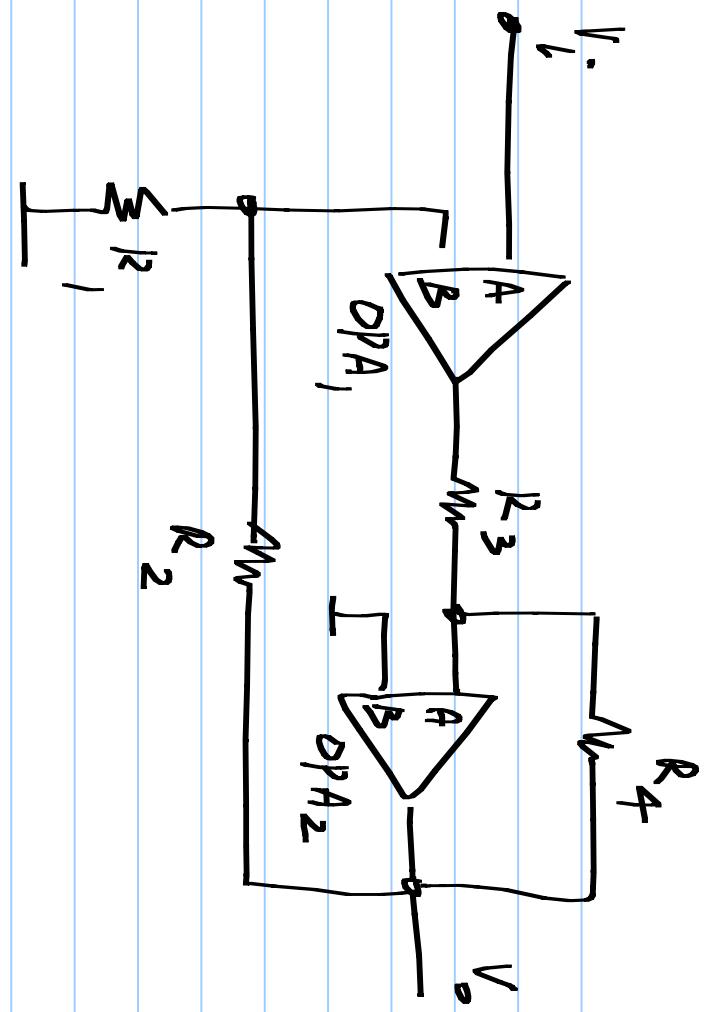


P3.

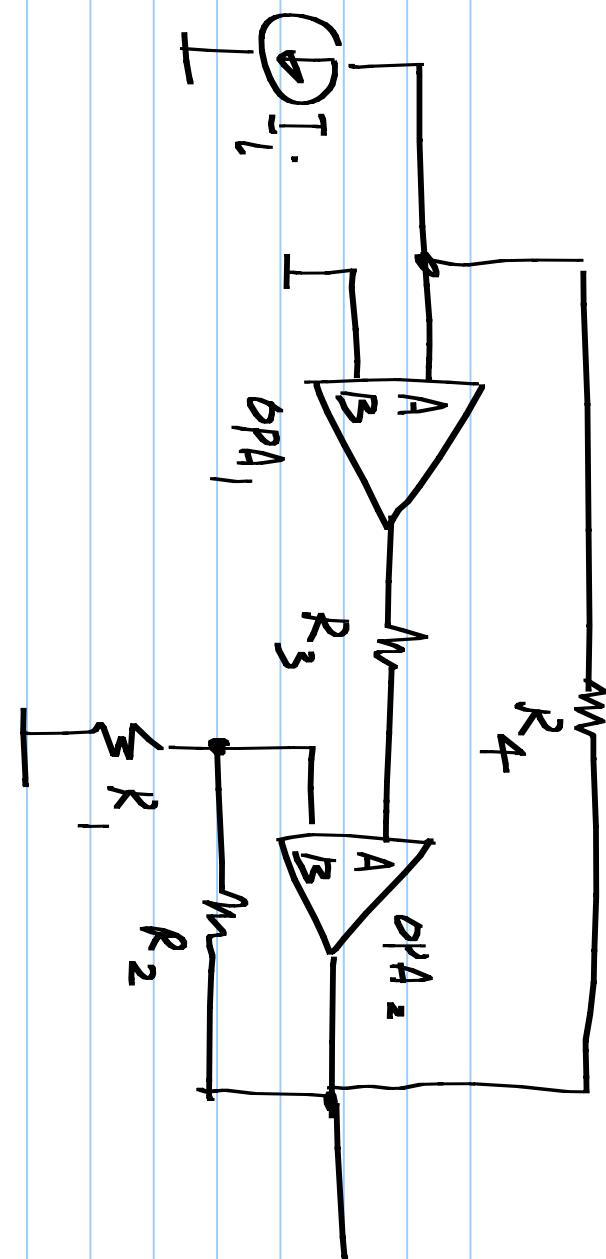


P4:

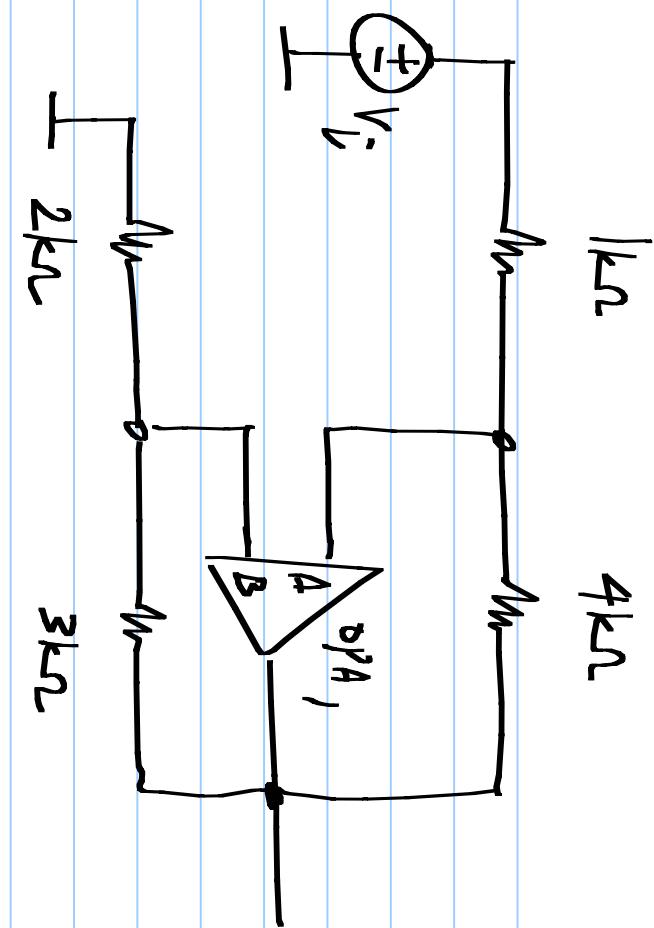

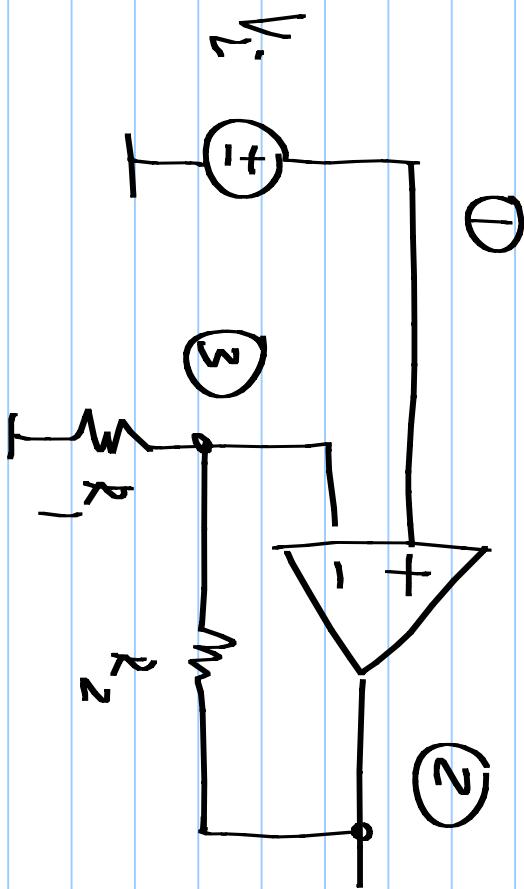P5. Write the modified nodal analysis equations for the following circuit




P6.

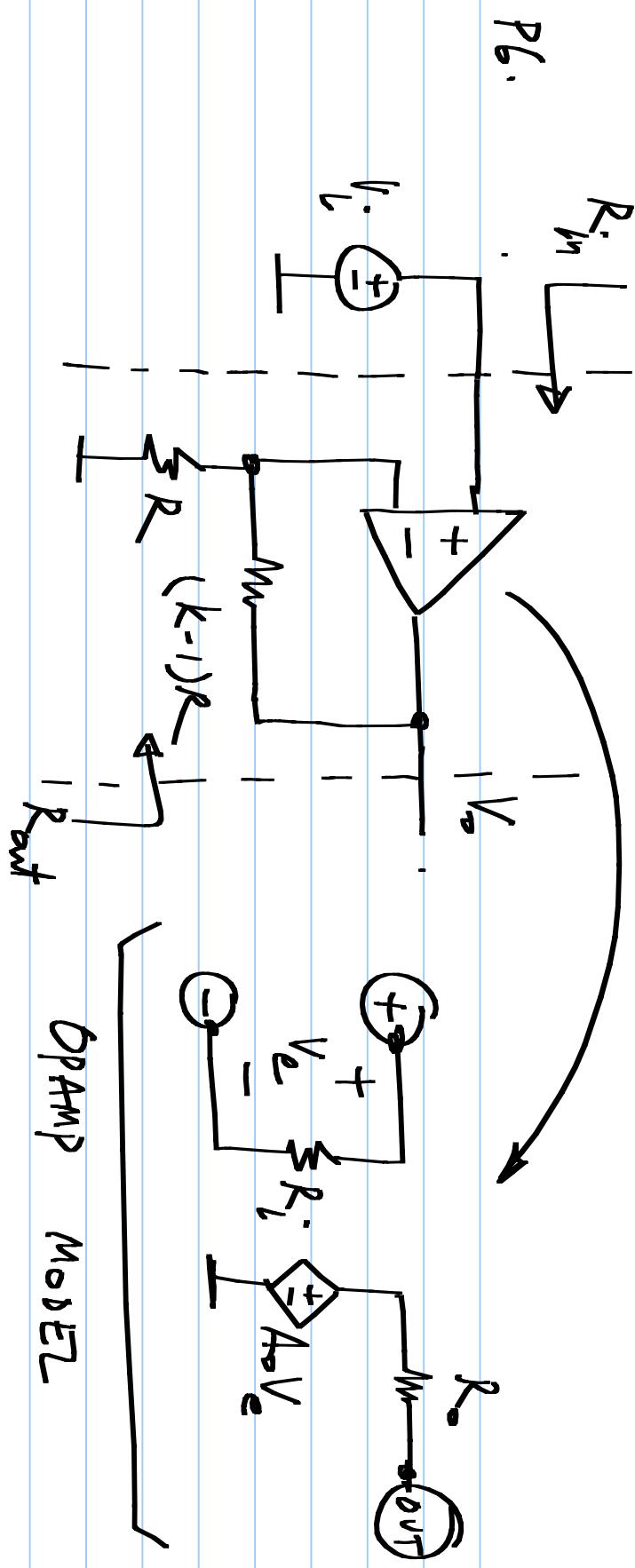


Determine V_o/V_i , R_{in} , R_{out} with the given opamp model.

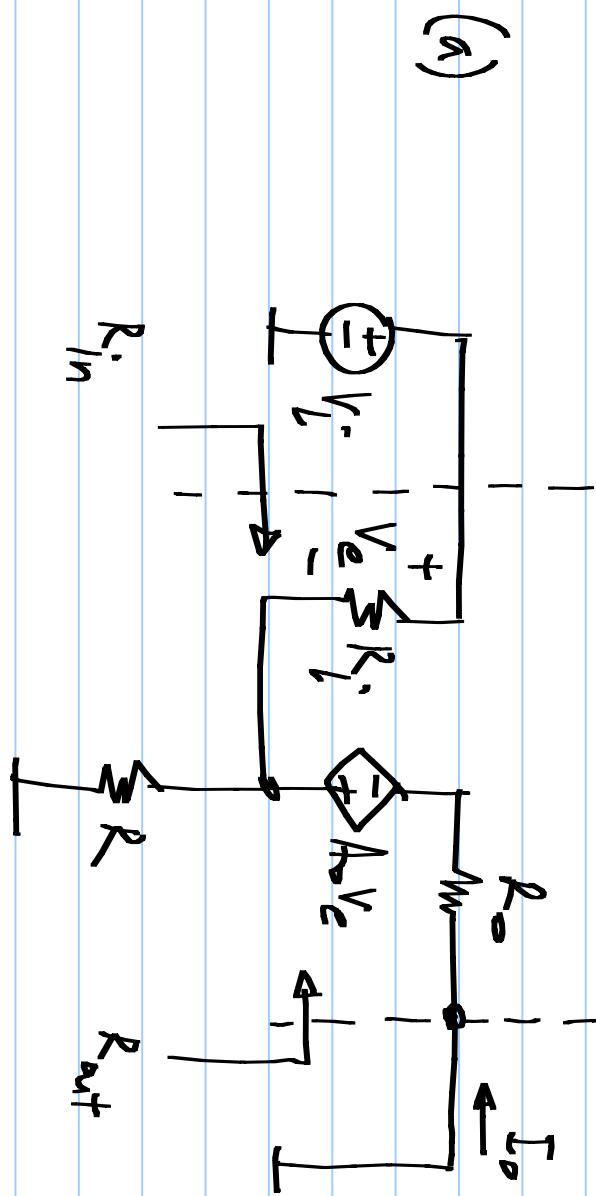p7. Determine the output/input ratio, and the input
and output resistances in the following circuits.
What happens as $A_o \rightarrow \infty$



(b)

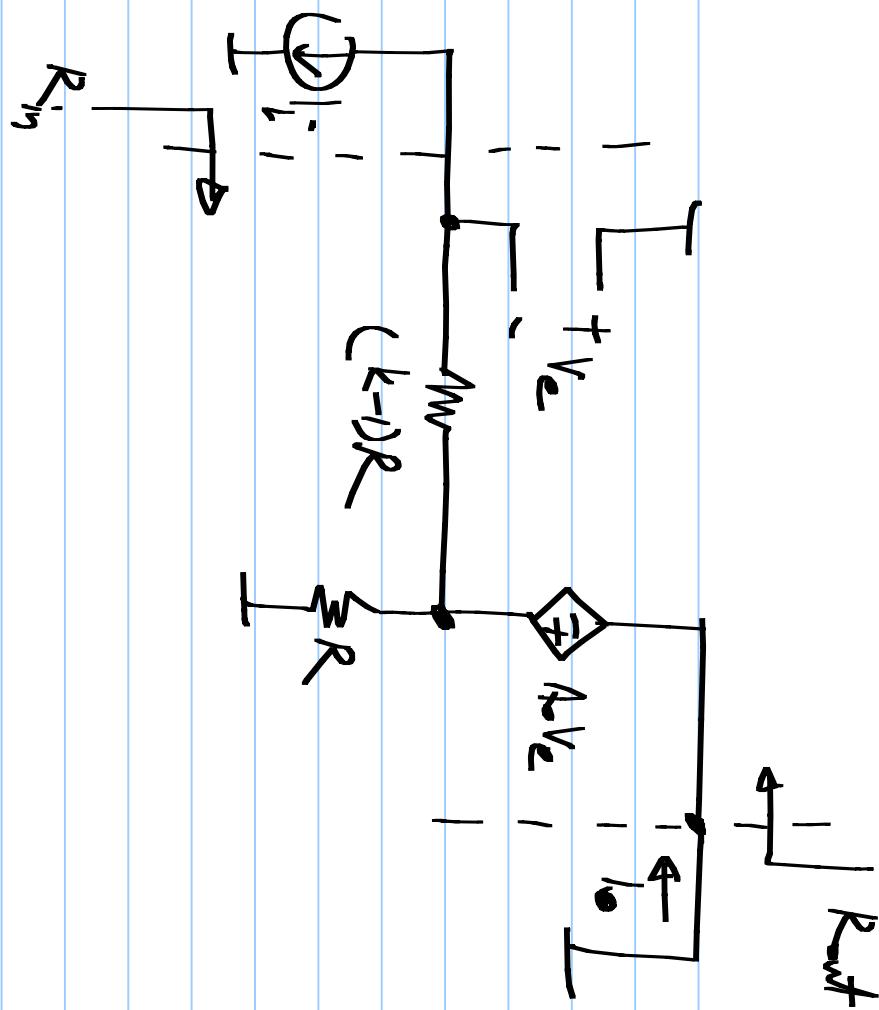

P8.

Determine the

opamp signs for
negative feedback.

Determine R_{in} , the
resistance seen by
the current source.

