

EC1010: Electrical and Magnetic circuits.

Note Title

1/28/2013

Problem set # 7 (Due on 15 Apr. 2013)

HKD: Hayt, Kemmerly, and Durbin

Engineering circuit analysis, 7th Edition


Tata McGraw Hill 2010, 2006

MK: Murthy and Kannath

Basic circuit analysis,

Tarico Books 1998

Problem 1 :

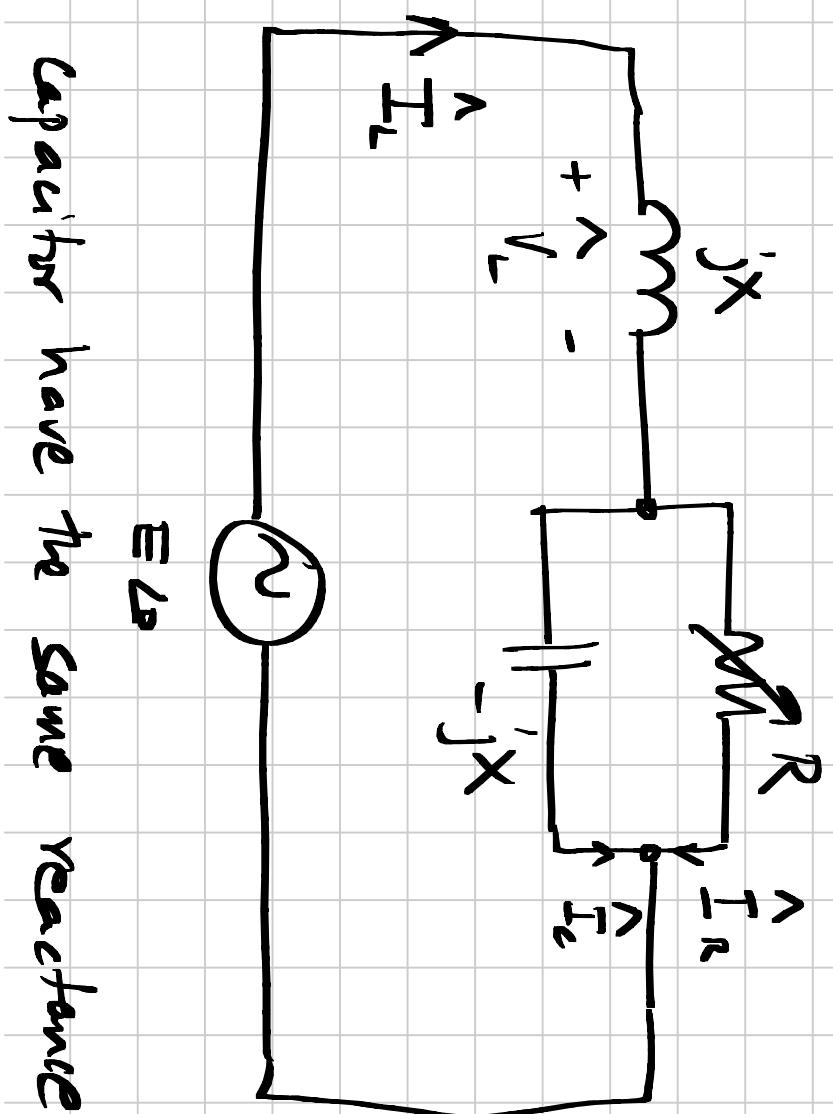

The inductor and capacitor have the same reactance at the

frequency of excitation.


(a) Calculate I_R , the current through the resistor, in terms of E , X & R .

(b) Draw a phasor diagram indicating the current through and voltage across R , L , C and the source.

(c) Draw the loci of (i) V_C (ii) I_C (iii) I_L and V_L as R is varied from 0 to ∞ .

Problem 2


$$Y(j\omega) \rightarrow$$

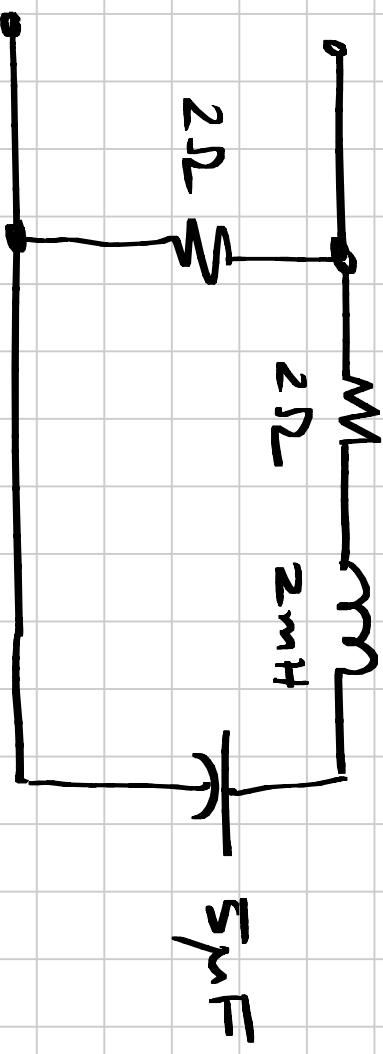

compute $Y(j\omega)$ and draw its locus as ω varies from 0 to ∞ .


Problem 3

$$Y(j\omega) \rightarrow$$

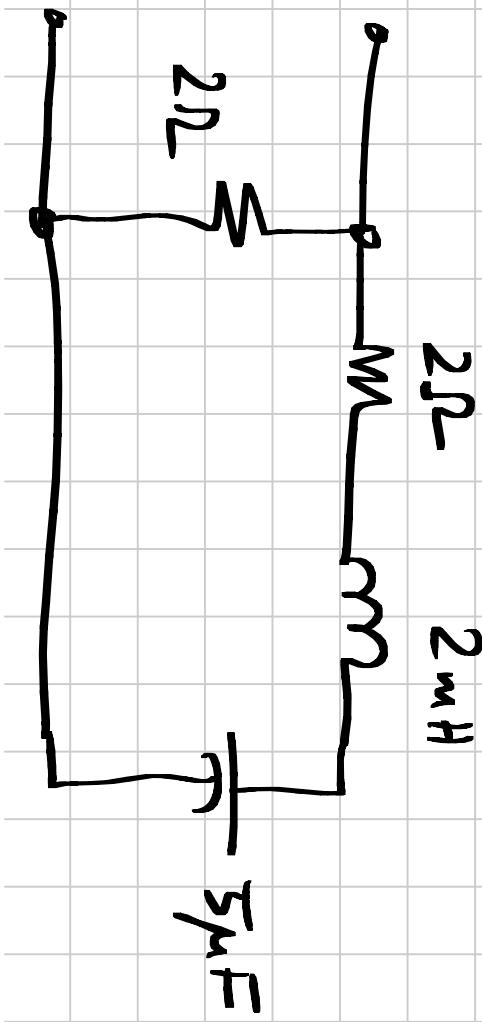

Draw the locus of $\gamma(j\omega)$ as ω varies from 0 to ∞ .


Problem 4

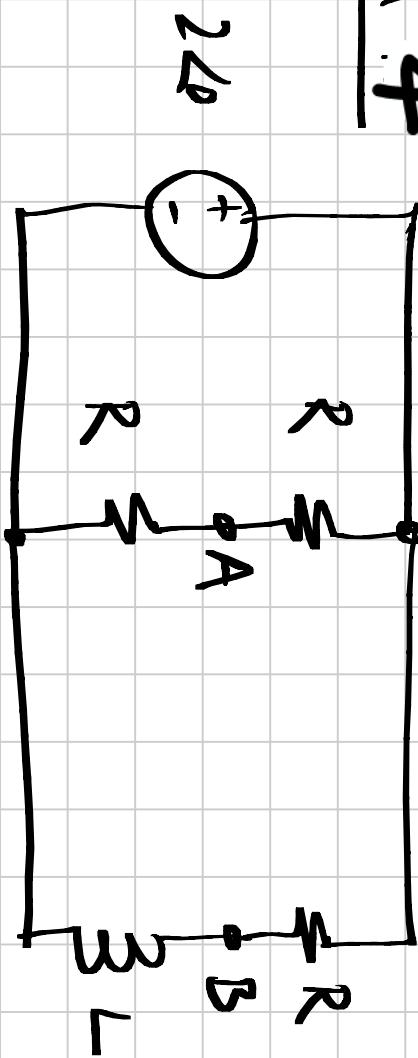

Use a locus diagram to show that the magnitude of V_{AB} does not change with frequency.


Problem 5

Plot the admittance locus of γ as C is varied, for some fixed ω .

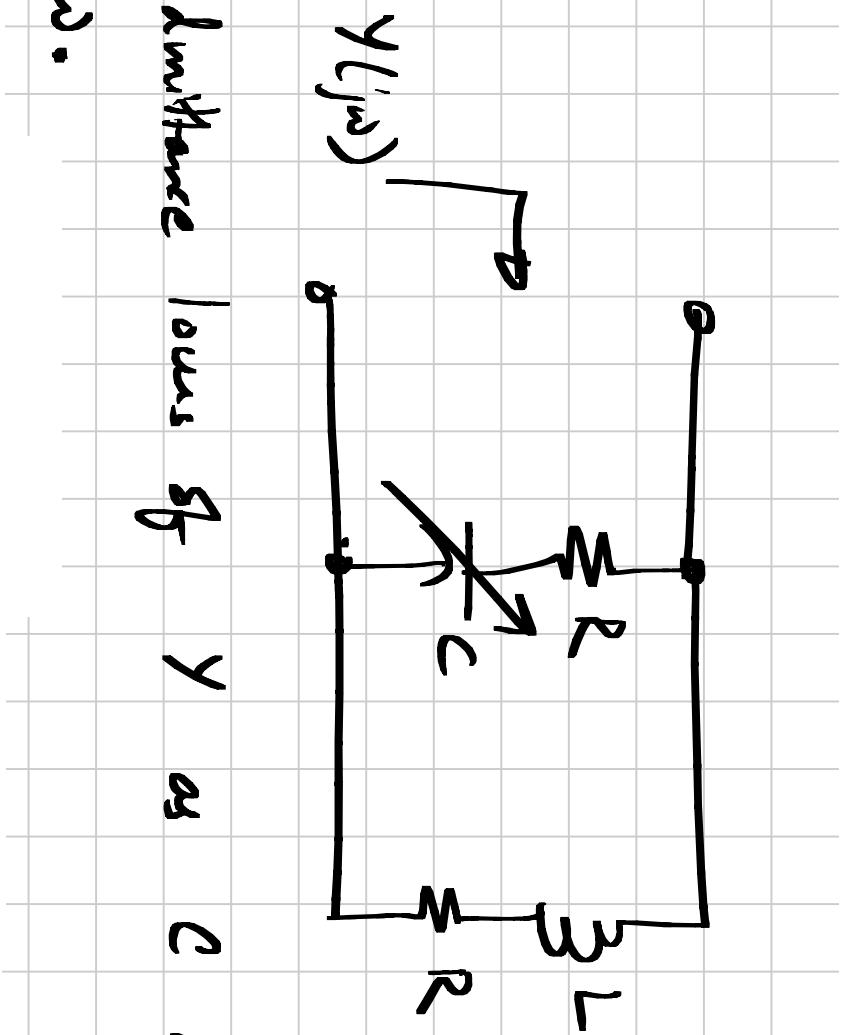

Part 2: 3 phase systems & power measurement

6.

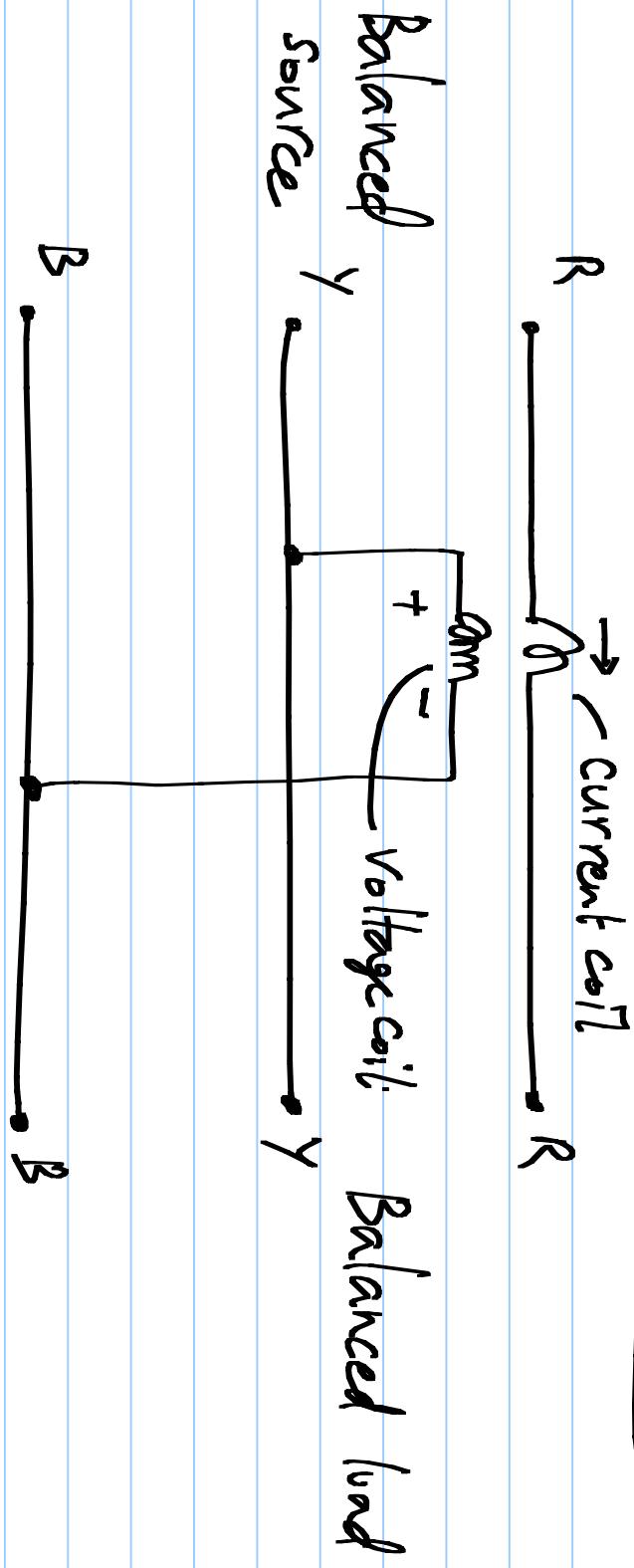

A wattmeter is connected as above between a balanced source & a balanced load. What does its reading represent.

7. M_S, ρ 10.4

8. M_S, ρ 10.5

9. M_S, ρ 10.6

10. M_S, ρ 10.7