

EC1010: Electrical and Magnetic circuits.

Note Title


1/28/2013

Problem set #3 (Due on 14th Feb. 2014)

HKD: Hayt, Kemmerly, and Durbin


Engineering circuit analysis, 8th Edition (Indian)
McGraw Hill 2013

①

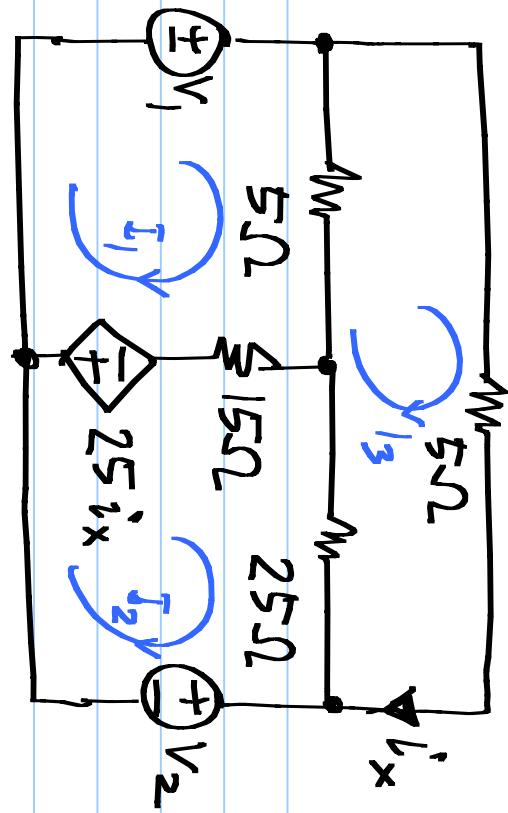

- * Set up the mesh analysis eqn. $[R]I = V$
- * Solve for I
- * Determine the power dissipated in the 25Ω resistor
- * Determine the power dissipated / supplied by all the sources

(2)

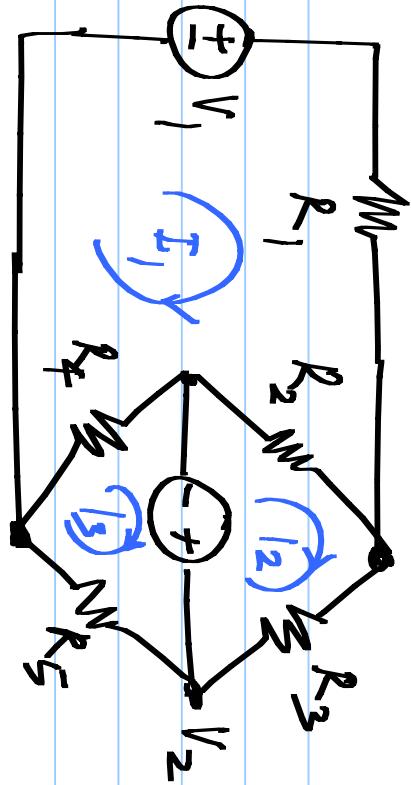


The mesh equations for the above circuit are as given below. Determine all component values:


$$\begin{bmatrix} 112\Omega & -90\Omega & -10\Omega \\ -90\Omega & 100\Omega & 0 \\ -10\Omega & 0 & 100\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -12V \\ 5V \\ -5V \end{bmatrix}$$

③ Let $P_{E_1+E_2}$ and $P_{E_1-E_2}$ be the powers dissipated in a network N consisting of linear time invariant resistances excited by two voltages E_1 and E_2 in the polarities shown in (a) & (b) respectively.

(a)

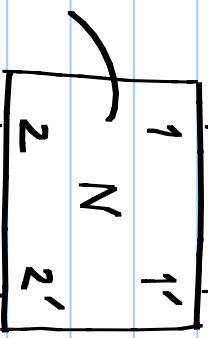

(b)

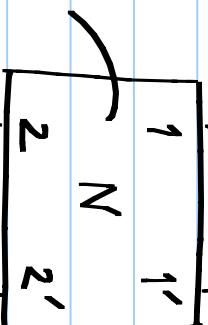

$$\begin{aligned} \text{Power dissipated} &= P_{E_1+E_2} = P_{E_1-E_2} \\ &= P_{E_1+E_2} \end{aligned}$$

Cont'd

Determine $P_{E_1} + P_{E_2}$ where P_{E_1} and P_{E_2} are the powers dissipated in N when E_1 and E_2 are acting alone as shown in (c) and (d) respectively.




$$\text{Power dissipated} = P_{E_1}$$

$$E_2 = 0$$

$$\text{Power dissipated} = P_{E_2}$$

4


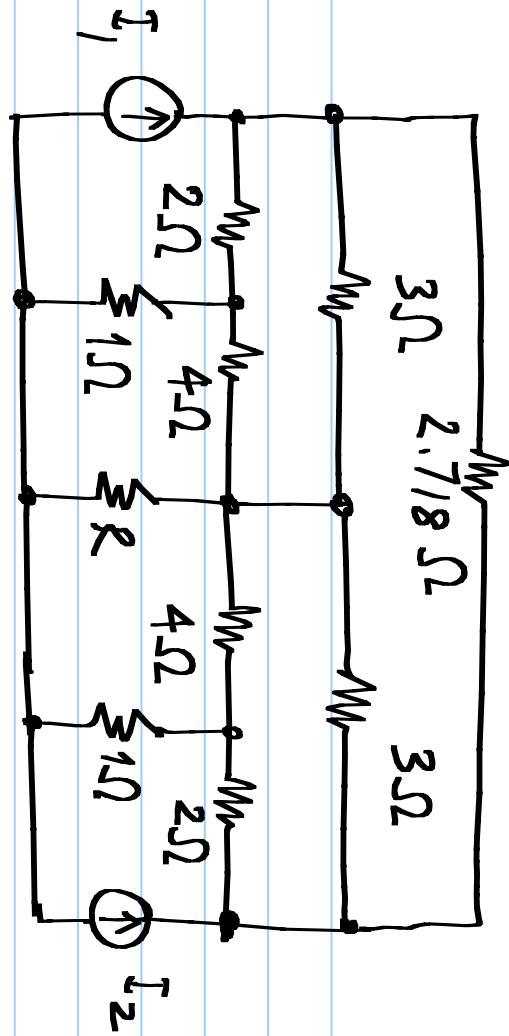


- (a) For $I_1 = I_2 = 1A$, determine R so that it dissipates the maximum power. What is the value of the max. power?
- (b) Repeat the above for $I_1 = 2A$ and $I_2 = -2A$
- (c) Repeat the above for $I_1 = 1A$ and $I_2 = 4A$

(5) N consists only of resistors and two pairs of terminals 1-1' and 2-2' are brought out (1). When 10V is connected to 1-1'

and $R_L = 2\Omega$ is connected to 2-2', the latter draws 2A.


When $R_L = 6\Omega$, it draws 1A.

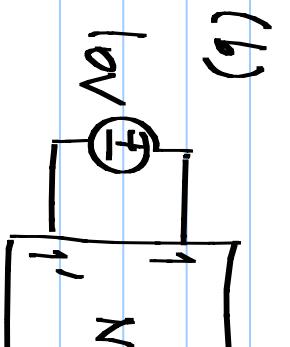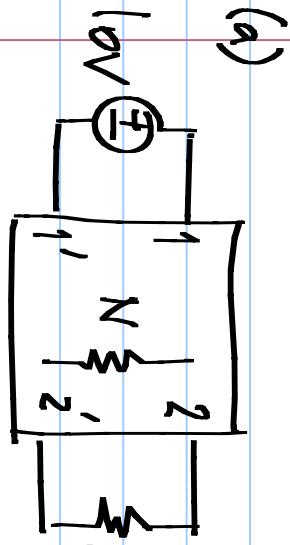

When I_L &
are connected
to 2-2' and R_L varied, the maximum power dissipated in R_L is 4.5W. Find I_L .

(b)

(6)

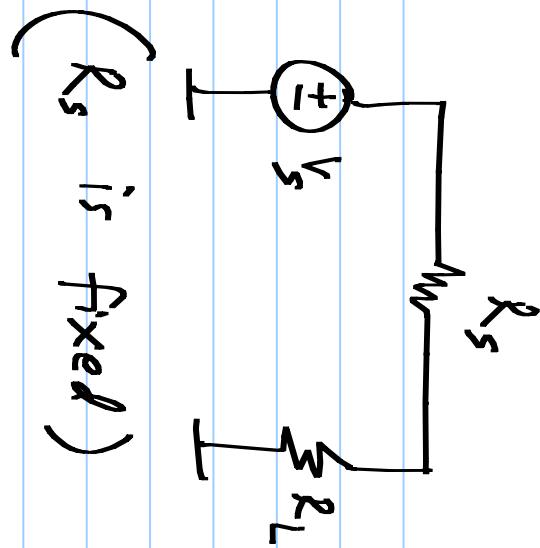

Show that the power P_L , dissipated in R_L can be expressed as

$$P_L = P_{\max} \left(1 - |\Gamma|_L^2 \right) \text{ where}$$


$$\Gamma_L = \frac{R_L - R_s}{R_L + R_s} \quad \text{and} \quad P_{\max}$$

independent of R_L .

Determine P_{\max} .

Γ_L is called "reflection coefficient" of the load R_L . What is Γ_L for (a) maximum power dissipated in R_L , (b) min. power dissipated in R_L

7

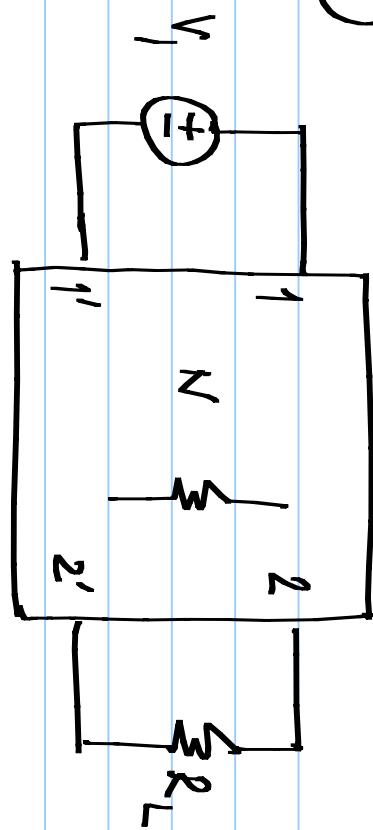

N consists only of resistors. The power in R_L equals 8W
when R_L is either 50Ω or 200Ω . Determine the
power dissipated in R_L when $R_L = 150\Omega$.