

EC1010: Electrical and Magnetic circuits.


Note Title

1/28/2013

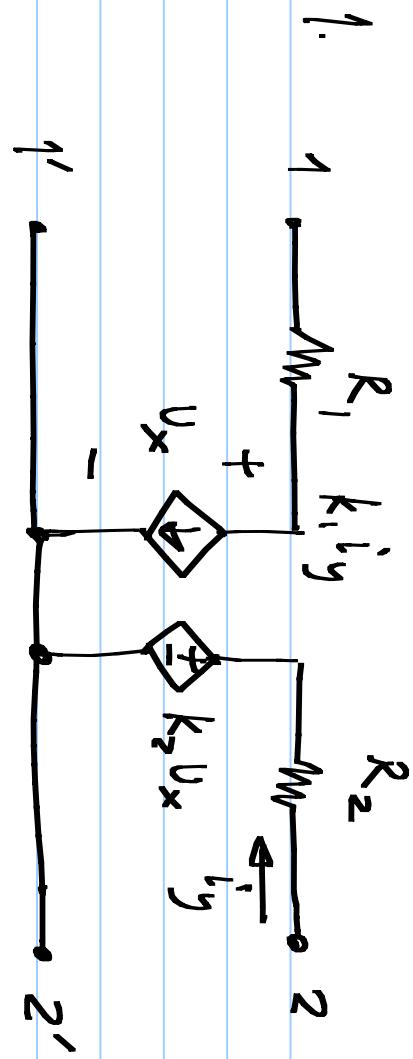Problem set #4 (Due on 21st Feb. 2014)


HKD: Hayt, Kemmerly, and Durbin

Engineering circuit analysis, 8th Edition (Indian)
McGraw Hill 2013



Determine the constraints between $\{R_1, R_2, k_1, k_2\}$ for the network above to be reciprocal.

2.

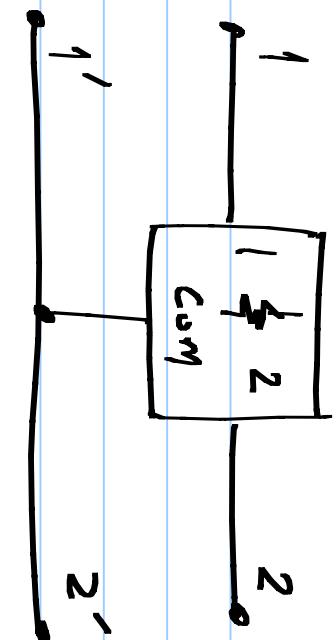


terminals is common to both ports). If the network is purely resistive, determine the constraint on y_{21} or z_{21} of the network.

The two port shown is a three terminal two port

3.

$1k\Omega$

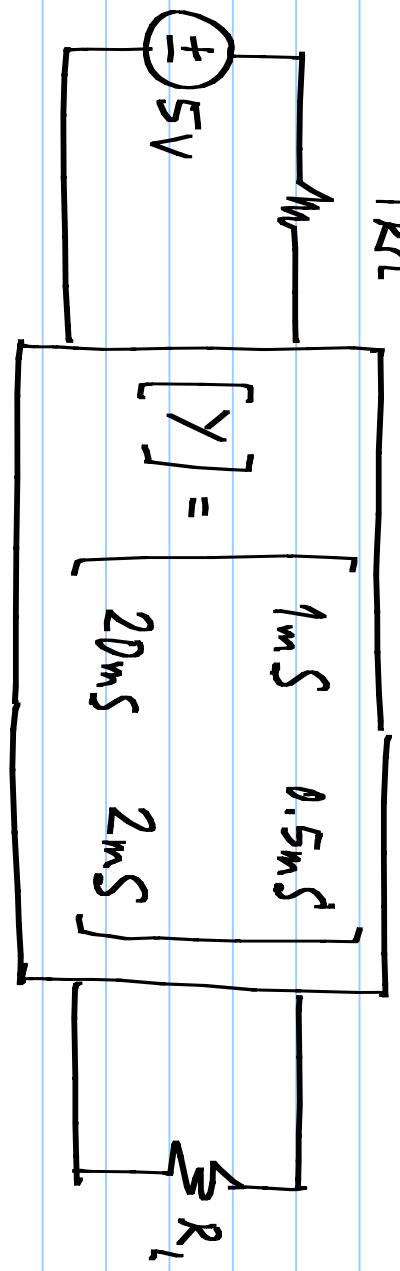


Determine R_L such that it dissipates maximum power. Also determine the maximum power.

4. We know that two port networks with only resistors are reciprocal, and those including controlled sources are not necessarily so. What about networks containing resistors and capacitors or inductors? Follow the steps used to determine reciprocity of resistive networks and draw your conclusions.


5

Case #1

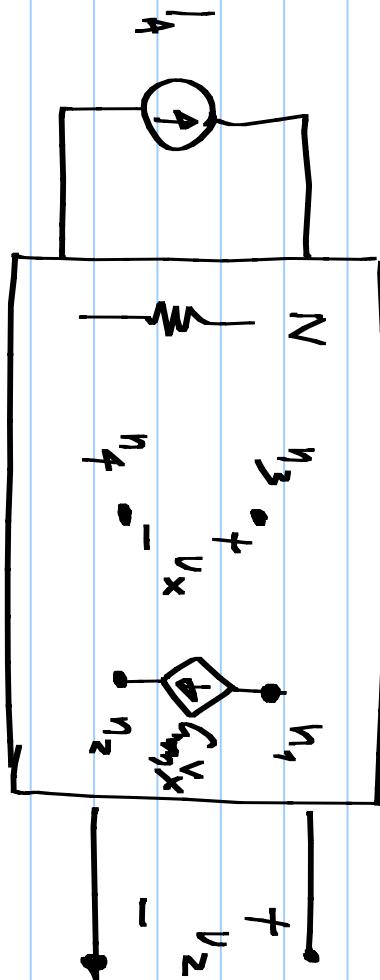

only resistors and a
single controlled source.
Connected to nodes $\eta_1 - \eta_2$

Case #2

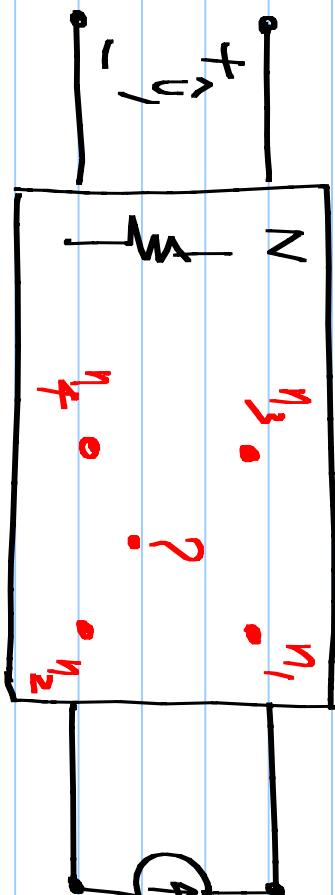

We know that such

networks are in general
not reciprocal.

Can you replace only the controlled source by another element

The network N has


(i.e.) a new element connected to $\eta_1 - \eta_4$ such that

$$\frac{V_1}{I_B} = \frac{V_2}{I_A}$$


(case #2) (case #1)

(Hint: Follow the steps of the proof of reciprocity theorem while keeping track of the controlled source branches separately).

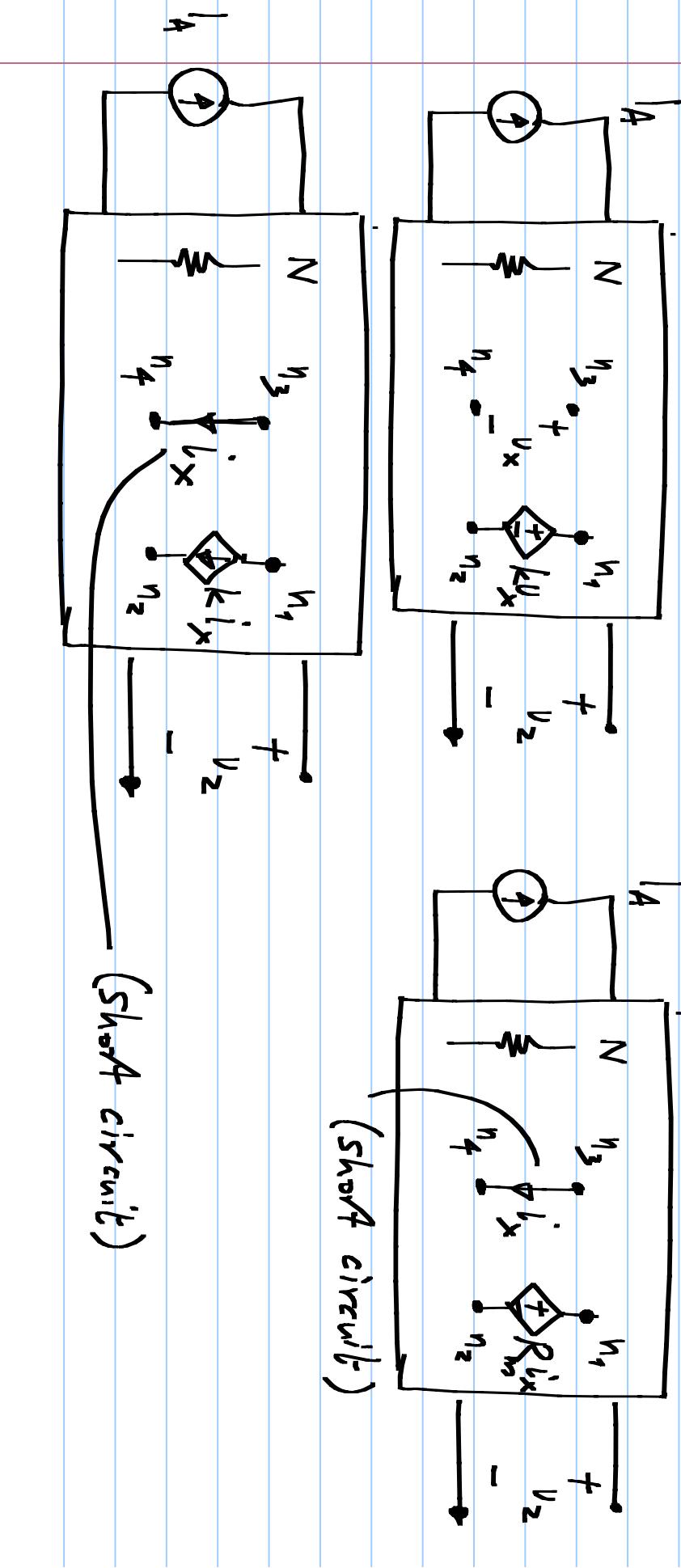6. If you are able to do the previous problem, repeat it for other controlled sources as shown below:




7

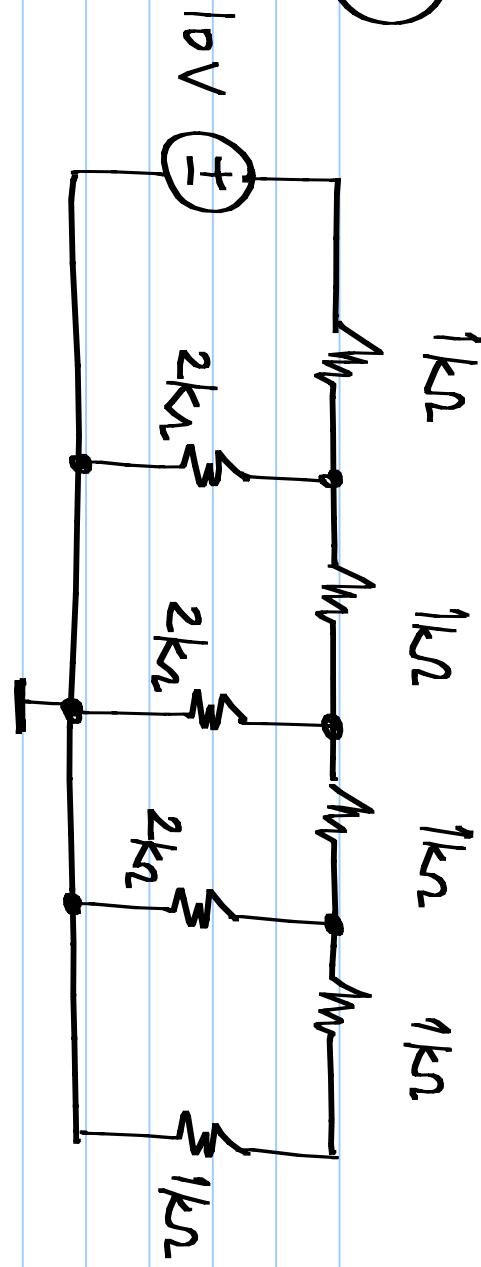


Determine all resistor currents and voltages.

8

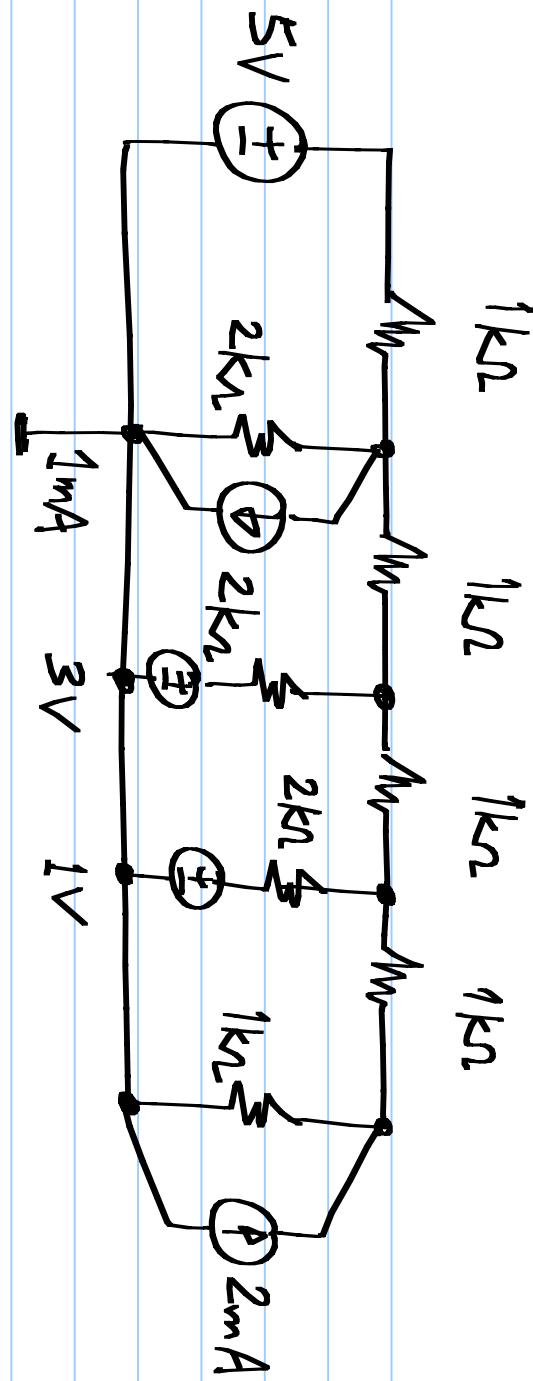


Determine the power delivered by the $5V$ source.

⑨

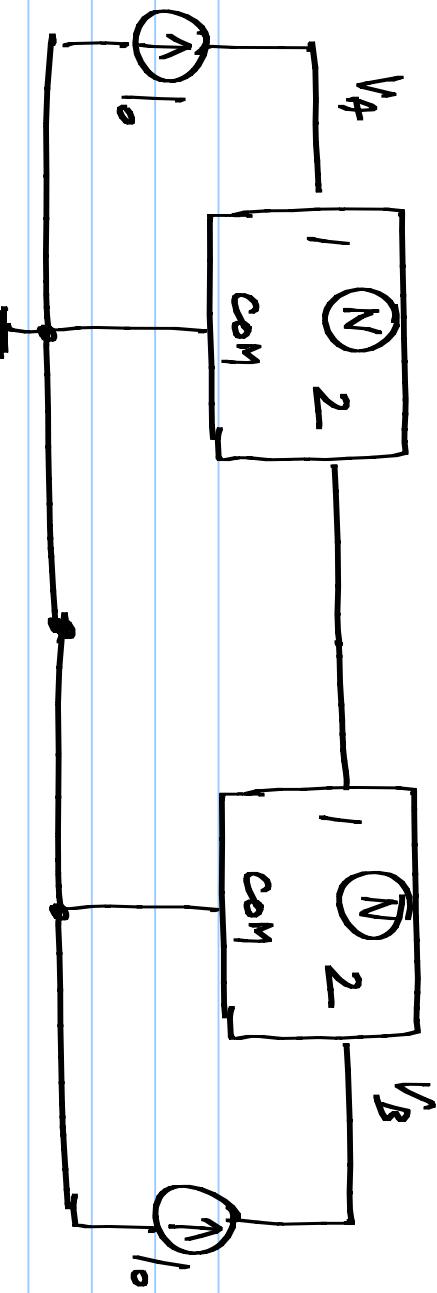

The circuit above is made using two identical resistive
3 terminal two port networks N driven by identical
current sources I_o . Determine V_A and V_B in terms of I_o
and Z parameters of N .

1)

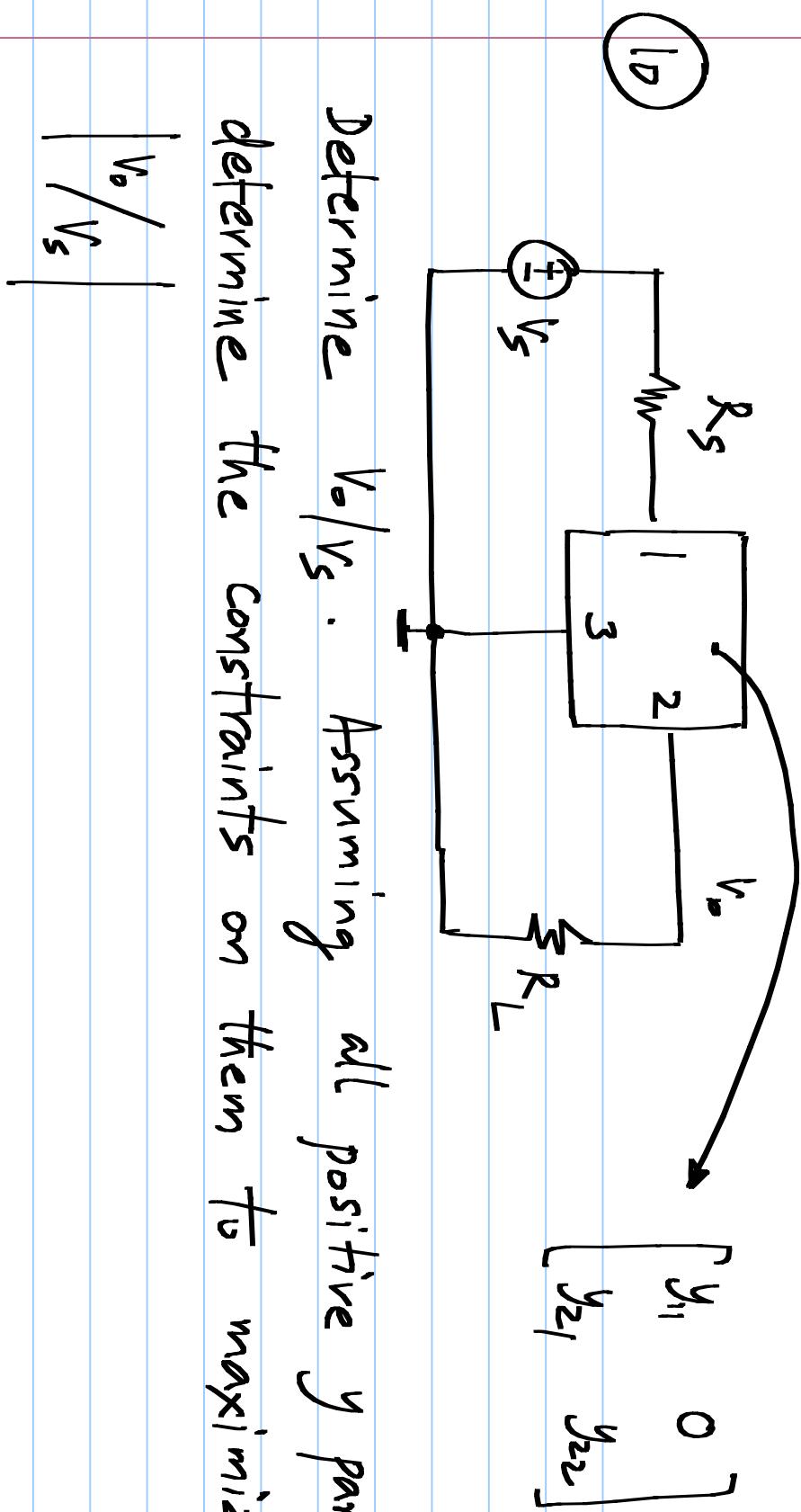

Determine V_o/V_s . Assuming all positive y parameters, determine the constraints on them to maximize

$$\left| \frac{V_o}{V_s} \right|$$