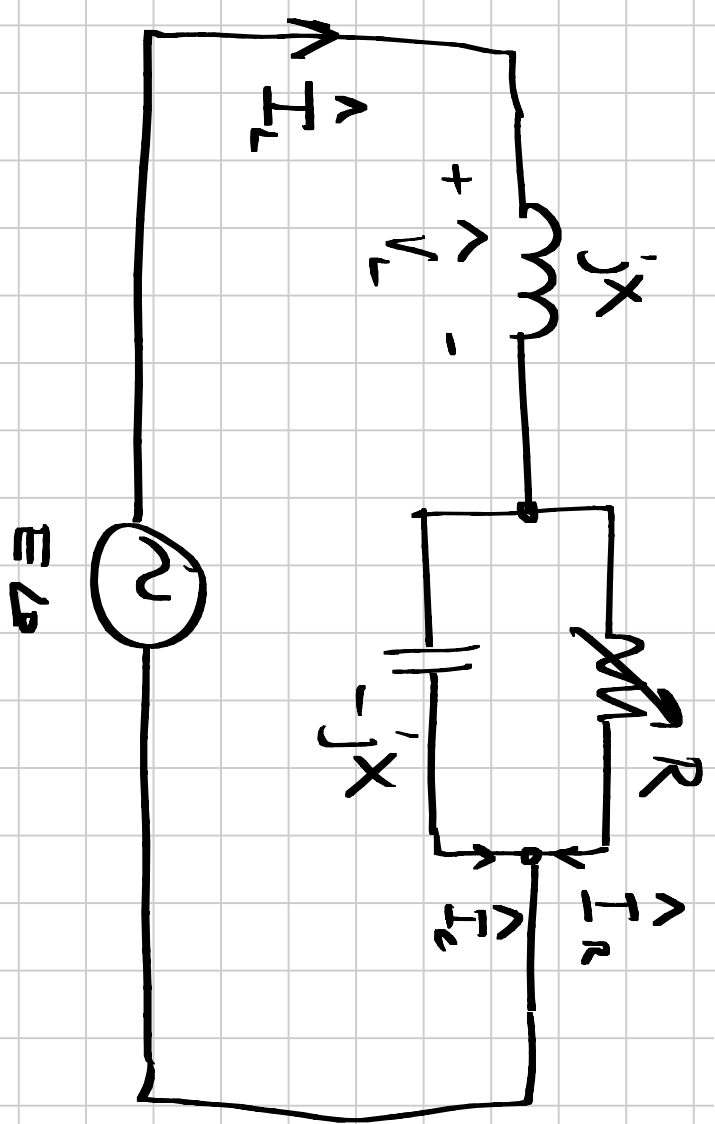


EECE 1010: Electrical and Magnetic Circuits.

Problem set # 9 (Due on 11<sup>th</sup> Apr. 2014)

Problem 1:



The inductor and capacitor have the same reactance at the


frequency of excitation.

(a) Calculate  $I_R$ , the current through the resistor, in terms of  $E$ ,  $X$  &  $R$ .

(b) Draw a phasor diagram indicating the current through and voltage across  $R$ ,  $L$ ,  $C$  and the source.


(c) Draw the loci of  $I_C$ ,  $V_C$ ,  $I_L$ ,  $V_L$  and  $V_s$  as  $R$  is varied from 0 to  $\infty$ .

## Problem 2

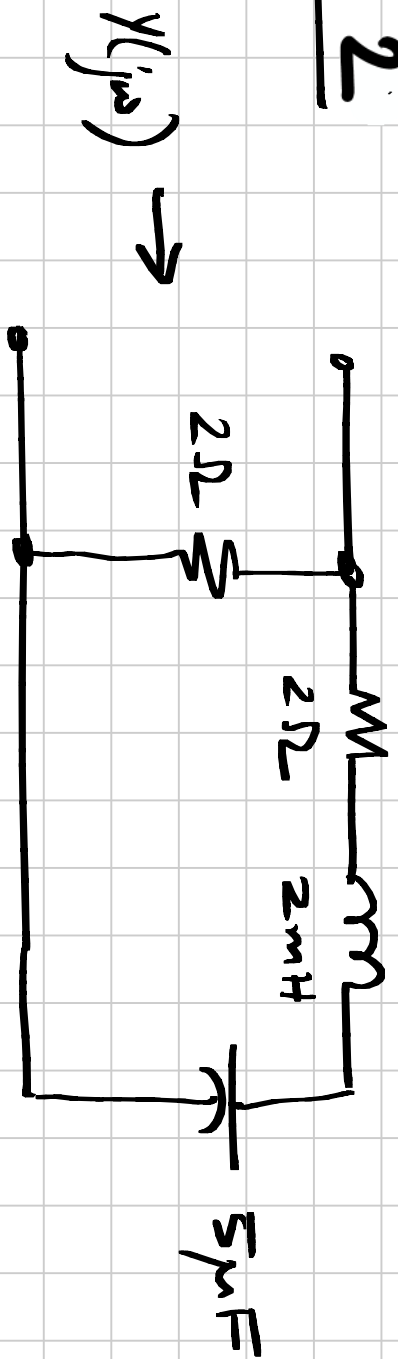


Compute  $Y(j\omega)$  and draw its locus as  $\omega$  varies from  $0$  to  $\infty$ .

## Problem 3

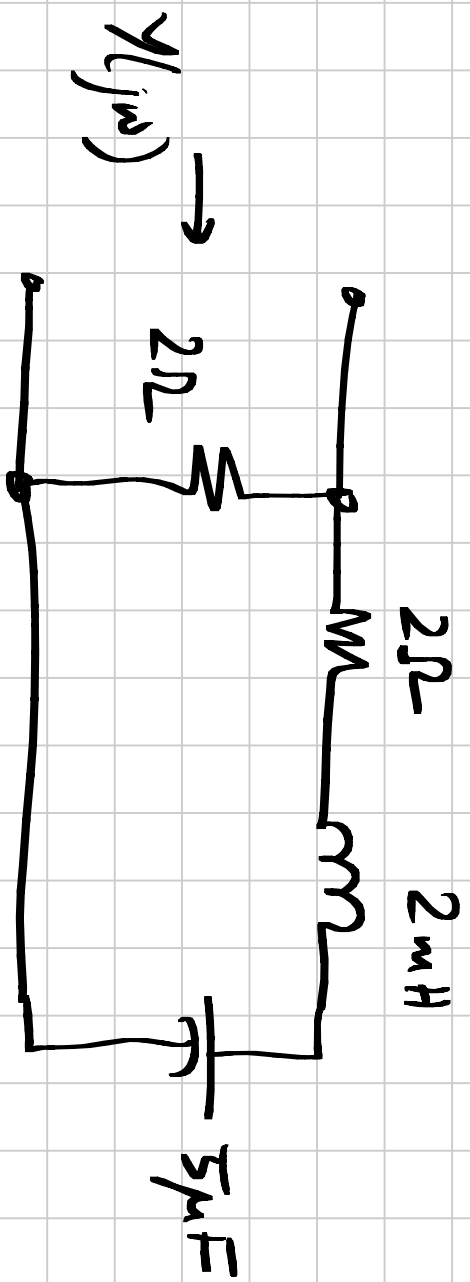


Draw the locus of  $Y(j\omega)$  as  $\omega$  varies from 0 to  $\infty$ .

Problem 4

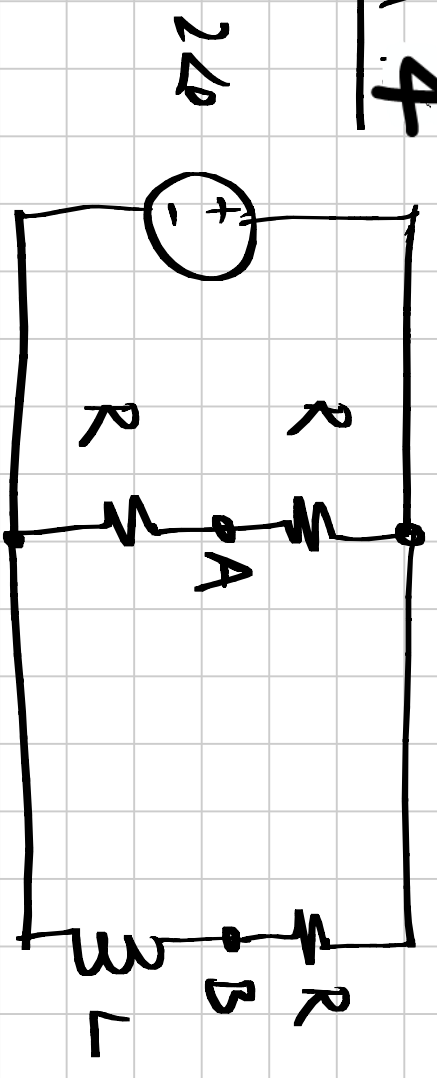


Use a locus diagram to show that the magnitude of  $V_B$  does not change with frequency.

## Problem 5

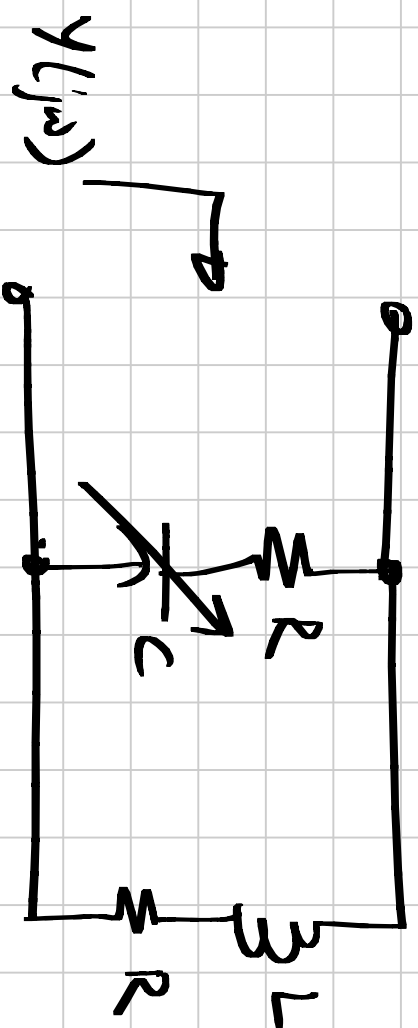

Plot the admittance locus of  $Y$  as  $C$  is varied, for some fixed  $\omega$ .

(6)

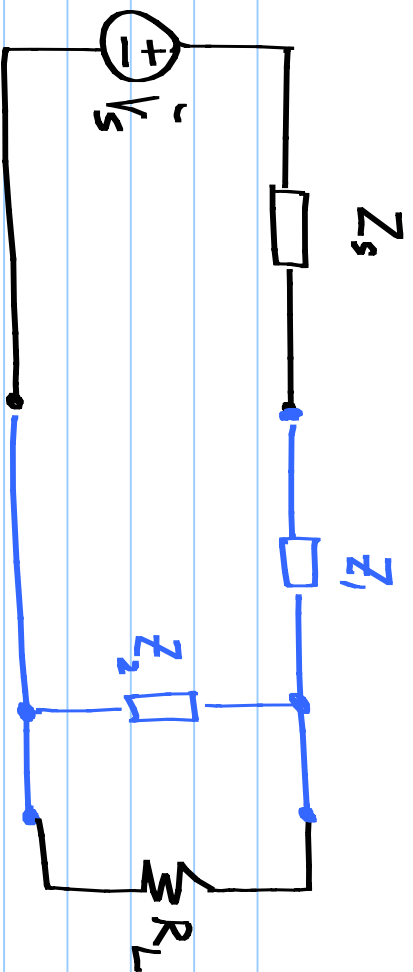

$\tilde{V}_s, Z_s$  is a source with a complex impedance.


The matching network, shown in blue consists of only lossless components (obviously, to avoid wasting any power).

It should be such that  $R_L$  draws the maximum available power from the source

Draw neat locus diagrams for all 4 possible choices for  $Z_1$  &  $Z_2$  and two possibilities for  $Z_3$  (positive & negative imaginary parts.)

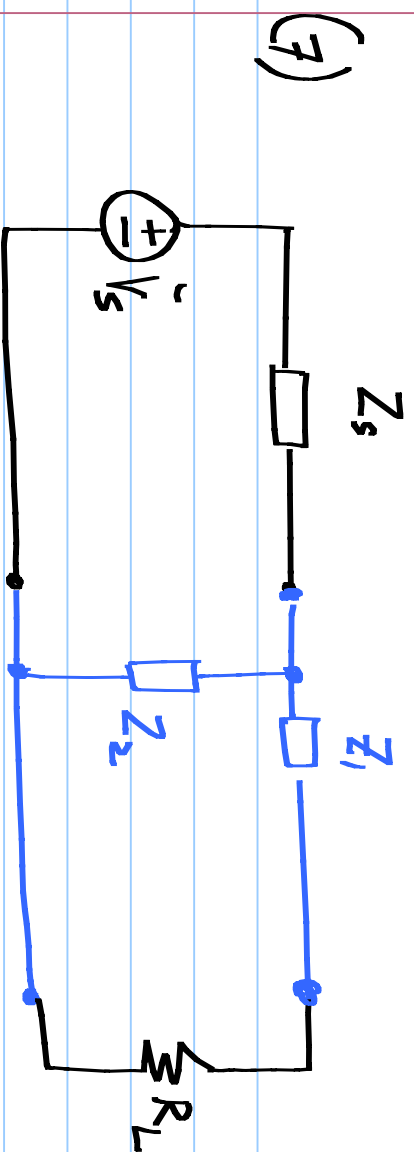Comment on values of  $R_L$  which can be matched and the type of elements in the matching network which give the most freedom to match





$\tilde{V}_s, Z_s$  is a source with a complex impedance.


The matching network, shown in blue consists of only lossless components (obviously, to avoid wasting any power).

It should be such that  $R_L$  draws the maximum available power from the source

Draw neat locus diagrams for all 4 possible choices for  $Z_1$  &  $Z_2$  and two possibilities for  $Z_3$  (positive & negative imaginary parts.)

Comment on values of  $R_L$  which can be matched and the type of elements in the matching network which give the most freedom to match

(8)

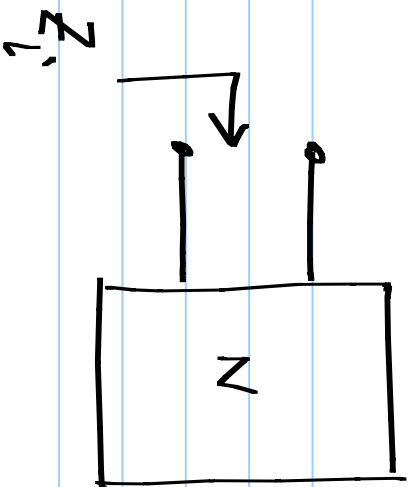

$N$  consists of an arbitrary interconnection of passive elements ( $R, L, C$ ). What can you say about the resistive part of  $z_i$ ?

(Reason out clearly)