


EECE 1010: Electrical and Magnetic circuits.

Problem set #10 (Due on 26 Apr. 2014)

MK: Murthy and Kamath

Basic circuit analysis,

Taico Books 1998

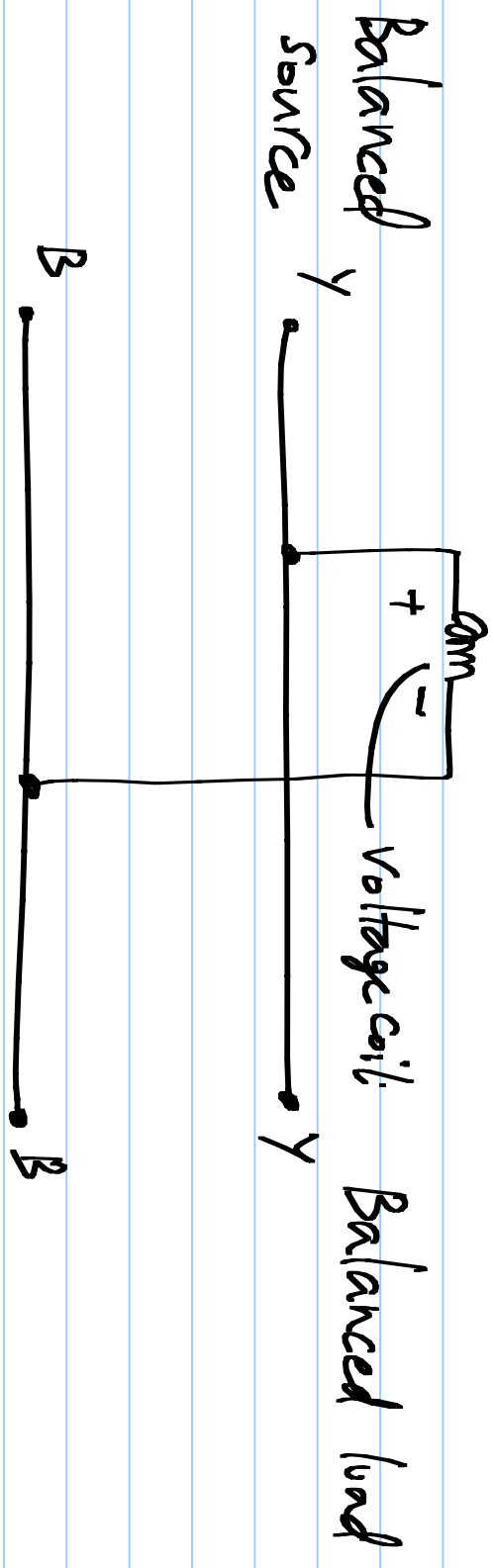

A wattmeter is connected as above between a balanced source & a balanced load. What does its reading represent.

2. MS, p 10.4

3. MS, p 10.15

4. MS, p 10.16

5. MS, p 10.17