

# ANALOG SYSTEMS : PROBLEM SET 4

## Problem 1

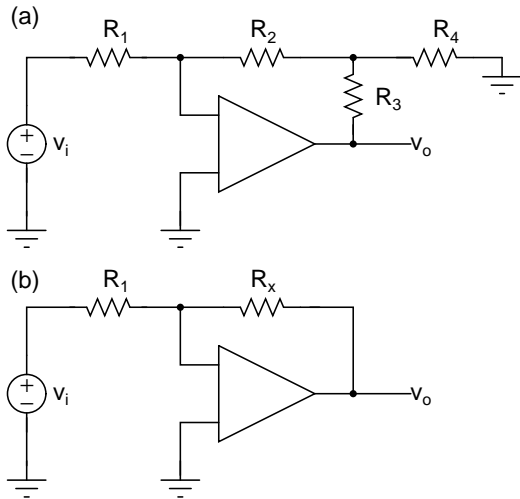


Figure 1: Circuits for Problem 1.

In the circuits above, determine the signs on the opamps for negative feedback operation, and determine  $v_o/v_i$ . When realizing a gain with a large magnitude, what might be the advantage of the circuit of (a) over that in (b)?

## Problem 2

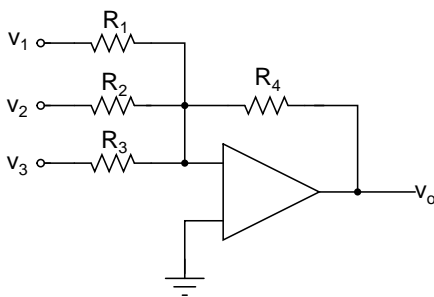


Figure 2: Circuit for Problem 2.

In the circuit above, determine the signs on the opamp to ensure negative feedback. Also determine  $v_o$  in terms of  $v_1$ ,  $v_2$  and  $v_3$ .

## Problem 3

In the figure, the opamp is operated with dual supplies of  $\pm 10$  V. The saturation limits of may be assumed to be

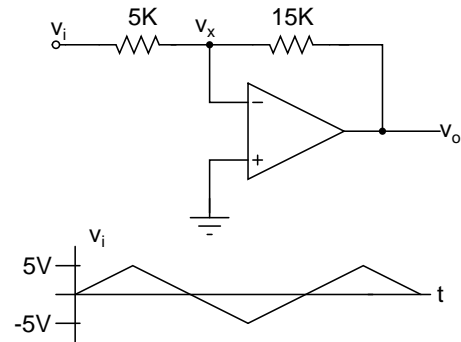


Figure 3: Circuit for Problem 3.

$\pm 9$  V. The input to the amplifier is shown. Sketch the output and the voltage  $v_x$  at the virtual ground node. What is the maximum input amplitude that will ensure a distortion free output?

## Problem 4

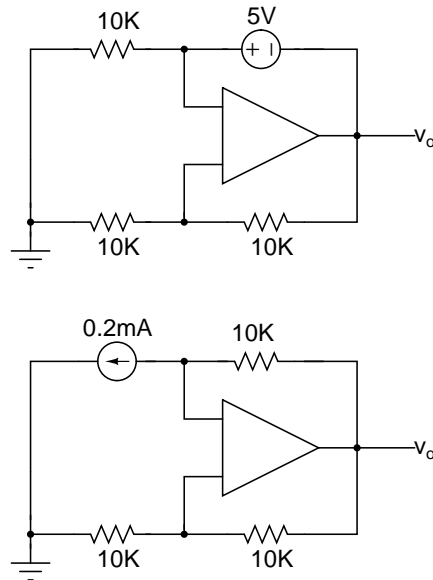


Figure 4: Circuits for Problem 4.

In the circuits above, mark the signs on the opamp for negative feedback operation, and determine  $v_o$ .

## Problem 5

In the circuits above, mark the signs on the opamp for negative feedback operation, and determine  $v_o$ .

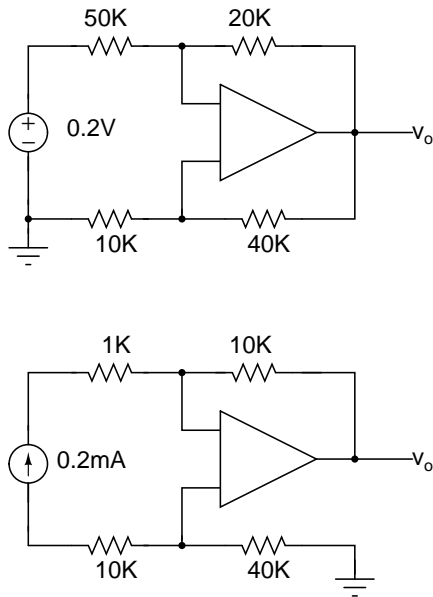


Figure 5: Circuits for Problem 5.

### Problem 6

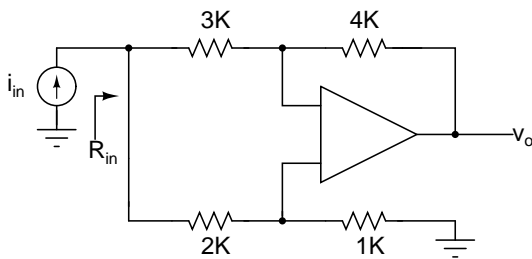


Figure 6: Circuits for Problem 6.

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine  $v_o$ . Determine the input resistance looking in, as denoted by  $R_{in}$ .

### Problem 7

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine  $v_o$  in terms of  $v_1, \dots, v_6$ .

### Problem 8

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine  $v_o$ .

### Problem 9

In the circuit above, mark the signs on the opamp for negative feedback operation, and determine the Norton equivalent for the circuit looking across the load resistor  $R_L$ .

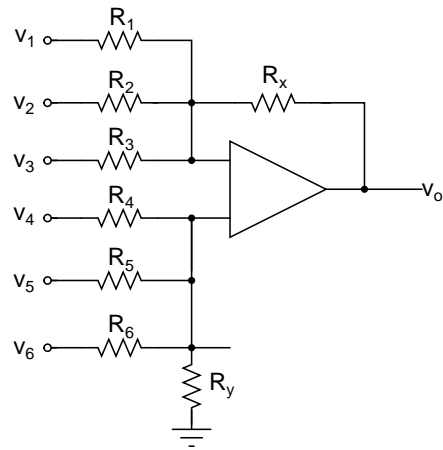


Figure 7: Circuit for Problem 7.

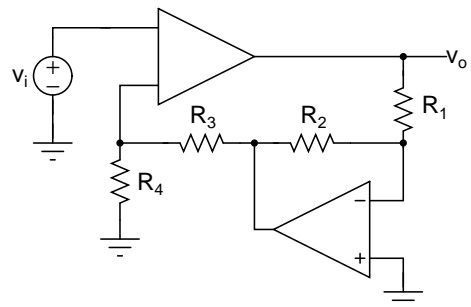


Figure 8: Circuit for Problem 8.

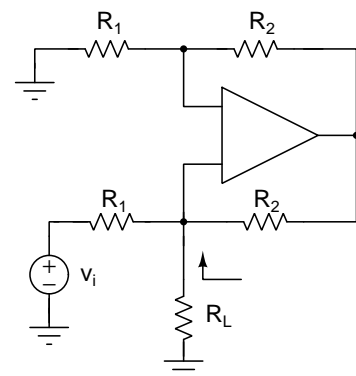


Figure 9: Circuit for Problem 9.

## Problem 10

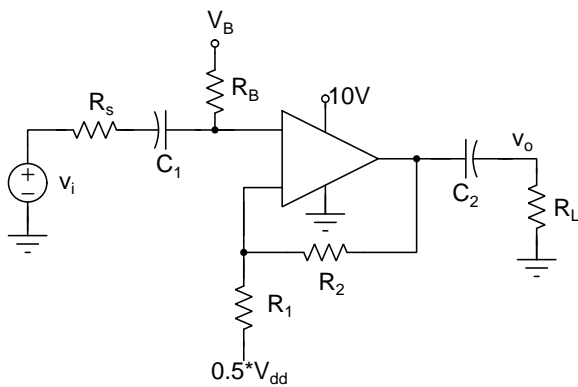


Figure 10: Circuit for Problem 10.

The circuit above shows an amplifier intended for audio applications. The lowest frequency of interest, therefore, is 20 Hz. The opamp is operated with a **single** supply. Assume  $V_{DD} = 10$  V.

- Mark the signs on the opamp for negative feedback operation. Determine  $V_B$  so that no dc current flows through  $R_1$ .
- $R_1 = 10$  K,  $R_s = 50$  K and  $R_L = 1$  K.  $C_1 = 1$   $\mu$ F. Determine  $R_B$  so that the ac voltage across  $C_1$  at the lowest frequency of interest is less than 1% of  $v_i$ .
- Determine  $C_2$  so that the ac voltage across it at the lowest frequency of interest is less than 1% of the ac amplitude across the load resistor.
- Determine  $R_2$  to achieve an ac gain of 50. Sketch the magnitude of the transfer function from  $v_i$  to  $v_o$ .
- Determine the largest input amplitude of a 1 kHz sinusoid that will result in a distortion free output. The opamp saturates if its output attempts to go to within 1 V of its supply rails.

## Problem 11

This problem illustrates another aspect of negative feedback, namely pre-distortion. In the amplifier above, the opamp is non-ideal. We will consider two cases. In the first, the opamp's input characteristic is as shown in Fig. 11(a). Plot the error voltage  $v_e$  between the input terminals of the opamp as  $v_i$  is swept from  $-v_{max}/n$  to  $v_{max}/n$ . Assume that  $A/n \gg 1$ .

In class we assumed that the opamp characteristic saturates abruptly. In reality, saturation occurs in a gentler fashion. An example is shown in Fig. 11(b). On the same graph as you plotted for the previous part, plot  $v_e$  as  $v_i$  is swept. What do you notice?

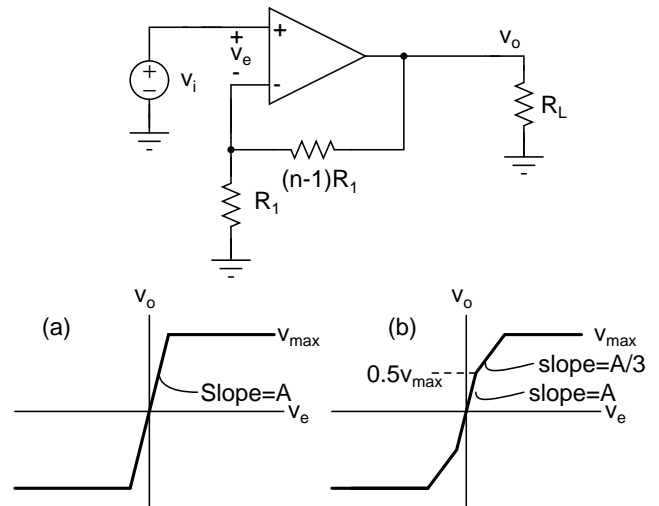


Figure 11: Circuit for Problem 11.

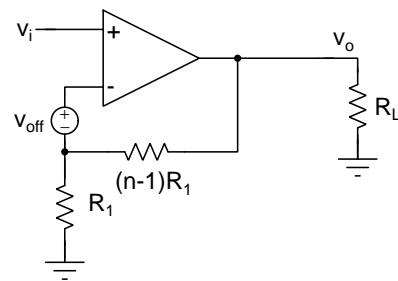


Figure 12: Circuit for Problem 12.

## Problem 12

This circuit explores another non-ideality of an opamp, namely **offset**. In an ideal opamp,  $v_o = Av_e$ , with  $A \rightarrow \infty$ . In reality, it turns out that if the opamp does not saturate, its output can be expressed as  $v_o = A(v_e - v_{off})$ , with  $A \rightarrow \infty$ . Draw the characteristics of an ideal opamp assuming saturation, and that of the opamp with an offset voltage. What is the output dc offset of the amplifier of Fig. 12?

## Problem 13

The figure above shows three different ways of achieving an amplifier with a gain of  $n^2$ , where  $n^2 \gg 1$ . If  $v_{off,1,2} = 0$  and the opamps have infinite gain, all three are equivalent. When the opamps have a finite gain  $A$ , the gains will deviate from the ideal value of  $n^2$ . Determine the output offset voltage and gain in each of the three cases. Make suitable approximations, such as  $1/(1+x) \approx 1-x$  for small  $x$  etc. Which of the amplifiers above is least tolerant of finite opamp gain? Which is the most tolerant?

## Problem 14

In many precision sensing applications, amplifier offset can be (very) problematic. This problem illustrates the idea of **chopping**, which is one way of solving the offset problem. The amplifier's offset is modeled by  $v_{off}$ . The input  $u$  is multiplied by a square wave with 50% duty cycle, processed by the amplifier (whose gain is  $A$ ). The output of the amplifier is multiplied by the same square wave, and passed through a low-pass filter.  $p(t)$  has a fundamental frequency of  $f_c$ , as shown in Fig. 14. For the purposes of this problem, you can assume that the filter is ideal and has a cut-off frequency smaller than  $f_c$ .

Assuming  $u$  is dc, plot the signals at **(a)**, the amplifier output, **(b)** and at  $y$ . What is  $y/u$ ?

Repeat the exercise above assuming that the amplifier, in addition to offset, has finite bandwidth. For simplicity, assume that the transfer function of the amplifier is

$$A(s) = \frac{A_o}{1 + s\tau} \quad (1)$$

where  $\tau f_c \ll 1$ .

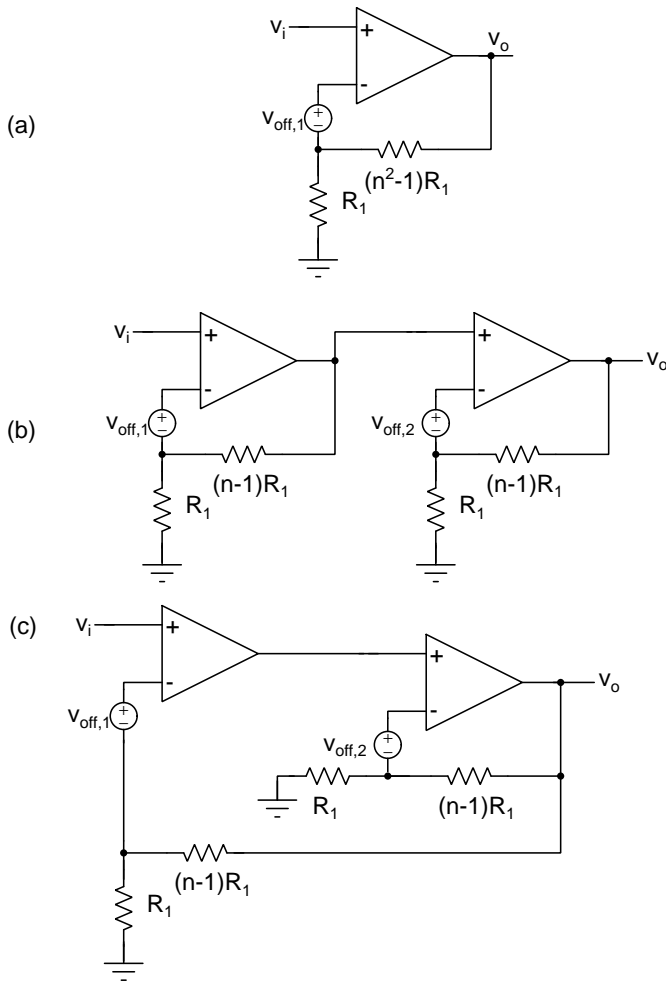


Figure 13: Circuit for Problem 13.

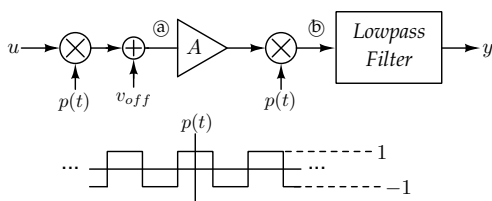


Figure 14: Circuit for Problem 14.

## Problem 15

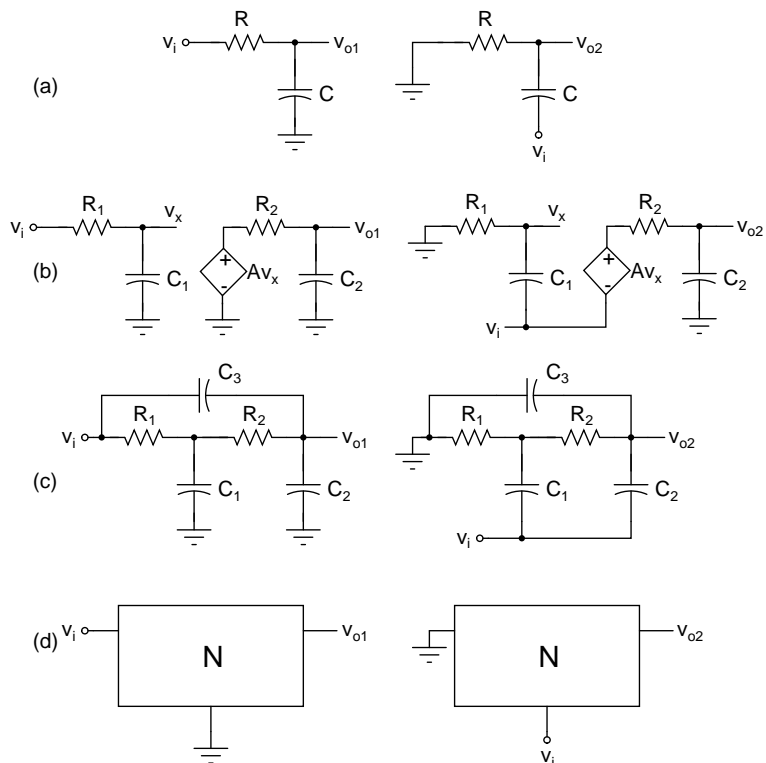


Figure 15: Circuit for Problem 15.

For each of the networks in parts (a), (b) and (c) above, determine  $H_1(s) = V_{o1}(s)/V_i(s)$  and  $H_2(s) = V_{o2}(s)/V_i(s)$ . Is there a pattern you notice? Generalize it to an arbitrary linear network of Fig. 15(d).

### Problem 16

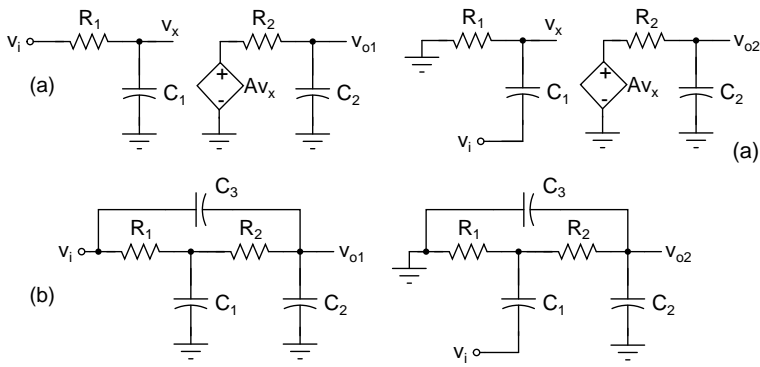


Figure 16: Circuit for Problem 16.

For each of the networks in parts (a), (b) above, determine  $H_1(s) = V_{o1}(s)/V_i(s)$  and  $H_2(s) = V_{o2}(s)/V_i(s)$ . Does the pattern you noticed in the previous problem still hold?

### Problem 17

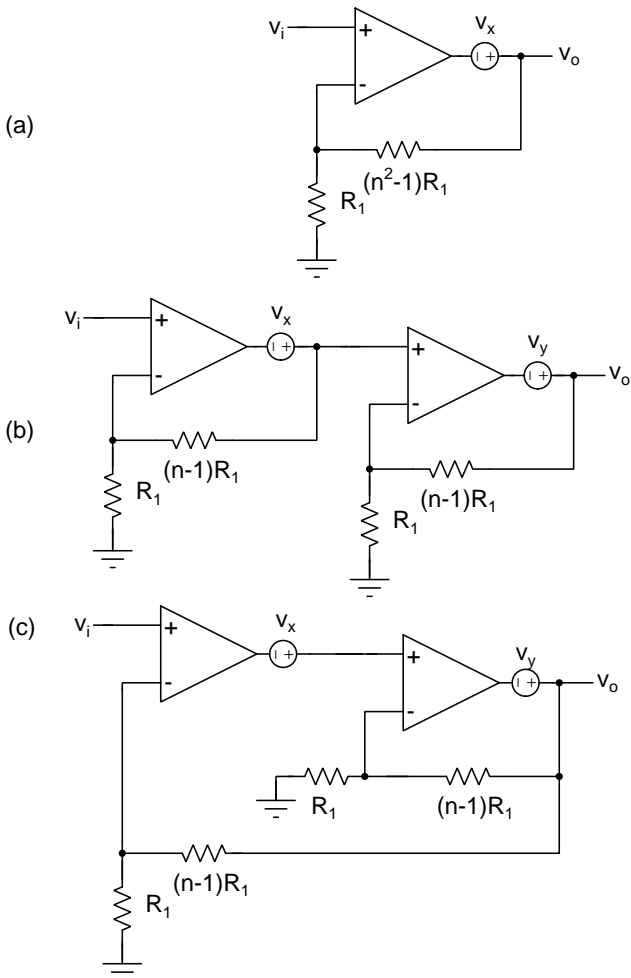


Figure 17: Circuit for Problem 17.

For each of the circuits above, the opamps are ideal. Determine  $v_o$ .

### Problem 18

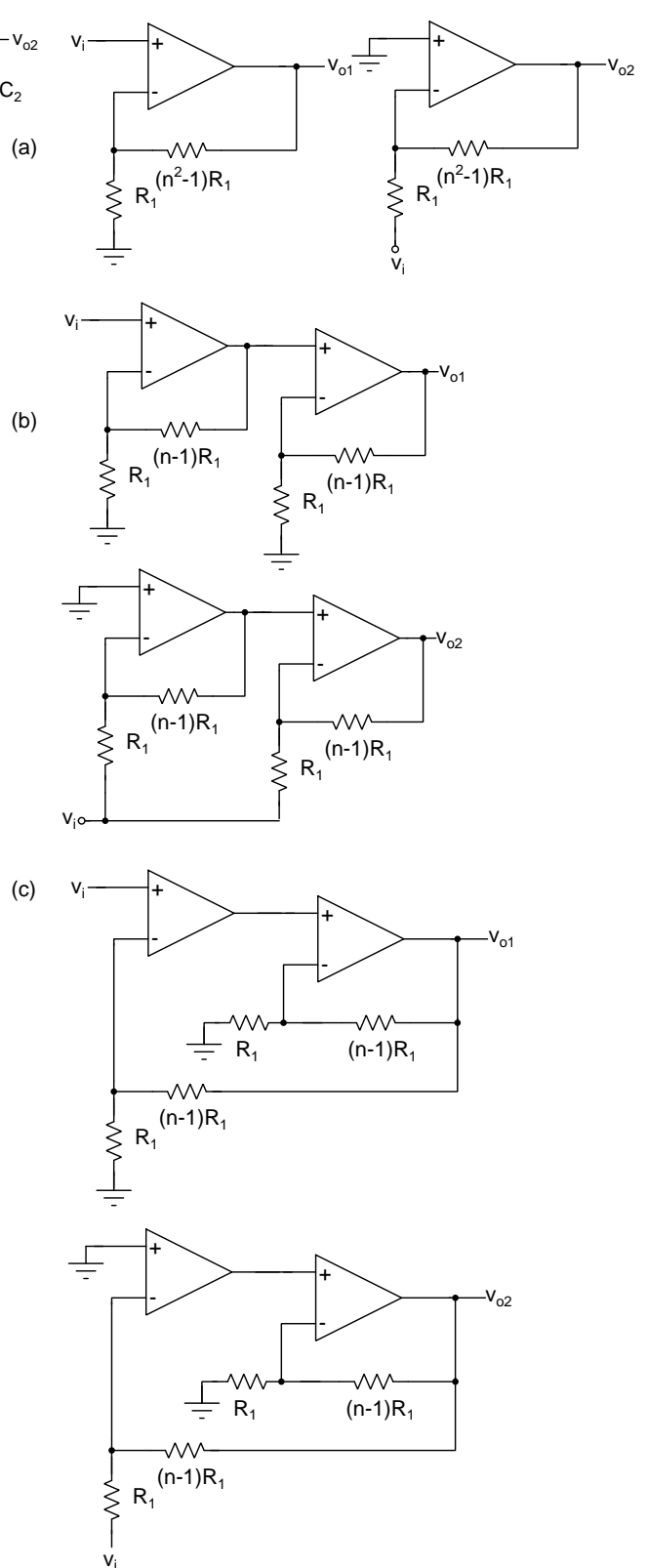


Figure 18: Circuit for Problem 18.

The opamps are ideal. For each of the networks in parts (a), (b) and (c) above, determine  $H_1 = v_{o1}/v_i$  and  $H_2(s) = v_{o2}/v_i$ . Is there a pattern you notice?

Recall that the ideal opamp is a VCVS with infinite

gain and one of its output terminals grounded and inaccessible. How is it that the pattern of Problem 15 holds here, though not in Problem 16?

## Problem 19

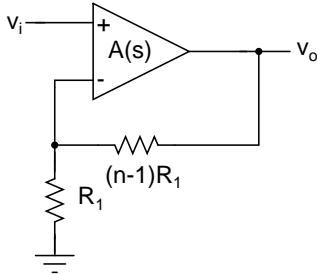


Figure 19: Circuit for Problem 19.

In class, we first assumed that the opamp was a VCVS with infinite gain. We then said – well, in reality, the gain is not infinite, but a large number. In either case, the VCVS had no “memory”, meaning that it is infinitely quick; a change in the input is instantly reflected in the output.

Not surprisingly, it turns out that the opamp is not infinitely fast either. We now, therefore, need to talk about the **transfer function**  $V_o(s)/V_i(s)$ . This problem will explore the effect of the “slowness” of the opamp on the feedback system. Recall from your prior classes that, for a system to be stable, its poles must be in the left half s-plane.

- For  $A(s) = \frac{A_o}{1 + \frac{s}{\omega_o}}$ , determine the closed-loop transfer function  $V_o(s)/V_i(s)$ . Determine the 3-dB bandwidth of the loop-gain function. Also determine the 3-dB bandwidth of the closed loop amplifier. How is it related to that of the loop-gain? Plot the locus of the poles of the closed loop system as  $A_o$  is varied from  $0 - \infty$ . Comment on the stability of the closed-loop system.
- Let us assume a more complicated model for  $A(s)$ . Let  $A(s) = \frac{A_o}{(1 + \frac{s}{\omega_o})^2}$ . Determine the closed-loop transfer function  $V_o(s)/V_i(s)$ . Express the transfer function in the form

$$\frac{V_o(s)}{V_i(s)} = \frac{G}{\frac{s^2}{\omega_p^2} + \frac{s}{Q_p \omega_p} + 1}, \quad (2)$$

where  $G$  is the dc gain. Plot the locus of the poles of the closed loop system as  $A_o$  is varied from  $0 - \infty$ . Comment on the stability of the closed-loop system.

- Let us assume an even more complicated model for  $A(s)$ . Let  $A(s) = \frac{A_o}{(1 + \frac{s}{\omega_o})^3}$ . Determine the closed-loop transfer function  $V_o(s)/V_i(s)$ . Plot the locus of the poles of the closed loop system as  $A_o$  is varied from  $0 - \infty$ . Comment on the stability of the closed-loop system.