

# ANALOG SYSTEMS : PROBLEM SET 11

## Problem 1

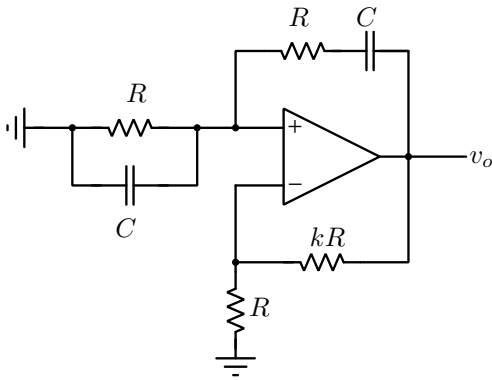


Figure 1: Circuit for Problem 1.

Fig. 1 shows a sinewave oscillator. Determine  $k$  so that it just begins to oscillate. All opamps are ideal.

## Problem 2

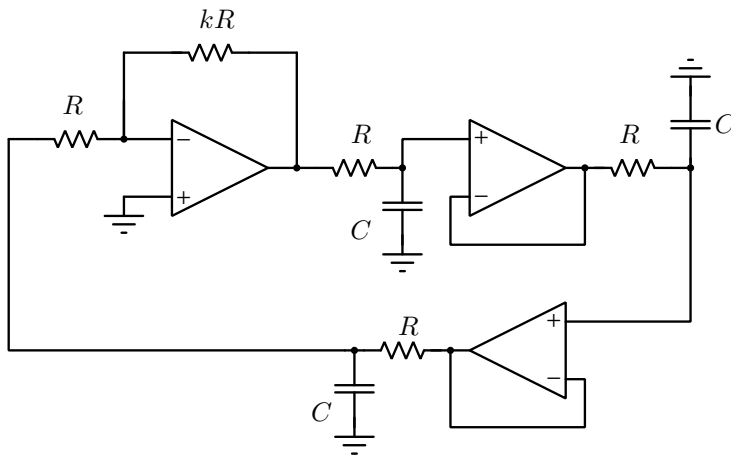


Figure 2: Circuit for Problem 2.

All opamps are ideal in Fig. 2. Determine  $k$  so that it just begins to oscillate.

## Problem 3

Repeat for the circuit of Fig. 3.

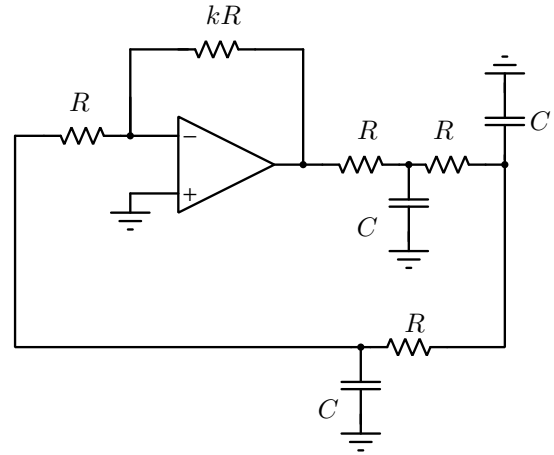


Figure 3: Circuit for Problem 3.

## Problem 4

Fig. 4(a) shows an LCR network with a limiting VCCS. The  $Q$  of the RLC parallel network can be assumed to be  $\gg 1$ . The characteristic of the VCCS is shown in Fig. 4(b). The slope of the VCCS is denoted by  $G_1$  and the maximum/minimum current it can source/sink is given by  $\pm I_{max}$ .

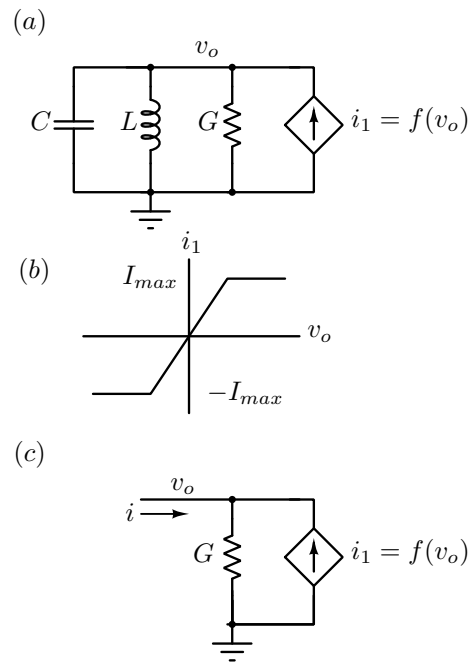


Figure 4: Circuit for Problem 4.

Determine the condition on  $G_1$  for oscillation to start up. Assuming that this condition is satisfied, draw the  $i - v_o$  characteristic of the element shown in Fig. 4(c). Assume

that  $v_o = A \sin(\omega t)$ . Determine and plot the amplitude of the fundamental component of the current  $i$  as  $A$  is varied from 0 to  $\infty$ . What will be amplitude of oscillation of the circuit in part (a) of the figure, in steady state? You may assume that  $v_o$  is a sinusoid at the fundamental frequency.