

# EC 201: Problem Set 4


Note Title

9/11/2008

Shanthi@ee.iitm.ac.in

$$\mu_{n,\text{ox}} \frac{W}{L} = 50000 \mu\text{A}/\text{V}^2$$

$$V_T = 0.5 \text{ V}$$

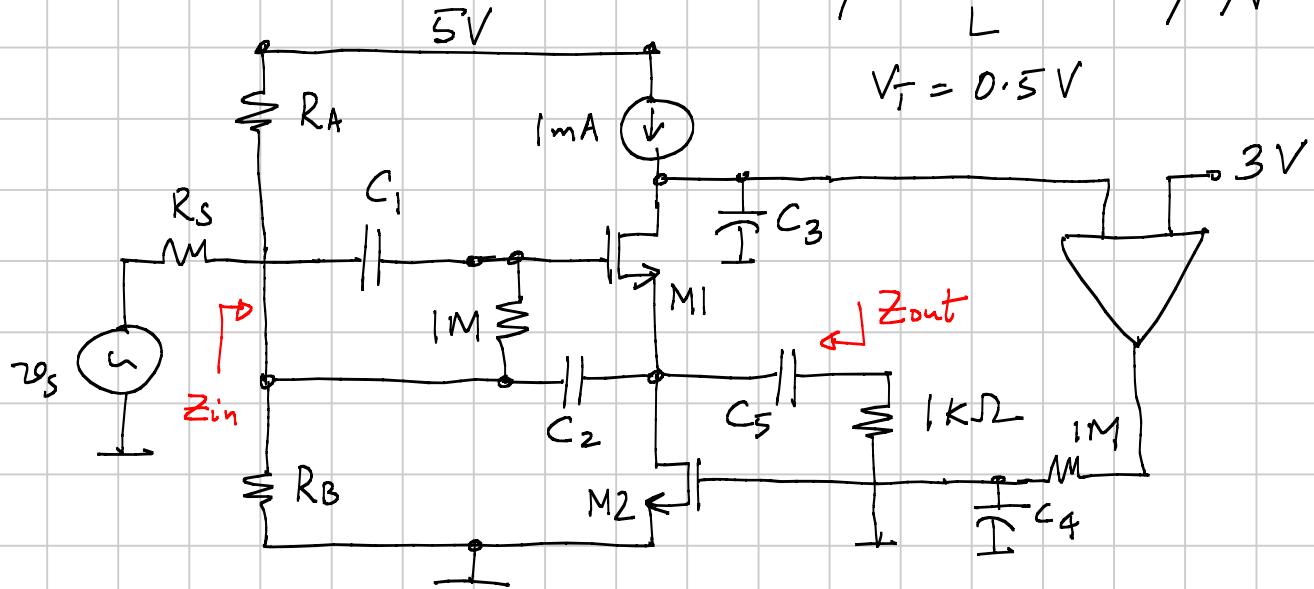

The circuit above shows yet another way of stabilizing the operating point of a transistor. The opamp is ideal.

(a) Determine the signs on the opamp for DC negative feedback.

(b) Determine \$R\_A\$ & \$R\_B\$ so that the swing limits for positive and negative inputs are equal.


\$R\_A \parallel R\_B\$ must be \$1\text{M}\Omega\$.

Assume that the incremental voltage at the gate of \$M\_1\$ is \$v\_s\$.

(c) Given the results in (b) above, determine  $Z_{in}$  &  $Z_{out}$ .

(d) Now,  $C_2$  is removed. Calculate  $Z_{in}$  &  $Z_{out}$ . What do you notice?

### Problem 2

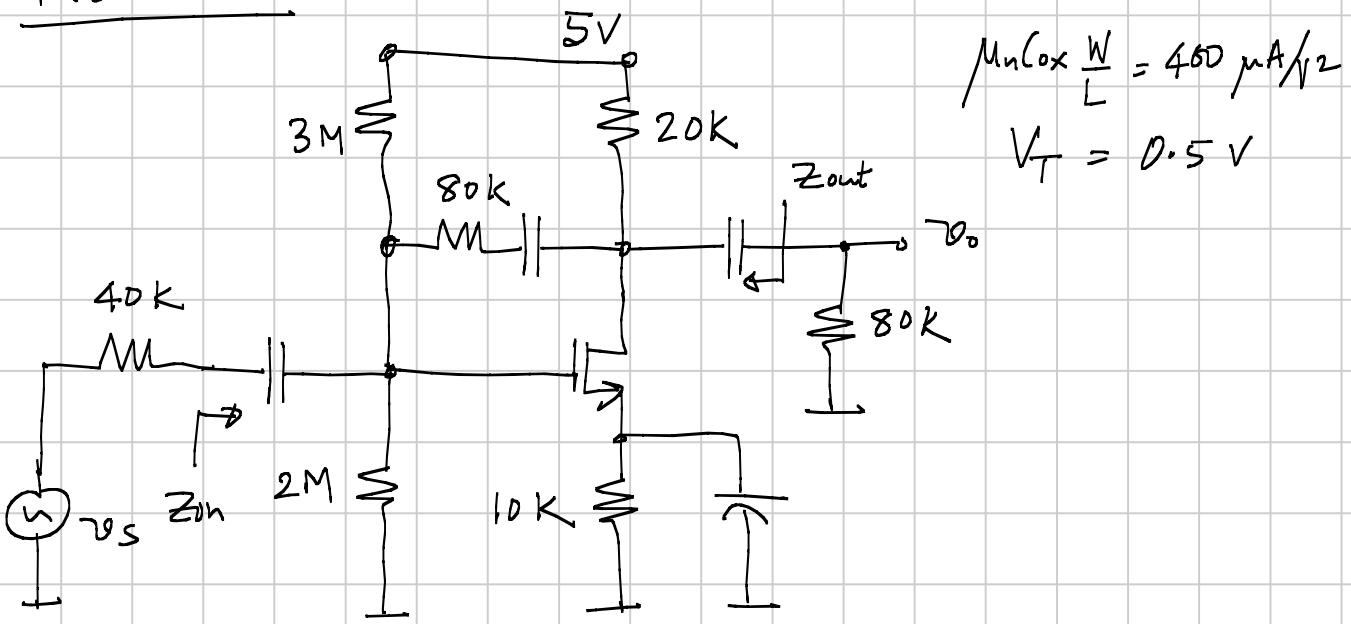

(a) Determine the quiescent operating point of the transistor.

(b) Find the incremental gain  $\frac{v_o}{v_s}$ ,  $Z_{in}$  &  $Z_{out}$ .


(c) Find the maximum amplitude permissible for the input sinewave, so that clipping is avoided.

(d) Repeat (b) if the 80k feedback

resistor is changed to  $40\text{ k}\Omega$ .

What do you notice when you compare  $Z_{in}$  &  $Z_{out}$  with those obtained in part (b) ?

### Problem 3

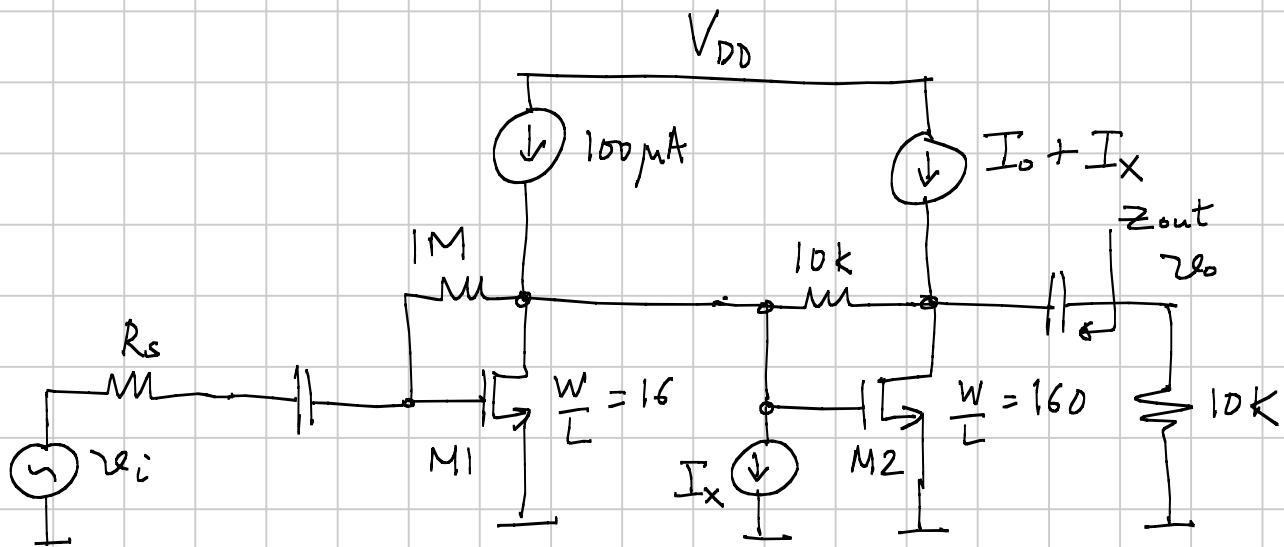

$$\mu_n C_{ox} = 200 \mu\text{A}/\sqrt{\text{V}}$$

(a) Determine  $I_o$  so that the quiescent current through M<sub>1</sub> is  $100\text{ }\mu\text{A}$ . What is the quiescent  $V_{DS}$  of M<sub>2</sub> (in terms of  $I_x$ )?

(b) Find the incremental  $\frac{v_o}{v_i}$  and  $Z_{out}$ .

(c) Choose  $I_x$  so that the output JUST clips at both extremes. What is maximum permissible input amplitude?