

EC201-ANALOG CIRCUITS : PROBLEM SET 3

shanthi@ee.iitm.ac.in

Problem 1

The MOSFET in Fig. 1 has $V_T = 0.7V$, and $\mu_n C_{ox} = 500 \mu A/V^2$. The drain current in the device is 1 mA.

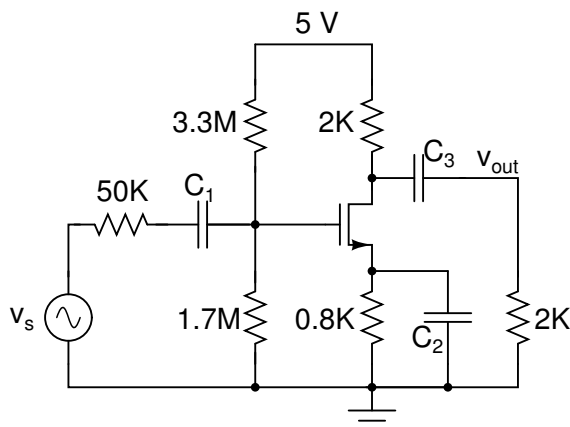


Figure 1: Problem 1

- Determine the small signal gain from v_s to v_{out} .
- Determine the (W/L) of the device and the quiescent V_{GS} and V_{DS} .
- The lowest frequency contained in v_s is 100 rad/s. Determine the minimum values of C_1 , C_2 and C_3 required so that the natural frequencies associated with their charging/discharging is atleast 10 times smaller than the smallest input frequency.
- Determine the voltage swing limits at v_{out} . What is the amplitude of the largest sinusoidal input signal that can be applied before the output begins to clip ?
- The supply voltage is changed to 5.5V. Determine the small signal gain of the amplifier.
- Due to a change in temperature, V_T increases by 100 mV. What is the new small signal gain of the amplifier ?

Problem 2

The MOSFETs in Fig. 2 have $V_T = 0.7V$, and $\mu_n C_{ox} = 500 \mu A/V^2$. Like in Problem 1, the drain current in M2 is 1 mA, and has the same (W/L) as in that problem.

- Determine the small signal gain from v_s to v_{out} .
- Determine the (W/L) of M1 and the quiescent V_{GS} and V_{DS} .

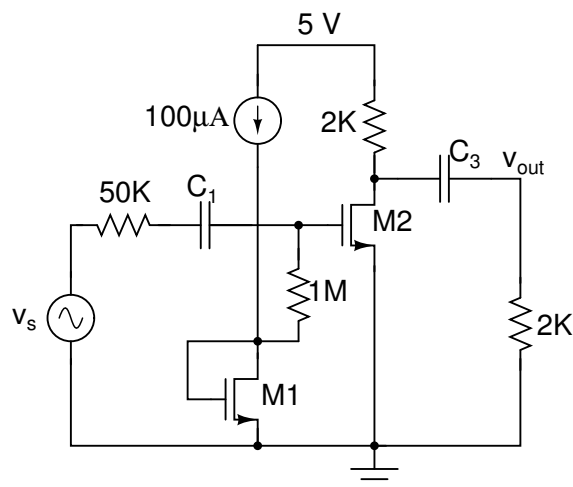


Figure 2: Problem 2

- The lowest frequency contained in v_s is 100 rad/s. Determine the minimum values of C_1 and C_3 required so that the natural frequencies associated with their charging/discharging is atleast 10 times smaller than the smallest input frequency.
- Determine the voltage swing limits at v_{out} . What is the approximate amplitude of the largest sinusoidal input signal that can be applied before the output begins to clip ?
- The supply voltage is changed to 5.5V. Determine the small signal gain of the amplifier. How does this compare with the results of Problem 1 ? Why ?
- What is the small signal gain of the amplifier if (a) $V_{T,M1} = 0.8V, V_{T,M2} = 0.7V$ (b) $V_{T,M1} = 0.7V, V_{T,M2} = 0.8V$ and (c) $V_{T,M1} = 0.8V, V_{T,M2} = 0.8V$? How does this compare with the results of Problem 1 ? Why ?

Problem 3

The MOSFETs in Fig. 3 have $V_T = 0.7V$, and $\mu_n C_{ox} = 500 \mu A/V^2$. Like in Problem 1, the drain current in M2 is 1 mA, and has the same (W/L) as in that problem.

- Determine the small signal gain from v_s to v_{out} .
- Determine the (W/L) of M1 and the quiescent V_{GS} and V_{DS} .
- The lowest frequency contained in v_s is 100 rad/s. Determine the minimum values of C_1 and C_3 required so that the natural frequencies associated with their charging/discharging is atleast 10 times smaller than the smallest input frequency.

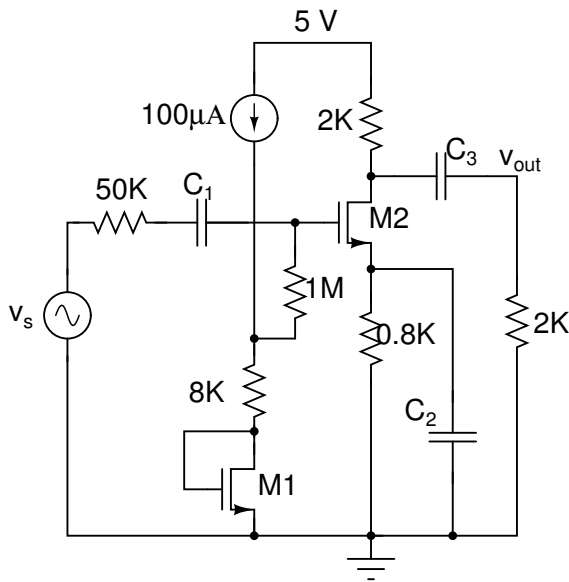


Figure 3: Problem 3

- Determine the voltage swing limits at v_{out} . What is the amplitude of the largest sinusoidal input signal that can be applied before the output begins to clip?
- The supply voltage is changed to 5.5V. Determine the small signal gain of the amplifier. How does this compare with the results of Problem 1 & 2? Why?
- What is the small signal gain of the amplifier if (a) $V_{T,M1} = 0.8V, V_{T,M2} = 0.7V$ (b) $V_{T,M1} = 0.7V, V_{T,M2} = 0.8V$ and (c) $V_{T,M1} = 0.8V, V_{T,M2} = 0.8V$? How does this compare with the results of Problem 1 & 2? Why?

Problem 4

This problem illustrates the effects of battery internal resistance on the small signal performance of an amplifier. The MOSFETs in Fig. 4 have $V_T = 0.7V$, and $\mu_n C_{ox} = 500 \mu A/V^2$. Like in Problem 1, the drain current in M2 is to be 1 mA. R_b represents the internal resistance of the battery. To determine the operating point, neglect the drop across R_b due to the current flowing through the gate-bias resistors. For the first three parts, set $C_b = 0$.

- For $R_b = 0$, determine the (W/L) of the FET and the quiescent V_{GS} and V_{DS} . Determine the small signal y-parameters of the two port enclosed in the box. What do you observe about y_{12} ? Why? Is there *any* AC negative feedback around M2?
- Repeat the above exercise for $R_b = 500 \Omega$. Comment on the results.
- To avoid degradation in performance due to the DC drop across R_b , a student deliberately increases the battery voltage to 5.5V, so that the device operating point is identical to that in the first part of this problem. Determine the small signal y-parameters of the two port enclosed in the box. What do you observe about y_{12} ? Why? Is there *any* AC negative feedback around M2?

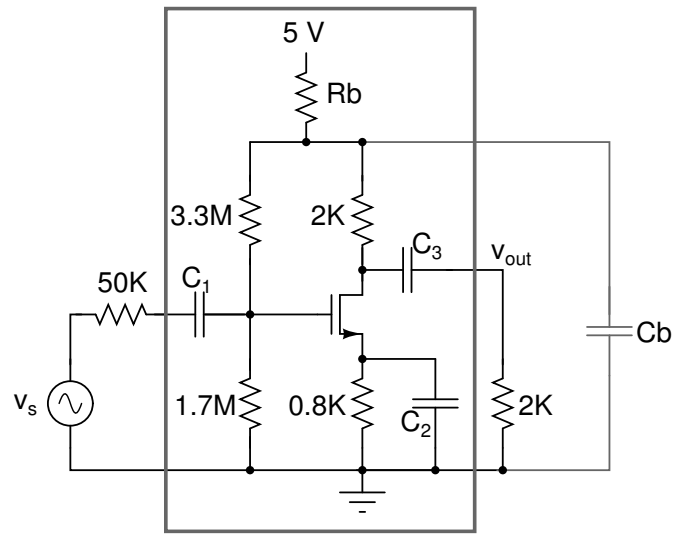


Figure 4: Problem 4

- Based on the observations above, the student adds a **huge** capacitor C_b between the battery output and ground. Does this solve the problem(s) faced in part 3 above? Why?

Problem 5

The MOSFET in Fig. 5 has $V_T = 0.7V$, and $\mu_n C_{ox} = 500 \mu A/V^2$.


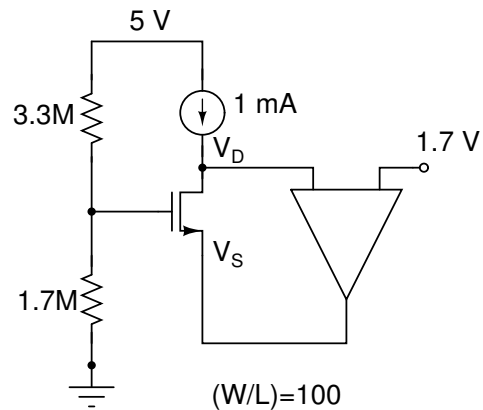


Figure 5: Problem 5

- Reason through the circuit of Fig. 5 and figure out *why* this makes sense.
- Determine the signs on the opamp for negative feedback operation.
- Determine the potentials at nodes V_D and V_S .

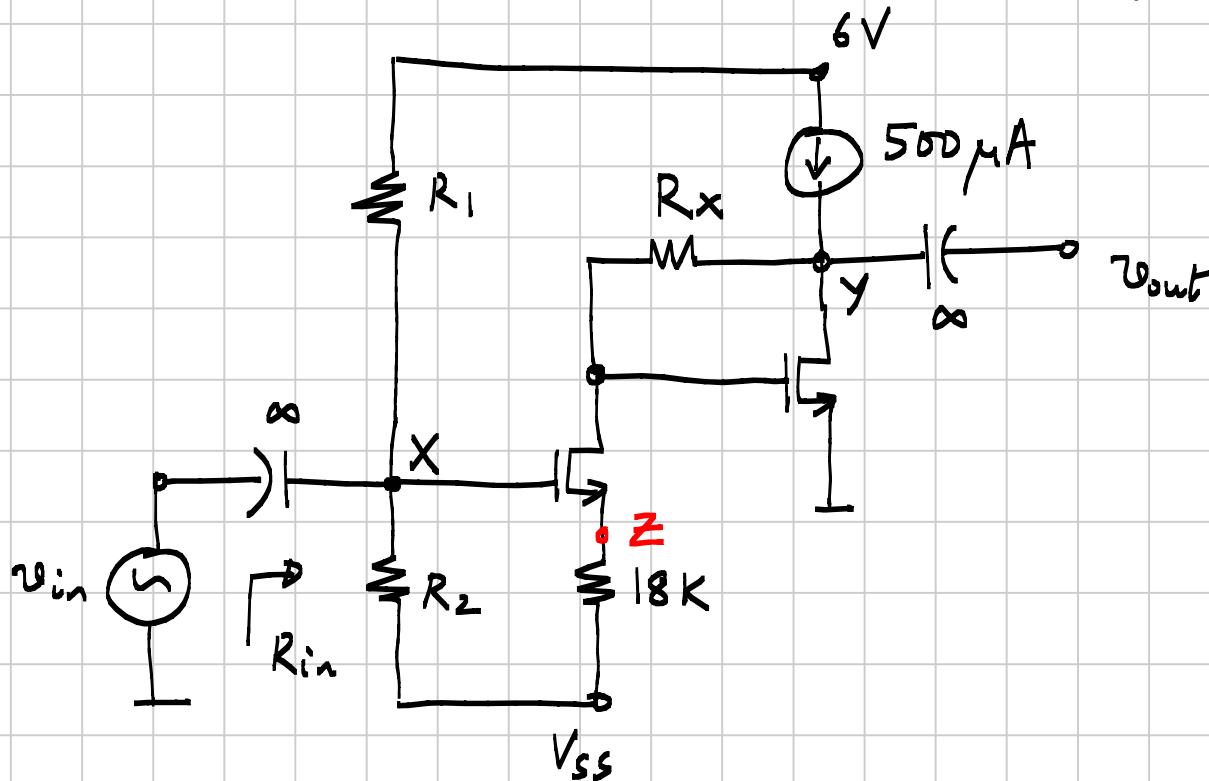Problem 6

* For this problem, both transistors are identical, with $V_T = 0.5\text{ V}$, $\lambda = 0$, $\mu_n C_{ox} \frac{W}{L} = 500 \mu\text{A}/\text{V}^2$.



The quiescent currents through both transistors are equal. Determine R_x , V_{ss} , R_1 , & R_2 so that

- v_{in} can be coupled without using C_1
- $R_{in} = 1\text{ M}\Omega$
- $\frac{v_{out}}{v_{in}} = 2$, after accounting for finite g_m of the transistors


After determining the values above, find the quiescent voltage at node Y and the maximum sinusoidal amplitude one can use at the input so that

the output is not distorted.

Now, an infinite capacitor is connected from node z to ground. What is $\frac{v_{out}}{v_{in}}$ now?


Problem 7

*

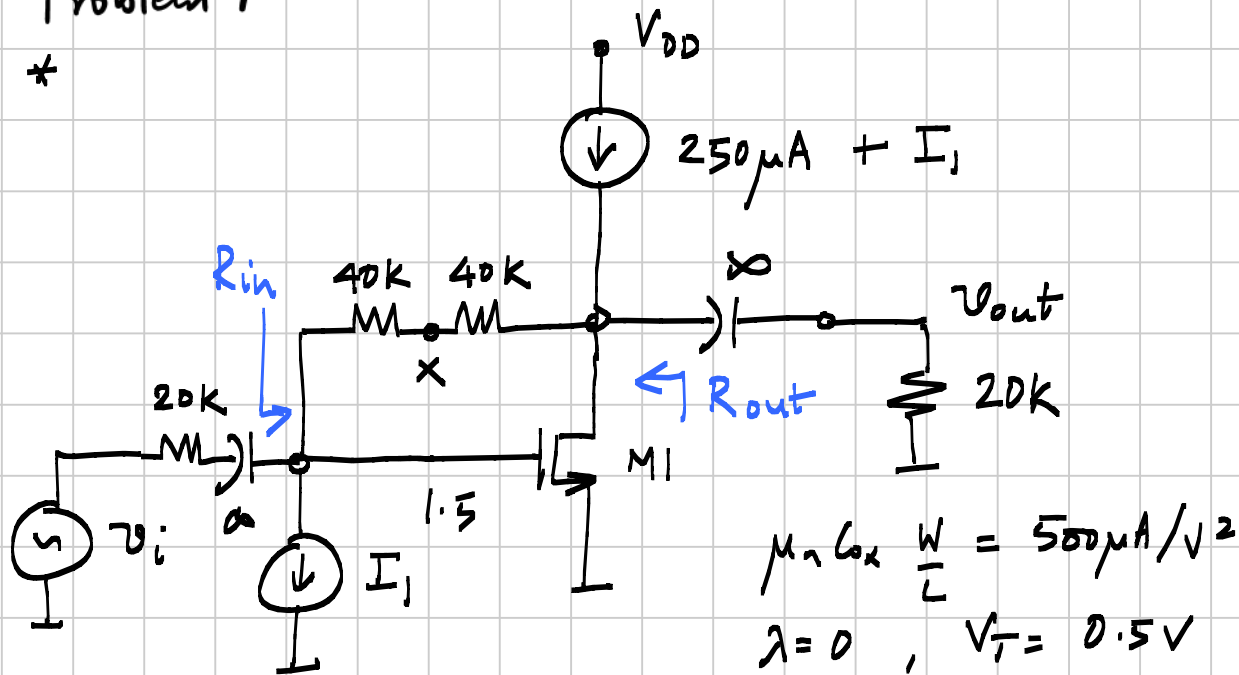

- Determine the quiescent current of $M1$.
- Assuming large β_m , what gain do you expect from v_{in} to v_{out} ? What is the actual gain?
- Determine the input & output impedances R_{in} & R_{out} .
- Determine I_1 so that the output sinusoid just clips at both extremes for an input amplitude of 1 V. For this part, assume β_m is very large.
- An infinite capacitor is now connected between the node marked x and ground. Determine the incremental gain from v_i to v_{out} .

* Problem 8

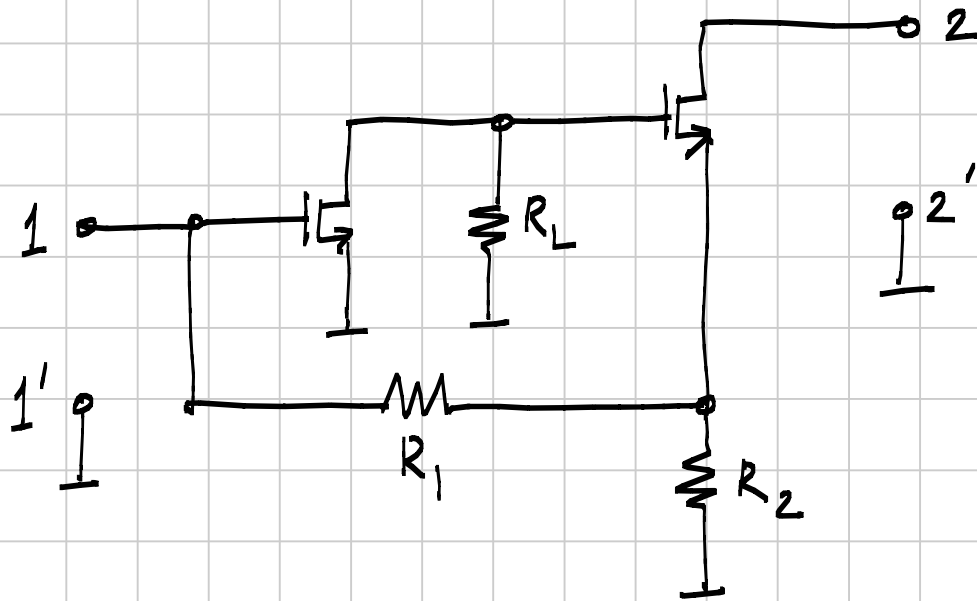


The circuit above is the incremental equivalent of an amplifier. The transistors have transconductances denoted by g_m .

- Determine the input impedance @ port 1 when port 2 is shorted.
- Determine the output impedance @ port 2 when port 1 is shorted.
- What kind of controlled source is this?
- If $g_m \rightarrow \infty$, determine the transfer function of the above controlled source.


Problem 9

*

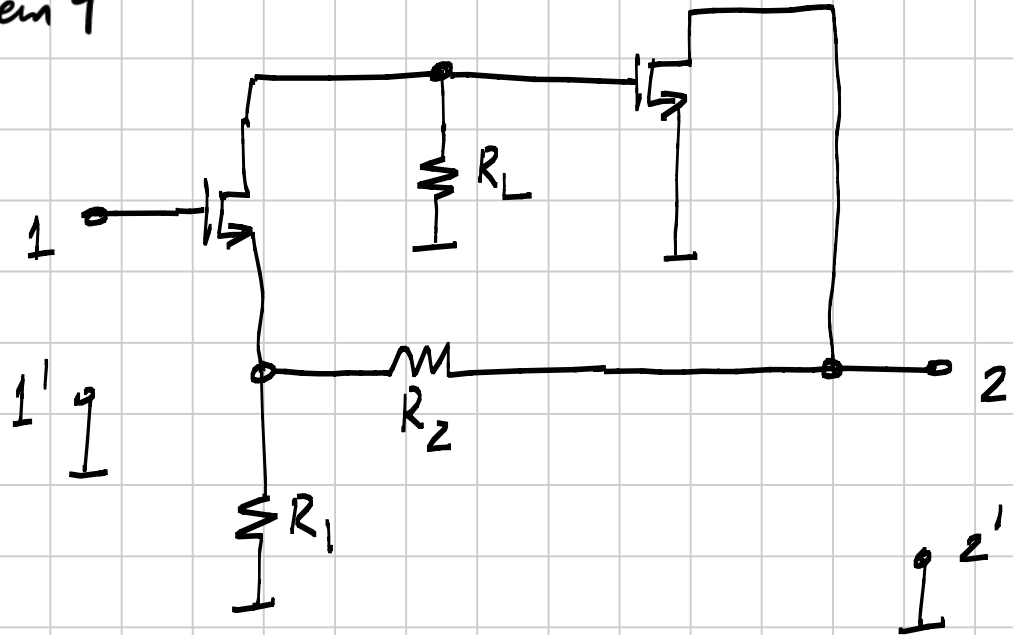

Repeat the previous problem for the incremental circuit shown above.

Problem 10

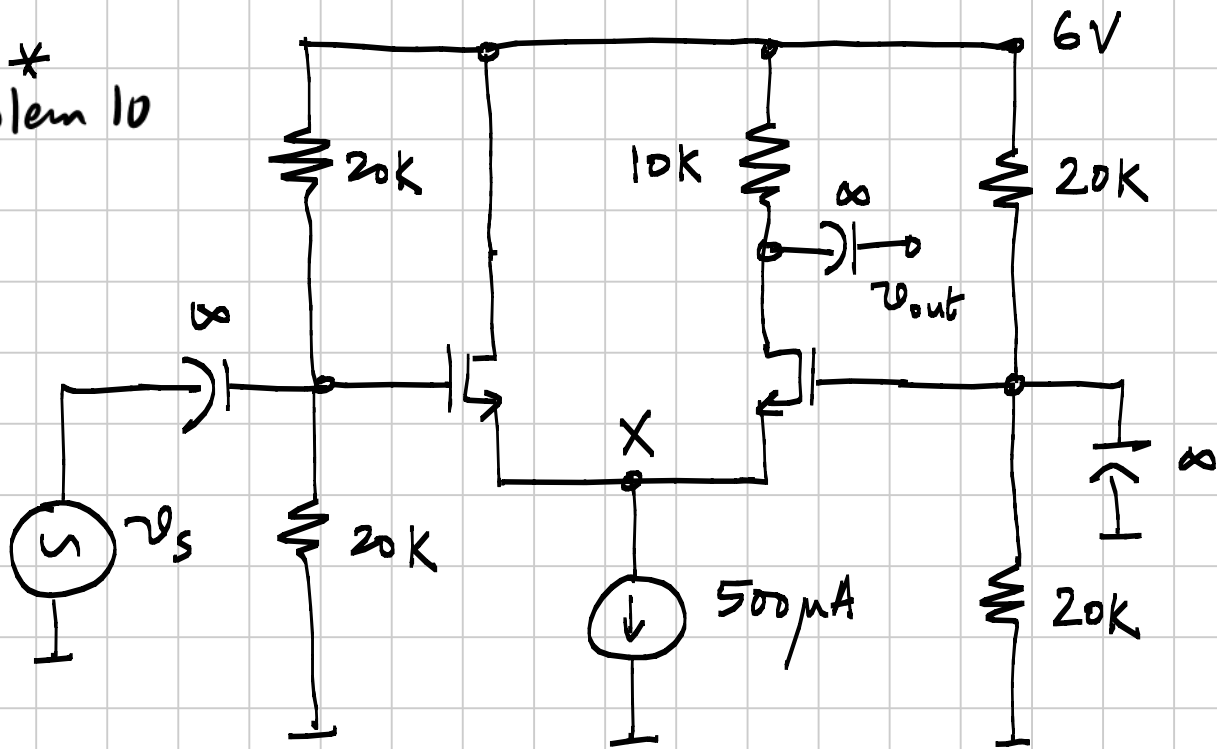




$$V_T = 0.5V \quad \mu_n C_{ox} \frac{W}{L} = 500 \mu A/V^2$$

$$\lambda = 0$$


In the circuit above

- (a) Find the operating point.
- (b) The incremental gain v_{out}/v_{in} .

Prob 11* Determine the signs on the opamps for negative feedback operation.

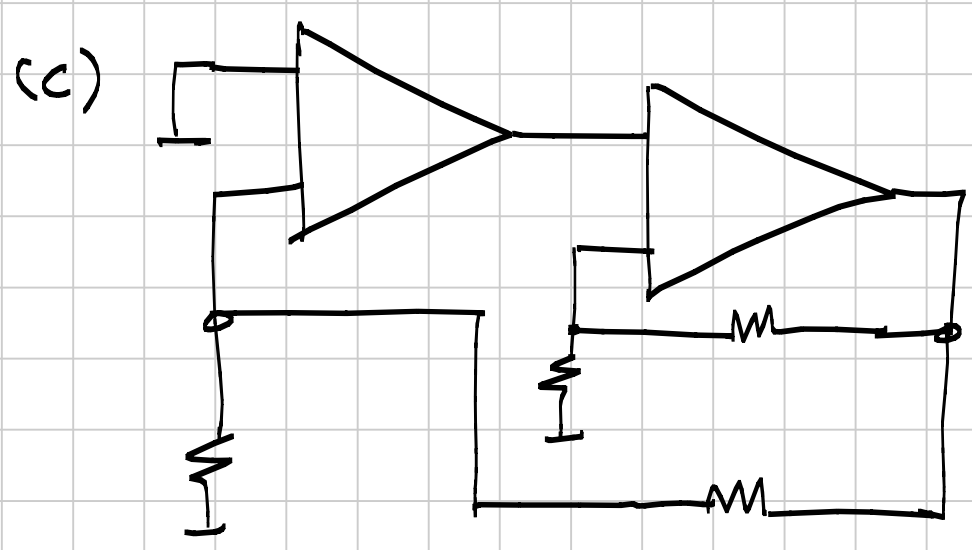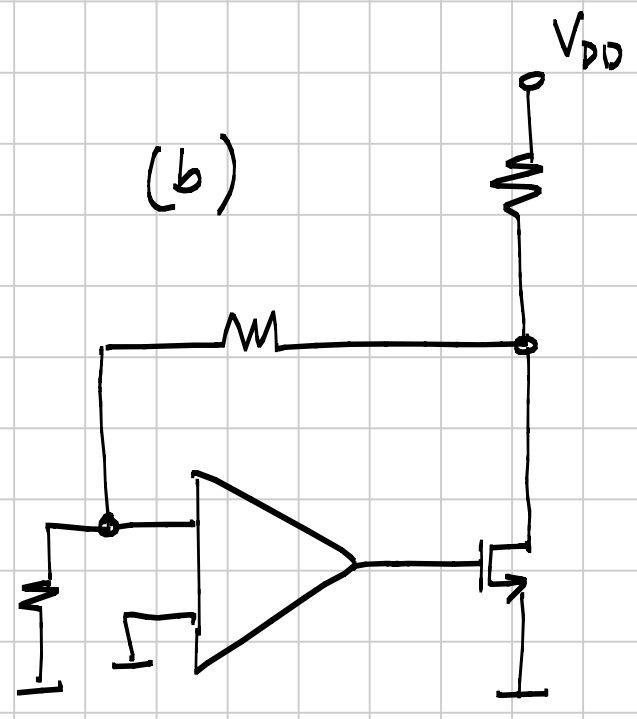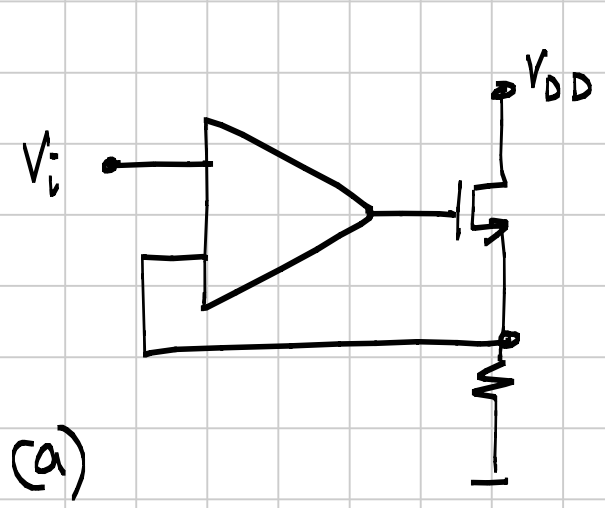

* Problem 12

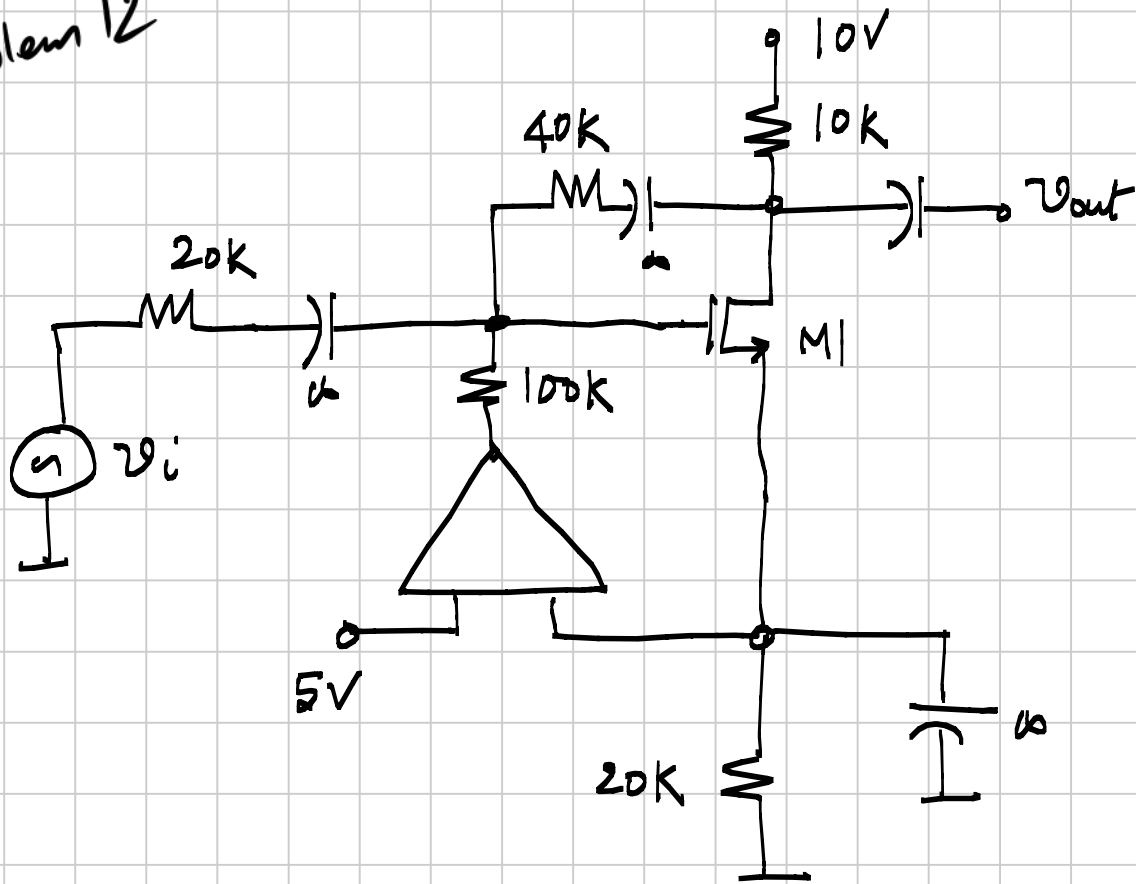

- (a) Determine the signs on the opamp for negative feedback operation
- (b) Determine the quiescent potential @ the gate of M1.
- (c) What is the incremental gain $\frac{v_{out}}{v_i}$?