

Problem set 8: Bipolar junction transistor circuits

$$\text{NPN: } V_{BE,ON} = 0.7V$$

$$V_{CE,SAT} = 0.7V$$

$$V_{AN} = 25V$$

$$\beta_N = 100$$

$$\text{PNP: } V_{EB,ON} = 0.7V$$


$$V_{EC,SAT} = 0.7V$$

$$V_{AP} = 25V$$

$$\beta_P = 100$$

Use $\beta_N = \beta_P = \infty$ and $V_{AN} = V_{AP} = \infty$ for operating point calculations unless otherwise specified.

① Current mirror:

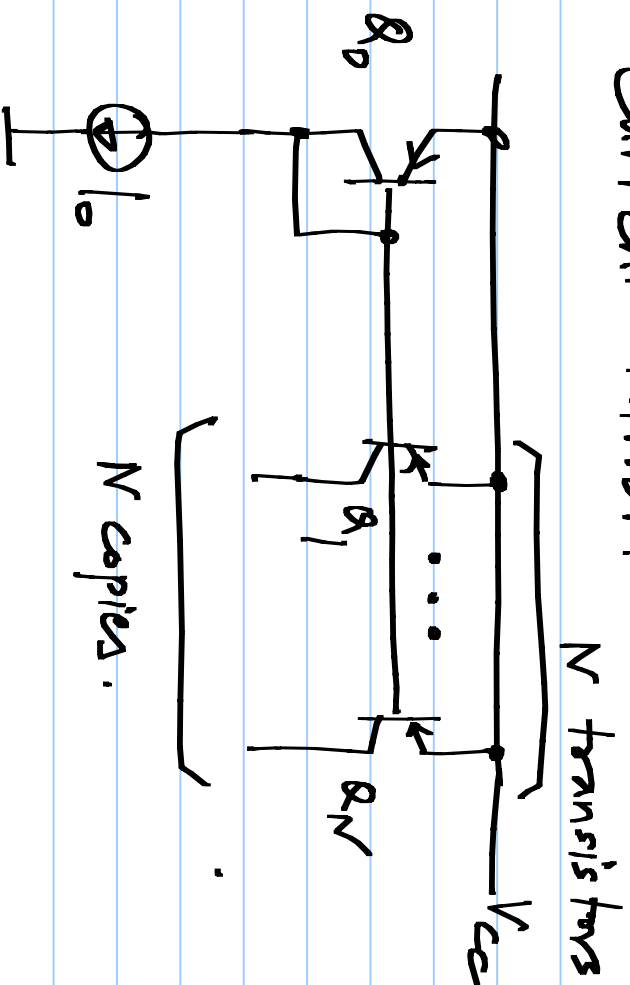


Assuming $\beta_p = 200$,
calculate the
maximum number

(N) of current sources
that can be made


while maintaining an error of 5% or less in the
copied currents.

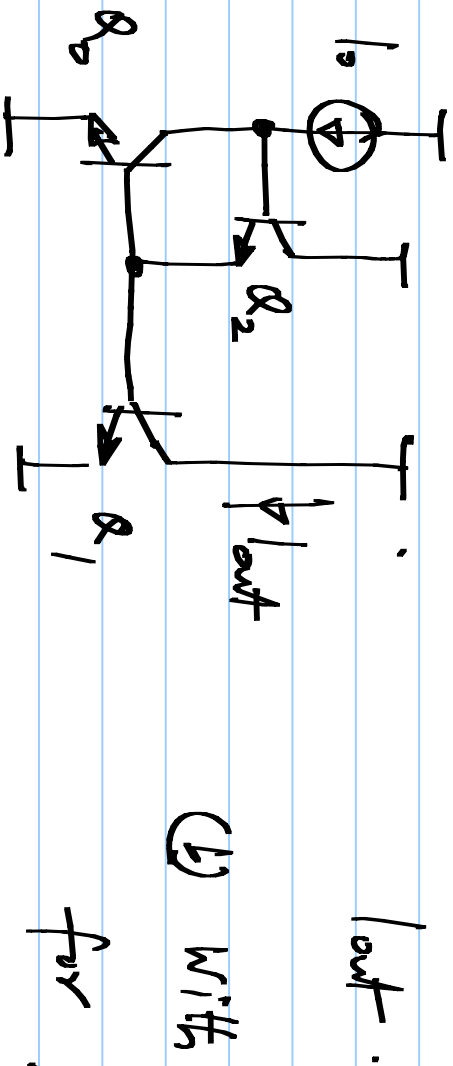② Improved current mirror: (a) Assuming a finite β_N , calculate



(b) With this arrangement, for $\beta_N = 200$, how many copies of the current can be realized with a 5% or smaller error?

③

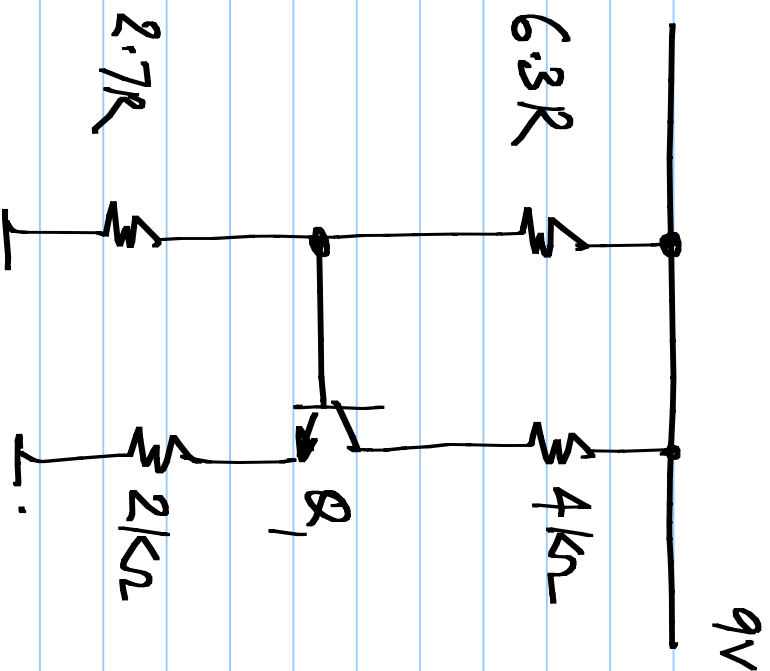

(a) operating point:

Calculate I_c , V_{CESAT} of

Q_1

(b) Assuming $\beta_V = 100$, calculate R such that the shift in base voltage (compared to $\beta_V = \infty$) is 50mV or less.

$$(\beta_N = 100)$$

With the value of R calculated in the previous problem, calculate:


$$\frac{v_o}{v_s}, R_i, R_o \text{ and}$$

swing limits on v_s

such that Q_1 stays

within the active region and away from cutoff ($i_{B1} = 0$)

C_1, C_2, C_3 are very large

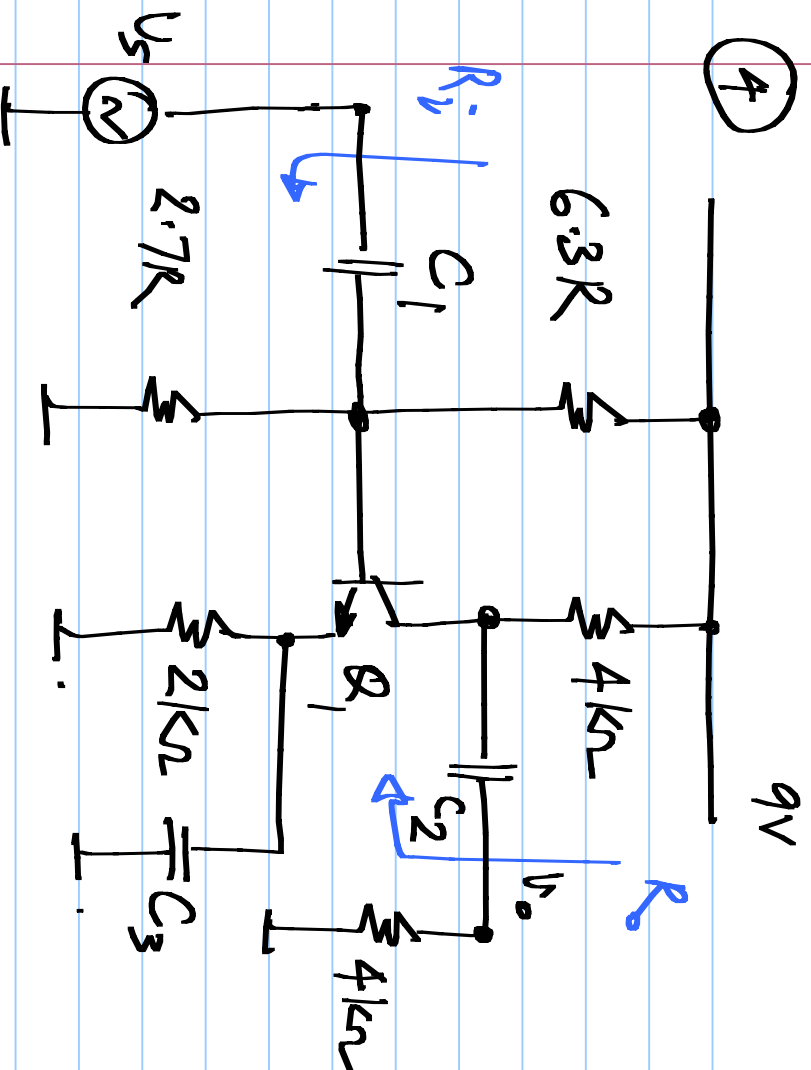

$$(\beta_N = 100)$$

With the value of R calculated in

problem ③ calculate:


$$\frac{V_o}{V_s}, R_i, R_i', R_o \text{ and}$$

swing limits on V_s


such that Q_1 stays

within the active region and away from cutoff ($I_{BQ} = 0$)

C_1, C_2 are very large

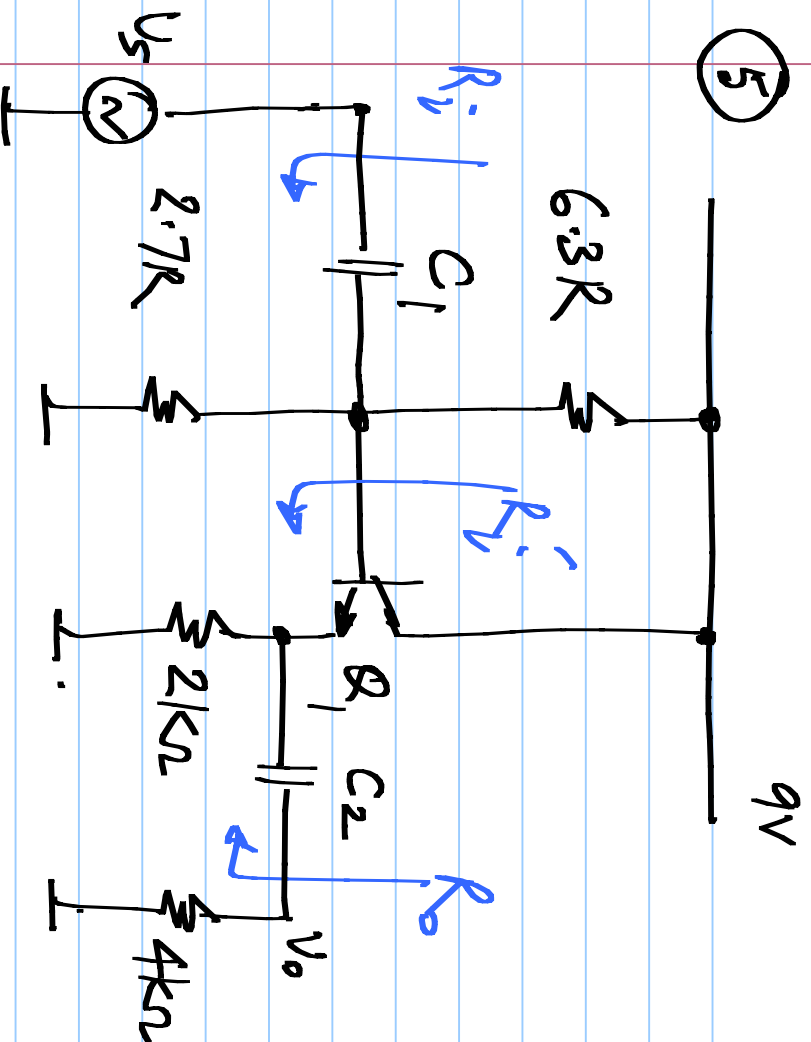

6

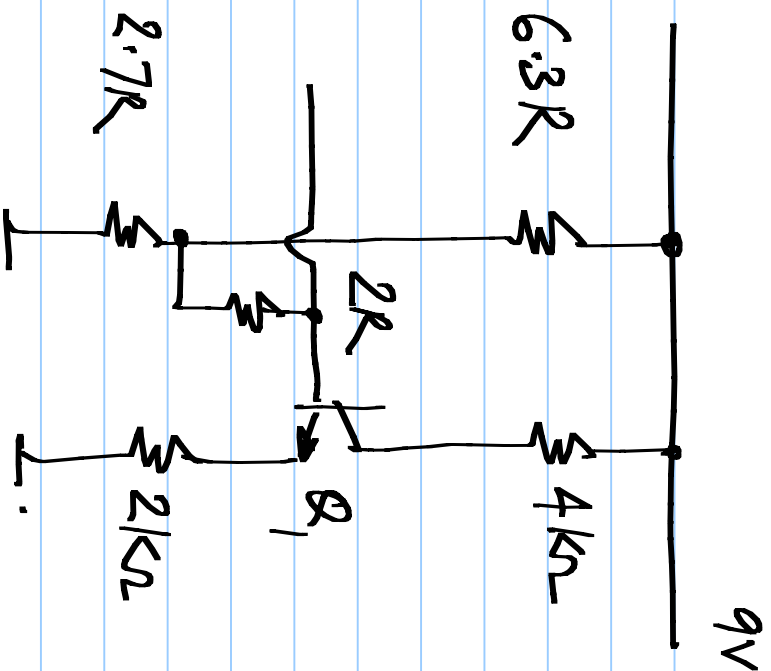

(a) operating point:

Calculate I_C , $V_{CE\text{SAT}}$ of

Q_1

(b) Assuming $\beta_V = 100$, calculate R such that the shift in base voltage (compared to $\beta_V = \infty$) is 50mV or less.

$$(\beta_N = 100)$$

With the value of R calculated in

problem ⑤ calculate:


$$\frac{v_o}{v_s}, R_i, R_o \text{ and}$$

swing limits on v_s


such that Q_1 stays

within the active region and away from cutoff ($i_{B1} = 0$)

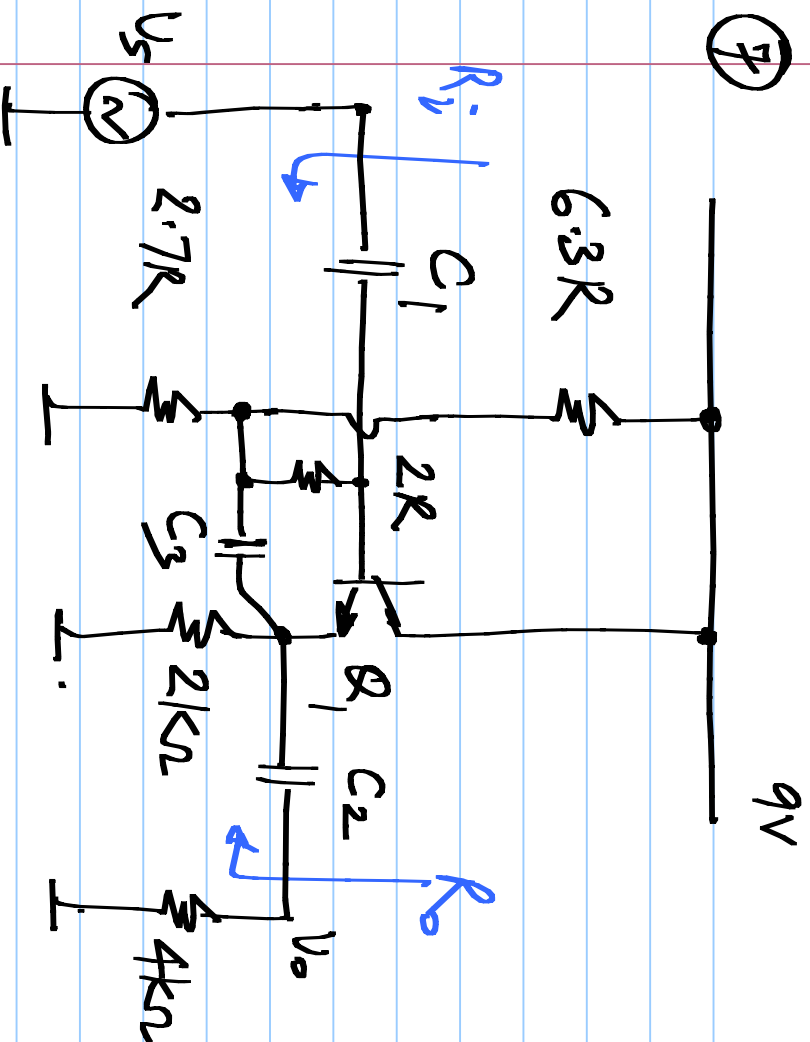C_1, C_2, C_3 are very large; compare to P5



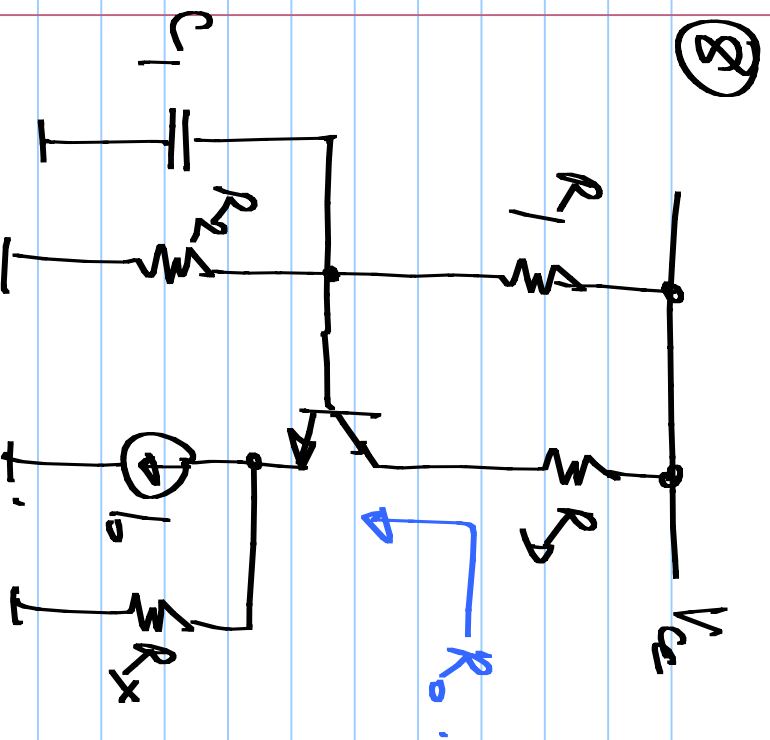[Repeat this for $R_x = \infty$ and finite R_x]



With finite R_D and V_A , calculate the output resistance R_o . This circuit could represent a common-base amplifier or a voltage controlled current source as seen from the output. Compare it to the analogous

MOS transistor circuit.