

# Modified nodal analysis

## EE2015: Electrical Circuits and Networks

Nagendra Krishnapura  
<https://www.ee.iitm.ac.in/~nagendra/>

Department of Electrical Engineering  
Indian Institute of Technology, Madras  
Chennai, 600036, India

18 August 2017

Generalized nodal analysis with extra variables for systematically writing down nodal equations

- Accommodates all components
  - $R, L, C, M$
  - Independent current and voltage sources
  - Controlled sources (VCVS, VCCS, CCVS, CCCS)
- More variables than in nodal analysis
  - Node voltages
  - Currents through voltage sources (independent and controlled)
  - Currents through inductors
  - Controlling currents of current controlled sources

$$[\mathbf{G}] \mathbf{v} = \mathbf{I}_s$$

- $[\mathbf{G}]$ : Conductance matrix
  - Not all entries necessarily conductances
- $\mathbf{v}$ : Variable vector
  - Node voltages
  - Currents through voltage sources
  - Currents through inductors
  - Controlling currents of current controlled sources
- $\mathbf{I}_s$ : Vector of independent sources
  - Current and voltage sources

Every circuit element contributes to  $[\mathbf{G}]$  or  $\mathbf{I}_s$ ; Independent voltage source contributes to both.


$$\mathbf{v} = \begin{bmatrix} v_1 \\ \vdots \\ v_N \\ i_{V,1} \\ \vdots \\ i_{V,P} \\ i_{C,1} \\ \vdots \\ i_{C,Q} \end{bmatrix} \begin{array}{l} \text{Node voltages} \\ \\ \text{Voltage source currents} \\ \\ \text{Controlling currents} \end{array}$$

- First label the elements and form the variable vector

$$\begin{array}{l} \text{node 1} \\ \vdots \\ \text{node } N \\ \text{Voltage source 1} \\ \vdots \\ \text{Voltage source } P \\ \text{Contr. current 1} \\ \vdots \\ \text{Contr. current } Q \end{array} \left[ \begin{array}{cccc} v_1 & \cdots & v_N & \\ & & & i_{V,1} & \cdots & i_{V,P} & i_{C,1} & \cdots & i_{C,Q} \\ & & & & & & & & & \\ & & & & & & & & & \\ & & & & & & & & & \\ & & & & & & & & & \\ & & & & & & & & & \\ & & & & & & & & & \\ & & & & & & & & & \end{array} \right]$$


- First label the elements and form the variable vector

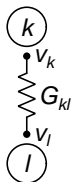- Each element contributes to certain rows and columns of  $[\mathbf{G}]$  or certain rows of  $\mathbf{v}$
- Element stamp indicates the rows and columns and corresponding contributions
- For each element, add the stamp to the appropriate entry of  $[\mathbf{G}]$  or  $\mathbf{v}$



$$\begin{array}{l}
 \text{node } k \\
 \text{node } l
 \end{array}
 \begin{bmatrix}
 v_k & v_l \\
 G_{kl} & -G_{kl} \\
 -G_{kl} & G_{kl}
 \end{bmatrix}
 \equiv
 \begin{array}{l}
 \text{node } k \\
 \text{node } l
 \end{array}
 \begin{bmatrix}
 & v_k & & v_l & \\
 & \vdots & & \vdots & \\
 \cdots & G_{kl} & \cdots & -G_{kl} & \cdots \\
 & \vdots & & \vdots & \\
 \cdots & -G_{kl} & \cdots & G_{kl} & \cdots \\
 & \vdots & & \vdots &
 \end{bmatrix}$$


- Contributes to  $[\mathbf{G}]$

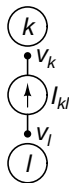

$$\begin{array}{l}
 \text{node } k \\
 \text{node } l
 \end{array}
 \begin{bmatrix}
 I_{kl} \\
 -I_{kl}
 \end{bmatrix}
 \equiv
 \begin{array}{l}
 \text{node } k \\
 \text{node } l
 \end{array}
 \begin{bmatrix}
 \vdots \\
 I_{kl} \\
 \vdots \\
 -I_{kl} \\
 \vdots
 \end{bmatrix}$$

- Contributes to  $\mathbf{I}_s$




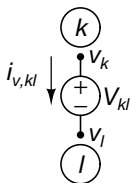

$$[\mathbf{G}] : \begin{array}{l} \text{node } k \\ \text{node } l \\ i_{v,kl} \end{array} \begin{bmatrix} v_k & v_l & i_{v,kl} \\ 0 & 0 & +1 \\ 0 & 0 & -1 \\ +1 & -1 & 0 \end{bmatrix}$$


$$\mathbf{I}_s : \begin{array}{l} \text{node } k \\ \text{node } l \\ i_{v,kl} \end{array} \begin{bmatrix} 0 \\ 0 \\ V_s \end{bmatrix}$$

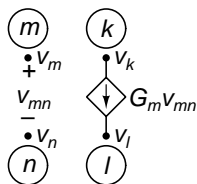- Contributes to  $[\mathbf{G}]$  and  $\mathbf{I}_s$




$$[\mathbf{G}] : \begin{array}{l} \text{node } k \\ \text{node } l \end{array} \begin{bmatrix} v_m & v_n \\ G_m & -G_m \\ -G_m & G_m \end{bmatrix}$$

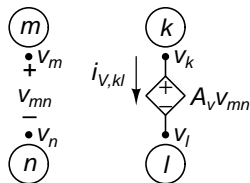- Contributes to  $[\mathbf{G}]$
- Note the asymmetry (rows  $k, l$ , columns  $m, n$ )



$$[\mathbf{G}] : \begin{array}{l} \text{node } k \\ \text{node } l \\ i_{v,kl} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_n & i_{v,kl} \\ 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & -1 \\ +1 & -1 & -A & +A & 0 \end{bmatrix}$$


- Contributes to  $[\mathbf{G}]$

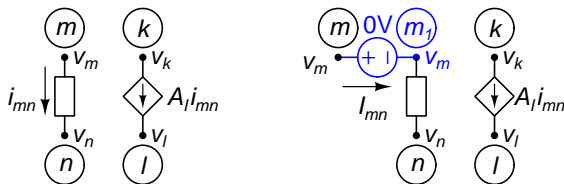

$$[\mathbf{G}] : \begin{array}{c} \text{node } k \\ \text{node } l \\ \text{node } m \\ \text{node } m_1 \\ i_{mn} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_{m_1} & i_{mn} \\ 0 & 0 & 0 & 0 & +A_l \\ 0 & 0 & 0 & 0 & -A_l \\ 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & +1 & -1 & 0 \end{bmatrix}$$



- Add a 0 V source in series with the current-sensing branch
- Extra node  $m_1$
- Row  $i_{mn}$  corresponds to the 0 V voltage source equation
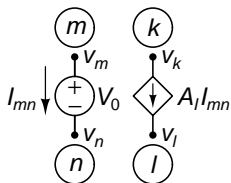
# MNA stamp: CCCS (current through a voltage source)




$$[\mathbf{G}] : \begin{array}{l} \text{node } k \\ \text{node } l \\ \text{node } m \\ \text{node } n \\ i_{mn} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_n & i_{mn} \\ 0 & 0 & 0 & 0 & +A_l \\ 0 & 0 & 0 & 0 & -A_l \\ 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & +1 & -1 & 0 \end{bmatrix}$$

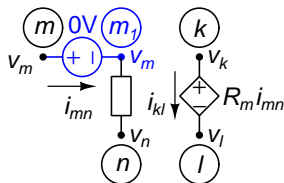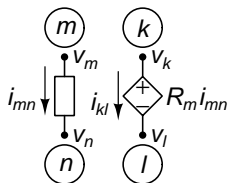- No need for extra voltage source
- Rows for  $i_{mn}$  and nodes  $m, n$ : 0 V voltage source stamp



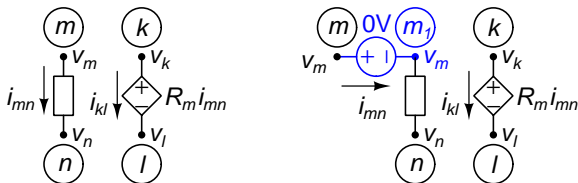
$$[\mathbf{G}] : \begin{array}{l} \text{node } k \\ \text{node } l \\ \text{node } m \\ \text{node } m_1 \\ i_{mn} \\ i_{kl} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_{m1} & i_{mn} & i_{kl} \\ 0 & 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & +1 & 0 \\ 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & +1 & -1 & 0 & 0 \\ +1 & -1 & 0 & 0 & -R_m & 0 \end{bmatrix}$$



$$[G] : \begin{array}{l} \text{node } k \\ \text{node } l \\ \text{node } m \\ \text{node } m_1 \\ i_{mn} \\ i_{kl} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_{m_1} & i_{mn} & i_{kl} \\ 0 & 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & +1 & 0 \\ 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & +1 & -1 & 0 & 0 \\ +1 & -1 & 0 & 0 & -R_m & 0 \end{bmatrix}$$

- Add a 0 V source in series with the current-sensing branch
- Extra node  $m_1$
- Row  $i_{mn}$  corresponds to the 0 V voltage source equation
- Row  $i_{kl}$  corresponds to the CCVS equation

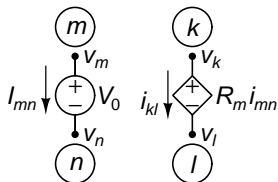
# MNA stamp: CCVS (current through a voltage source)



$$\mathbf{[G]} : \begin{array}{l} \text{node } k \\ \text{node } l \\ \text{node } m \\ \text{node } n \\ i_{mn} \\ i_{kl} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_{m1} & i_{mn} & i_{kl} \\ 0 & 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & 0 & +1 & 0 \\ 0 & 0 & 0 & 0 & -1 & 0 \\ 0 & 0 & +1 & -1 & 0 & 0 \\ +1 & -1 & 0 & 0 & -R_m & 0 \end{bmatrix}$$

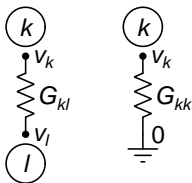
- No need for extra voltage source
- Rows for  $i_{mn}$  and nodes  $m, n$ : 0 V voltage source stamp





$$\begin{array}{l} \text{node } k \\ \text{node } l \end{array} \begin{bmatrix} v_k & v_l \\ G_{kl} & -G_{kl} \\ -G_{kl} & G_{kl} \end{bmatrix} \equiv \begin{array}{l} \text{node } k \\ \text{node } k \end{array} \begin{bmatrix} v_k \\ G_{kk} \end{bmatrix}$$

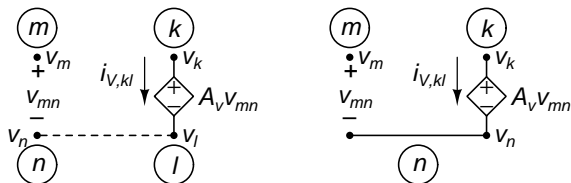- If one of the nodes  $k$ ,  $l$ ,  $m$ ,  $n$  is the reference node, the corresponding row/column will not be present




$$[\mathbf{G}] : \begin{array}{l} \text{node } k \\ \text{node } l \\ i_{V,kl} \end{array} \begin{bmatrix} v_k & v_l & v_m & v_n & i_{V,kl} \\ 0 & 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & 0 & -1 \\ +1 & -1 & -A & +A & 0 \end{bmatrix}$$

$$\begin{array}{l} \text{node } k \\ \text{node } n \\ i_{V,kl} \end{array} \begin{bmatrix} v_k & v_m & v_n & i_{V,kl} \\ 0 & 0 & 0 & +1 \\ 0 & 0 & 0 & -1 \\ +1 & -A & +A & -1 & 0 \end{bmatrix}$$

- If two or more nodes are the same, the corresponding terms add up

- Add 0 V voltage sources for controlling-current branches if necessary
- Assign variables for voltage source currents
- Form the variable vector  $\mathbf{v}$
- Place each element's stamp appropriately in  $[\mathbf{G}]$  and  $\mathbf{I}_s$
- For each element of  $[\mathbf{G}]$  and  $\mathbf{I}_s$ , add all the stamp contributions
- Solve  $\mathbf{v} = [\mathbf{G}]^{-1} \mathbf{I}_s$


## MNA example 1: Variable vector

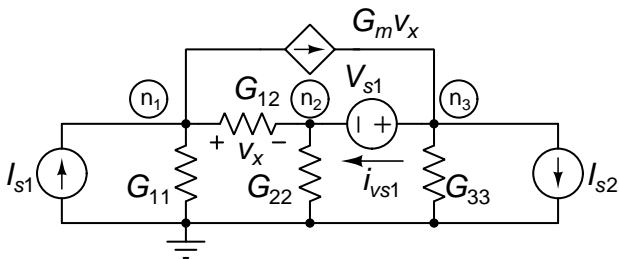

$$[\mathbf{G}] \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_{vs1} \end{bmatrix} = \mathbf{I}_s$$


- 4 node circuit; 3 node voltages
- Variable vector:  $[v_1 \ v_2 \ v_3 \ i_{vs1}]^T$
- One extra variable:  $i_{vs1}$
- $[\mathbf{G}]$ :  $4 \times 4$  matrix;  $\mathbf{I}_s$ : 4 element vector

# MNA example 1: Elements

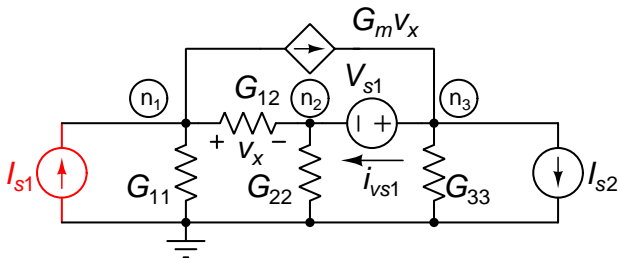


$$\mathbf{I}_s : \begin{bmatrix} I_{s1} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

# MNA example 1: Elements

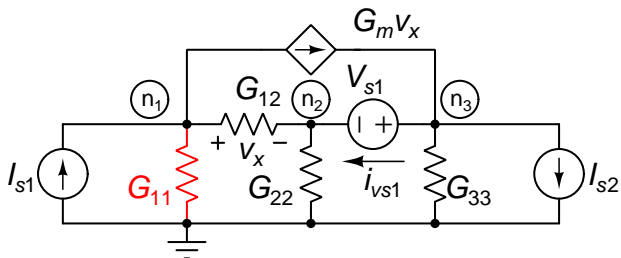


$$[\mathbf{G}] : \begin{bmatrix} G_{11} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

# MNA example 1: Elements

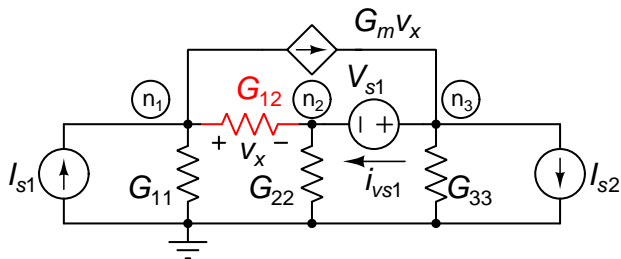

$$[\mathbf{G}] : \begin{bmatrix} G_{12} & -G_{12} & 0 & 0 \\ -G_{12} & G_{12} & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$


# MNA example 1: Elements

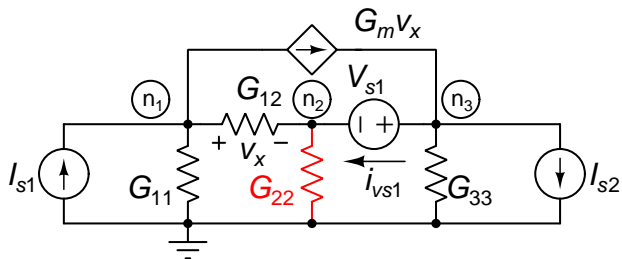

$$[\mathbf{G}] : \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & G_{22} & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$




# MNA example 1: Elements

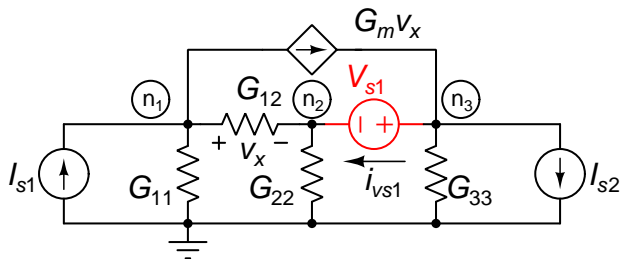


$$[\mathbf{G}] : \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & +1 \\ 0 & -1 & +1 & 0 \end{bmatrix} \mathbf{I}_s : \begin{bmatrix} 0 \\ 0 \\ 0 \\ V_{s1} \end{bmatrix}$$

# MNA example 1: Elements

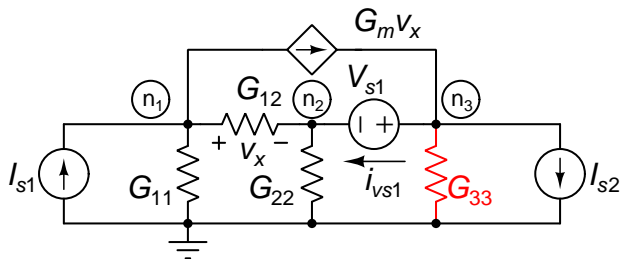


$$[\mathbf{G}] : \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & G_{33} & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

# MNA example 1: Elements

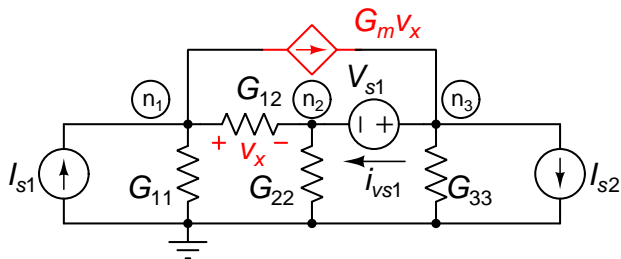


$$[\mathbf{G}] : \begin{bmatrix} G_m & -G_m & 0 & 0 \\ 0 & 0 & 0 & 0 \\ -G_m & G_m & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

# MNA example 1: Elements

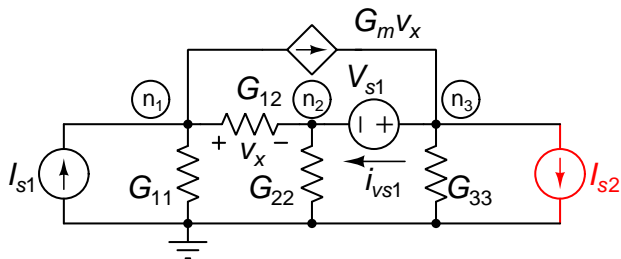


$$\mathbf{I}_s : \begin{bmatrix} 0 \\ 0 \\ -I_{s2} \\ 0 \end{bmatrix}$$
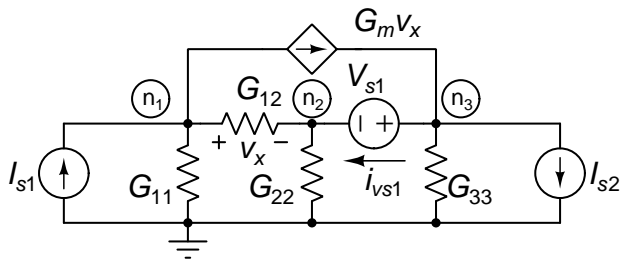
# MNA example 1: Complete set of equations




$$\begin{bmatrix} G_{11} + G_{12} + G_m & -G_{12} - G_m & 0 & 0 \\ -G_{12} & G_{12} + G_{22} & 0 & -1 \\ -G_m & G_m & G_{33} & +1 \\ 0 & -1 & +1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_{vs1} \end{bmatrix} = \begin{bmatrix} I_{s1} \\ 0 \\ -I_{s2} \\ V_{s1} \end{bmatrix}$$

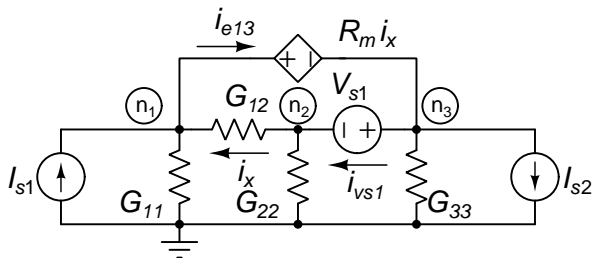- Solve to get  $[v_1 \ v_2 \ v_3 \ i_{vs1}]^T$
- Find all branch  $v$ ,  $i$  from KCL, KVL, and element relationships



- 0 V voltage source has to be added to the controlling branch


## MNA example 2: Variable vector

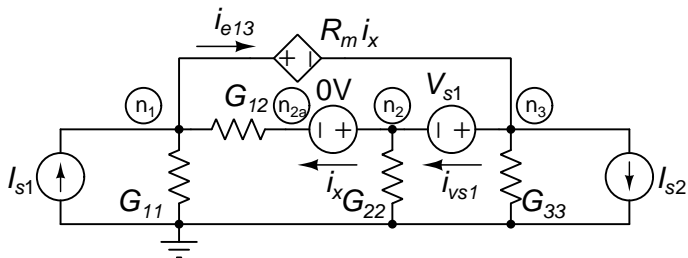

$$[\mathbf{G}] \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_{vs1} \\ i_{e13} \\ i_x \end{bmatrix} = \mathbf{I}_s$$

- 4 node circuit; 3 node voltages
- Variable vector:  $[v_1 \ v_2 \ v_3 \ i_{vs1} \ i_{e13} \ i_x]^T$
- One extra variable:  $i_{vs1}$
- $[\mathbf{G}]$ :  $4 \times 4$  matrix;  $\mathbf{I}_s$ : 4 element vector


## MNA example 2: Variable vector

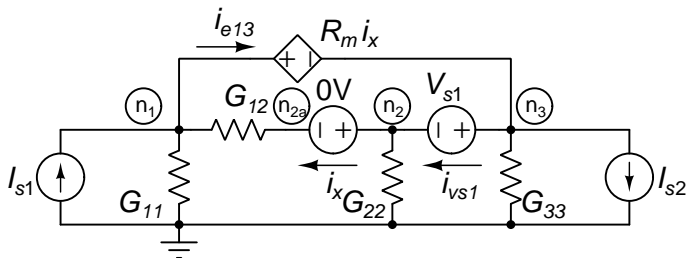

$$[\mathbf{G}] \begin{bmatrix} V_1 \\ V_2 \\ V_{2a} \\ V_3 \\ i_{vs1} \\ i_{e13} \\ i_x \end{bmatrix} = \mathbf{I}_s$$

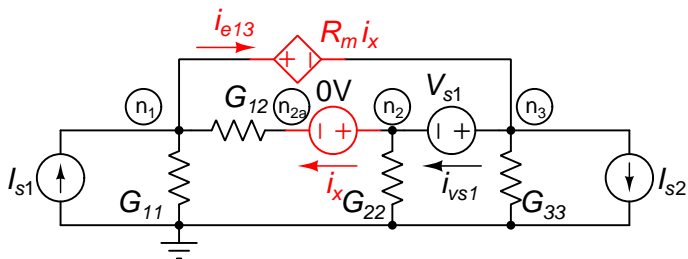- Originally a 4 node circuit; 3 node voltages; 4 extra variables






$$\begin{bmatrix}
 0 & 0 & 0 & 0 & 0 & +1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & +1 \\
 0 & 0 & 0 & 0 & 0 & 0 & -1 \\
 0 & 0 & 0 & 0 & 0 & -1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 +1 & 0 & 0 & -1 & 0 & 0 & -R_m \\
 0 & +1 & -1 & 0 & 0 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 v_1 \\
 v_2 \\
 v_3 \\
 v_{2a} \\
 v_3 \\
 i_{vs1} \\
 i_{e13} \\
 i_x
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{bmatrix}$$

- $[G]$  due to the CCVS


## MNA example 2: Remaining elements

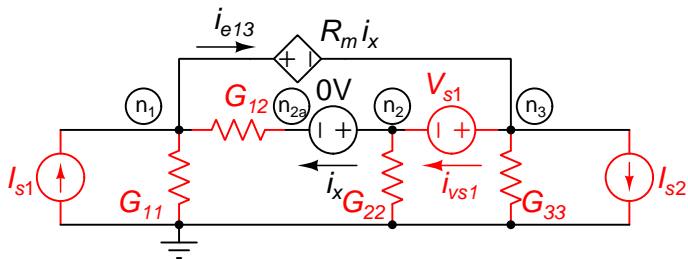

$$\begin{bmatrix}
 G_{11} + G_{12} & 0 & -G_{12} & 0 & 0 & 0 & 0 \\
 0 & G_{22} & 0 & 0 & -1 & 0 & 0 \\
 -G_{12} & 0 & G_{12} & 0 & -1 & 0 & 0 \\
 0 & 0 & 0 & 0 & +1 & 0 & 0 \\
 0 & -1 & 0 & +1 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 v_1 \\
 v_2 \\
 v_{2a} \\
 v_3 \\
 i_{vs1} \\
 i_{e13} \\
 i_x
 \end{bmatrix}
 =
 \begin{bmatrix}
 I_{s1} \\
 0 \\
 0 \\
 -I_{s2} \\
 V_{s1} \\
 0 \\
 0
 \end{bmatrix}$$

- Same as the earlier example, without  $G_m$

# MNA example 2: Complete equation setup

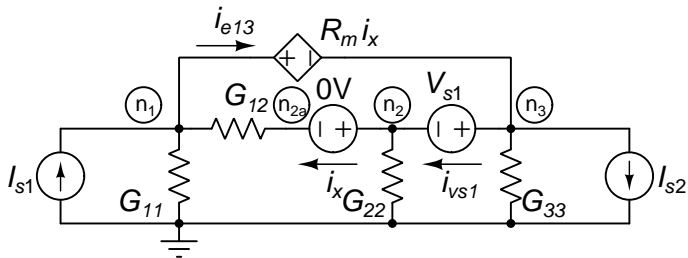

$$\begin{bmatrix}
 G_{11} + G_{12} & 0 & -G_{12} & 0 & 0 & +1 & 0 \\
 0 & G_{22} & 0 & 0 & -1 & 0 & +1 \\
 -G_{12} & 0 & G_{12} & 0 & 0 & 0 & -1 \\
 0 & 0 & 0 & 0 & +1 & +1 & 0 \\
 0 & -1 & 0 & +1 & 0 & 0 & 0 \\
 +1 & 0 & 0 & -1 & 0 & 0 & -R_m \\
 0 & +1 & -1 & 0 & 0 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 v_1 \\
 v_2 \\
 v_{2a} \\
 v_3 \\
 i_{vs1} \\
 i_{e13} \\
 i_x
 \end{bmatrix}
 =
 \begin{bmatrix}
 I_{s1} \\
 0 \\
 0 \\
 -I_{s2} \\
 V_{s1} \\
 0 \\
 0
 \end{bmatrix}$$