
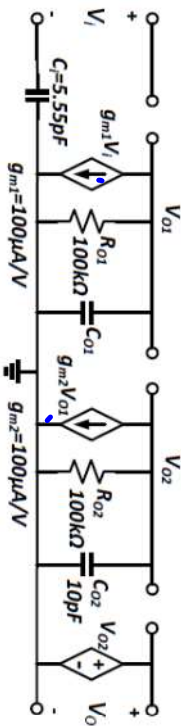


**Question-1**

(10 marks)

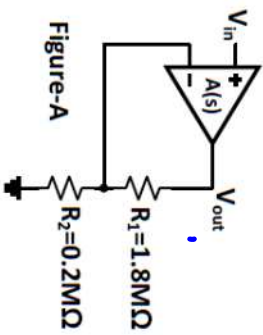


Closed loop amplifier shown in Figure-A needs to be designed for stable operation. Derive the loop gain transfer function and specify the poles and zeroes.

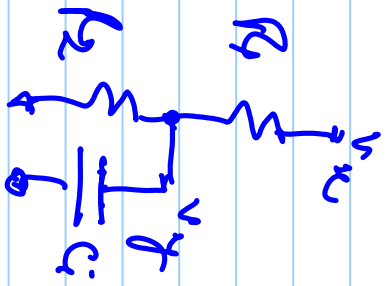- a) Find the loop gain transfer function (2 marks)
- b) Calculate the value of capacitor  $C_{o1}$  to achieve the phase margin of 60 degrees (4 marks)
- c) Draw the bode magnitude and phase plot of the loop gain transfer function. Clearly mention values of gain, phase, location of poles, zeroes and unity gain frequency. (4 marks)

$$\omega_{p1} = \frac{1}{R_{o1}C_{o1}}, \quad \omega_{p2} = \frac{1}{R_{o2}C_{o2}}, \quad g_{m1}, R_{o1}, g_{m2}, R_{o2}$$

$$\beta = \frac{R_2}{R_1 + R_2} \Leftrightarrow R_1 \parallel R_2 \rightarrow Y$$



$$\frac{V_y(s)}{V_u(s)} = \beta = \frac{R_2}{R_1 + R_2} \times \frac{1}{(1 + sR_2/C_i)} = \frac{R_2}{R_1 + R_2} \frac{1}{1 + \frac{R_1 R_2}{R_1 + R_2} s}$$

$$\frac{V_y(s)}{V_u(s)} = \frac{R_2 \rightarrow Z_2}{R_1 + R_2 \rightarrow Z_2} = \frac{Z_2}{R_1 + Z_2} = \frac{1}{R_1 Z_2 + 1}$$

$$= \frac{1}{R_2} = \frac{R_2 \left( \frac{1}{R_2} + sC_i \right) + 1}{R_1 + R_2 C_i s + R_2}$$

$$\beta A(s) = \frac{R_2}{R_1 + R_2} \times \frac{g_{m1} R_{o1} g_{m2} R_{o2}}{(1 + R_{o1} C_{o1} s) (1 + R_{o2} C_{o2} s) \left(1 + \frac{R_1 R_2}{R_1 + R_2} C_3\right)}$$

$$\omega_{p1} = \frac{1}{R_{o1} C_{o1}} \quad \omega_{p2} = \frac{1}{R_{o2} C_{o2}} = \frac{1}{100k \times 10 \times 10^{-12}}$$

$$= 10^6 \text{ rad/sec}$$

$$R_1 || R_2 = \frac{1.8k \times 0.2}{2} = 180k \Omega$$

$$\omega_{p3} = \frac{1}{(R_1 || R_2) C_3} = \frac{1}{180k \times 5.5p} = 10^6 \text{ rad/sec}$$

$$w_{ng} B = \beta_0 A_0 \times w P_1 = \frac{w P_{2,3}}{3.7}$$

$$\beta_0 = \frac{R_2}{R_1 + R_2} = \frac{0.2}{1.8 + 0.2} = \frac{1}{10}$$

$$A_0 \leq 100 \times 10 = 10^4$$

$$\beta_0 A_0 = \frac{10^4}{10} = 10^3$$

$$\frac{1}{w P_1} = \frac{\beta_0 A_0 \times 3.7}{w P_{2,3}} = \frac{10^3 \times 3.7}{10^3} = 3.7 \times 10^{-3}$$

$$R_{01} C_{01} = 3.7 \times 10^{-3} \Rightarrow C_{01} = 3.7 \times 10^{-3} / 100k = 37nF$$

$$\omega f_{2,3} = \omega f_3 \quad \therefore \quad \omega P_{2,3} = 1 \text{ m rad/sec}$$

$$P_{M} = 90 - \tan^{-1} \frac{\omega \omega_{g_2}}{\omega f_2} - \tan^{-1} \frac{\omega \omega_{g_3}}{\omega f_3}$$


$$f_{\omega}^0 = 90 - 2 \tan^{-1} \frac{\omega \omega_{g_2}}{\omega P_{2,3}}$$

$$\tan^{-1} \frac{\omega \omega_{g_2}}{\omega P_{2,3}} = 45^\circ$$

$$\frac{\omega \omega_{g_2}}{\omega P_{2,3}} = \tan 45^\circ \quad \omega P_{2,3} = 3.7 \omega \omega_{g_2}$$

Question-2

(5 marks)

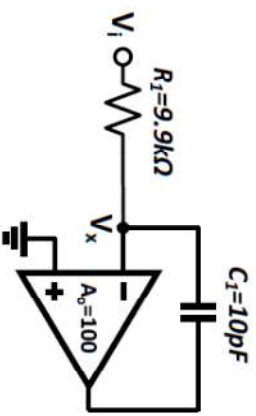


For the circuit shown above:

- a) Find the the transfer function  $V_X(s)/V_I(s)$  in terms of  $R_1$  and  $C_1$ . (2 marks)
- b) Find the expression for unit step response  $V_X(t)$  and draw the waveform (2 marks)
- c) Find the value of RC time constant (1 mark)



C looking at  $V_x$

Miller effect -  $C_1$

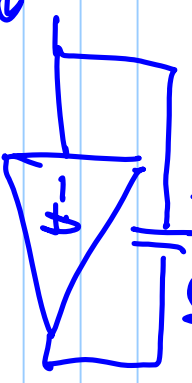

$$C_{in} = (1+A)C_1$$

$$A = 100$$


time constant


$$\approx R_1 (1+A)C_1$$

$$= 9.9k \times 101 \times 10pF = 10\mu s$$

$$(a) \frac{V_x(s)}{V_i(s)} = \frac{1}{1 + 10^4 RC_1 s}$$
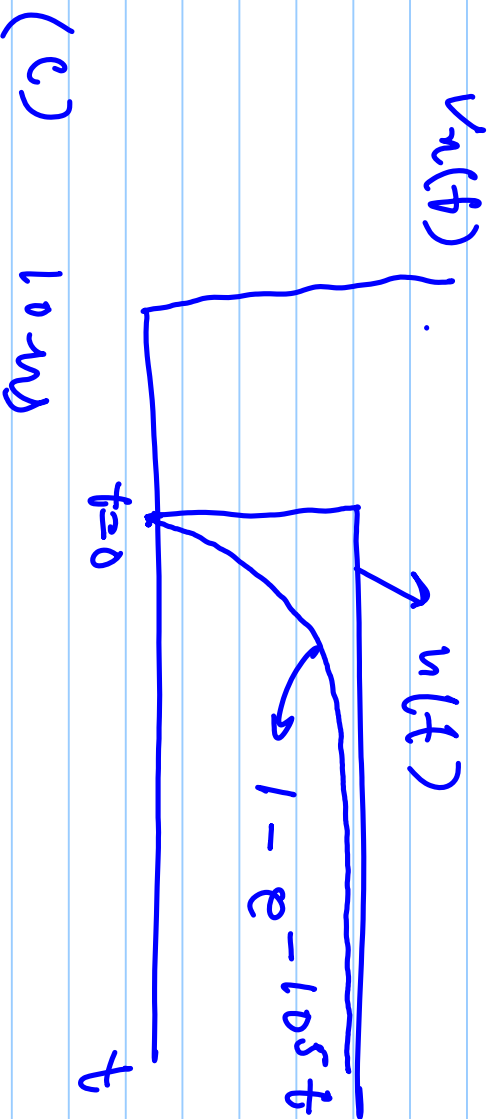
$$(b) \quad V_x(t) = 1 - e^{-t/\tau} = 1 - e^{-t/10^4 R C_1} = 1 - e^{-10^5 t}$$



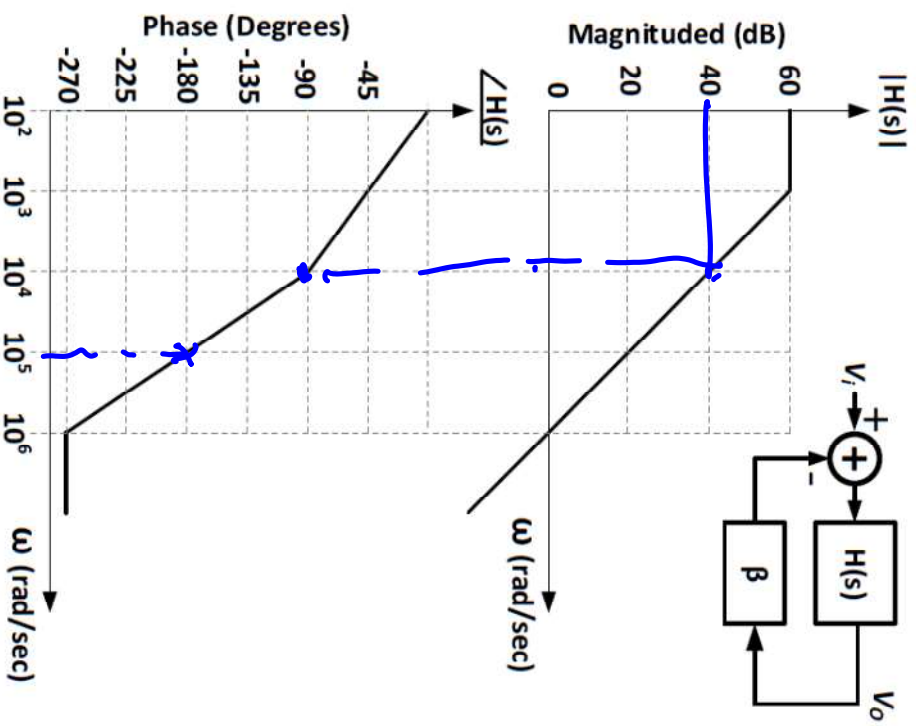

### Question-3

(5 marks)

A system with transfer function,  $H(s)$  of the given bode magnitude and phase response below, is supposed to be operated in closed loop with feedback factor,  $\beta$  as shown in figure below.

- Find the transfer function  $H(s)$  (2 mark)
- Determine if the system is stable or unstable for  $\beta=1$  (1 mark)
- Find the value of  $\beta$  to achieve phase margin of 90 degrees (2 marks)

$$\omega_{p1} = 10^3 \text{ rad/sec. (L.H.P)}$$

$$\omega_{z1} = 10^5 \text{ rad/sec (R.H.P)}$$

$$\omega_{p2} = 10^5 \text{ rad/sec (L.H.P)}$$



$$(a) \text{HRS} = \frac{10^3 (1 - s/10^2)}{(1 + s/10^3) (1 + s/10^2)} \quad \frac{10^3 (1 - s/10^5)}{(1 + s/10^3) (1 + s/10^5)}$$

(b) at Phase =  $-180^\circ$  gain  $> 0$  dB so system is unstable

$$(c) \beta = \frac{1}{100}$$