
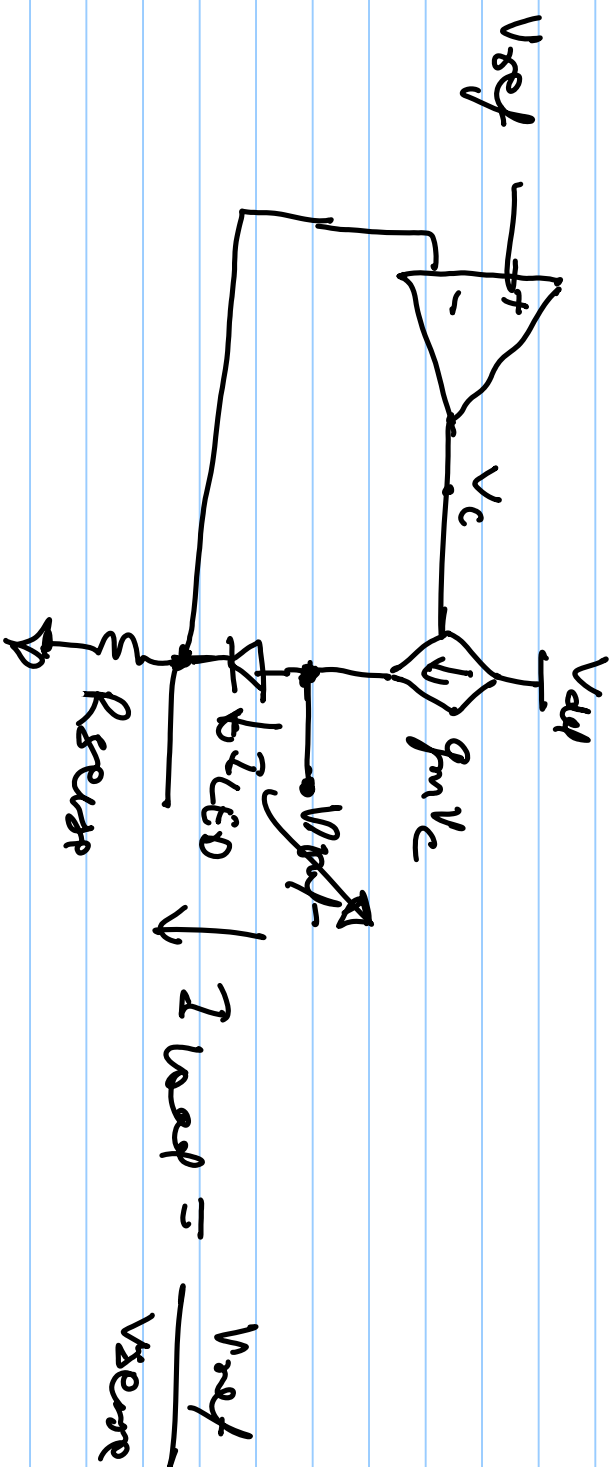


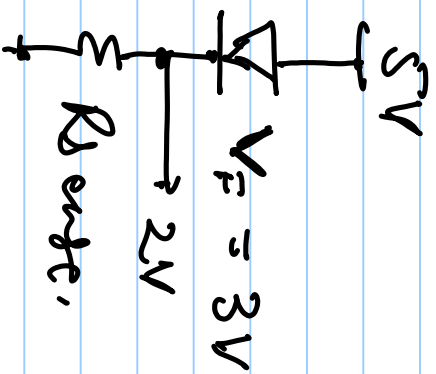- # Linear Regulators are also known as Low drop-out (LDO) Regulators when operated at low $(V_{in} - V_{out})$
- # Linear Regulators can also be used as current Regulators.






$$I_{LED} = \frac{2}{R_{sense}}$$

I_{LED} does not remain constant if V_{avg} is varying. $R_{sense} = 20 \Omega$


Switching Regulator

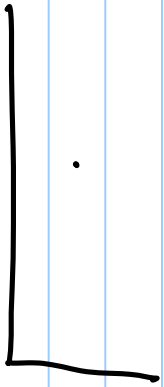


10V — 1A

η = 10% with linear Reg


$V_{req} = 10V$

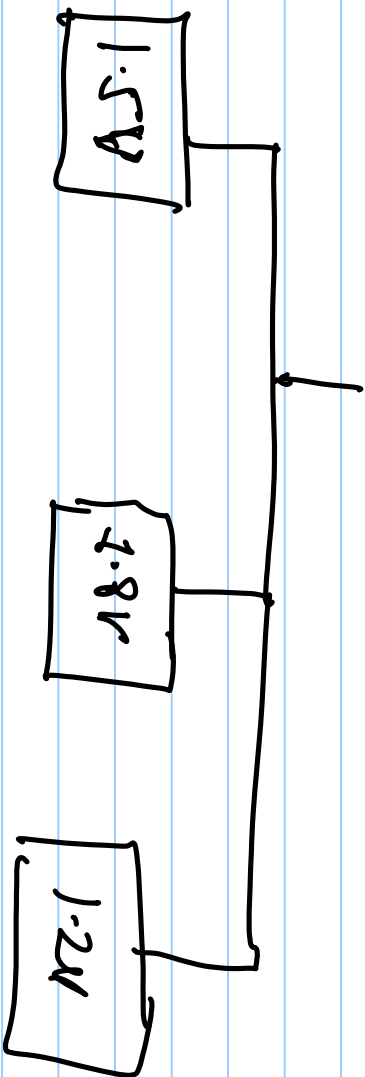

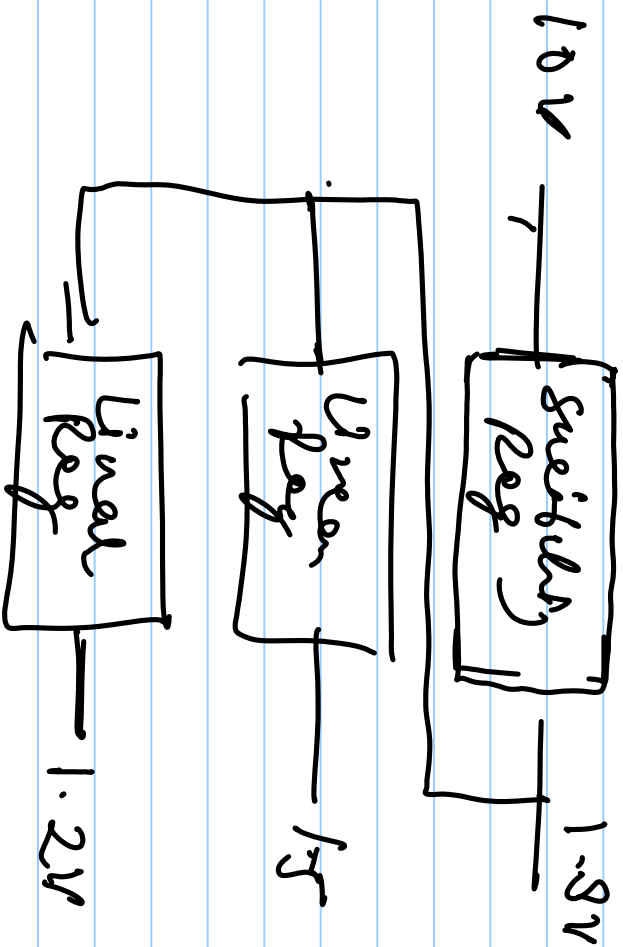


Switching Regulator can be of two types.

Switching Regulators

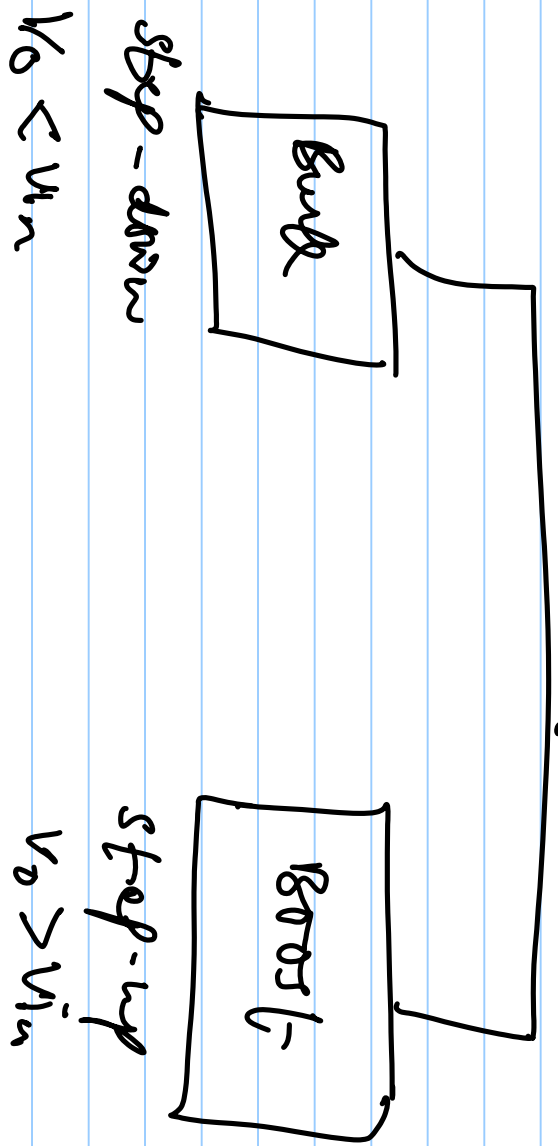

works on PNM principle.

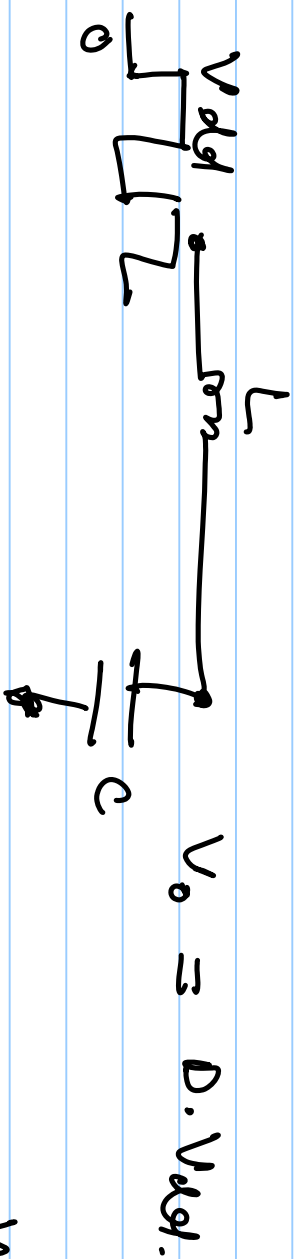


$$D \cdot V_{dg} + V_L = V_o$$

$$V_L = L \frac{di_L}{dt}$$

$$I_L = \frac{1}{L} \int_0^T V_L(t) dt + I_L(0)$$

In steady state

$$D \cdot V_{dg} = V_o$$

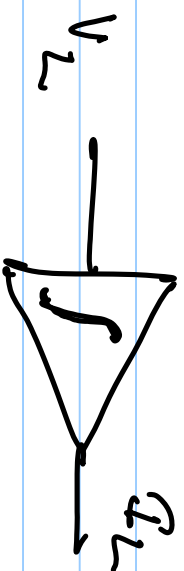



Practically inductors are not lossless



In steady state
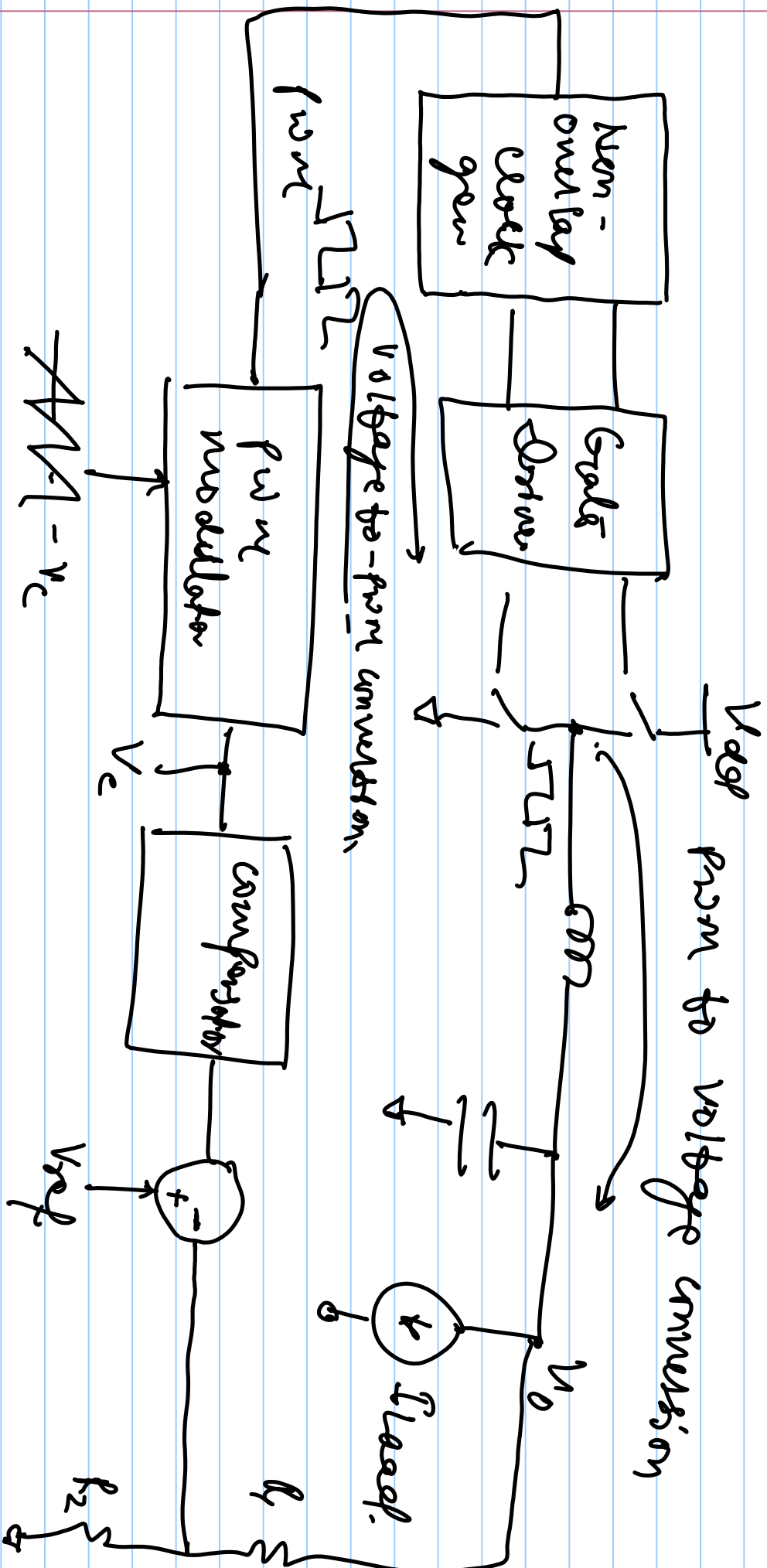
$$D \cdot V_{dc} = V_0 + I_{load} \cdot R_{DC}$$




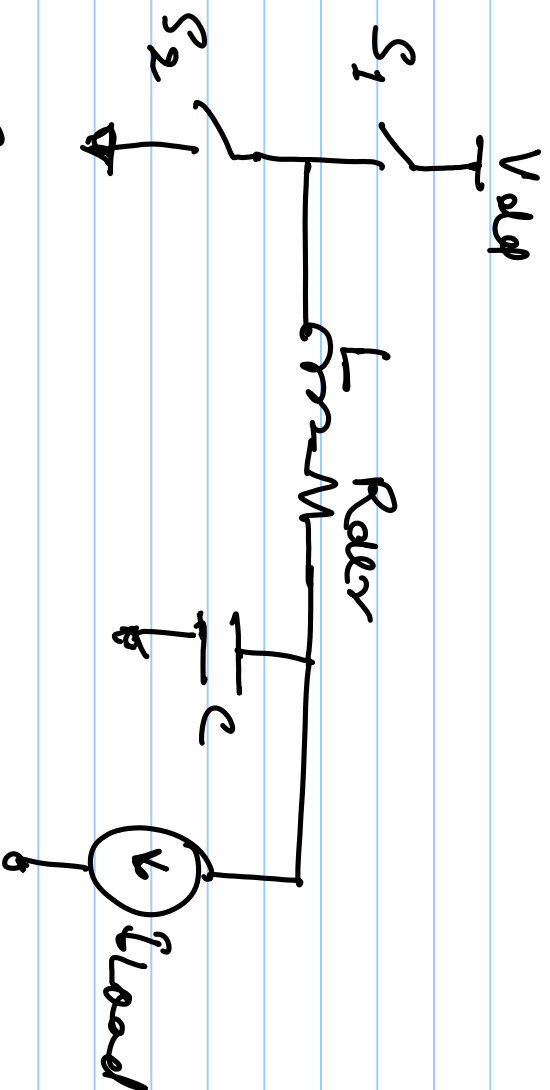

When S_1 and S_2 are ON they have some finite resistance \rightarrow order of $10s$ of $m\Omega$

ON resistance of S_1 is R_{on1}

and ON resistance of S_2 is R_{on2}

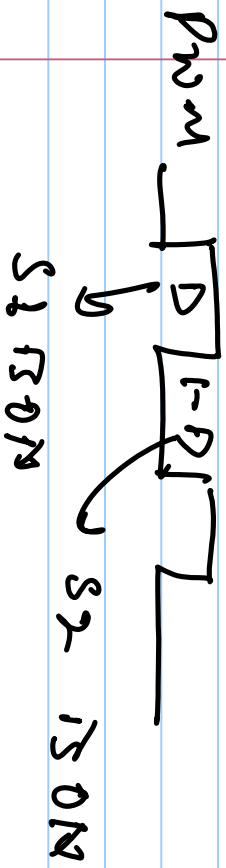

Total loss is $R_{total}^2 \times R_{total}$

$$R_{total} = D \cdot R_{m1} + (1-D) R_{m2} + R_{dcr}$$

$$\text{Total loss} = R_{total}^2 \times (D R_{m1} + (1-D) R_{m2} + R_{dcr})$$

$$R_{01} = R_{02} = 50 \text{ m}\Omega$$

$$R_{\text{load}} = 200 \text{ m}\Omega$$

$$I_{\text{load}} = 100 \text{ mA}$$

$$\begin{aligned} \text{Total loss} &= (50 \text{ m}\Omega + 200 \text{ m}\Omega) \times (100 \text{ mA})^2 \\ &= 2.5 \text{ mW} \end{aligned}$$

$$V_{\text{out}} = 4 \text{ V}, \quad V_{\text{in}} = 10 \text{ V}$$

$$P_{\text{out}} = 4 \text{ V} \times 100 \text{ mA} = 400 \text{ mW}$$

$$P_{in} = P_{out} + P_{loss}$$

$$= 402.5 \text{ mW}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{400 \text{ mW}}{402.5 \text{ mW}} =$$

