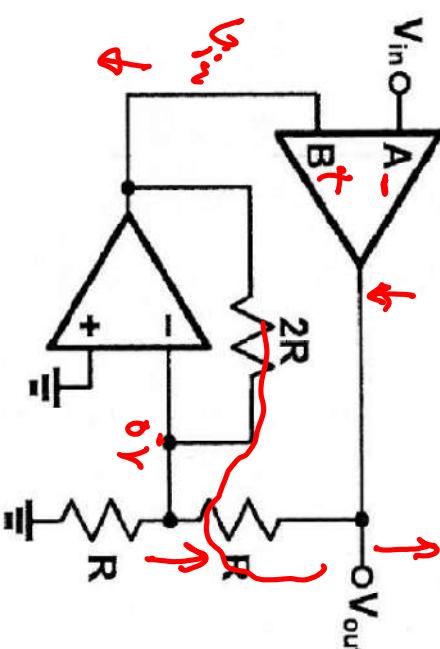


- 1) The circuit shown in the figure below operates in negative feedback configuration. Assume both opamps are ideal. Determine the signs of the opamp for proper negative feedback operation. State your reasoning carefully. (5 Marks)




- 2) Determine the ac gain V_{out}/V_{in} of the circuit of problem 1 above. (5 Marks)

$$\frac{V_o}{V_{in}} = ?$$

$$V_{in} = -\frac{2R}{R} \times V_{out} \Rightarrow \frac{V_o}{V_{in}} = -\frac{1}{2}$$

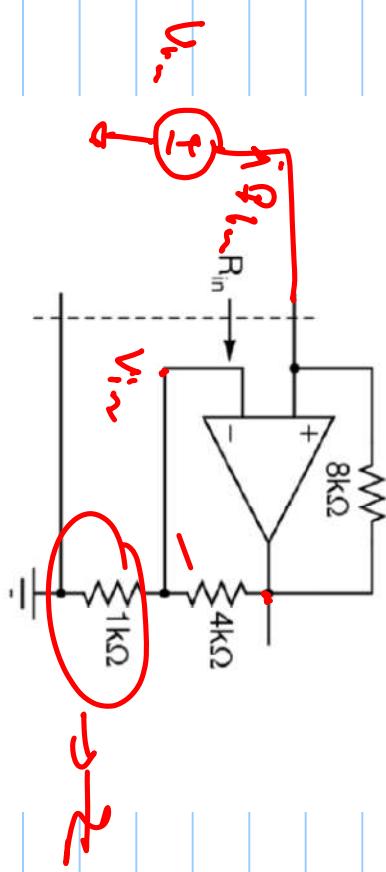3) Determine the input resistance of the circuit shown below. (5 Marks)



$$\frac{V_{in}}{R_{in}} = R_{in}$$


$$R_{in} = \frac{V_{in} - 5V_{in}}{8k} = -\frac{4V_{in}}{8k} = -\frac{1}{2k}V_{in}$$

$$\beta = \frac{1k}{1k + 4k} = \frac{1}{5}$$

$$V_{out} = \beta V_{in} \Rightarrow V_{in} = -2k \Omega = R_{in}$$


$$V_{out} = 5V_{in}$$

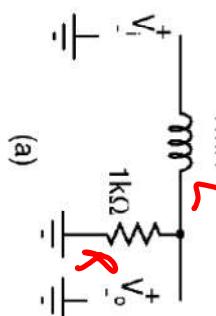- 4) For the circuit shown below, determine C such that the circuits in (a) and (b) have identical transfer functions (magnitude). (5 Marks)



(a)
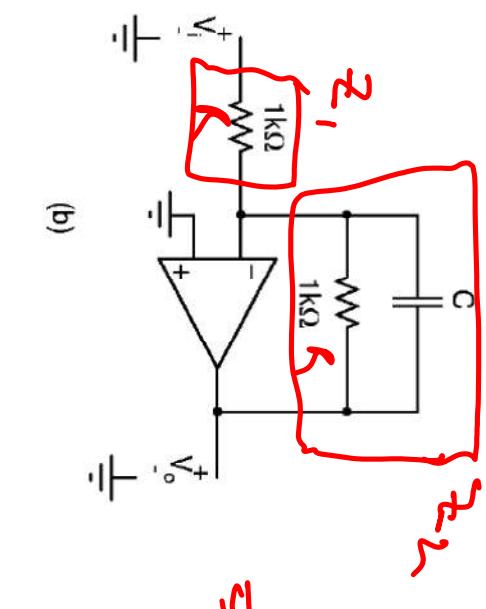
$$\frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{1}{1 + \frac{L}{R}s} \quad \text{--- (1)}$$



(b)

$$\begin{aligned} \frac{V_o}{V_i} &= -\frac{Z_2}{Z_1} = \frac{Y_1}{Y_2} = \frac{1/R}{1/R + sC} \\ &= \frac{1}{1 + RCs} \end{aligned}$$

Comparing ① & ②

$$\frac{L}{R} = R_C \rightarrow C = \frac{L}{R^2} = \frac{1 \text{ m}}{(1 \text{ k})^2} = \frac{10^{-2}}{10^6} = 1 \text{ nF}$$

2nd order system

Phase margin

$$H_{La}(s) = \frac{13 A_0}{((1 + \delta/\omega_{p_1})(1 + \delta/\omega_{p_2}))}$$
$$\rho_m = 180^\circ - \tan^{-1}\left(\frac{\omega_m \delta}{\omega_{p_1}}\right) - \tan^{-1}\frac{\omega_m \delta}{\omega_{p_2}}$$

if $\omega_{p_1} = \omega_m \delta$

$$\frac{1}{10}, \quad \omega_{p_2} = \omega_m \delta$$

$$\rho_m = 180^\circ - 290^\circ - 45^\circ \approx 15^\circ \text{ marginally stable}$$

For a stable system, $\rho_m > \delta_0$

$$\delta_0^\circ = 180 - \theta_0 - \tan^{-1} \frac{\omega_{ngf}}{\omega_{f2}}$$

$$\tan^{-1} \frac{\omega_{ngf}}{\omega_{f2}} = 30^\circ \Rightarrow \frac{\omega_{ngf}}{\omega_{f2}} = \tan 30^\circ = 0.57$$

$$\Leftrightarrow \omega_{f2} = \frac{\omega_{ngf}}{0.57} \approx 2\omega_{ngf}$$

$$de spin = \beta A_0$$

$$\omega_{ngf} < \omega_{f1} \times \beta A_0$$

