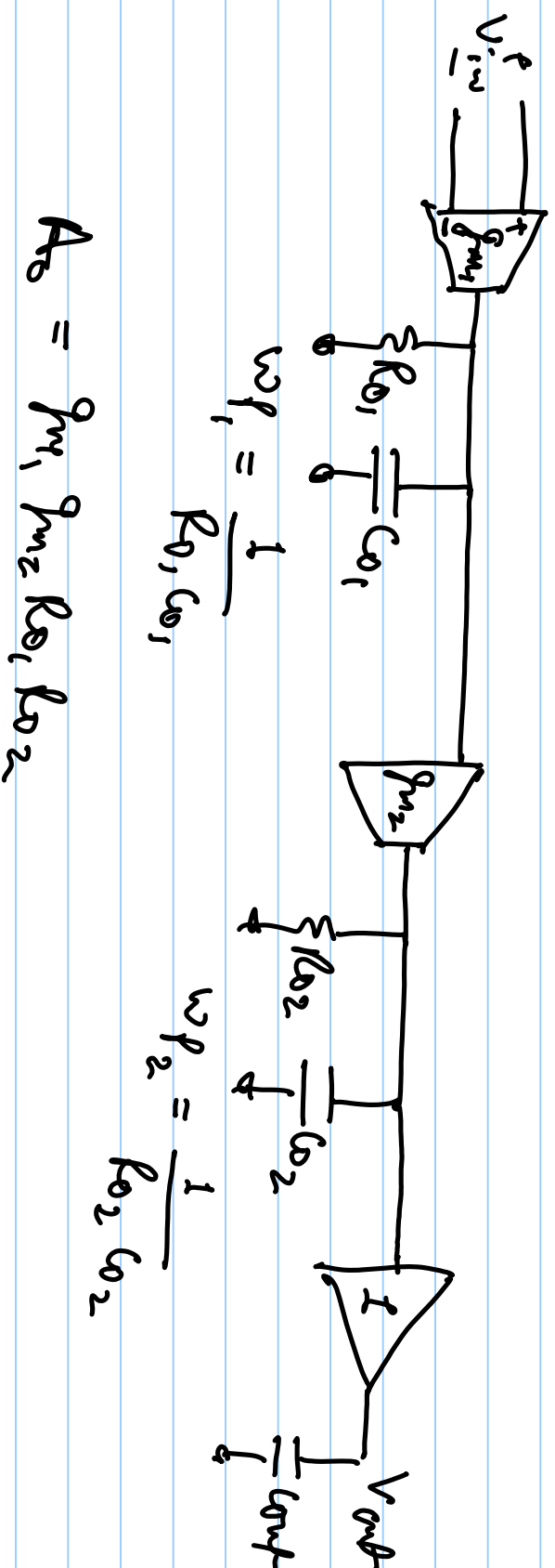


Compensation Techniques

① Dominant Pole Compensation.



$$A(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$


$$f_{m1} = 1000 \mu A/V, \quad R_{01} = 1 M \Omega, \quad C_{01} = 10 \text{ pF}$$

$$f_{m2} = 1000 \mu A/V, \quad R_{02} = 1 M \Omega, \quad C_{02} = 10 \text{ pF}$$

$$\omega_{p1} = \omega_{p2}$$

$$A_0 = 10^4 \rightarrow 80 \text{ dB}$$
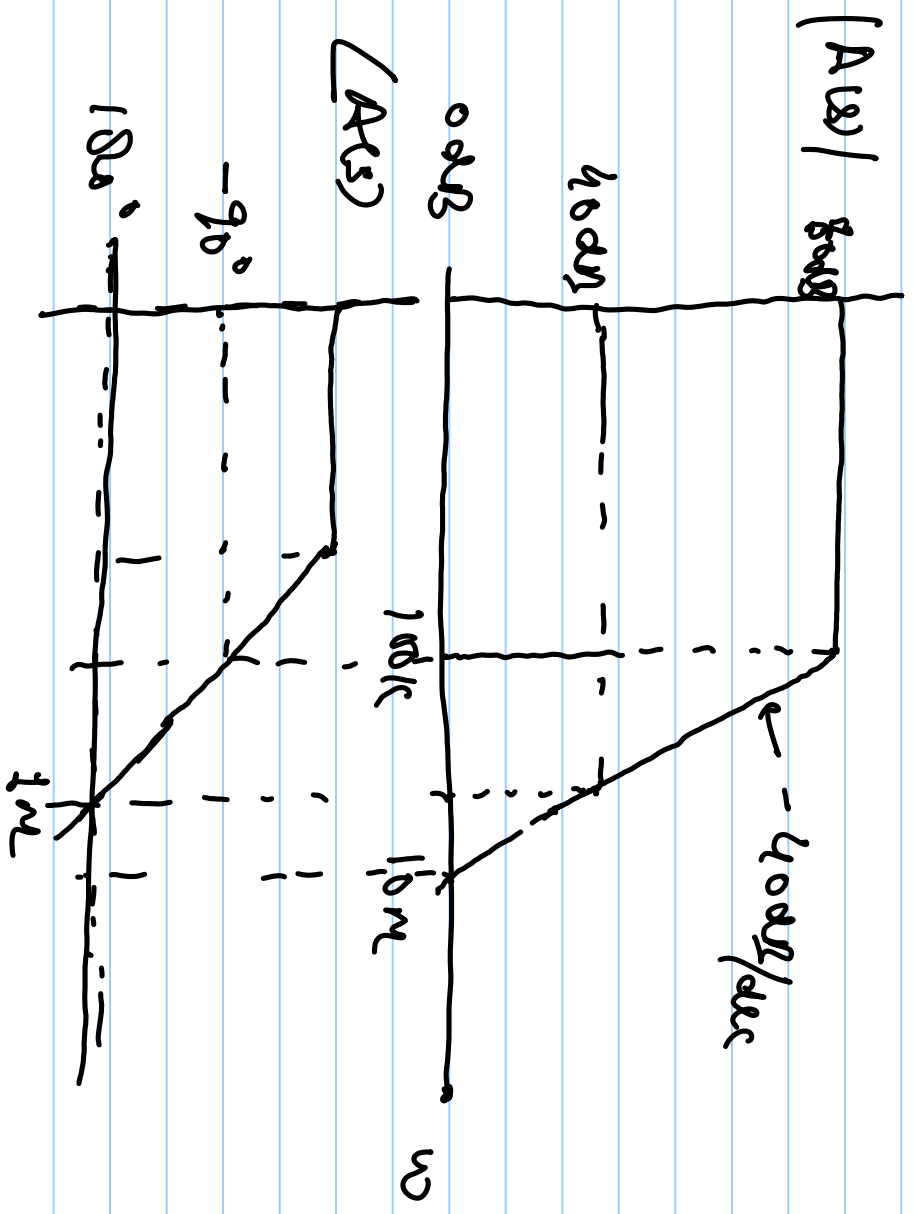
$$\omega_{p1} = \omega_{p2} = \frac{1}{1 M \times 10 \text{ pF}} = \frac{1}{10^6 \times 10^{-11}} = 10^5 = 100 \text{ k rad/sec}$$



For  $\mu$  of  $60^\circ$   $\omega_{P_2} \approx 1.7 \omega_{ngk}$  — (1)

$$\omega_{ngk} = A_0 \omega_{P_1} \quad \text{--- (2)}$$

from (1) & (2)

$$A_0 \omega_{P_1} = \frac{\omega_{P_2}}{1.7} \quad \Leftrightarrow \quad \omega_{P_1} = \frac{\omega_{P_2}}{1.7 A_0}$$

$$\omega_{P_2} = 1000 \text{ k rad/sec}$$

$$\omega_{P_1} = \frac{1000 \text{ k}}{1.7 \times 10^4} = \frac{10^5}{1.7 \times 10^4} = \frac{10}{1.7} = 5.88 \text{ rad/sec}$$

$$\omega_p = \frac{1}{R_1 C_1} = 5.88$$

$$\omega_p = \frac{1}{R_1 \times 5.88} = \frac{1}{1M \times 5.88} \approx 170 \text{ nF}$$