
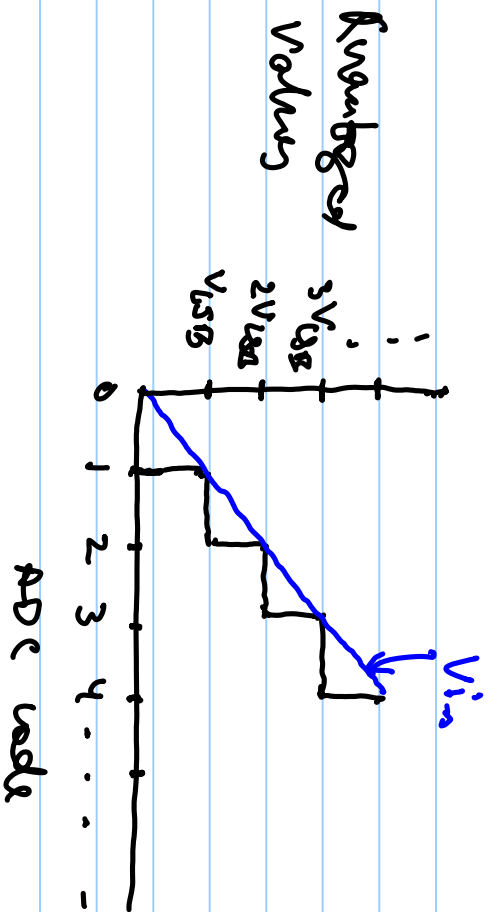


Quantization error

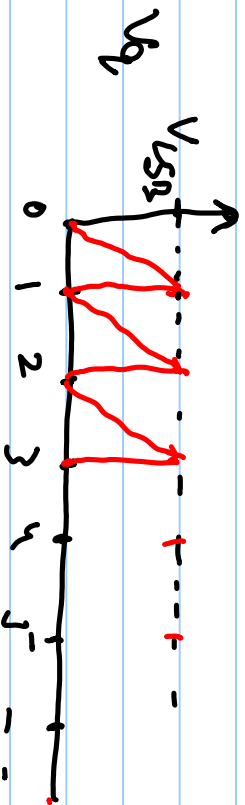


Quantization error, $V_q = V_{in} - \text{Quantized value}$



Switching Regulators

Switching losses

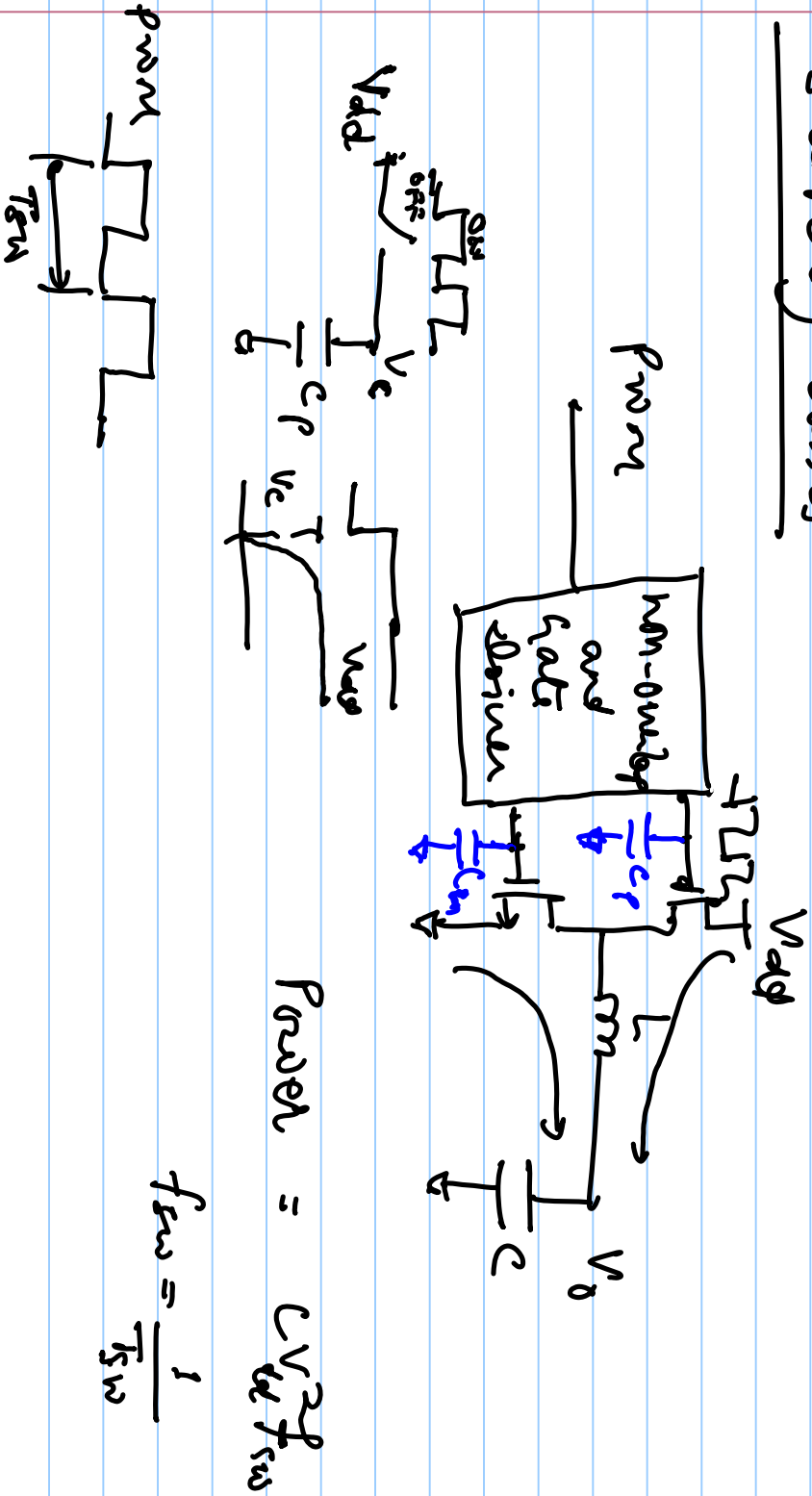

Total switching losses ($P_{\text{loss-sw}}$)

$$= C_p V_{dd}^2 f_{sw} + C_n V_{dd}^2 f_{sw} \\ = V_{dd}^2 f_{sw} (C_p + C_n)$$


$$V_{dd} = 5V, \quad C_p = C_n = 1\mu F$$

$$f_{sw} = 100 \text{ kHz}$$

$$P_{\text{loss-sw}} = (5)^2 (100 \times 10^3) (2 \times 10^{-9})$$

$$25 \times 10^5 \times 2 \times 10^{-9} = 5 \text{ mW}$$

Ripple in Buck converter

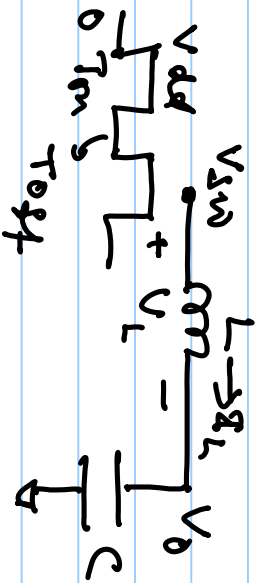


during ON time


$$V_L = V_{in} - V_o$$

$$I_L = \frac{1}{L} \int_0^{T_{ON}} V_L dt$$

$$= \frac{V_{in} - V_o}{L} T_{ON}$$

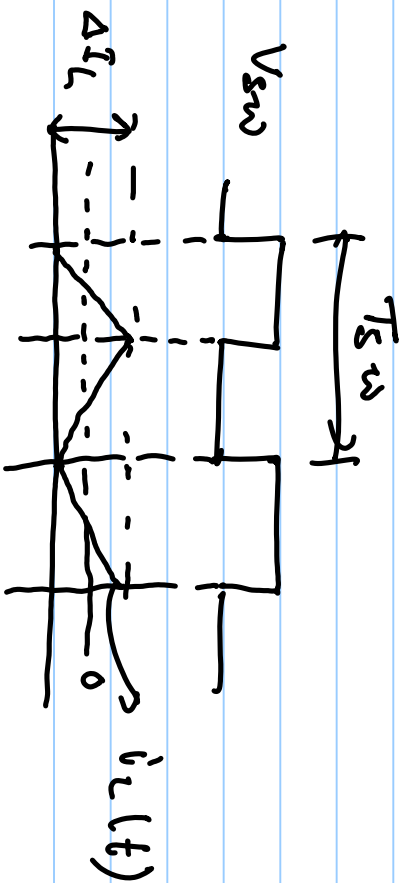
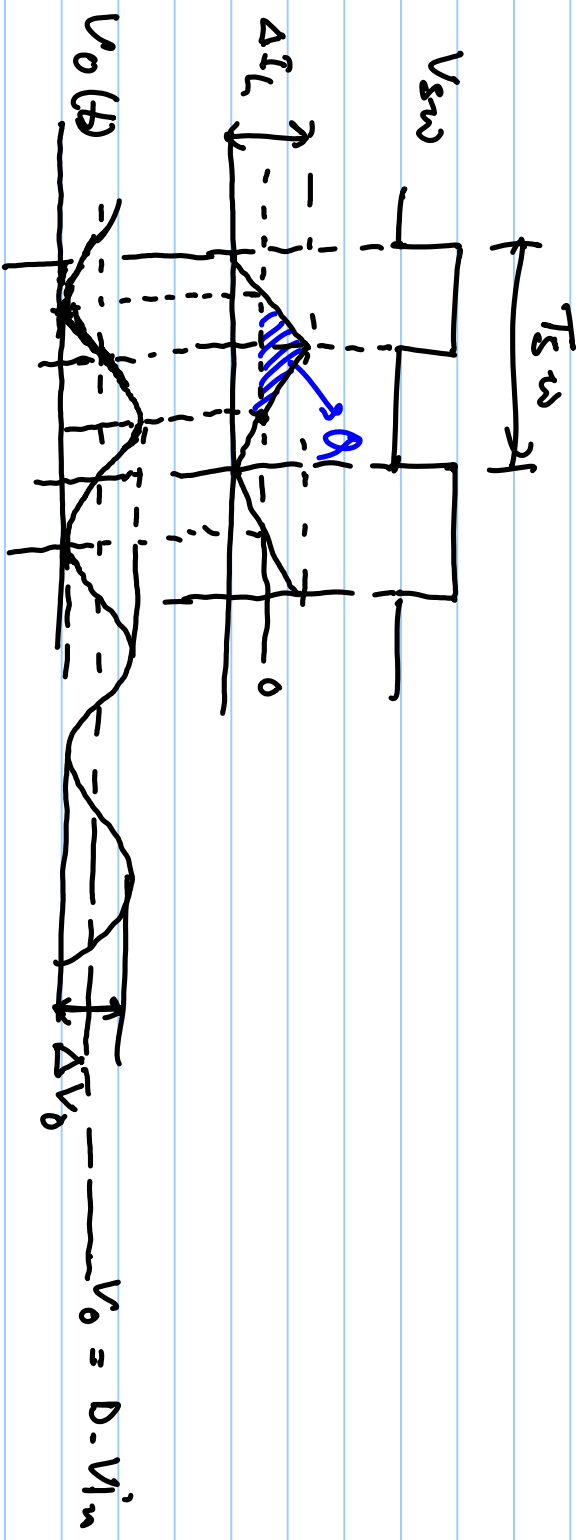
$$\Delta I_L = \frac{V_{in} - V_o}{L} T_{ON} = \frac{V_{in} - V_o}{L} D \cdot T_{ON}$$



$\Delta V_o =$ output ripple voltage

$$V_o(t) = V_o(\text{dc}) + \frac{1}{C} \int i_L(t) dt$$

total charge going into the capacitor.

$Q = \text{area of triangle}$

$$= \frac{1}{2} \times T_{sw} \times \frac{1}{2} \left(\frac{V_{in} - V_0}{L} \right) D \cdot T_{sw}$$

$$= \frac{1}{8} T_{sw}^2 V_{in} (1-D) D$$


$$\Delta V_0 = \frac{Q}{C} = \frac{1}{8} \frac{V_{in} \cdot D \cdot (1-D)}{L C \text{ } \mu\text{s}^2}$$

Boost conversion (step-up)

$$V_o > V_{DD}$$


V_{DD}

Switch Bank

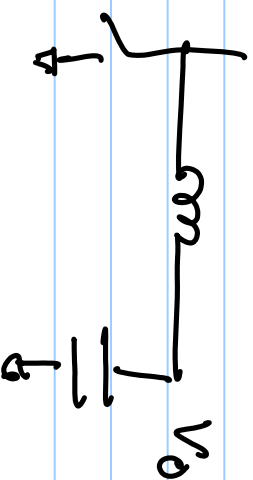

$$V_o = D \cdot V_{DD}$$

flip V_{DD} & V_o

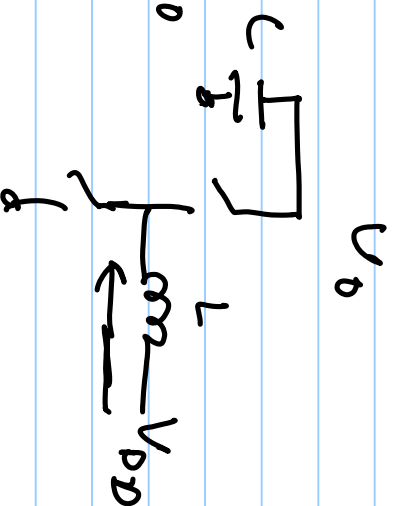


$$V_{DD} = D \cdot V_o$$

$$V_o = \frac{V_{DD}}{D}$$

$$D \rightarrow 1 - D$$

$$V_o = \frac{V_{DD}}{1 - D}$$

$$V_o \geq V_{OD}$$

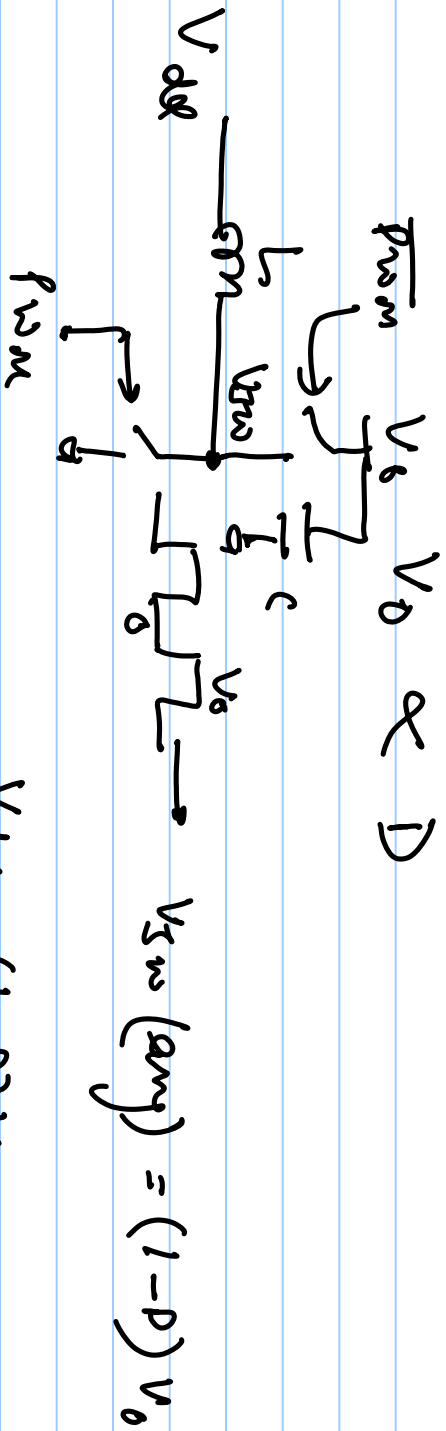

$$V_{DD} - (1 - D)V_o = 0$$

$$\Rightarrow V_o = \frac{V_{DD}}{1 - D}$$

for ideal converter

$$P_{in} = P_o$$

$$V_{dd} \cdot I_{dd} = V_o \cdot I_o = \frac{V_{dd}}{1-D} \cdot I_o$$

$$I_{dd} = \frac{I_o}{1-D}$$