

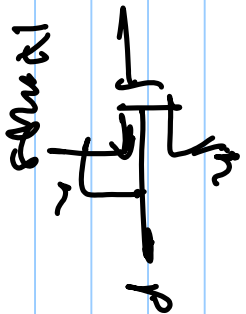
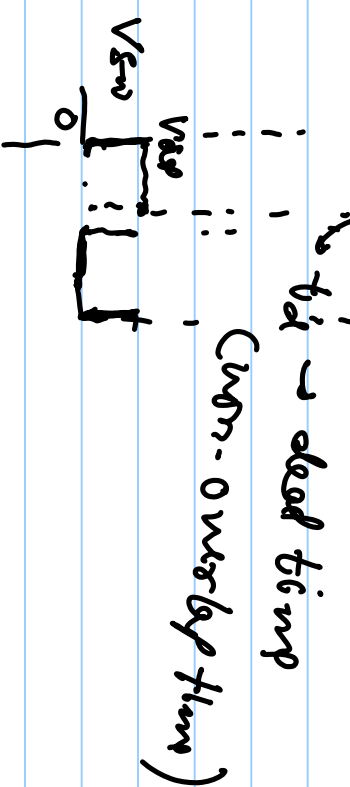
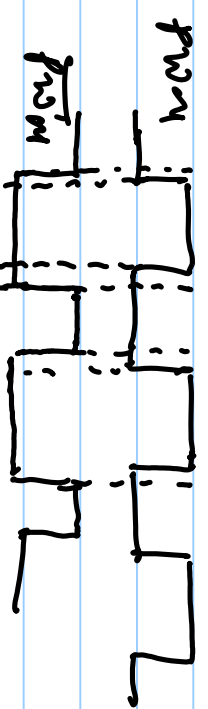


Dead time switching losses:

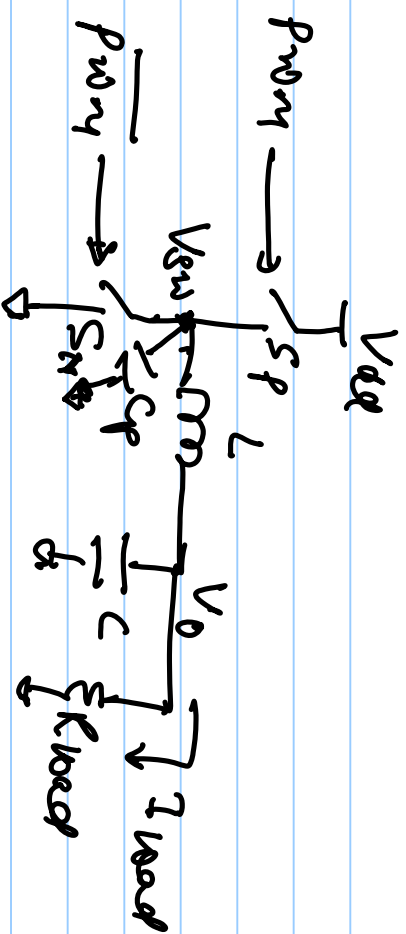



diode D is conducting during dead time

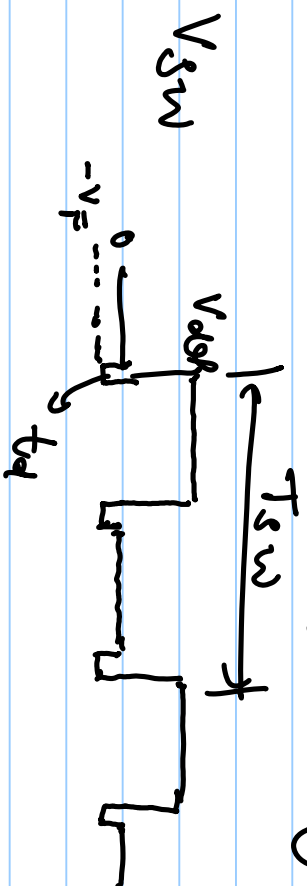



Total power consumption in diode

$$2 \times \frac{(V_f \times I_{load}) t_d}{T_{sw}}$$

Voltage Buck

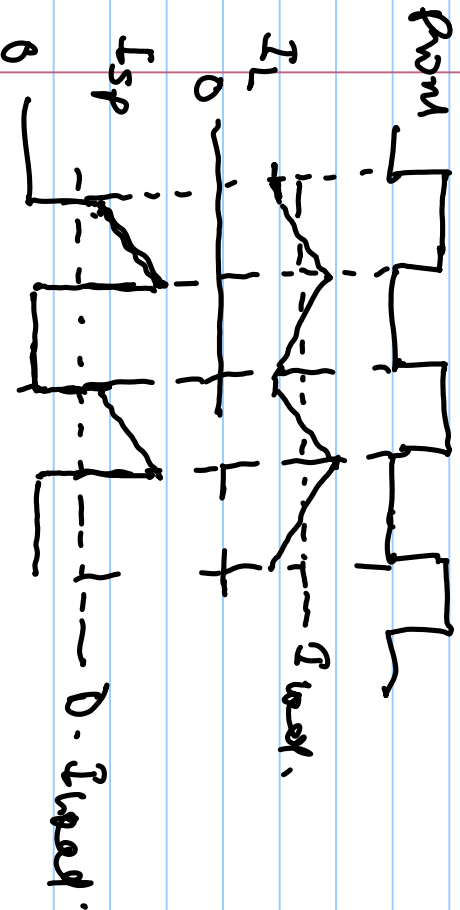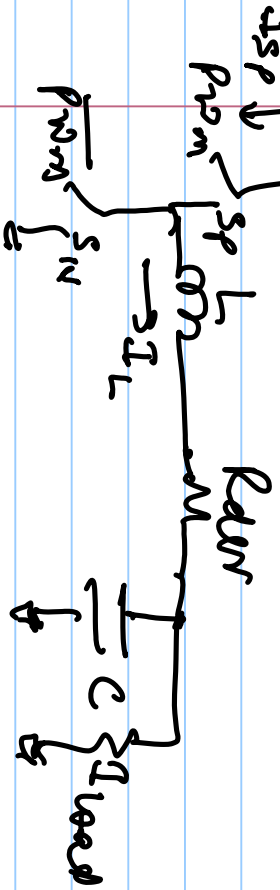


Boost

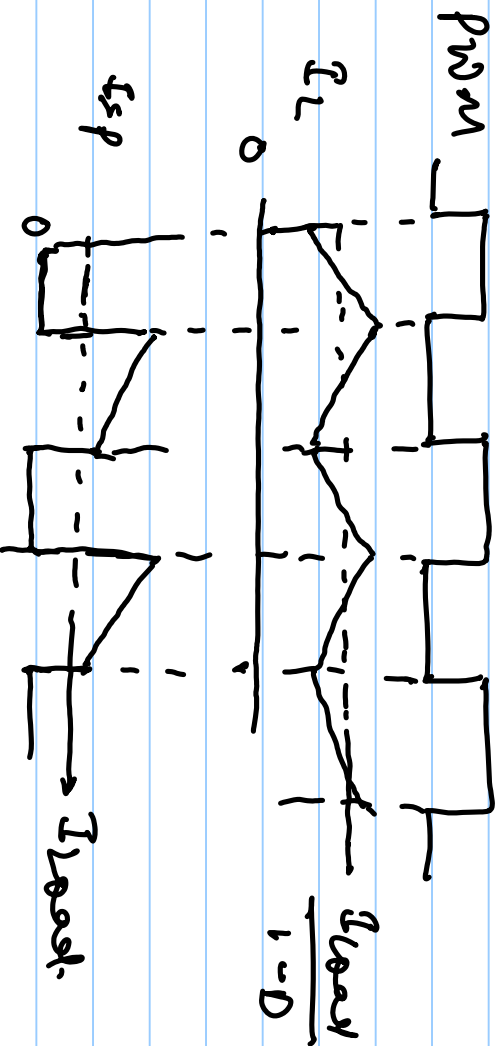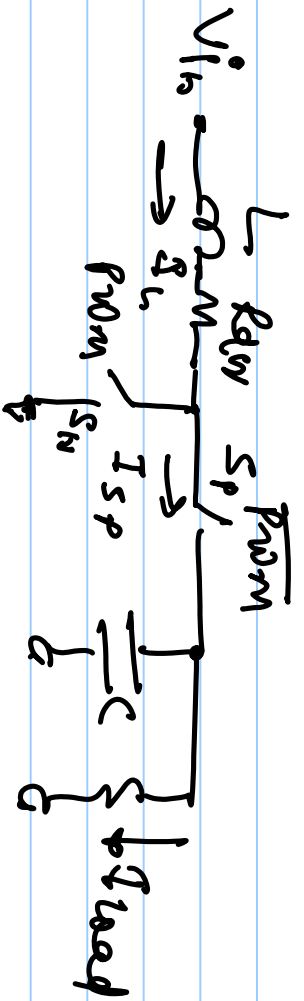


$$I_{load} \frac{1}{1-D} - I_{load} = I_{load} \left(\frac{1-D}{1-D} \right)$$

Common-Mode Inductor

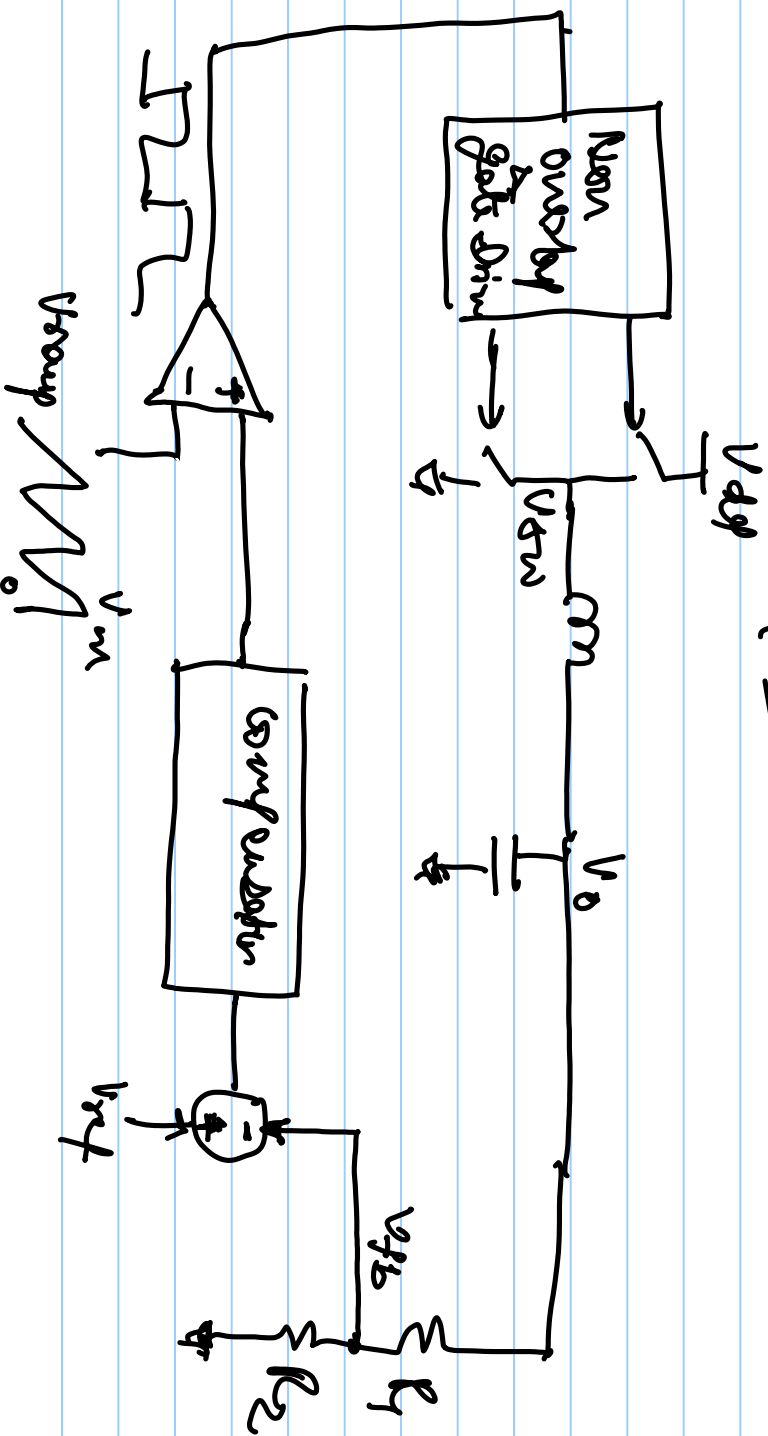


$$V_0 = \left(1 + \frac{R_1}{R_2} \right) V_{ref}$$

$$V_{ref} = \frac{V_{sec}}{\beta}$$

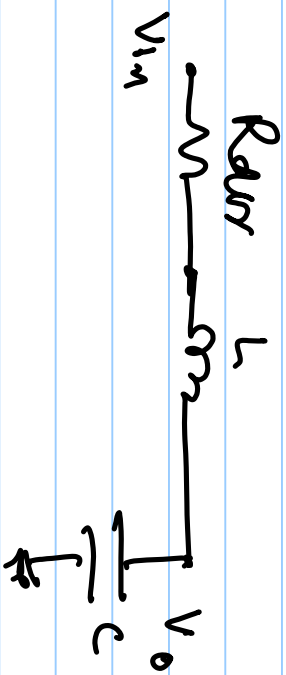



$$\frac{V_o(s)}{V_{in}} = \frac{1/LC}{s^2 + R_{ARM} \frac{s}{L} + \frac{1}{LC}}$$
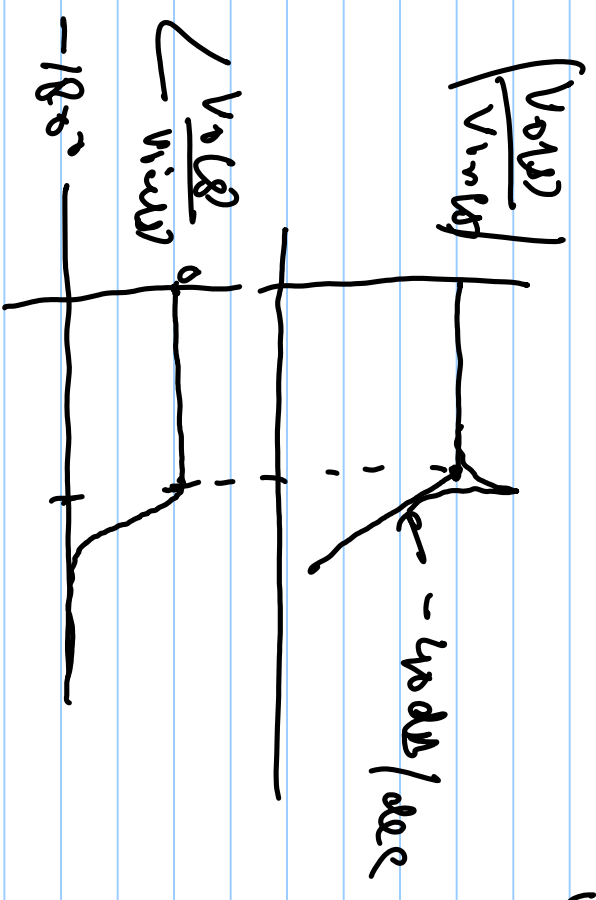
$$\omega_0 = \frac{1}{\sqrt{LC}} \quad , \quad \frac{\omega_0}{Q_0} = \frac{R_{ARM}}{L}$$



Buck is inherently unstable due to LC resonance poles hence require compensation.

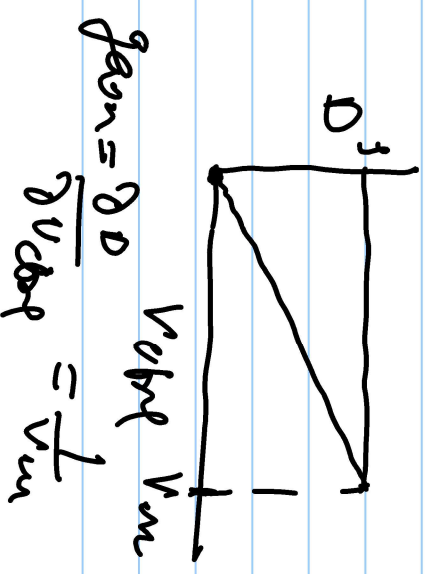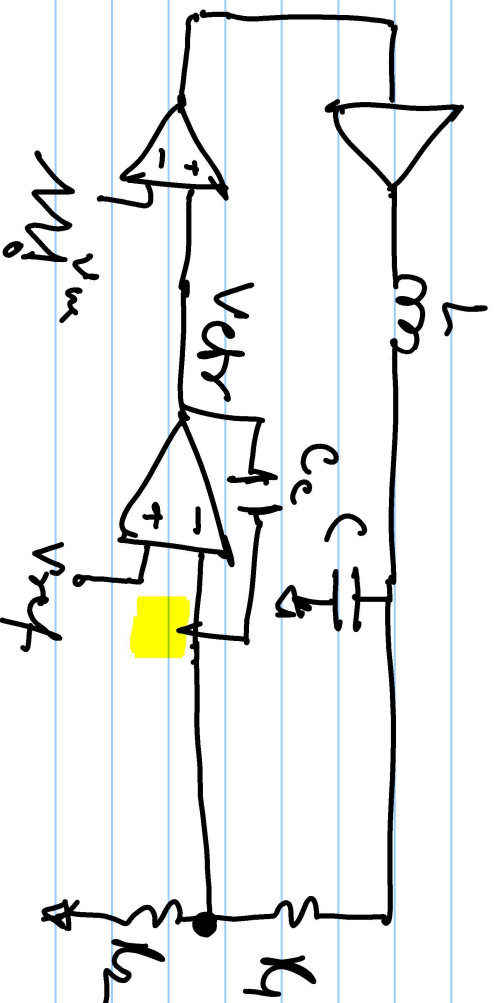We can do dominant pole compensation by using an integrator.



$$\text{Case } \frac{1}{R_1 C} \ll \omega < \frac{\omega_0}{Q}$$

$|L_2(s)|$

