

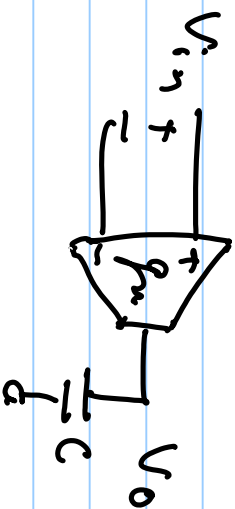


GM-C Filters


$$V_o = \frac{g_m}{C s} V_{in}$$

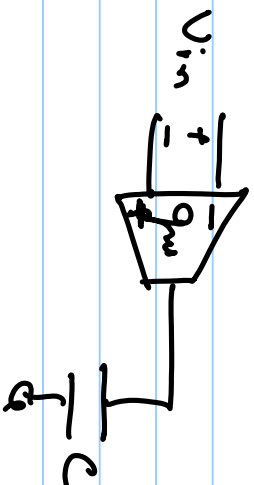
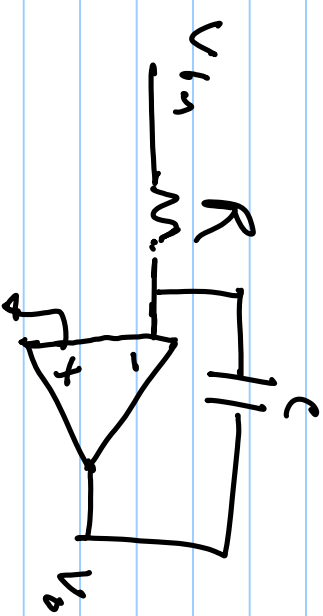
$$V_o = -\frac{g_m}{C s} V_{in} \Rightarrow$$



Adalan

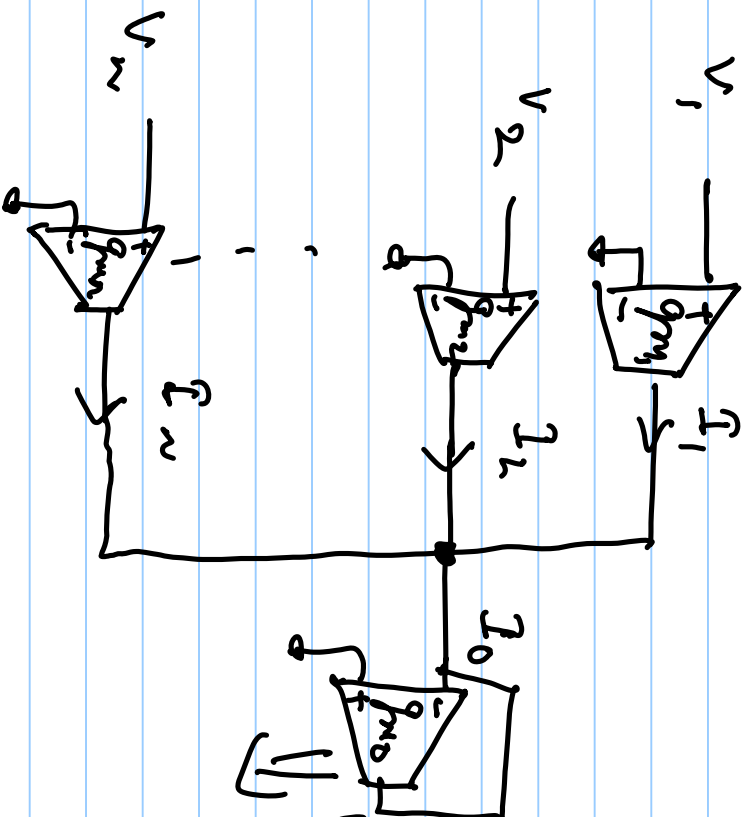

$$I_o = I_1 + I_2 + \dots + I_n$$


$$I_o = V_1 g_{m1} + V_2 g_{m2} + \dots + V_n g_{mn}$$



$$R = \frac{1}{g_{m0}}$$


$$V_o = \frac{1}{g_{m0}} (V_1 g_{m1} + V_2 g_{m2} + \dots + V_n g_{mn})$$

$$g_{m0} = g_{m1} = g_{m2} = \dots = g_{mn}$$

$$V_o = V_1 + V_2 + \dots + V_n$$

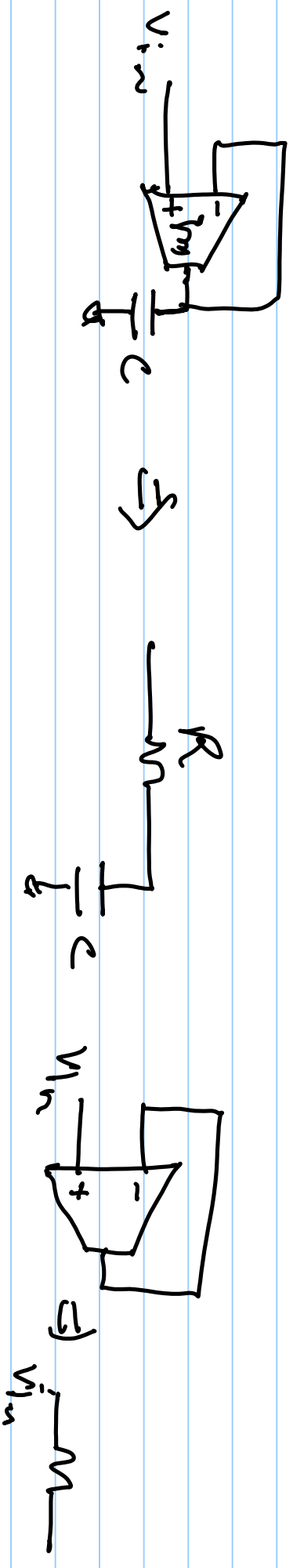


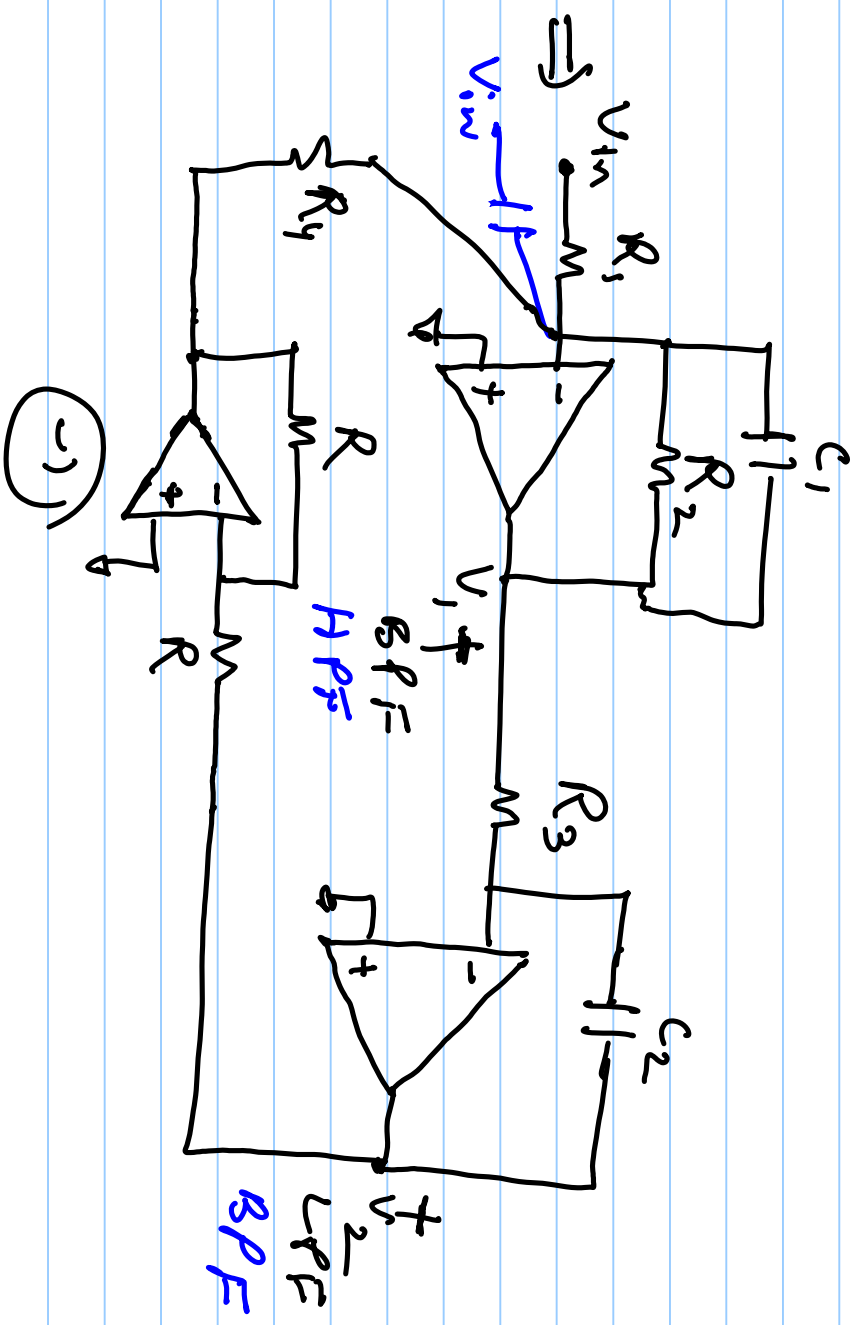
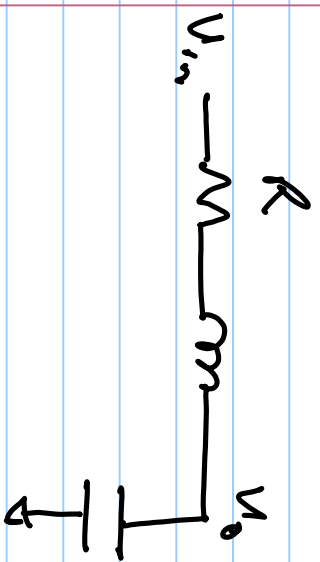


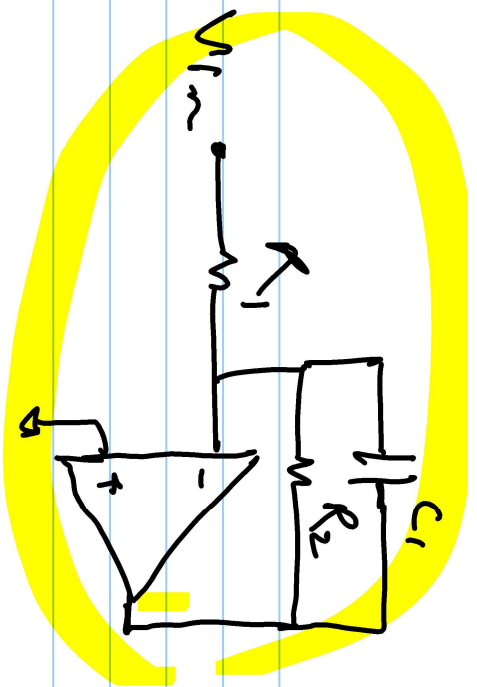


① $\Rightarrow$



① $\Rightarrow$

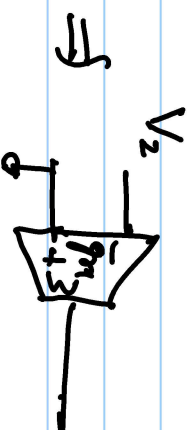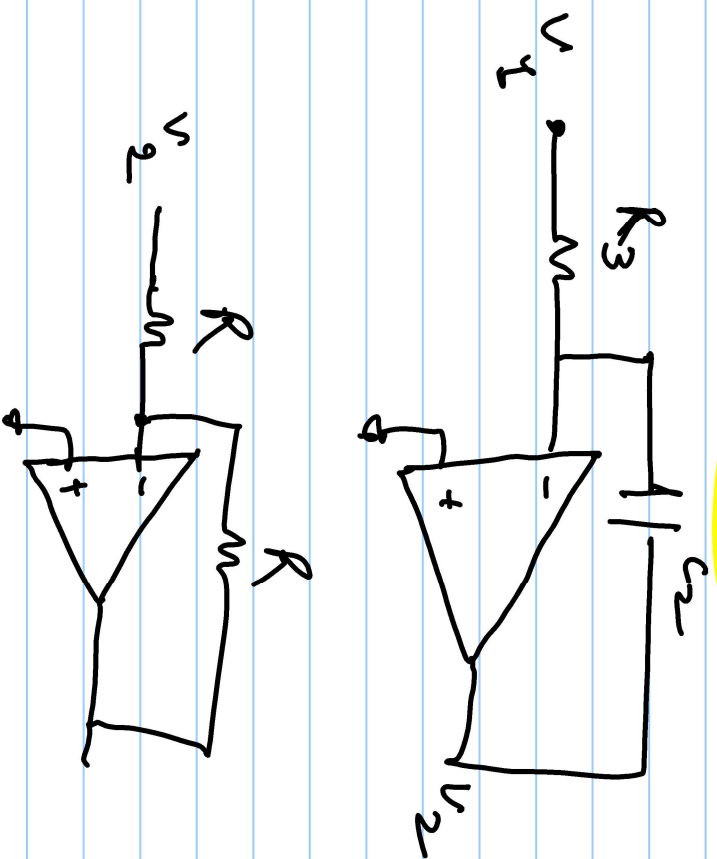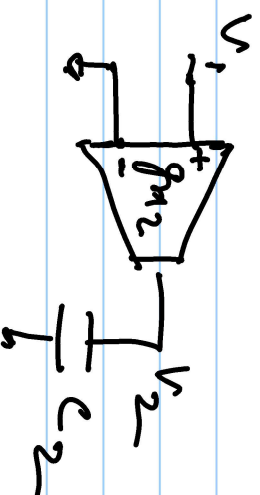

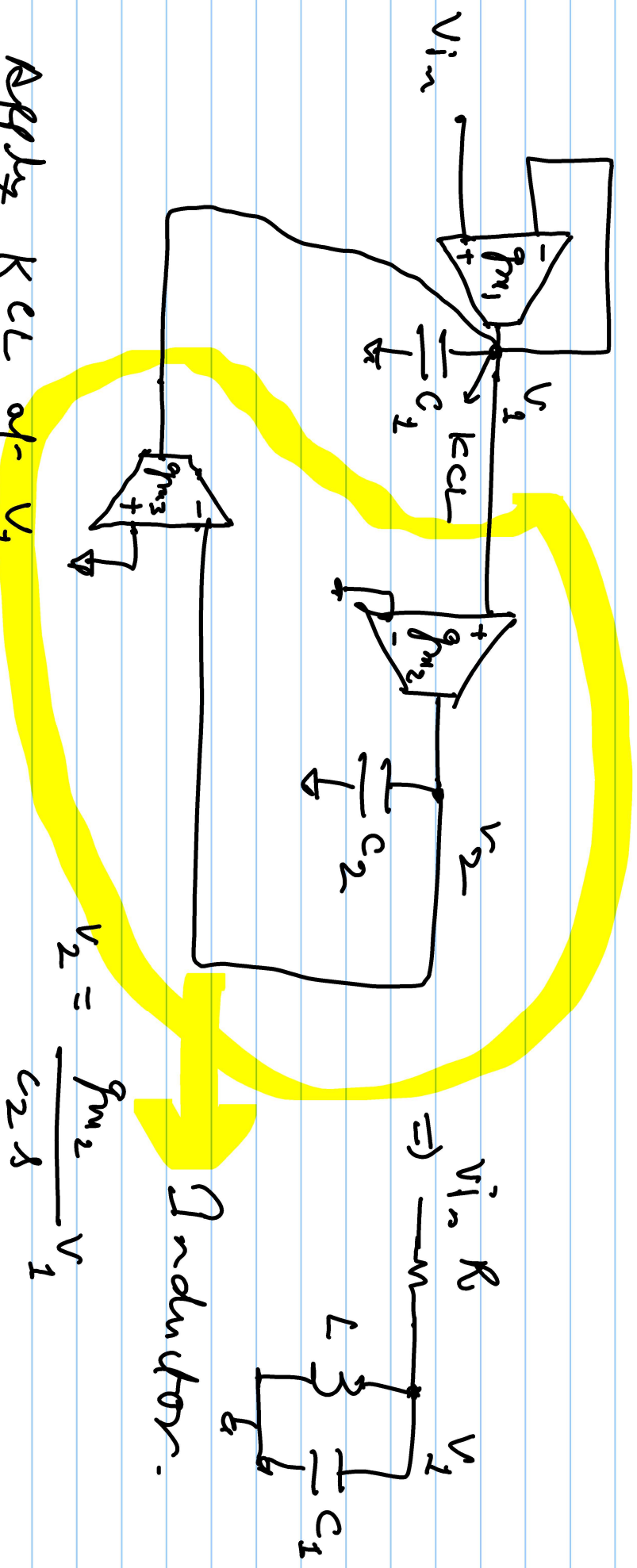

Apply KCL at V_1

$$(V_{in} - V_1)g_{m1} + (-V_2 g_{m3}) + (-V_1 C_1 s) = 0$$

$$V_2 = \frac{g_{m2}}{C_2 s} V_1$$

Inductor.

$$V_{i1} q_{m1} - V_{i1} q_{m1} - V_{i2} q_{m3} - V_{i1} c_{1s} = 0$$

$$\downarrow \frac{q_{m2}}{c_{2s}} V_1$$

$$V_{i1} q_{m1} - V_{i1} q_{m1} - \frac{q_{m2} q_{m3}}{c_{2s}} V_1 - V_{i1} c_{1s} = 0$$

$$V_{i2} q_{m1} = V_2 \left[q_{m1} + \frac{q_{m2} q_{m3}}{c_{2s}} + c_{1s} \right]$$

$$V_{i2} q_{m1} c_{2s} = V_2 \left[q_{m1} c_{2s} + q_{m2} q_{m3} + c_{1s} c_{2s}^2 \right]$$

$$\frac{V_I}{V_{in}} = \frac{g_{m1} C_2 s}{C_1 C_2 s^2 + g_{m1} C_2 s + g_{m2} g_{m3}}$$

$$= \frac{g_{m1} C_2}{g_{m2} g_{m3}} s$$


$$\frac{\frac{C_1 C_2}{g_{m2} g_{m3}} s^2 + \frac{g_{m1}}{g_{m2} g_{m3}} C_2 s + 1}{}$$

B-P F.

LC

$$LC = \frac{C_1 C_2}{g_{m2} g_{m3}}$$

$$L = \frac{C_2}{g_{m2} g_{m3}}$$

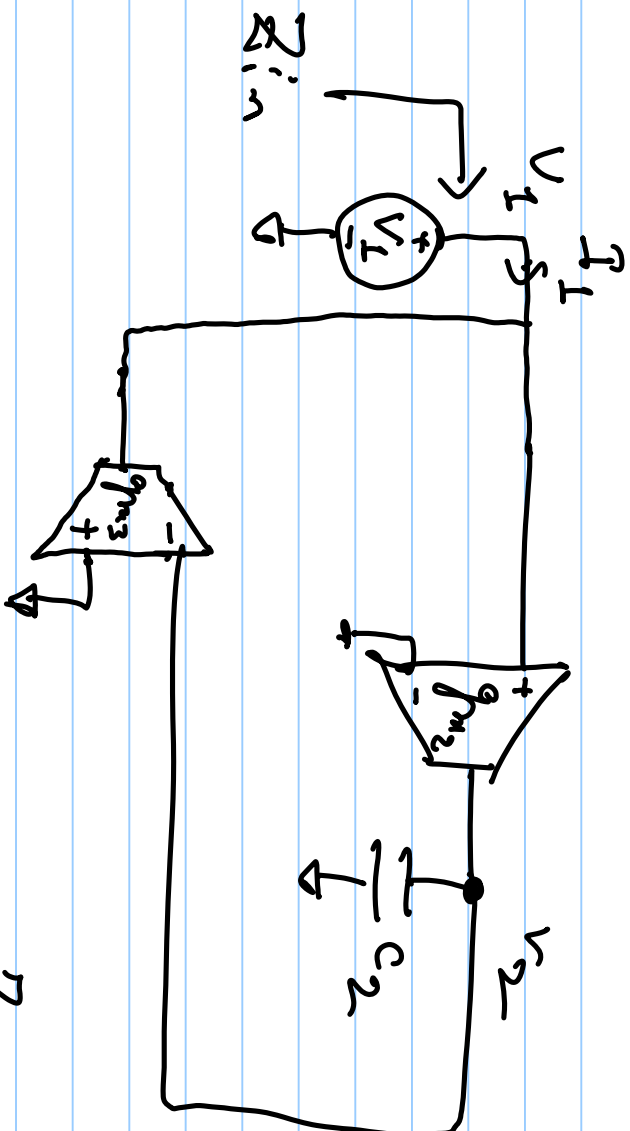

of-


$$Z_{1n} = \frac{V_1}{I_1}$$

$$V_2 \cdot \delta C_2 = V_1 g_{m2} \Rightarrow V_2 = \frac{g_{m2}}{\delta C_2} V_1$$

$$I_1 = V_2 \cdot g_{m3} = \frac{g_{m2} g_{m3}}{\delta C_2} V_1$$


$$\frac{V_1}{I_1} = \frac{e_2}{g_{m2}g_{m3}} \Rightarrow L_s \quad \left. \vphantom{\frac{V_1}{I_1}} \right\} L = \frac{e_2}{g_{m2}g_{m3}}$$

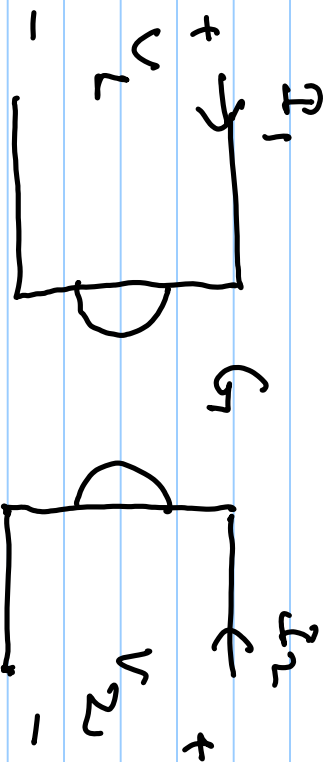This is called gyrator or impedance inverter.



$$I_1 = G V_2$$

$$I_2 = -G V_1$$

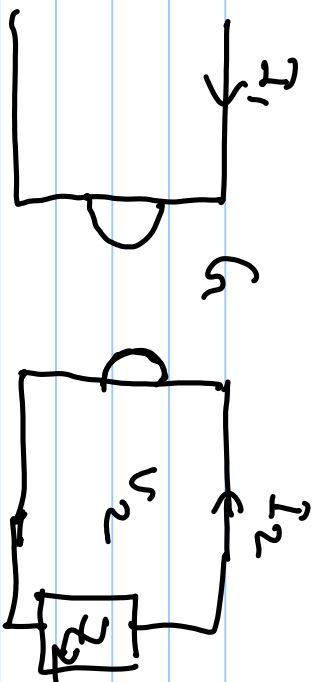



$$Z_1 = \frac{1}{G^2 Z_2}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & G \\ -G & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$I_1 = G V_2$$

$$I_2 = -G V_1$$

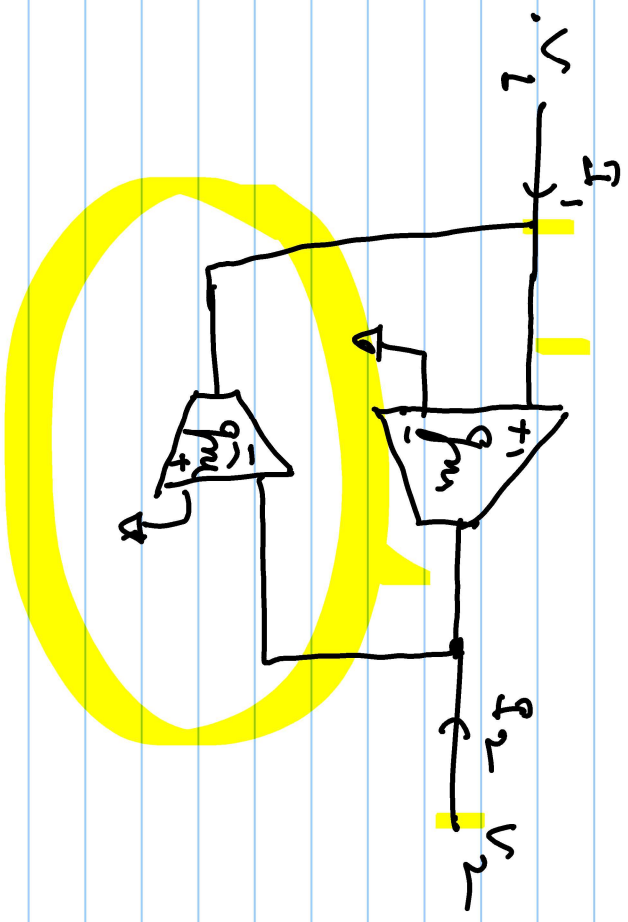

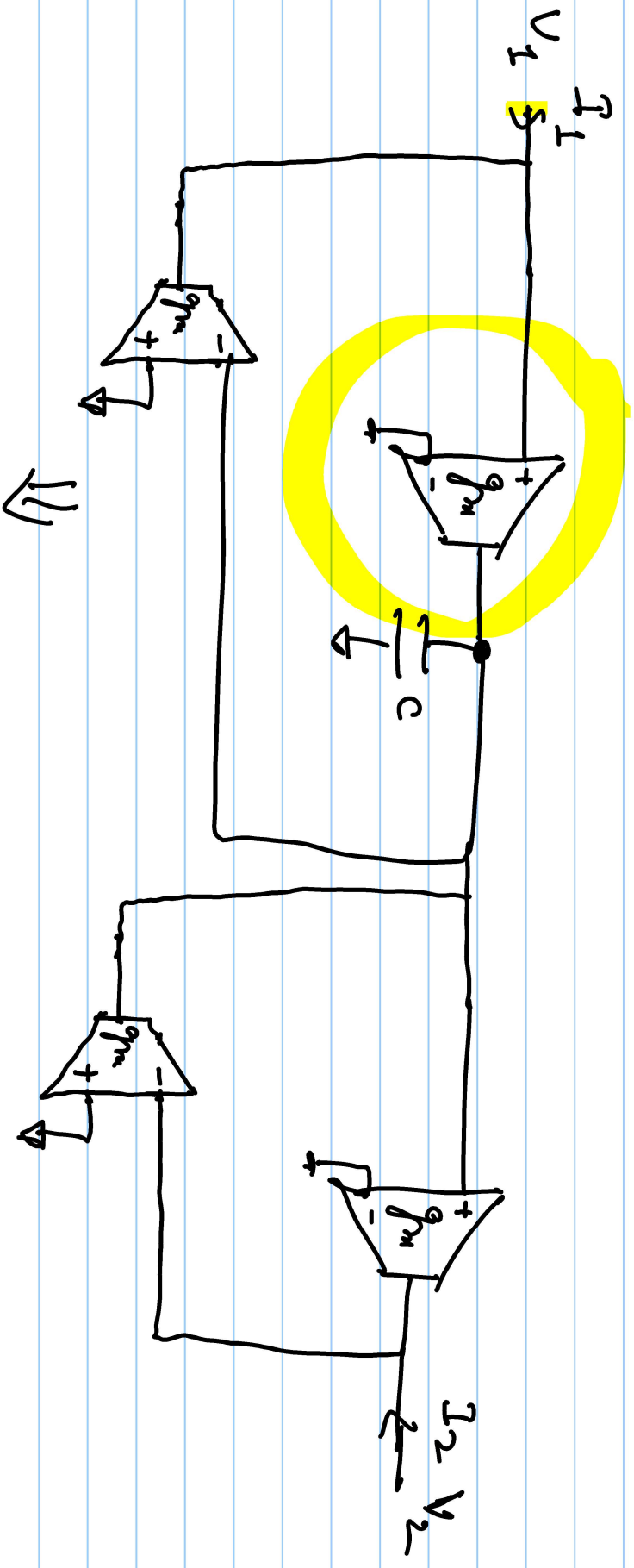

$$V_1 \xrightarrow{C/q_m} V_2$$

$\Rightarrow$ tunable inductor
controlled using q_m