

1) In the LDO shown below, assume that R is very large compared to other resistances in the circuit. The opamp has a gain $A(s)$ given by


$$A(s) = \frac{100}{1 + (2 \times 10^{-8})s}$$

(a) Determine the signs of the opamp for proper negative feedback operation. (1 Marks)


(b) What is the dc value of V_x ? (1 Marks)

(c) Perform dominant pole compensation on this feedback system for a phase margin of 45° , for maximum possible bandwidth. (4 Marks)

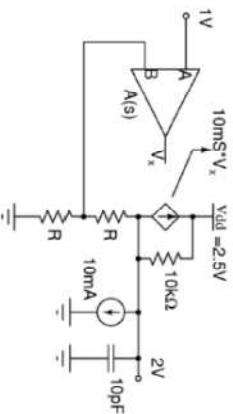(d) Draw the bode plots of magnitude and phase for the loop gain before and after compensation, clearly labelling DC gain, positions of poles and slopes at various points. (2 Marks)



(a) find A & B sign

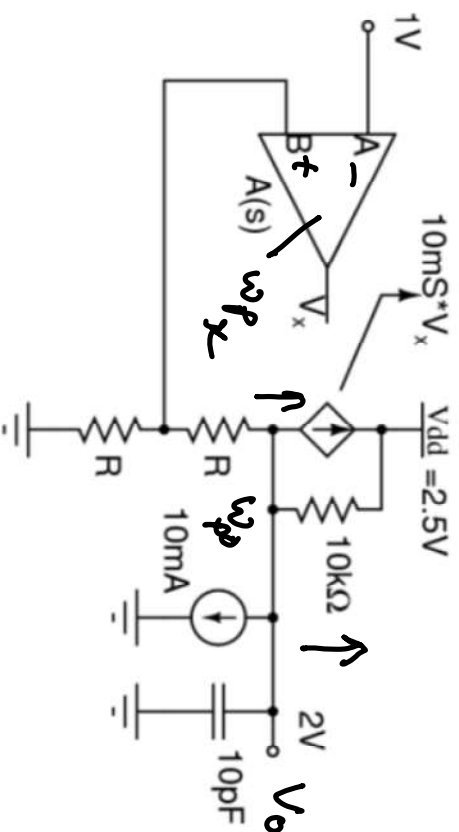

Sign from V_x to $V_o = -V_e$

$$A = - \quad B = +$$

$$(b) \quad V_x = ?$$


$$V_o = I_o \times R_o$$

$$I_o = I_{load} = 10 \text{ mA}$$

$$V_o = 2 \text{ V}$$

$$I_{load} = 10 \text{ mA}, \Rightarrow \text{from } V_x = -10 \text{ mA}$$
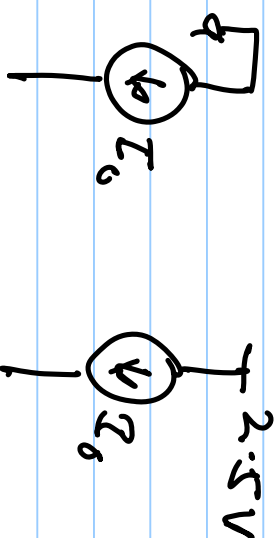
$$V_x = \frac{-10 \text{ mA}}{\text{from}} = \frac{-10 \text{ mA}}{10 \text{ m}} = -1 \text{ V}$$



$$(c) \quad A(s) = \frac{100}{1 + 2 \times 10^{-8} s}$$

Two pole system.

$$\omega_{p_1} = \frac{1}{2 \times 10^{-8}} = 50 \text{ Mrad/sec.}$$


$$\omega_{p_2} = \frac{1}{R_o C_o} = \frac{1}{10k \times 10 \times 10^{-12}} = 10 \text{ Mrad/sec.}$$

$$A_{\beta}(cc) = 100 \times (10 \times 10^6) = 10^4$$


$$L(u(s)) = Ap^3 = \frac{-10^4 \times 1/2}{(1+s/\omega_{px})(1+s/\omega_{p0})}$$

$$= \frac{-5000}{(1+s/\omega_{px})(1+s/\omega_{p0})}$$
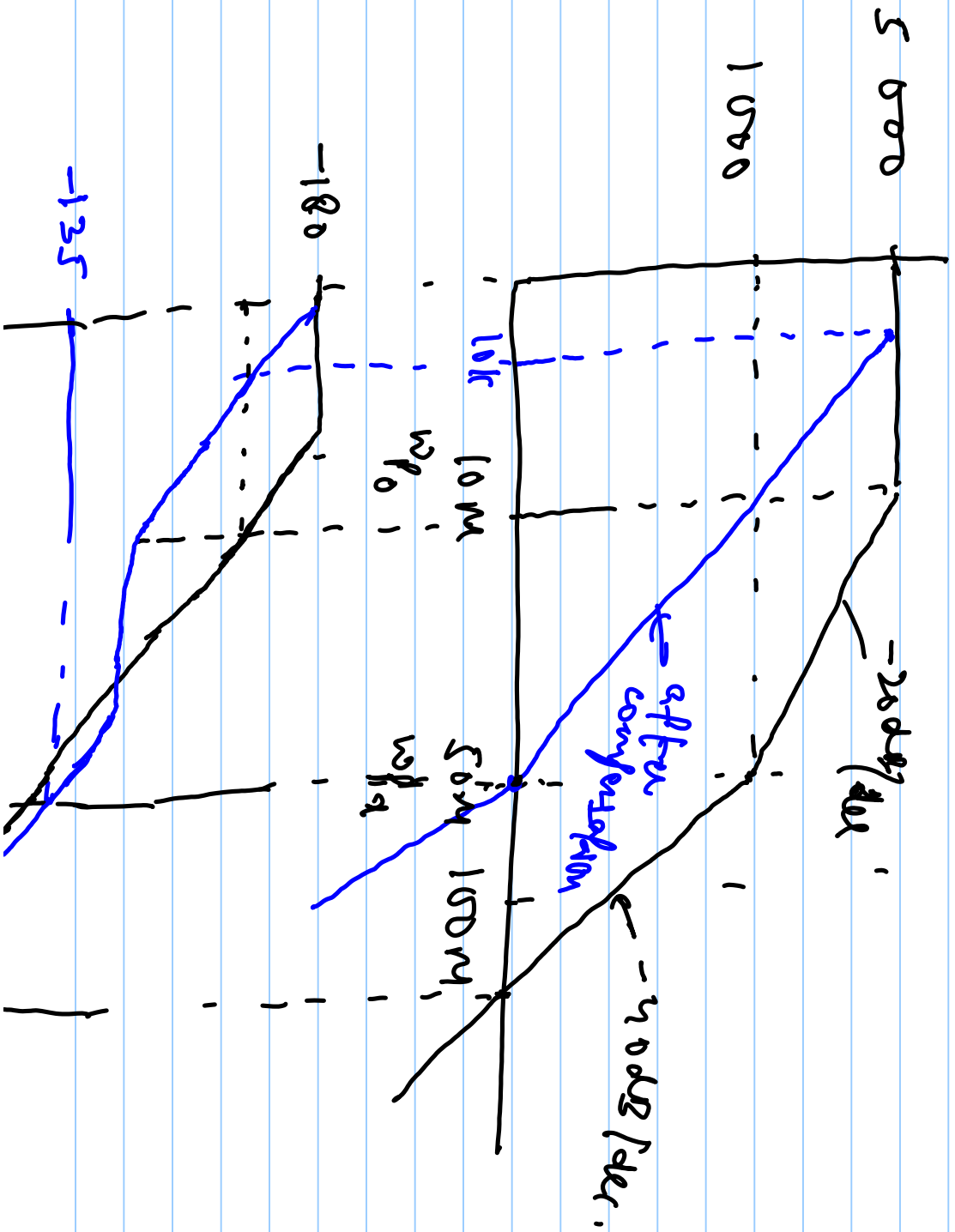
$$\omega_{px} = 50 \text{ Mrad/s} \quad \& \quad \omega_{p0} = 10 \text{ Mrad/s.}$$



-360° - - - - -

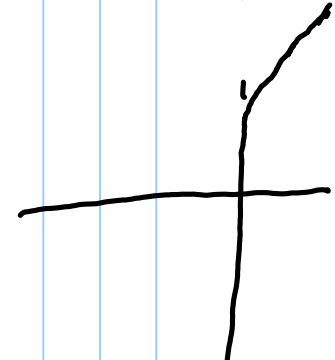

unstable system.

$$PM = 45^\circ$$

For maximum bandwidth dominant pole configuration should be done at lower freq. pole i.e. ω_{p0} .

$$\omega_{PM} = \omega_{p0} \text{ for } 45^\circ PM.$$

$$\omega_{\text{unity}} = \omega_{P_n} = 50 \text{ Mrad/sec.}$$

ω_{P_0} after compensation,

$$\omega_{P_0} = \frac{\omega_{\text{unity}}}{A_{P_0}} = \frac{50 \text{ Mrad/s}}{5000}$$


$$= \frac{50 \times 10^6}{8 \times 10^3} = 6.25 \text{ Mrad/sec.}$$

$$\omega_{P_0} = \frac{1}{R_0 C_0} \quad R_0 = 10 \text{ k}\Omega$$

$$C_0 = \frac{1}{6.25 \times 10^6} = 16 \text{ nF}$$

2

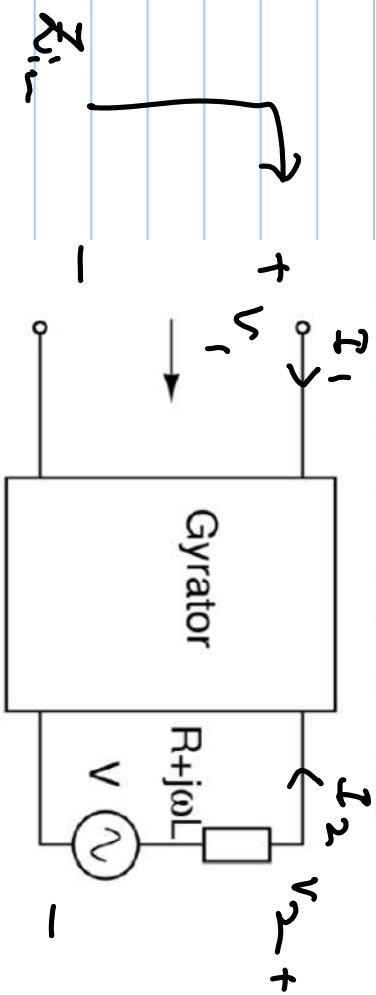2) The output port of a gyrator (with parameter G_m) is loaded with a voltage source V in series with an impedance $(R+j\omega L)$. Determine the equivalent circuit at its input. (6 Marks)



$$I_1 = G_m V_2 \quad \& \quad I_2 = -G_m V_1$$

$$V_2 = -I_2 (R + j\omega L) - V$$

$$I_1 = G_m V_2 = -G_m I_2 (R + j\omega L) - G_m V$$

$$I_2 = -G_m V_I$$

$$I_1 = -G_m (-G_m V_I) (R + g_L) - G_m V$$

$$I_1 = G_m^2 (R + g_L) \underbrace{V_I}_{g_s} - G_m V$$

$$I_1 = I_{2'} - I$$

$$I = G_m V$$

$$I_{2'} = G_m^2 (R + g_L) V_I$$

