

Oscillators


Unstable system mainly used as clock generator.

1. Tuned Oscillators

→ based on L.C

→ High - Q (Band Pass, narrow band)

→ Produces sinusoidal of f .

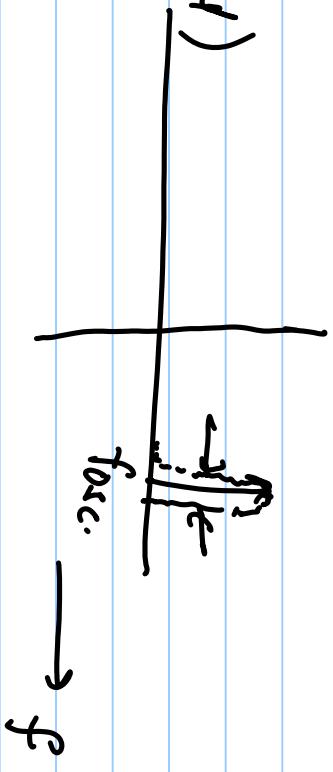

2. RC Phase shift based oscillators

→ Ring oscillator

→ Low pass oscillator. (wide band)

→ not very high - Q.

→ question

3. Relaxation Ordinates

- mostly based on non-linear element (complementors or schmitt trigger)
- Based on charging & discharging of capacitor.
- mostly give non-sinusoidal wave (triangular or sawtooth)

Filters & amplifiers are operated in L.H.P.


$$\Omega = \frac{1}{2\zeta}$$



stable


oscillation decay

0 < ζ < 1

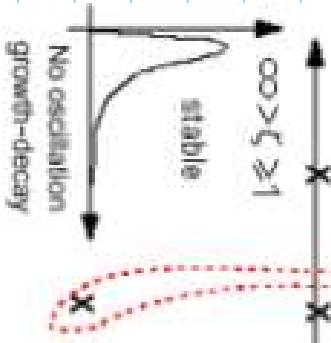

S-plane

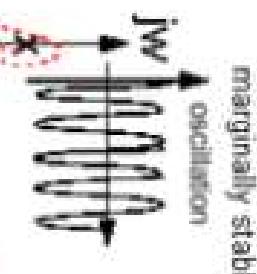
Oscillators are operated in R.H.P or $j\omega$ axis




marginally stable

oscillation


unstable

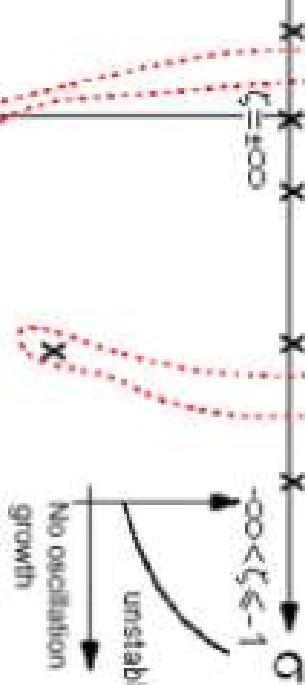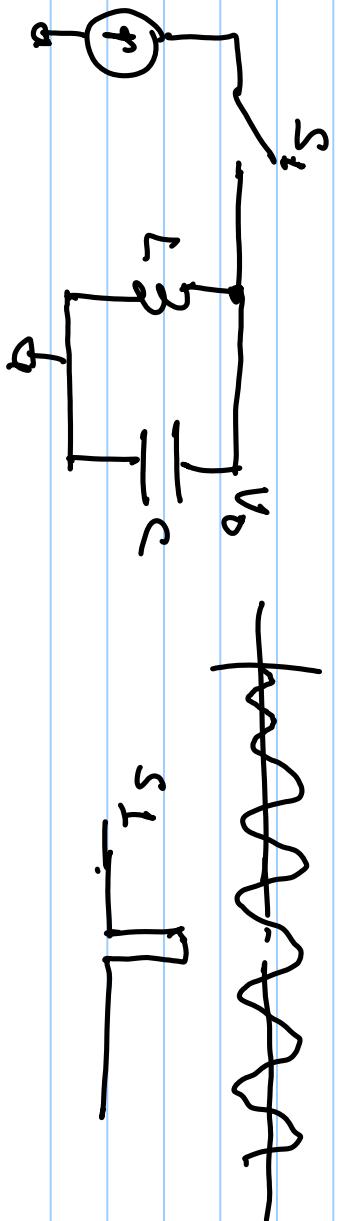-1 < ζ < 0
oscillation growth $\zeta = 0$ 





In practical L is not low - loss so oscillation will damp.

Damp LCR

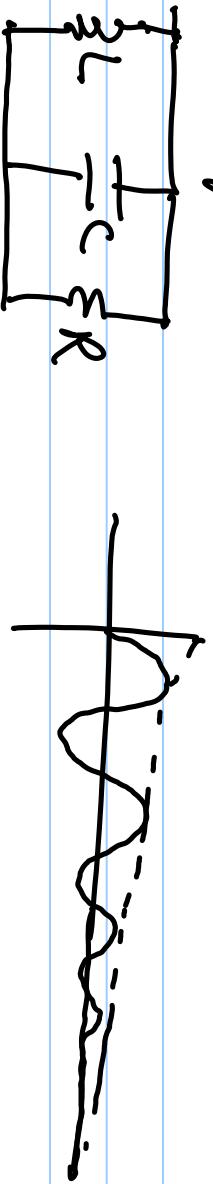




We need to cancel R by adding $-R$ (negative resistance)

Lamp LCR

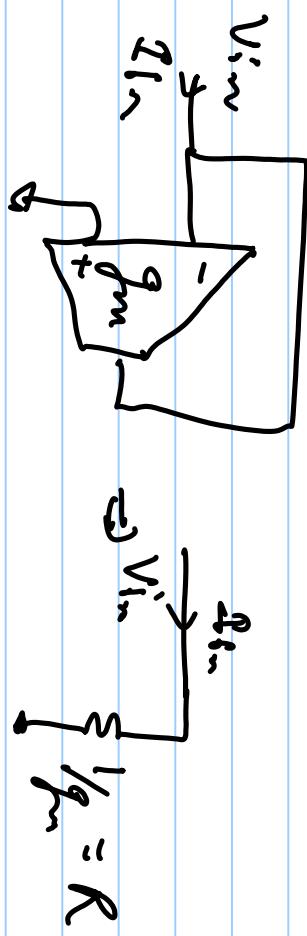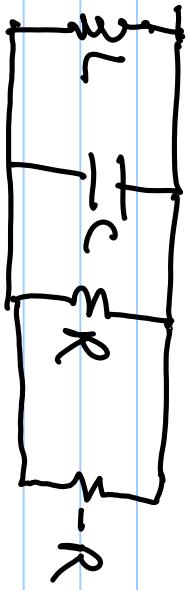


$$\frac{V_{Lm}}{V_{in}} = \frac{\omega_m}{\omega_f} = \frac{1}{R}$$

$$\omega_m = \frac{2\pi}{T}$$

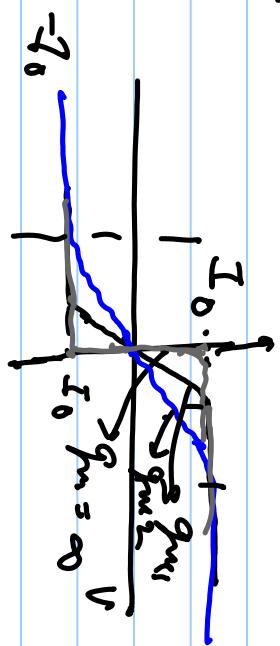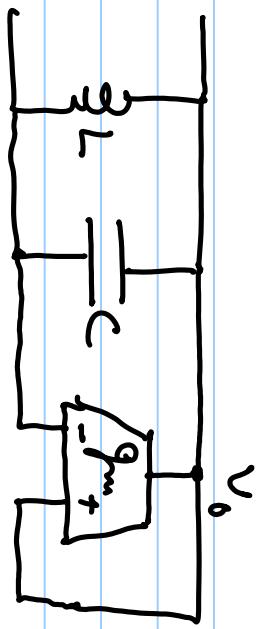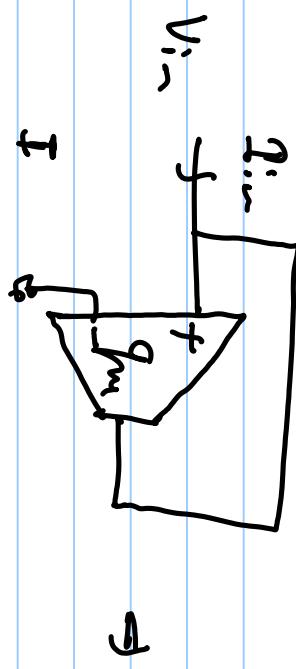


$$I_0 e^{-\frac{t}{T_m}} > I_0 e^{-\frac{t}{T_{f2}}}$$


$$\omega_m = \frac{2\pi}{T_m}$$

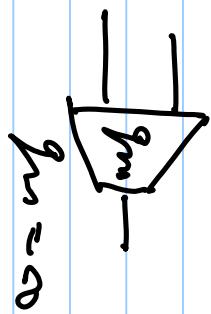


$$R_m = \infty$$

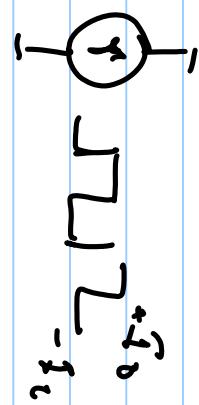



$$=$$

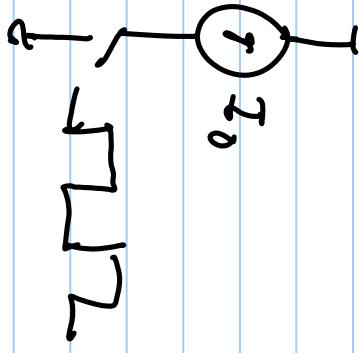



$$I_0$$

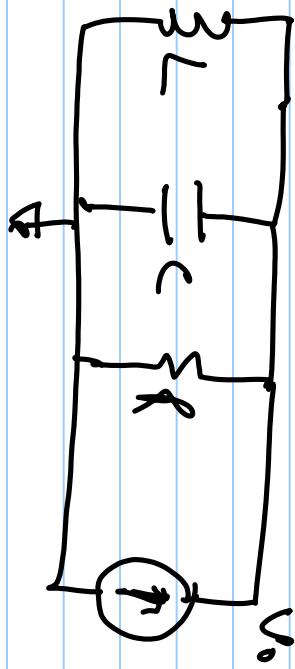
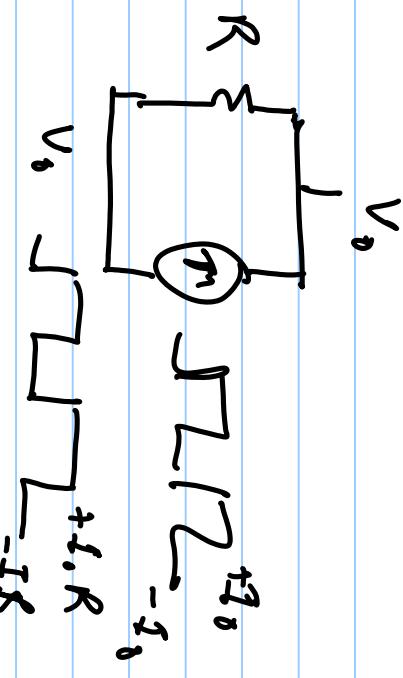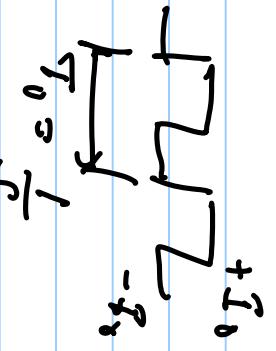
$$\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$$




|2|

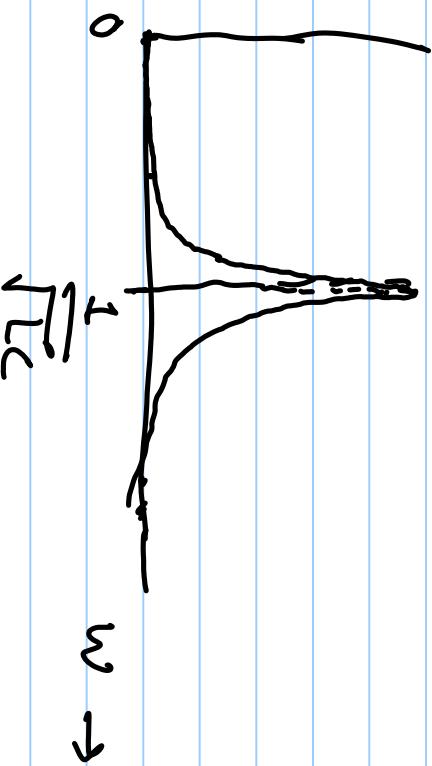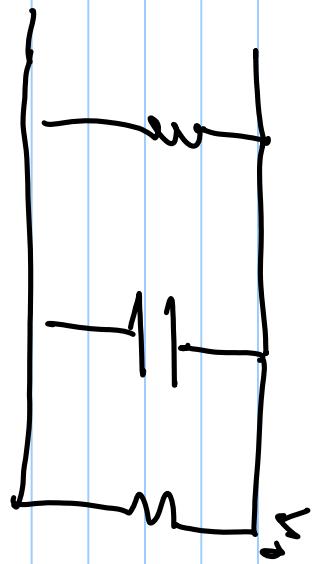

Only component appears of V_o is the fundamental
harmonic ($\omega_0 = \frac{1}{\sqrt{LC}}$) so we always get sinusoidal
oscillations irrespective of value of ρ_m

Ring Oscillator

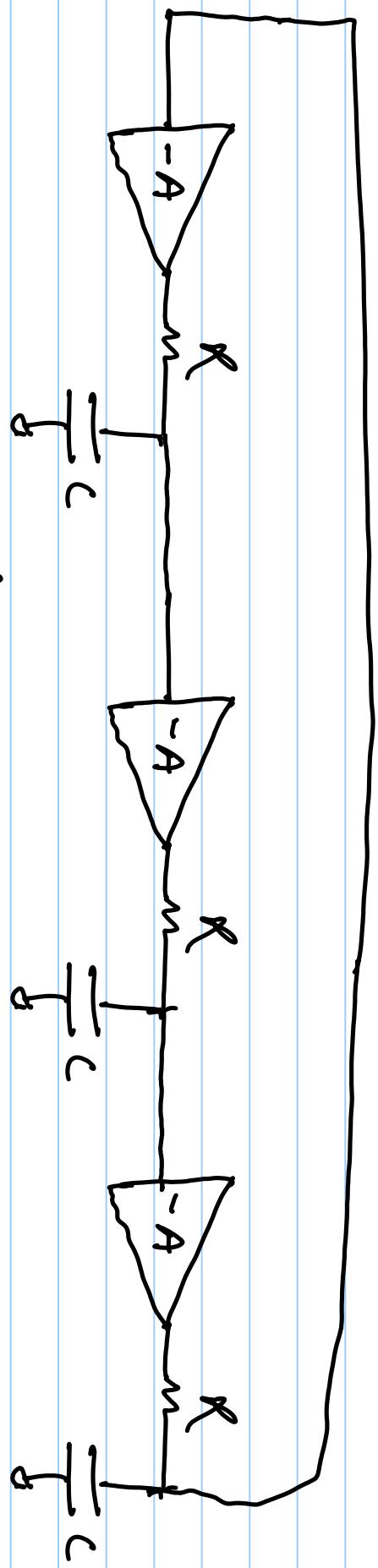


$$A \geq 1$$

each stage phase requires $= 60^\circ$.

$$\text{total phase shift} = 180^\circ + 180^\circ = 360^\circ$$


↓ + no feedback.

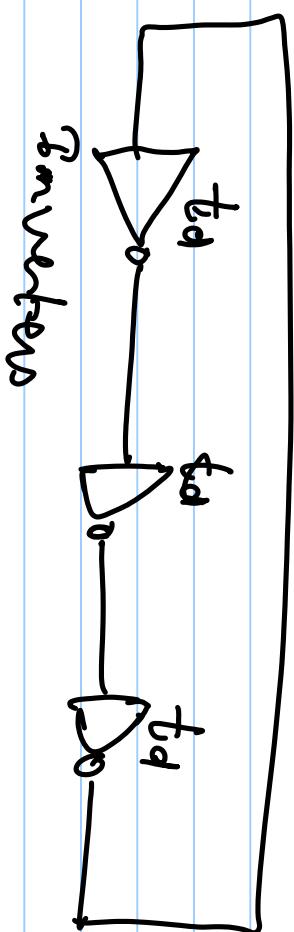

f_{osc} is frequency of oscillation,


$t_d \rightarrow$ inverter delay

$$T_{osc} = \frac{1}{f_{osc}}$$

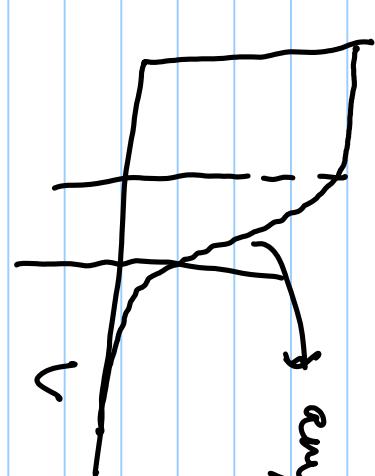


total phase shift introduced by inverters = 180°
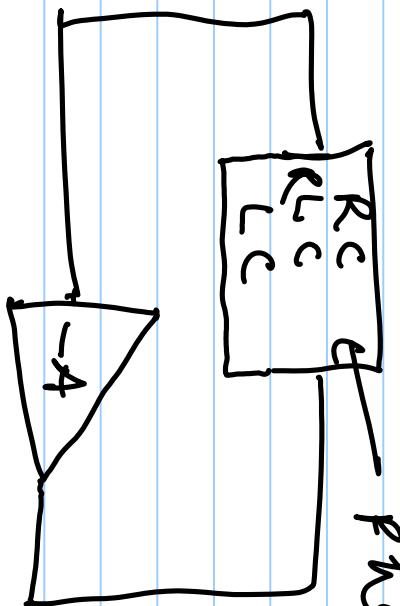
$$\Rightarrow \text{delay} = \frac{T_{osc}}{2} = 3t_d \Rightarrow T_{osc} = 6t_d$$



phase shift = 180°


Relaxation oscillator

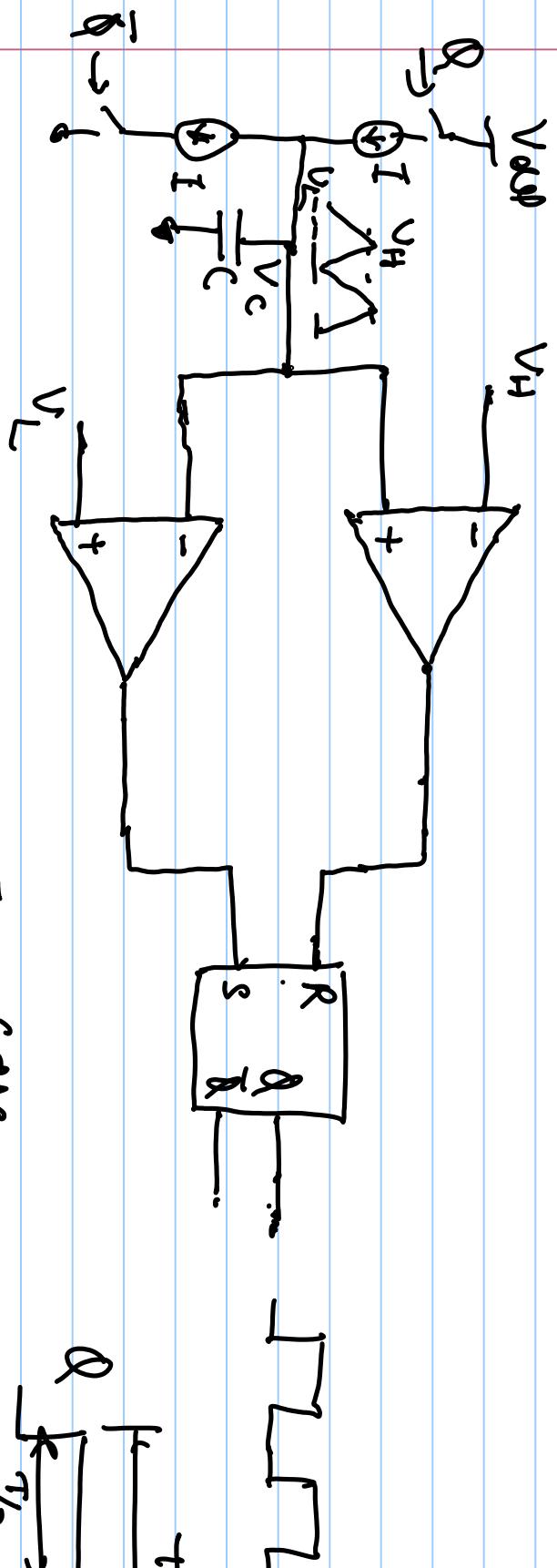

$$I = \frac{c \Delta V}{dt}$$

$$dt = T/2$$



$$\Delta V = V_H - V_L$$

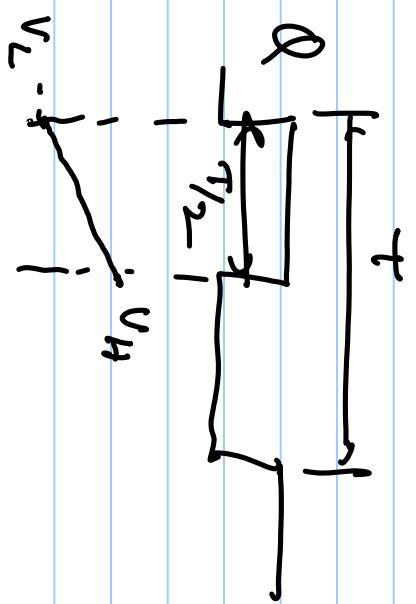


$$I = C \frac{(V_H - V_L)}{T/2} \Rightarrow \frac{I}{C} = \frac{2(V_H - V_L)}{T}$$

$$\frac{I}{T} = \frac{I}{2C(V_H - V_L)} = f_{osc}$$

$t_{on} \ll T_{osc}$

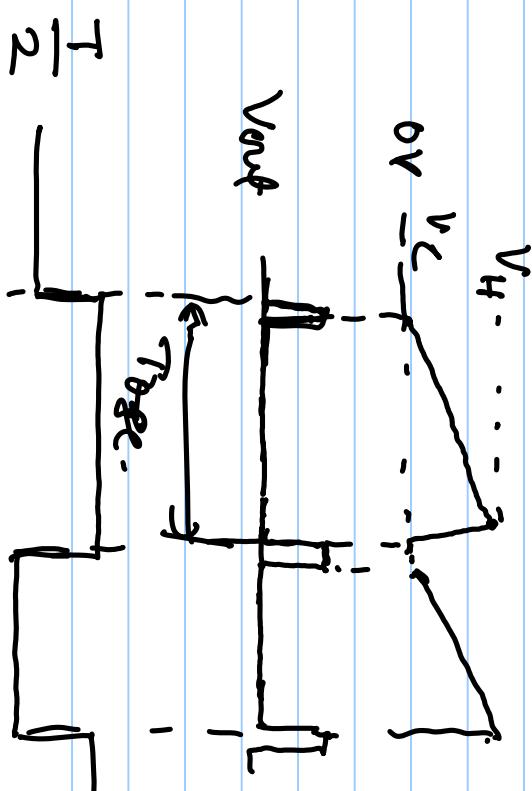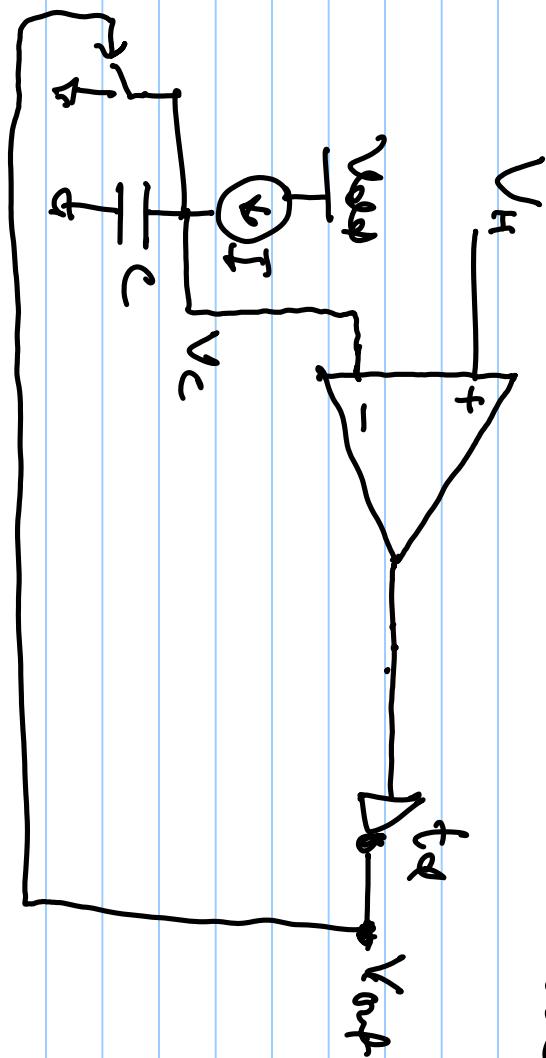


Wien Bridge osc. Meter.

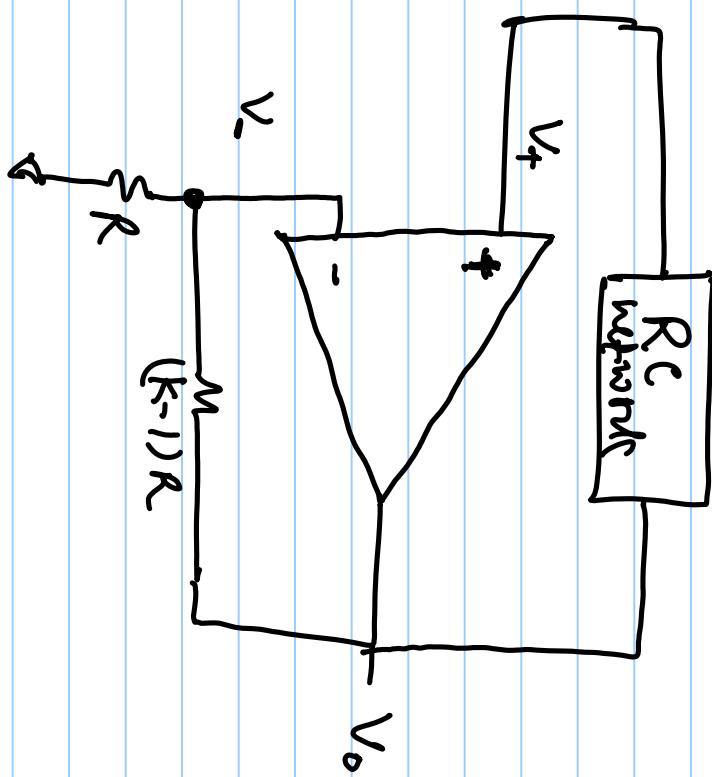

frequency at which

$$V_+ > V_-$$

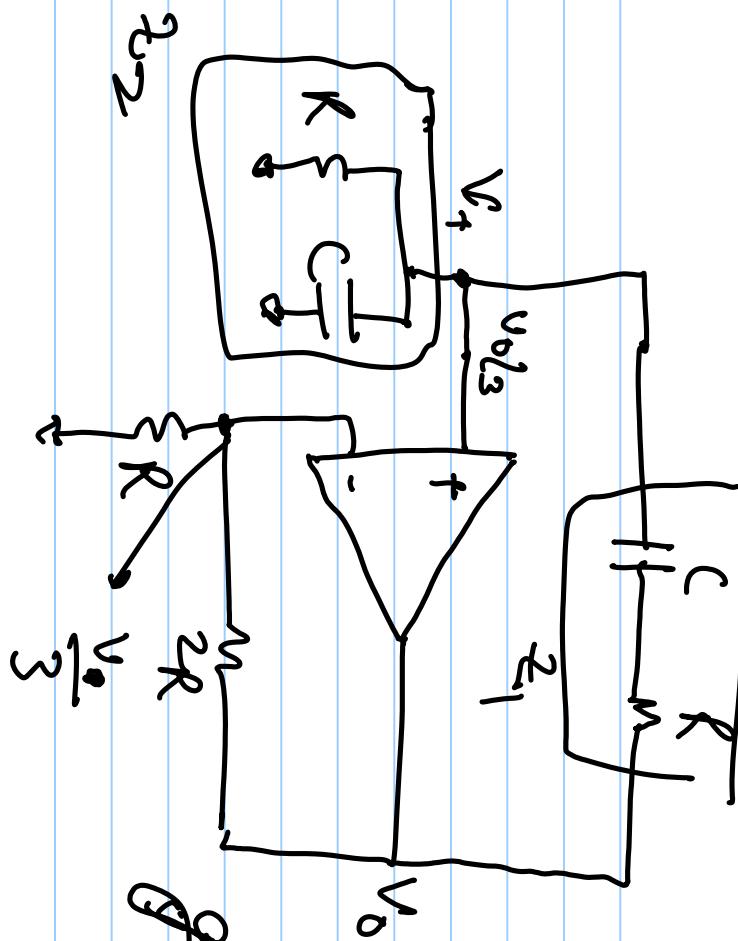

Gain, $K = 3$

$$\omega_0 = \frac{1}{RC}$$

$$V_t = \frac{Z_2}{Z_1 + Z_2}$$

Butterworth Filter

magnitude.


maximally flat response

$$Q > 0.7$$

$$Q = 0.7$$

pole response

$$\omega_{cav} - 20 \text{dB/dec.}$$

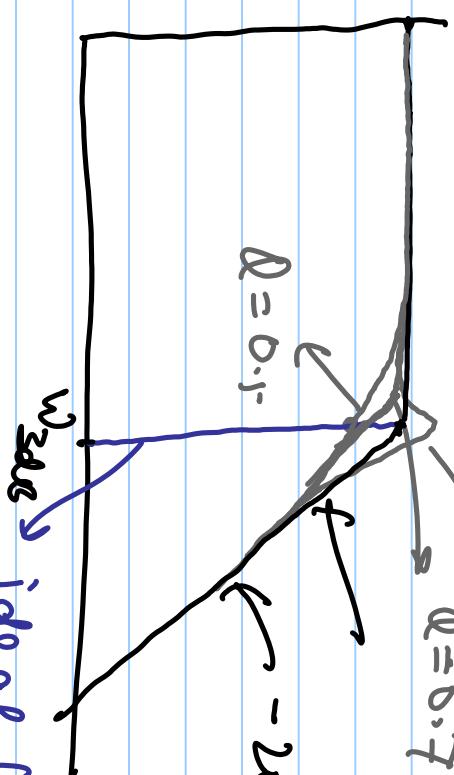

ideal (brick wall) Filter

$\omega_c = 0.7$ in 2nd order Butterworth curves flattest magnitude response.

$$H(s) = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q_0} s + \omega_0^2}$$

$$Q_0 = 0.7 = \frac{L}{\sqrt{2}}$$

$$|H(s) * H(-s)| = |H(s)|^2$$

$$\omega_0^2 \times \omega_0^2$$

$$H(s) * H(-s) = \frac{\omega_0^2}{(s^2 + \frac{\omega_0}{Q_0} s + \omega_0^2)(s^2 - \frac{\omega_0}{Q_0} s + \omega_0^2)}$$

$$\omega_0^4$$

$$= \frac{\omega_0^4}{(\lambda^2 + \omega_0^2)^2 - (\frac{\omega_0}{Q_0} s)^2}$$

$$\frac{\omega_0^4}{s^4 + \omega_0^4 + 2s^2\omega_0^2 - \frac{\omega_0^2}{k_e^2}s^2} =$$

$$\Omega_0 = \frac{1}{\sqrt{2}}$$

$$= \frac{\omega_0^4}{s^4 + \omega_0^4 + 2\cancel{s^2}\omega_0^2 - \cancel{2s^2\omega_0^2}} = \frac{\omega_0^4}{s^4 + \omega_0^4}$$

$$\left| H(s) \right|^2 = \frac{\omega_0^{2N}}{a_2 s^2 + a_4 s^4 + \dots + a_{2N} s^{2N} + \omega_0^{2N}}$$