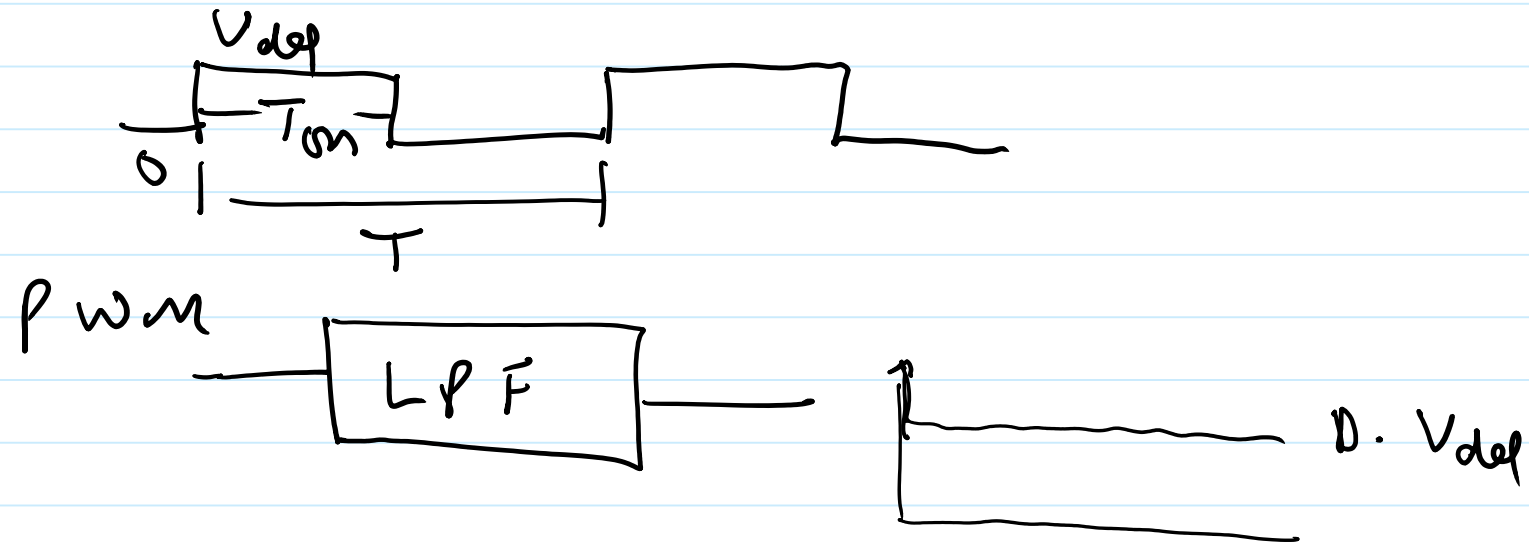


## PWM Signal

PWM  $\rightarrow$  Pulse Width Modulation







$$D = \frac{T_{on}}{T} = \text{duty cycle}$$

Fourier Series
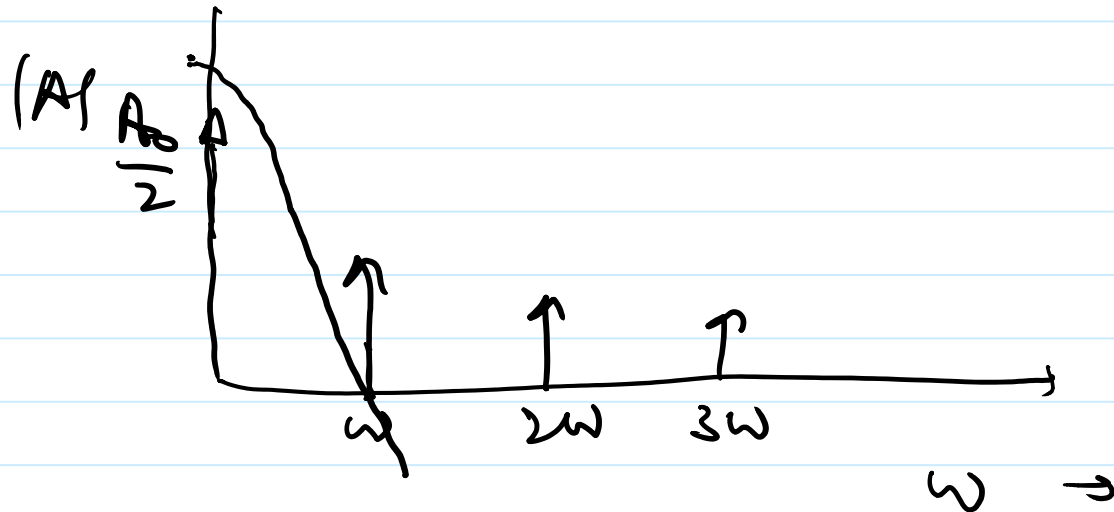
$$\underbrace{\frac{A_0}{2}}_{\text{dc component}} + \sum_{n=1}^{\infty} \left[ \underbrace{a_n \cos n\omega t + b_n \sin n\omega t}_{\text{Ac component}} \right]$$




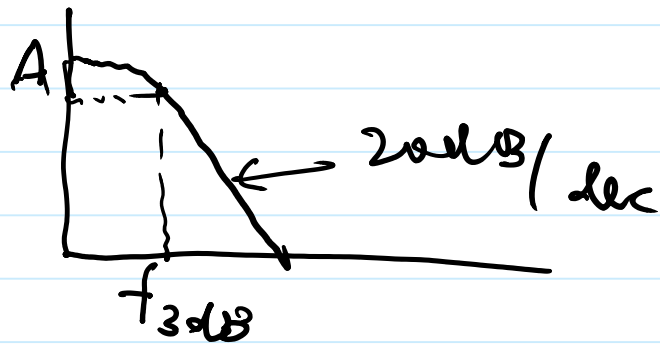if  $T$  is period of  $PWM$   
 Then LPF BW should be  $\ll \frac{1}{T}$



$$f_{3dB} \ll \frac{1}{T}$$

1


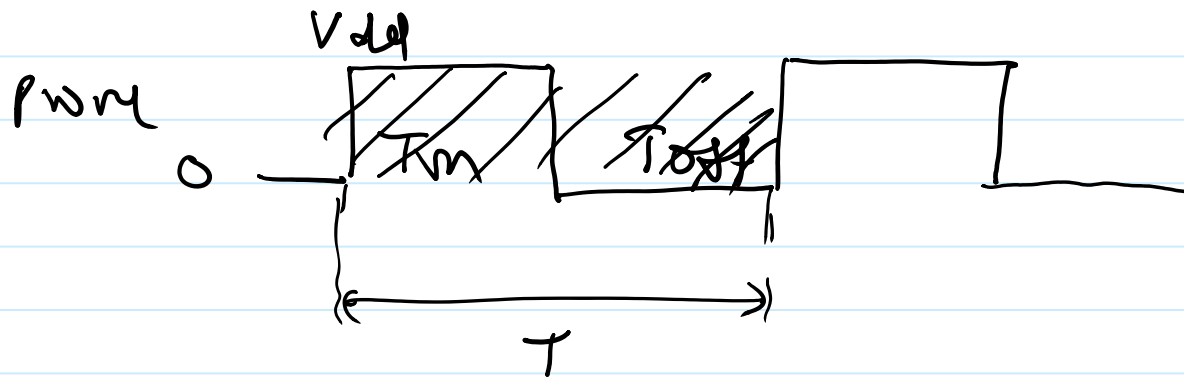


$$\text{Avg (pwm)} = \frac{1}{T} \int_0^T f(t) dt$$

$$= \frac{1}{T} \times V_{del} \times T_m$$

$$= \frac{T_m}{T} V_{del} = D \cdot V_{del}$$

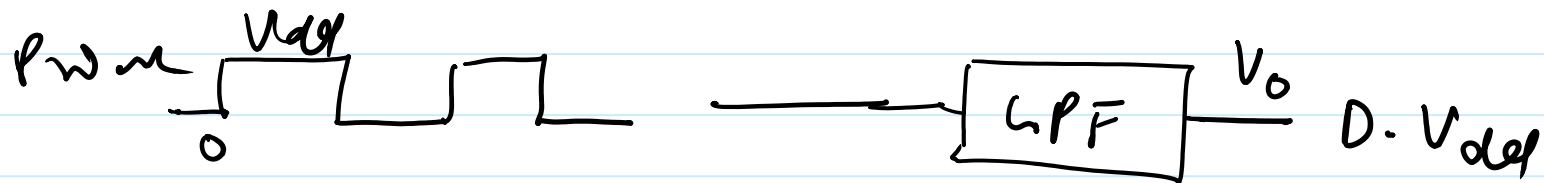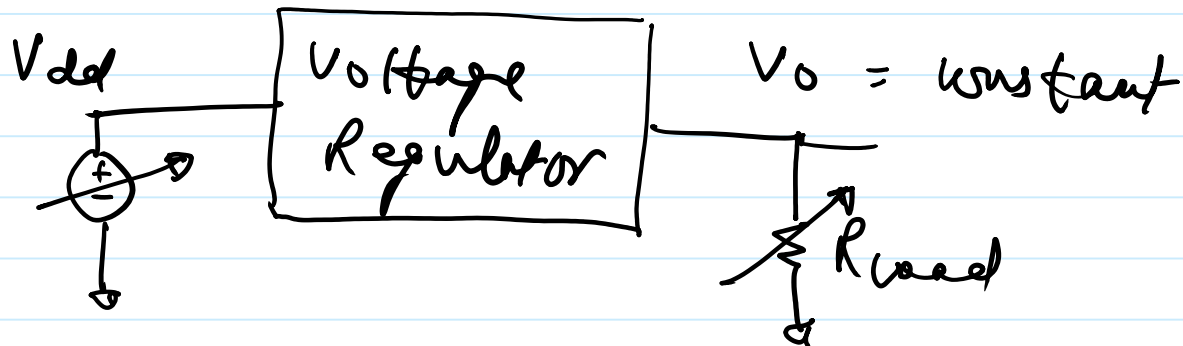PWM is used to implement voltage regulator





$$V_{dd} = 5V, \quad V_0 = 2.5V$$

$$V_0 = D \cdot V_{dd} \Rightarrow D = \frac{V_0}{V_{dd}} = \frac{2.5}{5} = 0.5$$


$$V_{dd} = 10V$$

$$D = \frac{2.5}{10} = 0.25$$

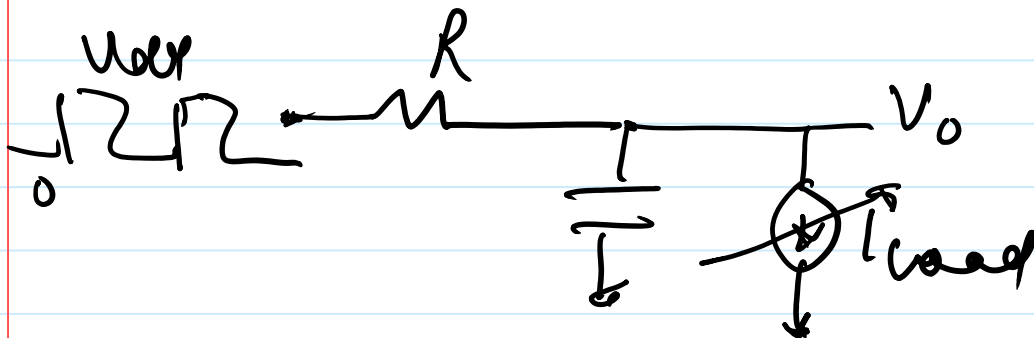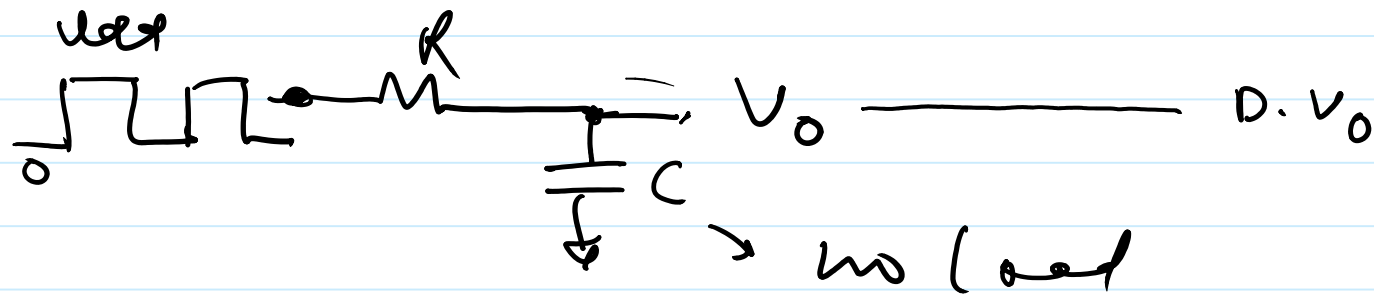
which means under varying  $V_{in}$  we need to vary  $D$  to keep  $V_o$  constant



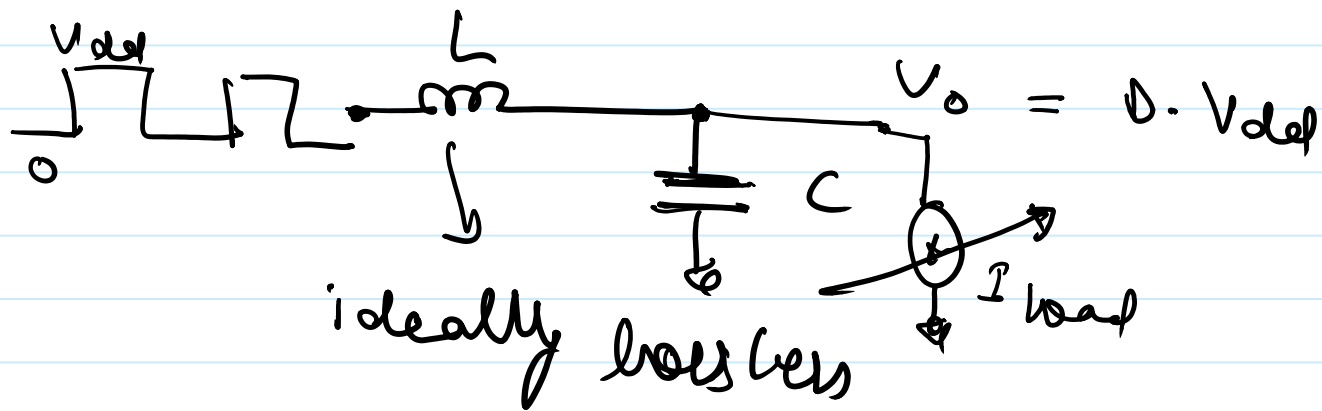
we can't use RC filter for regulator due to  $IR$  drop




$$V_o = D \cdot V_{dcl}$$

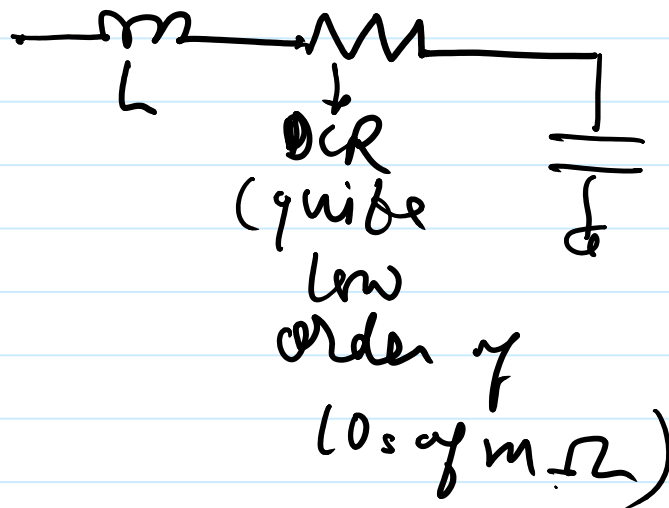




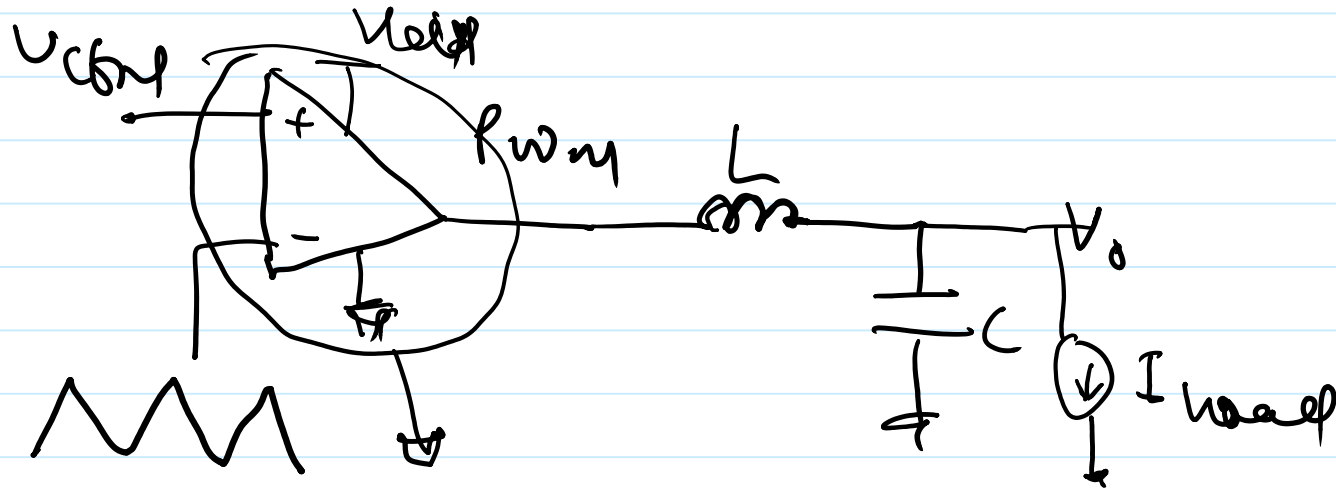

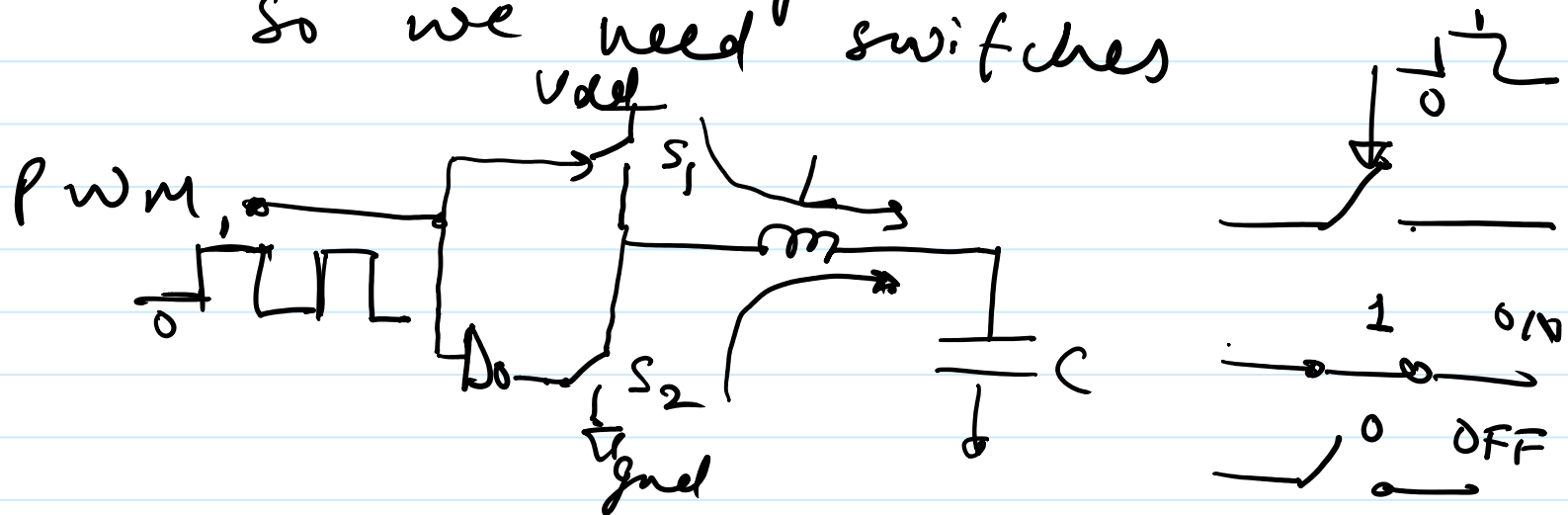
comparator  
 Can't drive large current  
 so we need switches




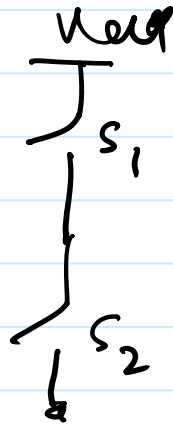


$S_1$  &  $S_2$  are low resistance switches

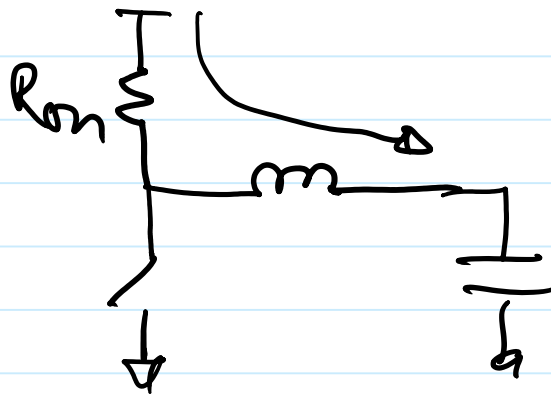$S_1$  is ON &  $S_2$  is OFF  $R_{on}$  is order of  $10\text{ m}\Omega$




$S_2$  is ON &  $S_1$  is OFF

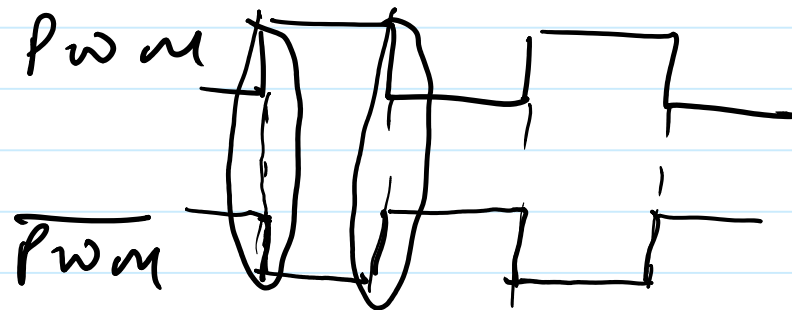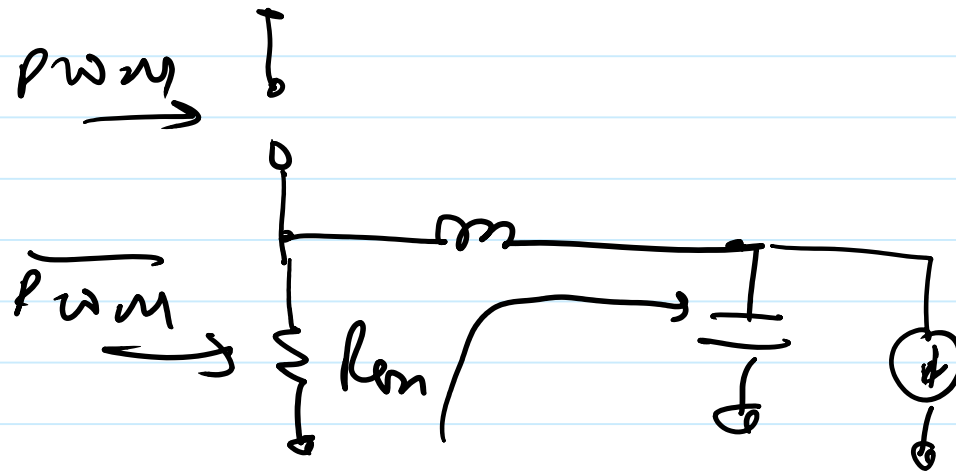

There is a possibility that both  $S_1$  &  $S_2$  may turn ON simultaneously during transition

Both  $S_1$  &  $S_2$  are ON

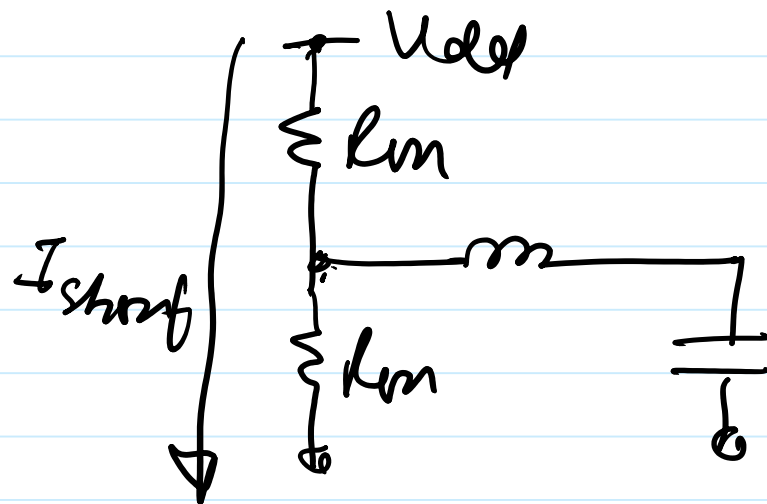

direct path from  $V_{dd}$  to gnd through  $R_m$

$$I_{short} = \frac{V_{dd}}{2R_m}$$

assume  $R_m = 10\text{m}\Omega$ ,  $V_{dd} = 5\text{V}$


$$I_{short} = \frac{5}{20\text{m}\Omega} = 250\text{A}$$


We need to ensure that both switches never turn ON simultaneously.

=> Break before make



or

non-overlap clock generator


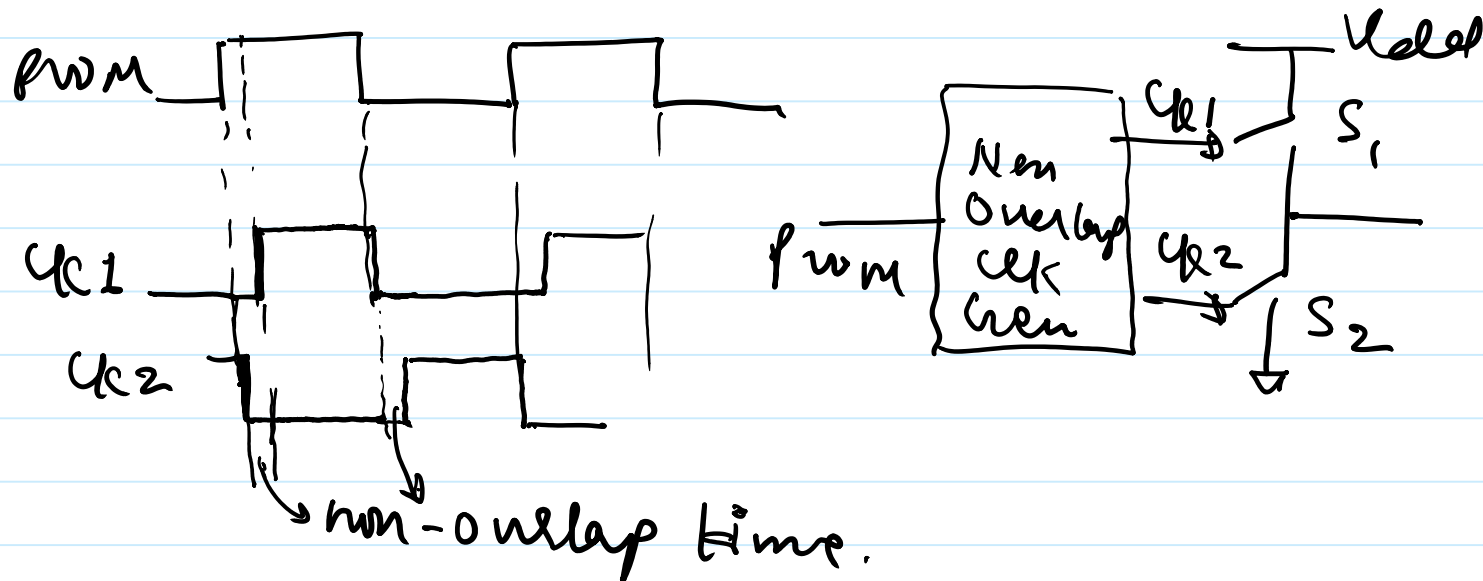


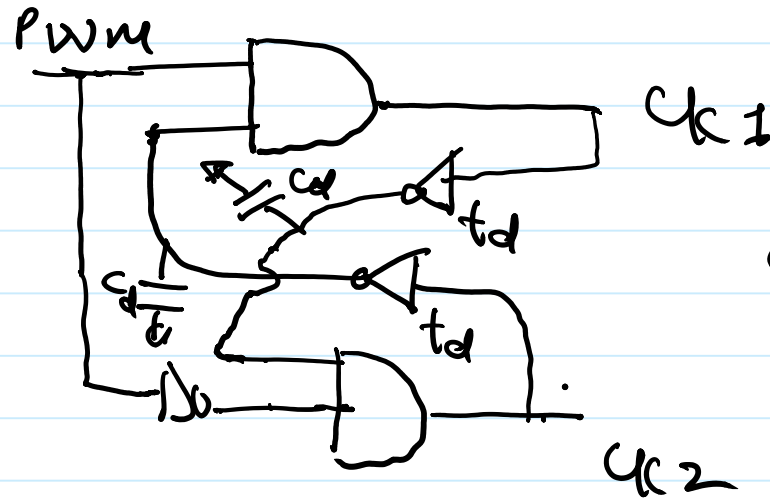

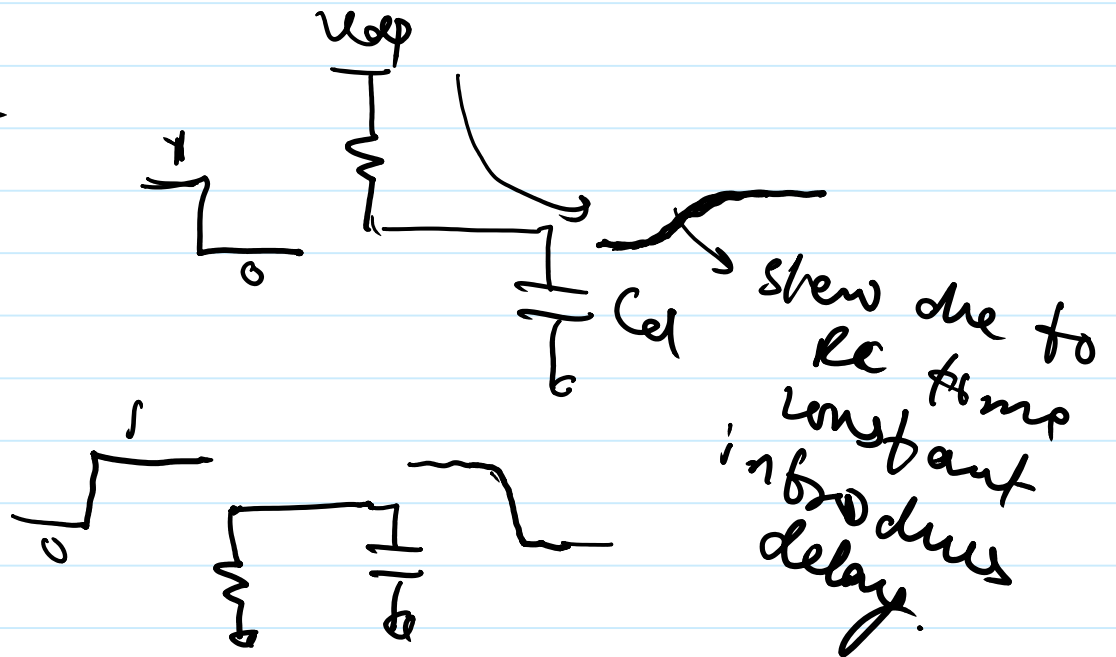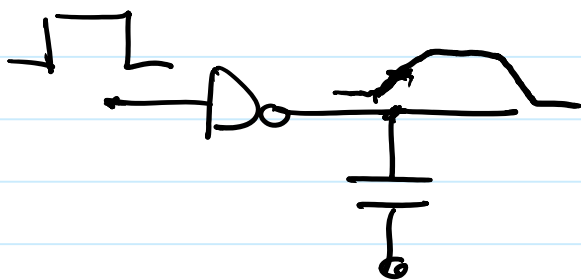$C_{gd}$  can be used to control non-overlap time




# Regulator

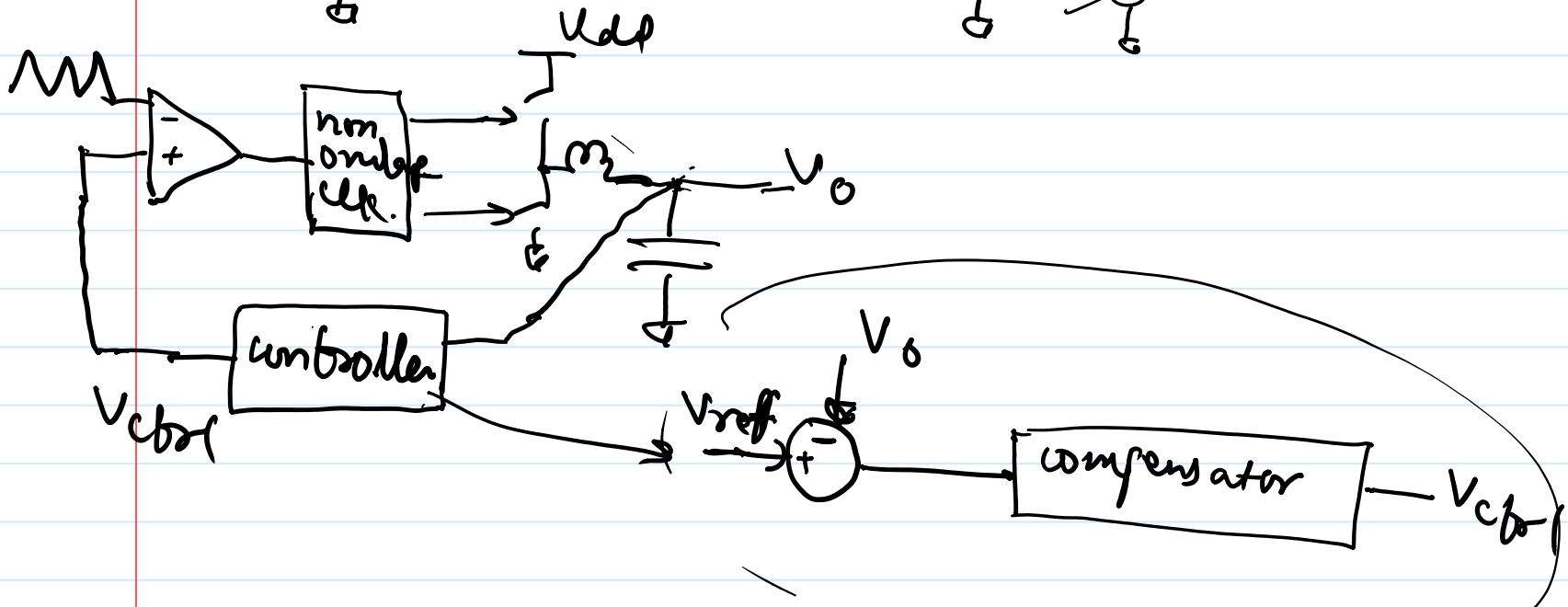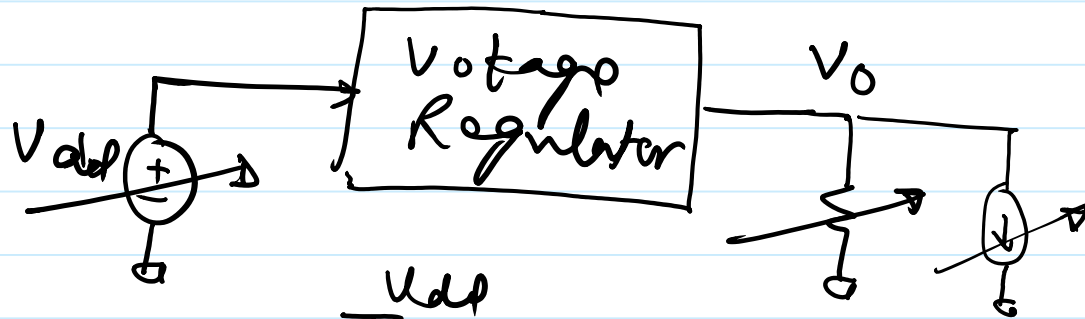






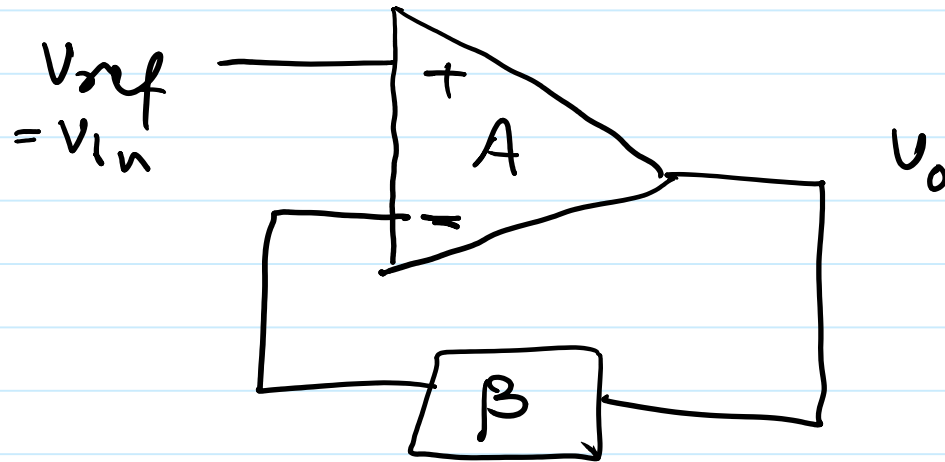

$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta}$$

if  $A\beta = -1$  ↖ loop gain =  $A\beta$

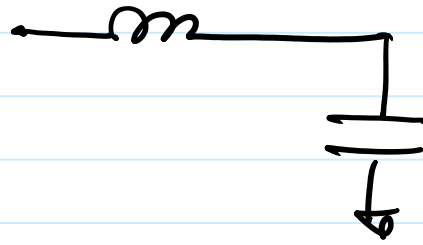$\frac{V_o}{V_{in}} = \infty \rightarrow$  -ve feedback becomes +ve



$$\text{poles} = \frac{1}{\sqrt{2}c}$$

