
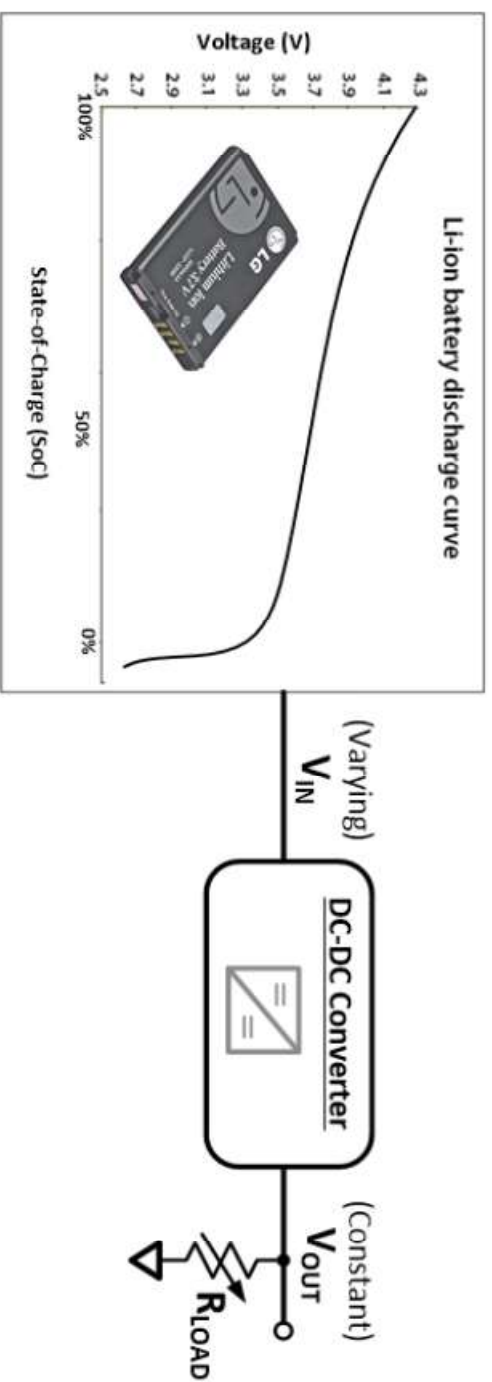


EE2019


Note Title

3/8/2019

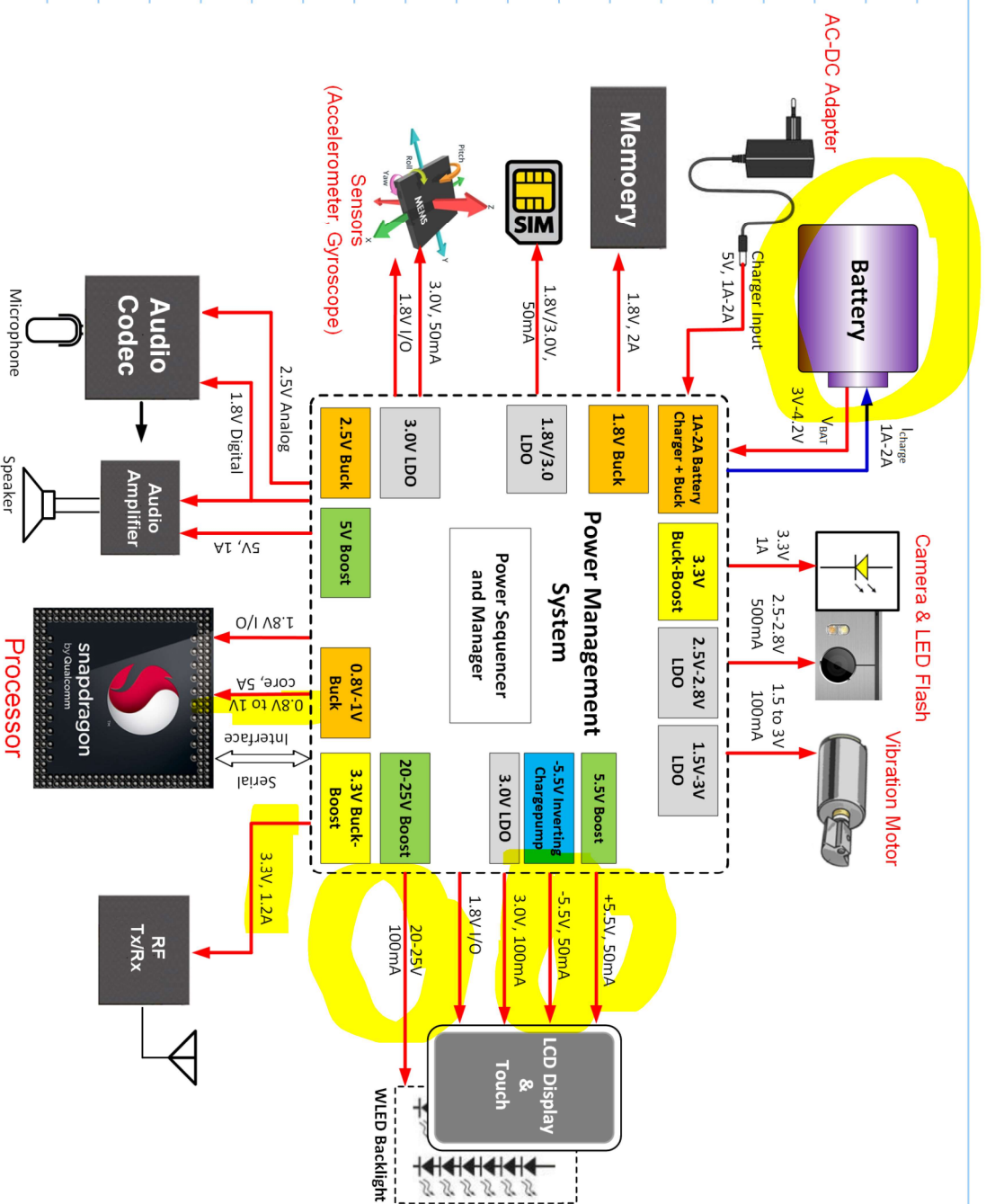





Types of Voltage Regulators

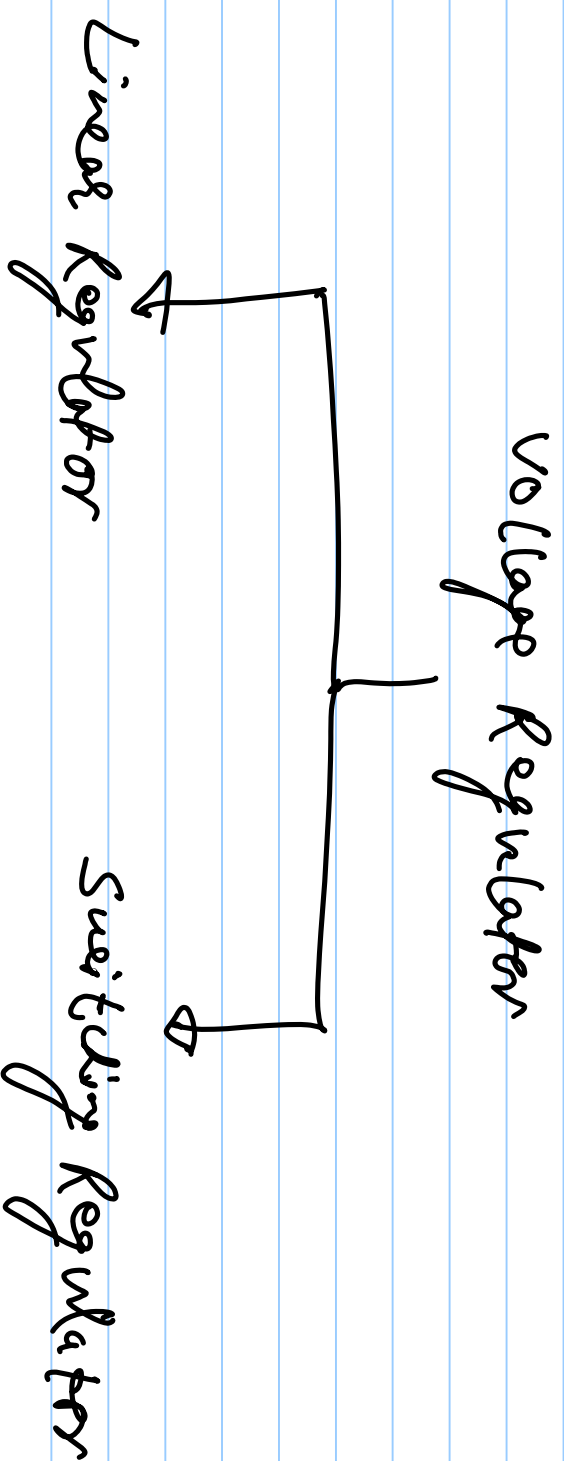


Linear Regulator:

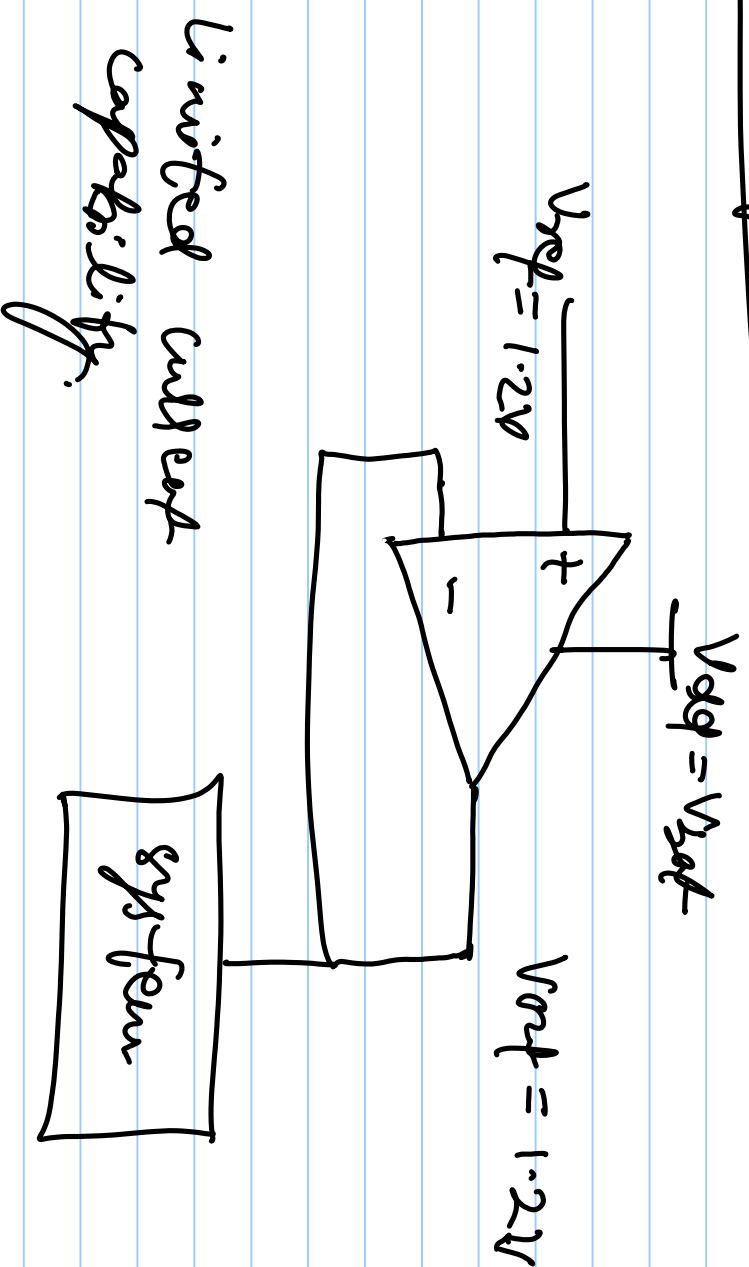


$$V_{in} = 5V, \quad V_{out} = 2.5V$$

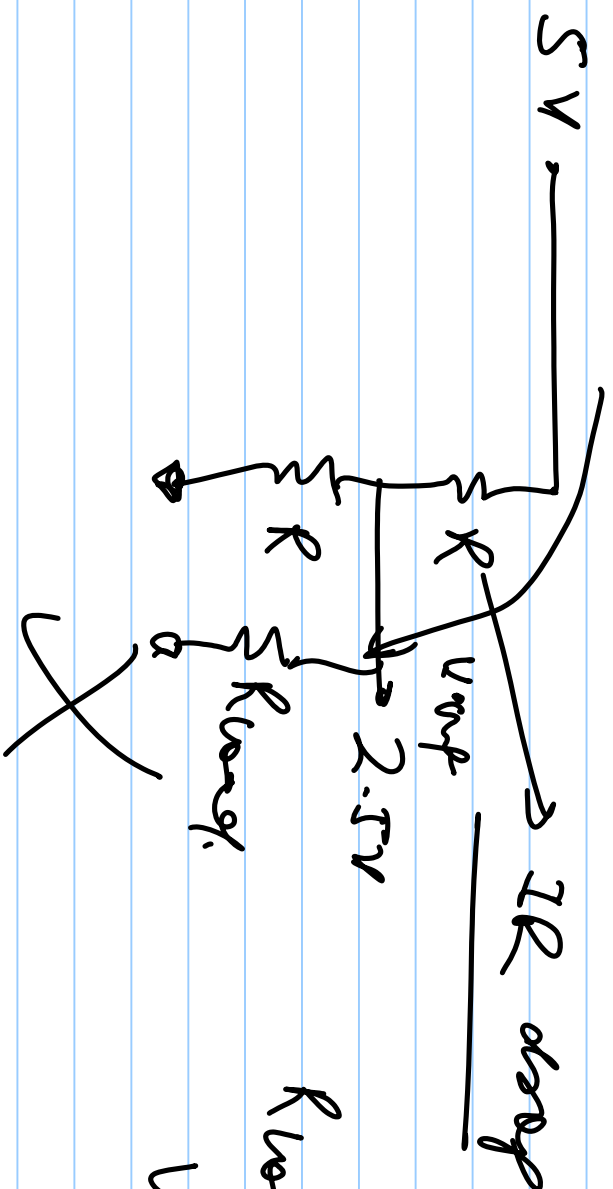

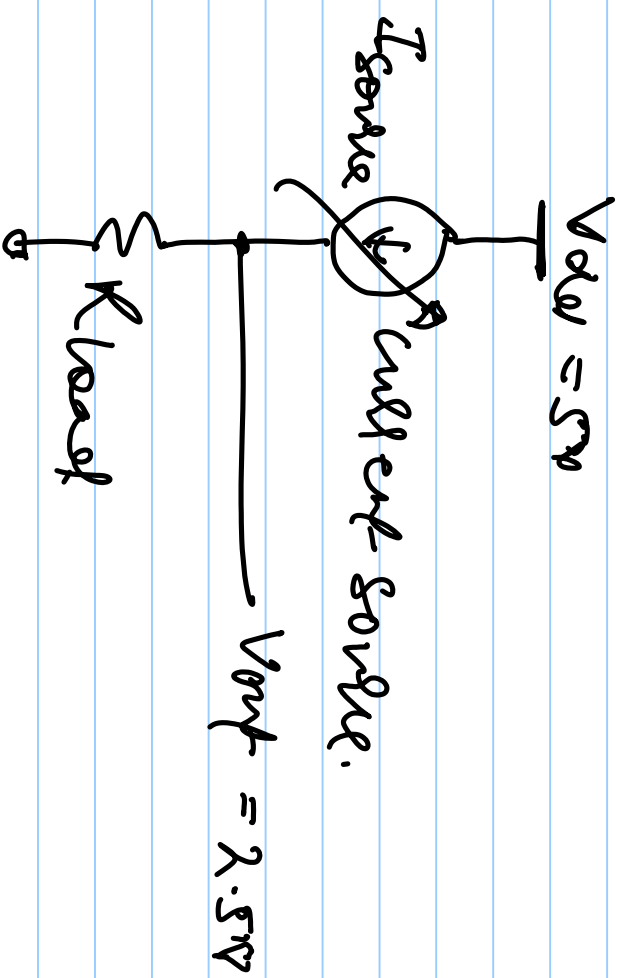R_{load} is not really to
 V_{out} is not constant



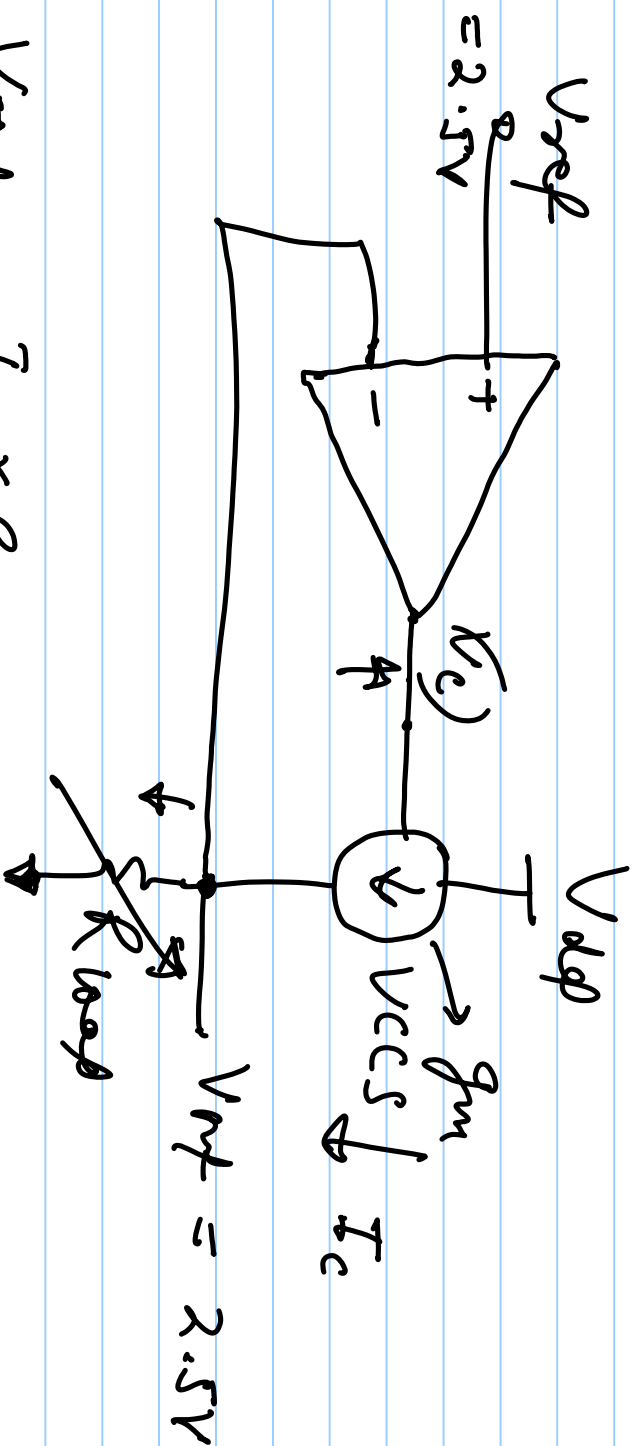
$$V_{out} = I_{source} \times R_{load} = 2.5V$$



$$V_{out} = I_c \times R_{load} = V_{ref} - g_m \cdot R_{load}$$

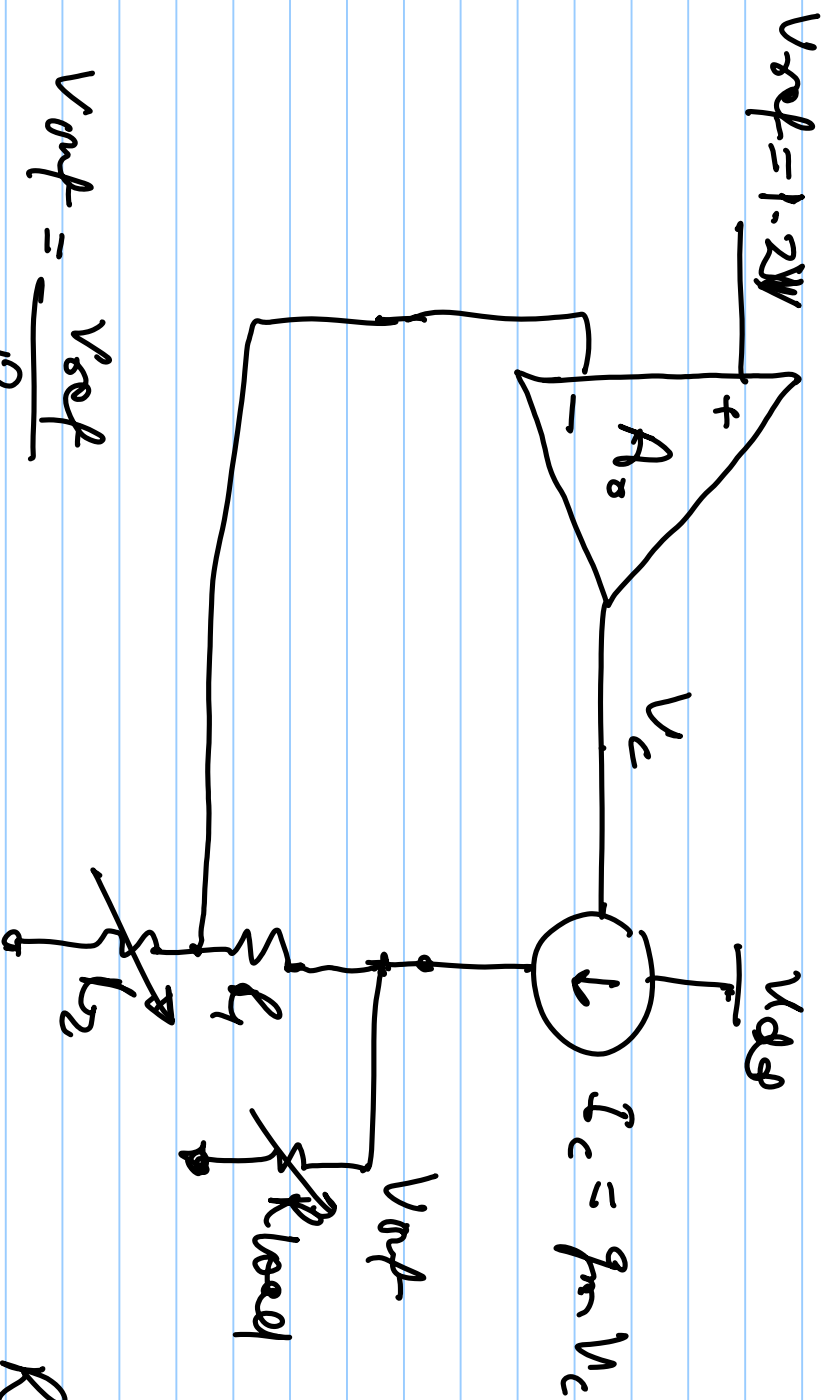
V_{out} is regulated by negative feedback when V_c is varied based on load current requirement.




$$V_{out} = \frac{V_{out}}{\beta}$$

$$\beta = \frac{R_2}{R_1 + R_2}$$

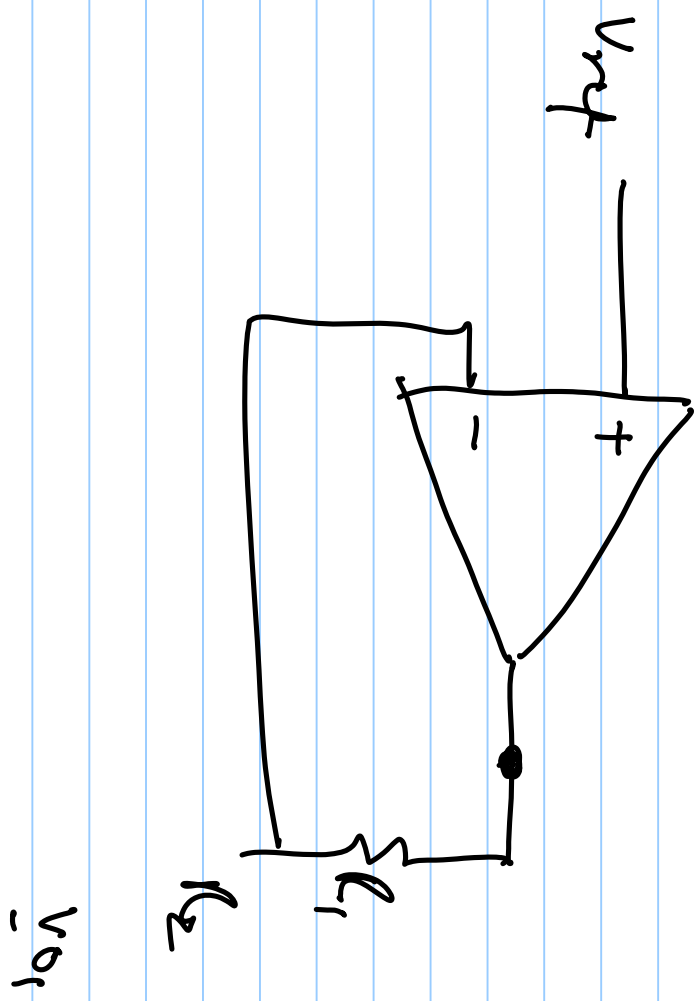V_{out} can be controlled by changing β .



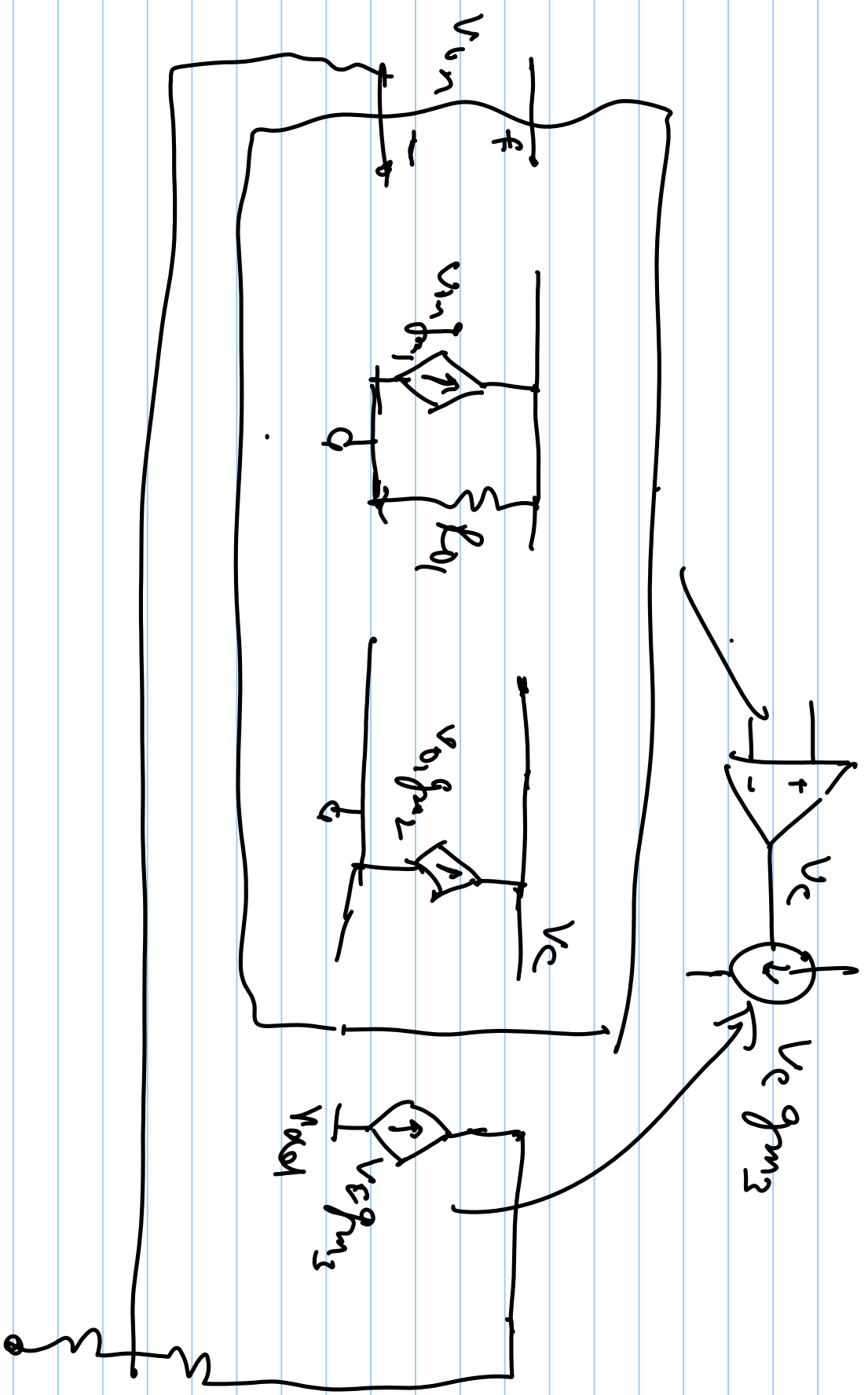

Line Regulation :- is change in V_{out} w.r.t. V_{in} or V_{dcl}



$$\text{Line Regulation} = \frac{\Delta V_{out}}{\Delta V_{dcl}}$$

Load Regulation :- change output voltage (V_{out}) w.r.t. load current


$$\text{Load Regulation} = \frac{\Delta V_{out}}{\Delta I_{load}}$$

Load Transient : Transient change in V_{out} w.r.t.

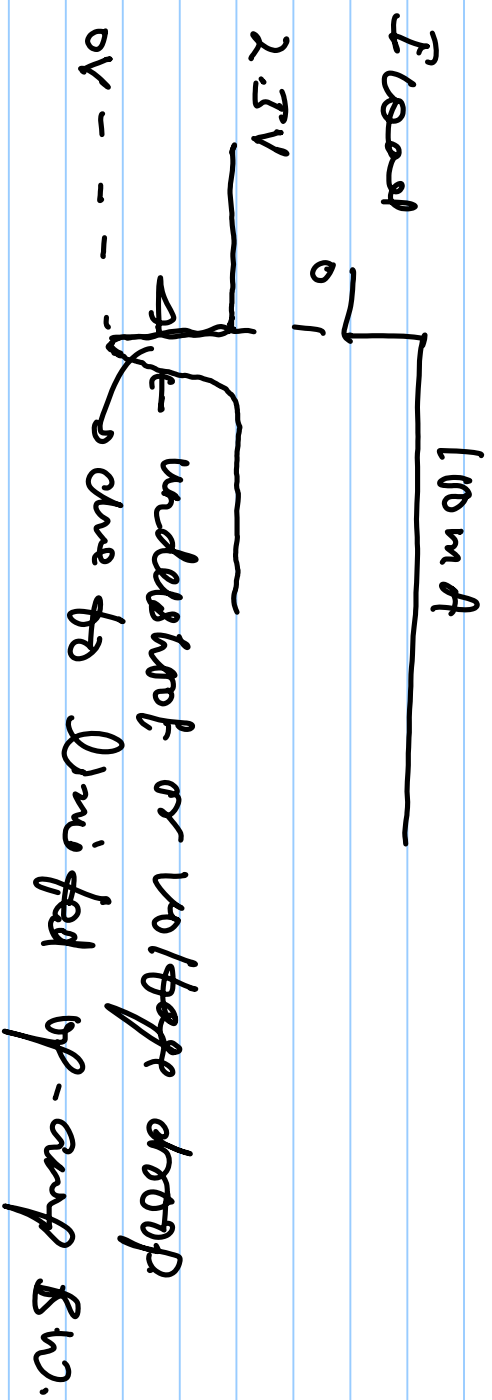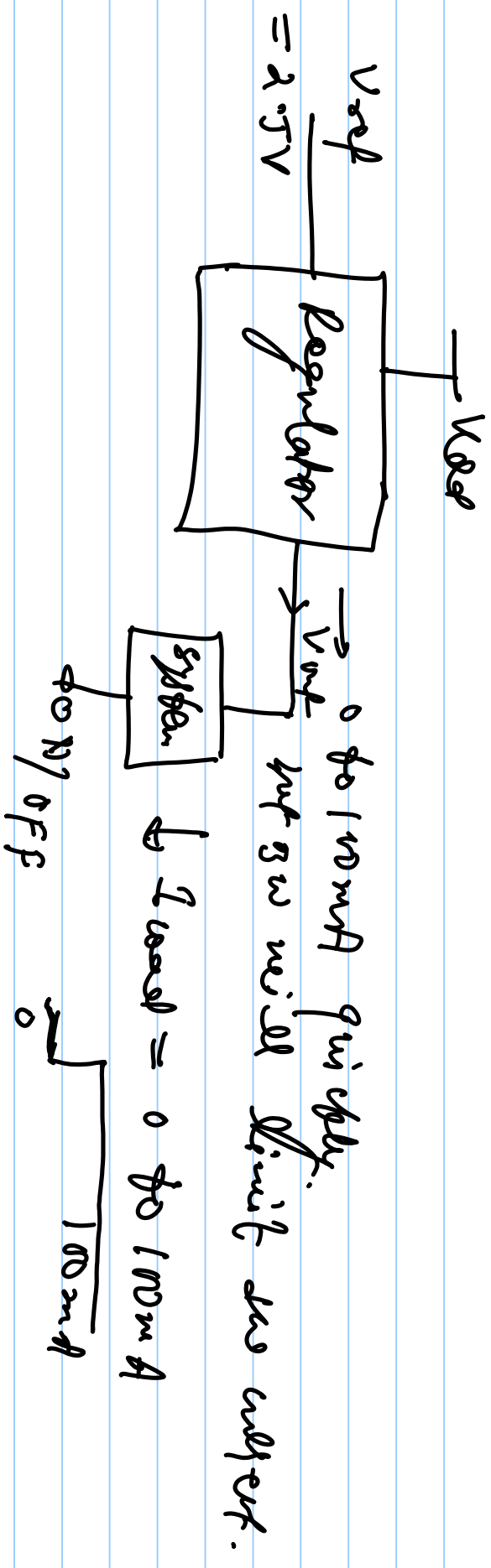load step $\rightarrow$ step response w.r.t. load



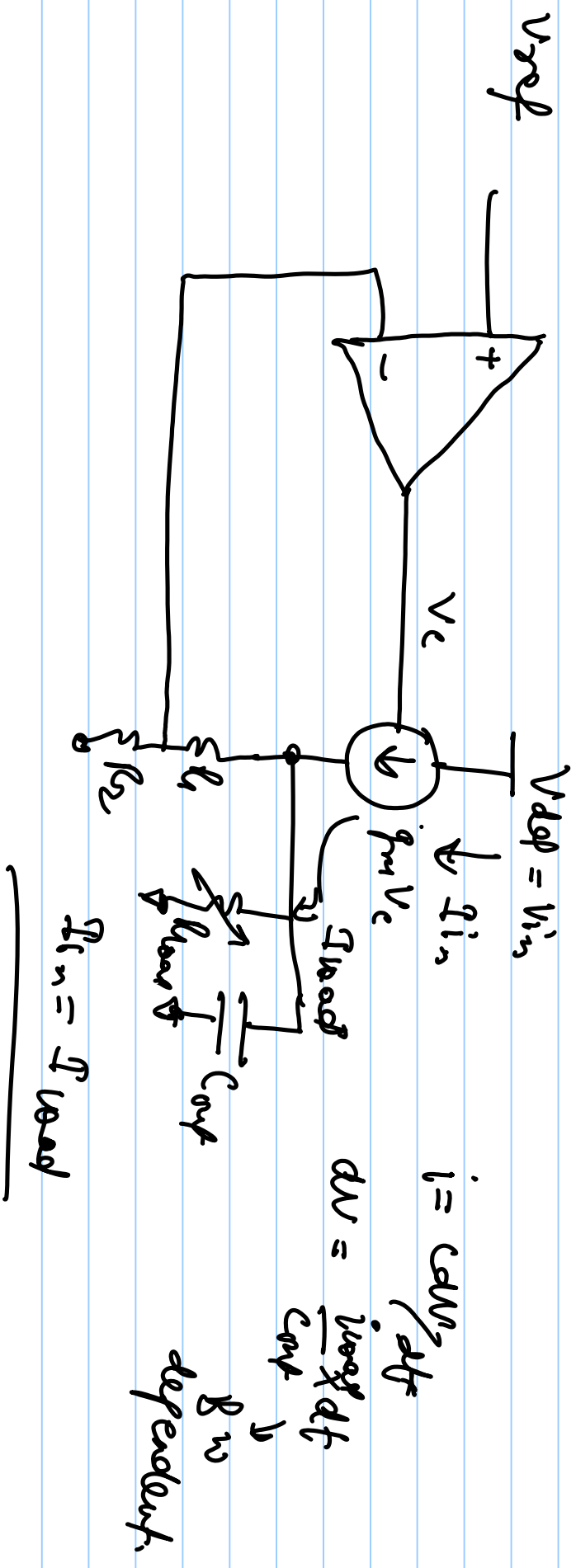undershoot can be reduced by adding capacitor at V_{out}



Efficiency of Linear Regulator.

$$\eta = \frac{\text{output power}}{\text{input power}}$$


$V_{in} \rightarrow$ Input supply $I_{in} \rightarrow$ current drawn from V_{in}

$V_{out} \rightarrow$ Output Voltage $I_{out} \rightarrow I_{load}$.

$$\eta = \frac{V_{out} \times I_{load}}{V_{in} \times I_{in}} = \frac{V_{out}}{V_{in}}$$

$$V_{in} = 5V, \quad V_{out} = 2.5$$
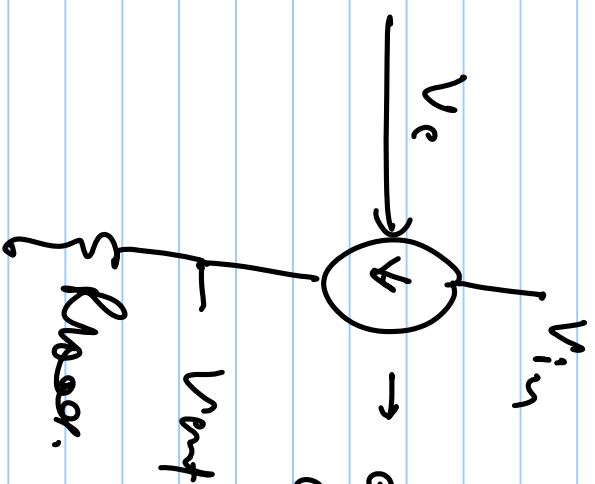
$$\eta = \frac{2.5}{3} = \frac{1}{2} \rightarrow 50\%$$




$$\text{drop} = V_{in} - V_{out}$$

$$\text{current} = I_{in}$$

Power loss

$$= (V_{in} - V_{out}) I_{load}$$

drop. at no load.

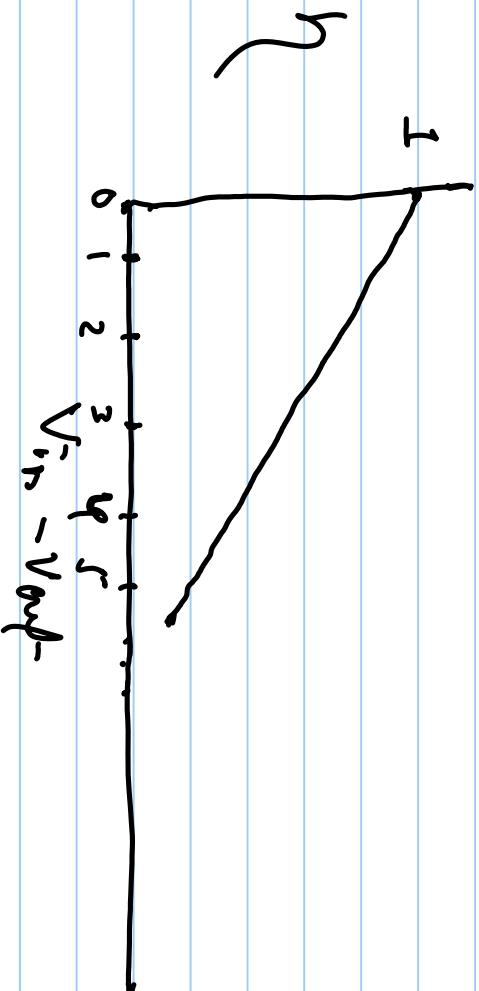

Linear Regulator has poor efficiency if drop-out voltage is large ($V_{in} - V_{out}$ is large).